
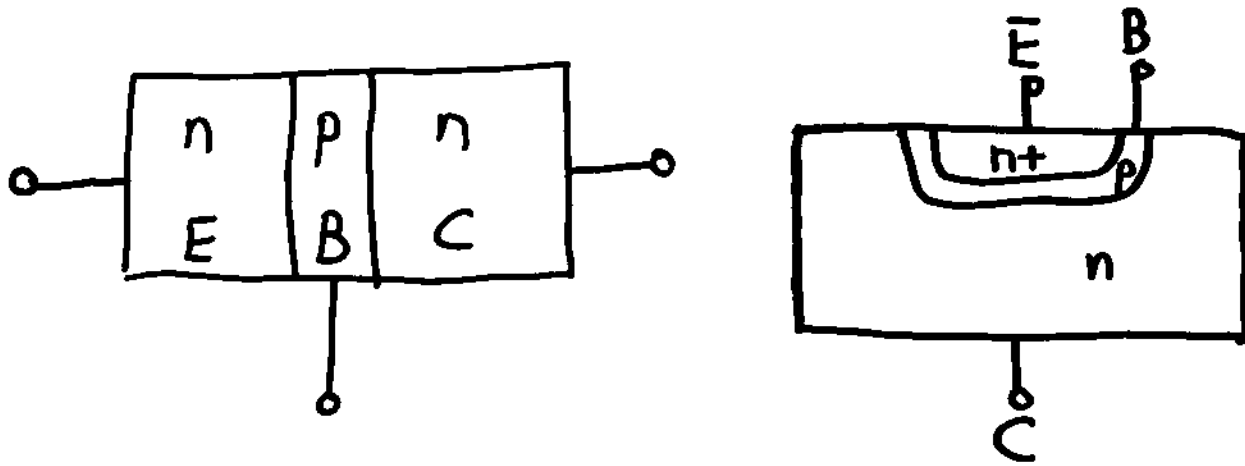


BJTs : Bipolar Junction Transistors

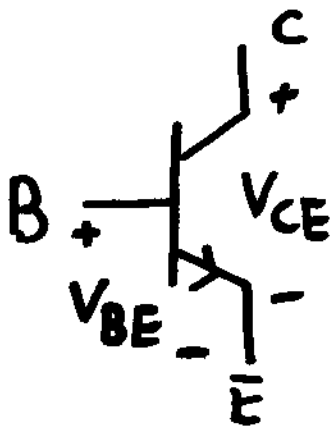


Three terminal device:



Emitter "emits" electrons

Collector "collects" electrons



Is it back-to-back diodes?

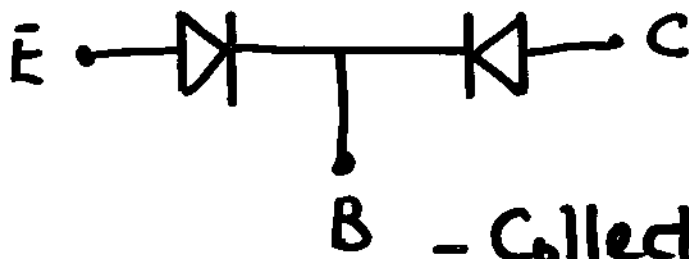

BJT has
very narrow
base region

- Collector voltage can
influence current
flow through base

Common-base Configuration

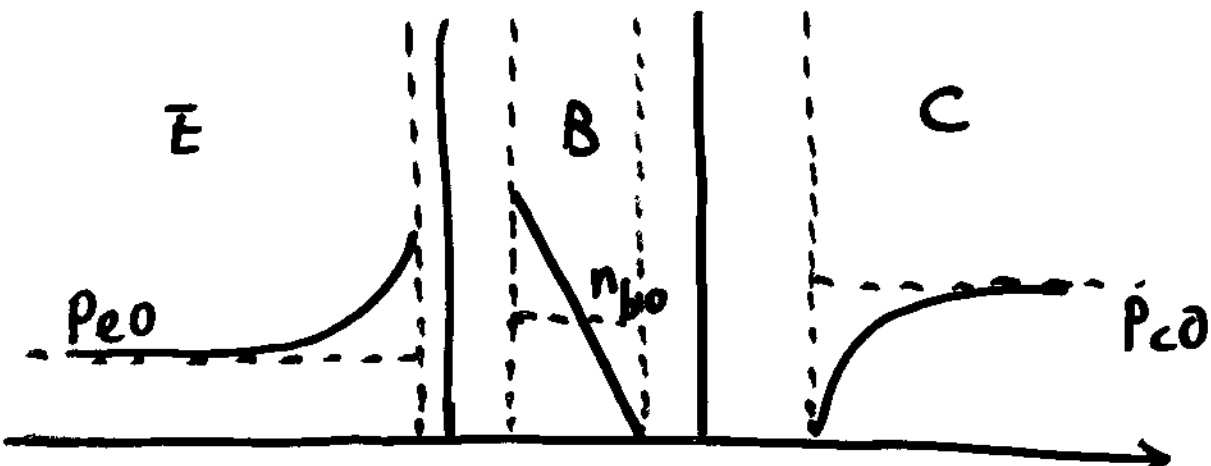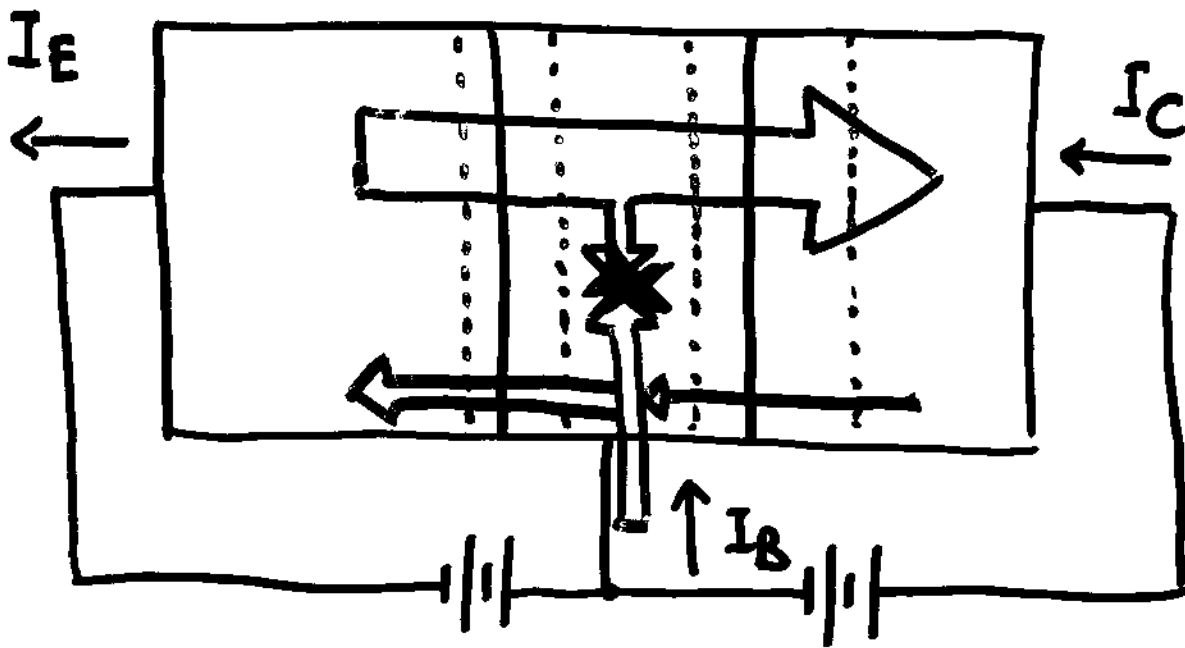

Minority carrier concentration

E doping is high $10^{19}/\text{cm}^3$
B " moderate $10^{17}/\text{cm}^3$
C " lower $10^{15}/\text{cm}^3$


Forward Active Operation

BE = Forward Biased

BC = Reverse Biased

- ① Electrons injected from E \rightarrow B
- ② Narrow base - electrons can diffuse through base
- ③ Some electrons "recombine" with hole in base. Holes are supplied with I_B
- ④ BC junction R.B. \Rightarrow large electric field @ junction
- ⑤ Electrons get swept across BC junction and "collected"

Currents & Gains

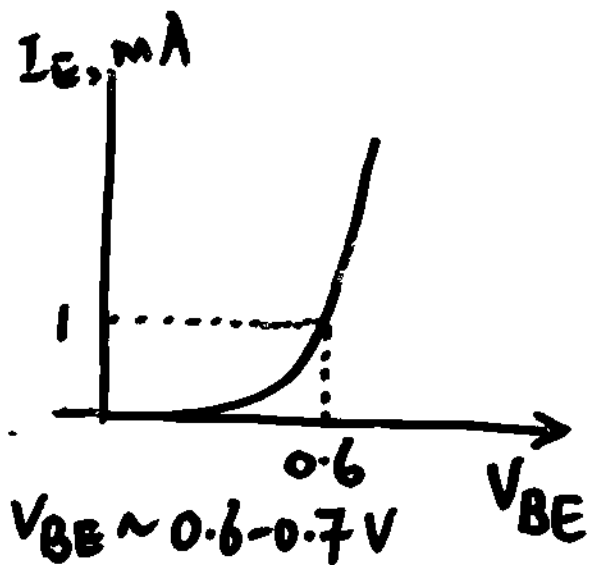

$$I_E \approx I_S e^{V_{BE}/V_T}$$

Essentially a diode

$$I_C = \alpha I_E$$

↳ Base transport factor
How much current goes through base

α : Common-base current gain

$$I_B \propto I_S e^{V_{BE}/V_T}$$

$$I_C = \beta I_B$$

β : Common-Emitter current gain

$$I_E = I_C + I_B$$

$$= (\beta + 1) I_B$$

$$\alpha = \frac{\beta}{\beta + 1}$$


$$I_C = \frac{\beta}{\beta + 1} I_E = \alpha I_E$$


$$I_E = I_C + I_B$$

$$I_B = (1 - \alpha) I_E$$




$$\beta = \frac{\alpha}{1 - \alpha}$$
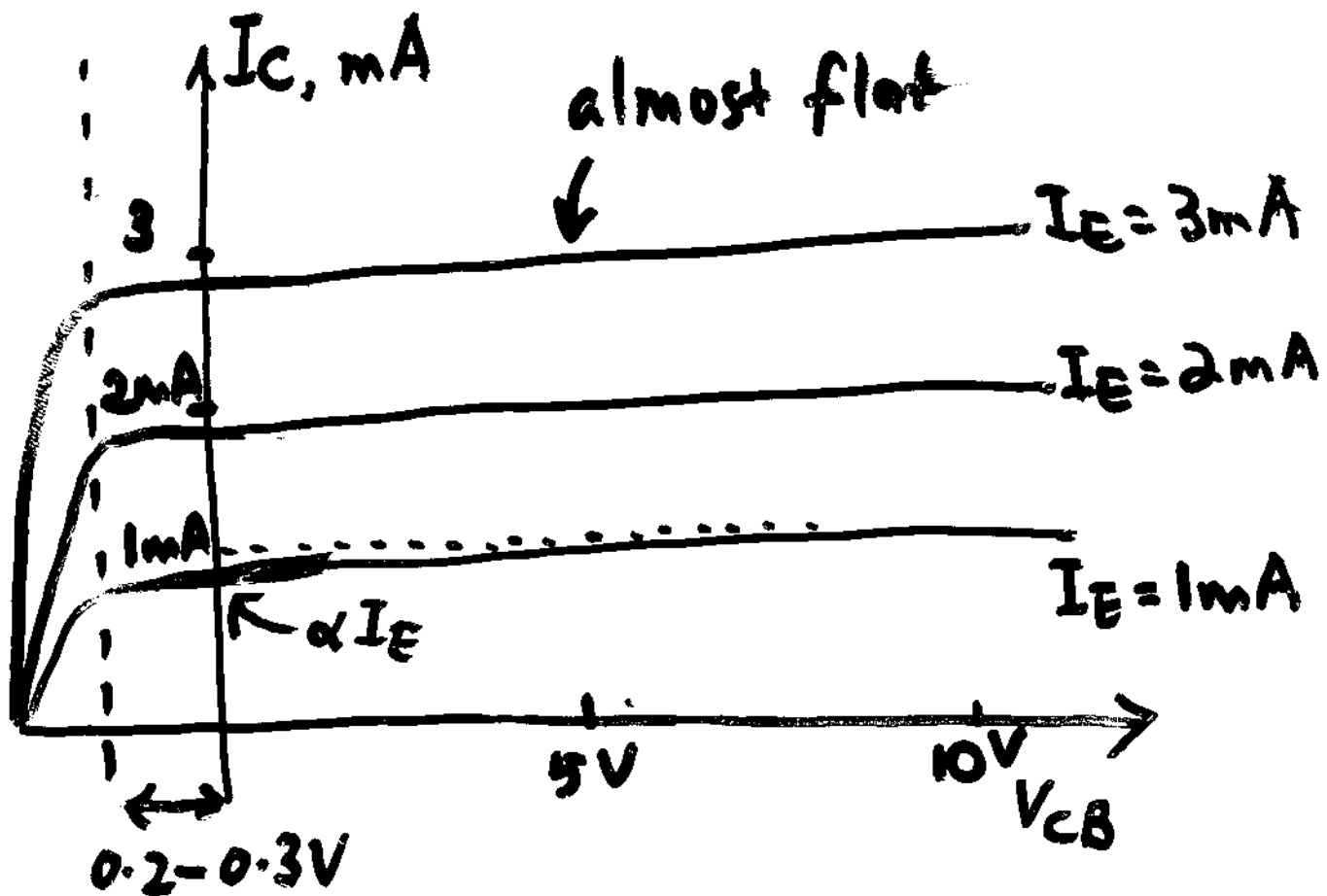
$$I_C = \frac{\alpha}{1 - \alpha} I_B = \beta I_B$$






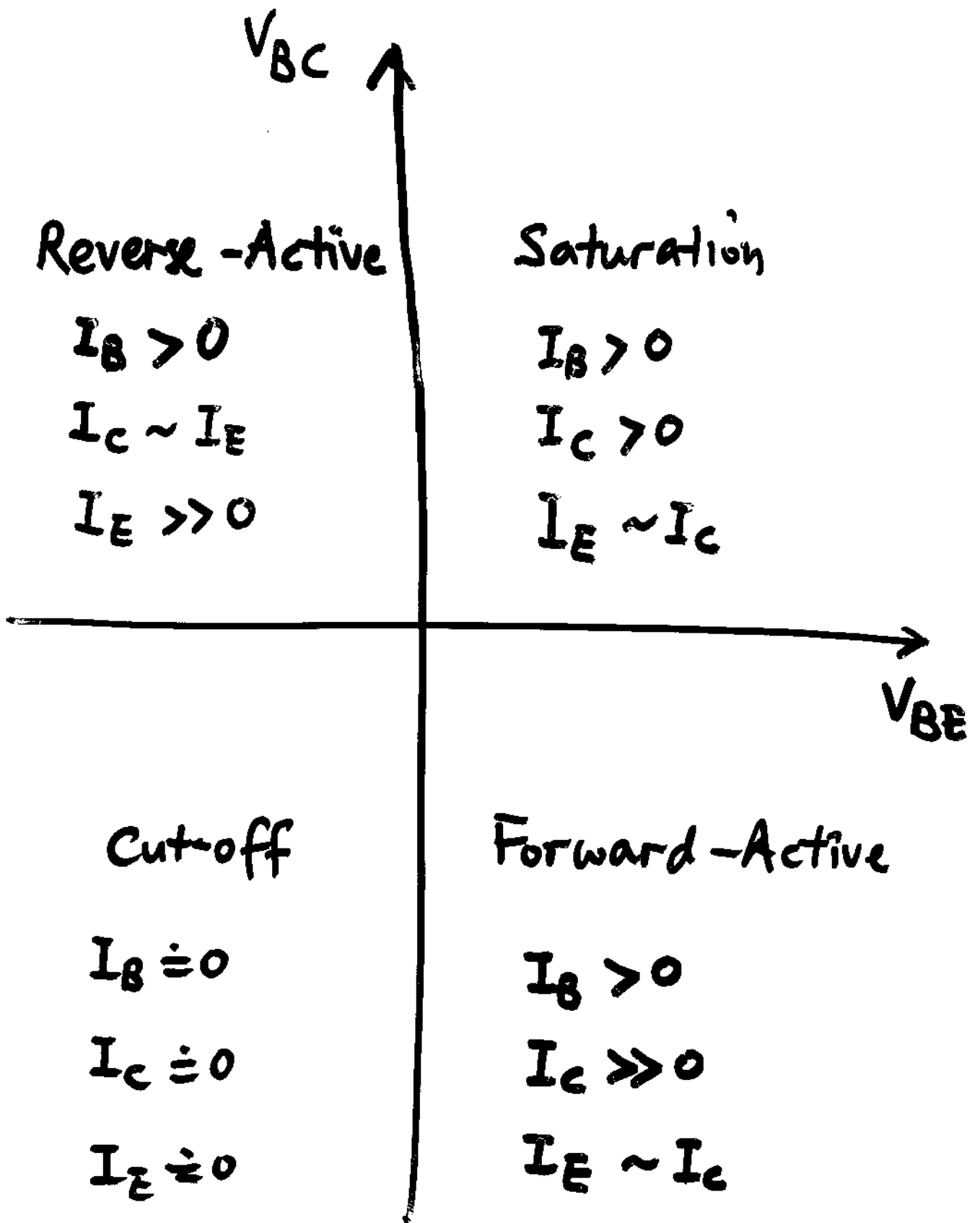

COMMON-EMITTER Configuration

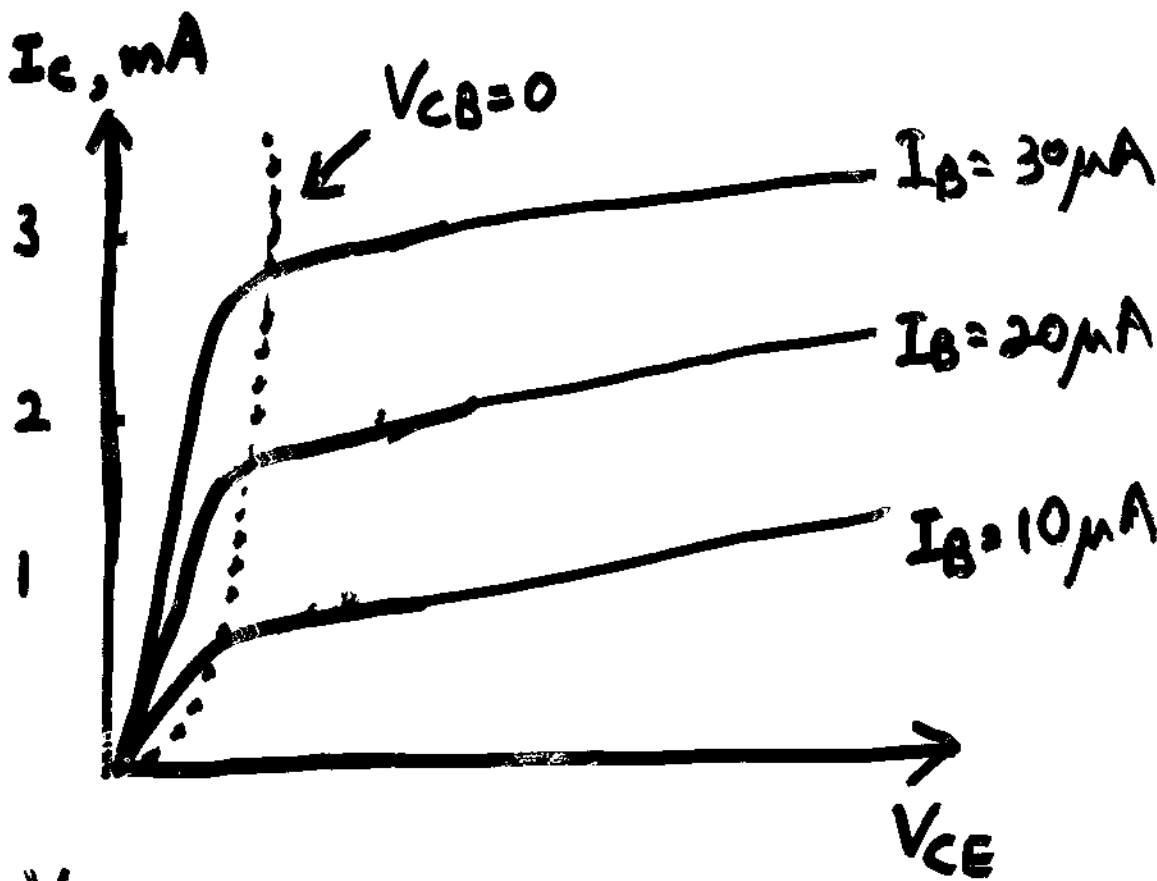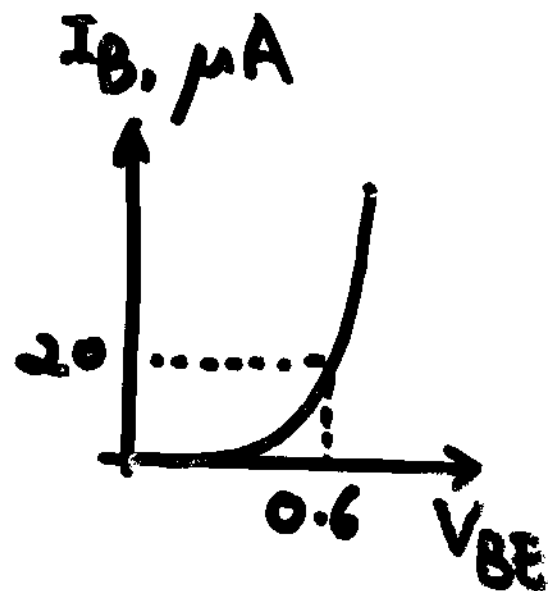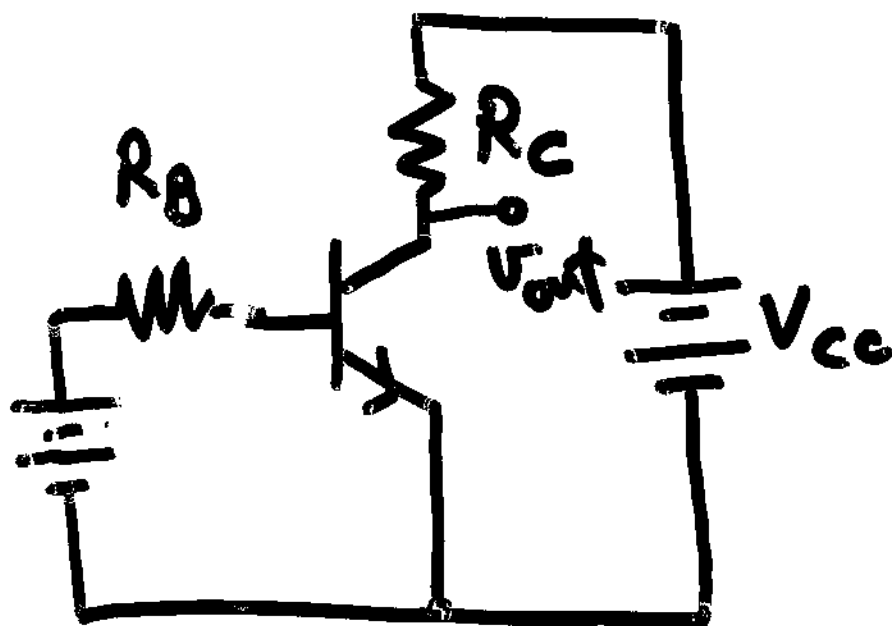

$$V_{CE(SAT)} \approx 0.2 V$$

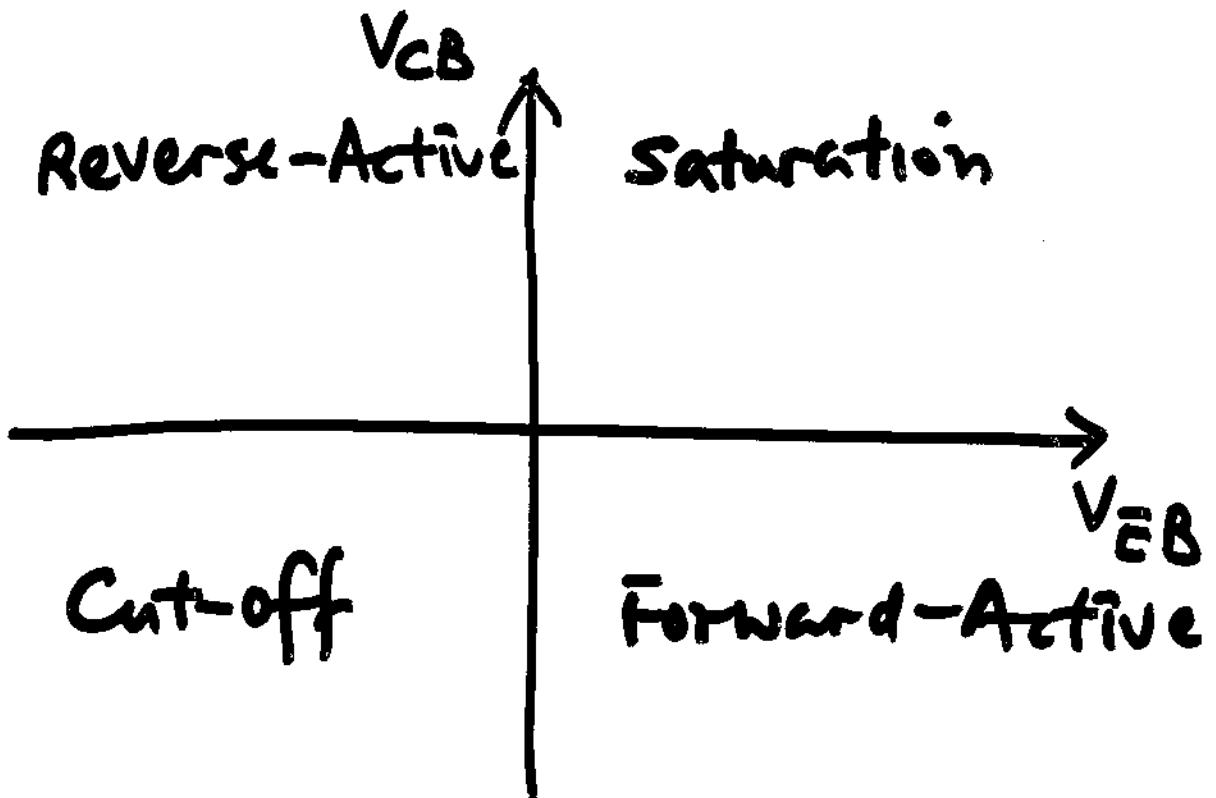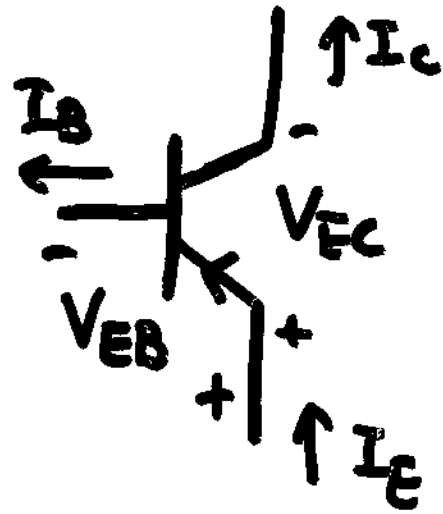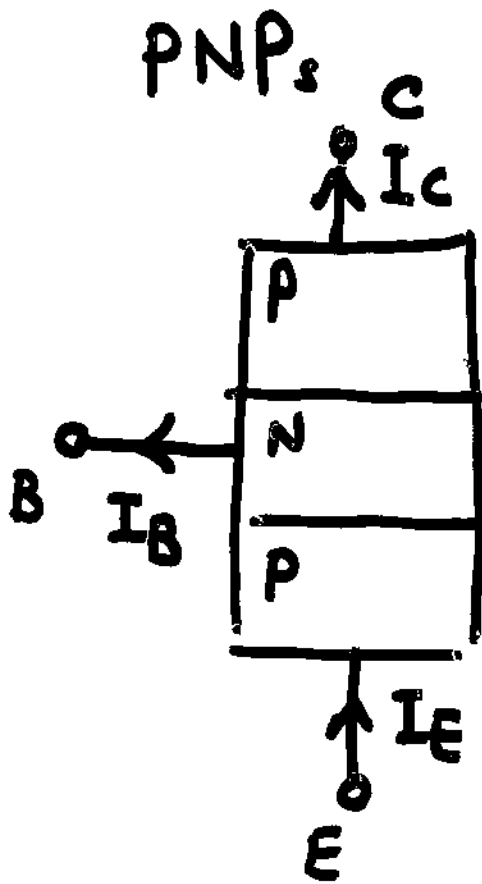

Identify the Regions

