
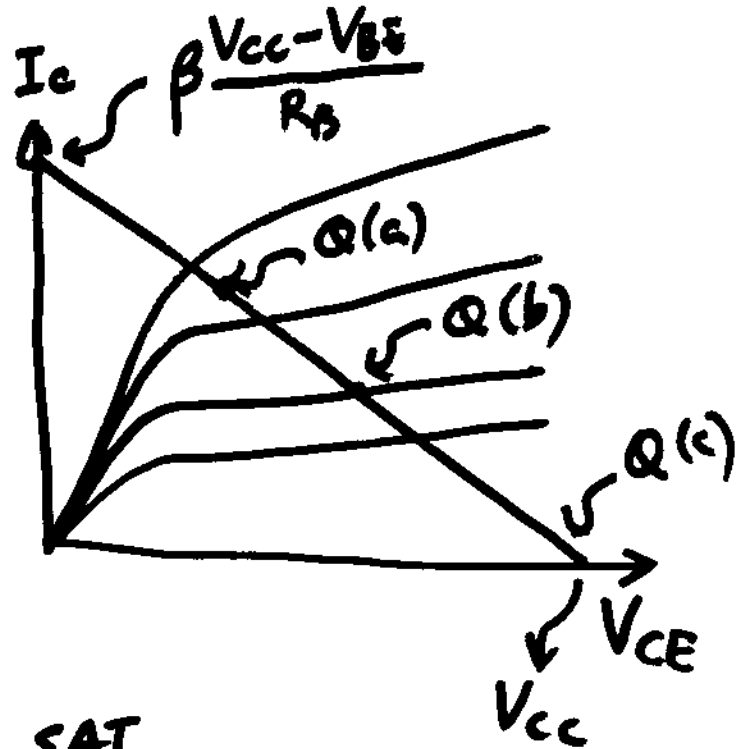


BJT Bias Circuits

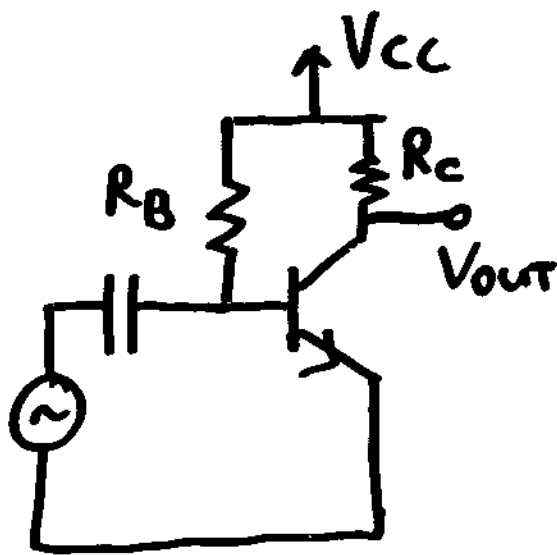

(a) Q-point near SAT

AC signal leads to fluctuation of V_{BE}

⇒ Changes in I_B

⇒ Pushes device into SAT $I_B \neq \frac{I_C}{\beta}$

⇒ Output not ^(linearly) controlled by input

(c) Pushes device into cut-off


⇒ Input cannot control output

(b) I_B fluctuations lead to (linearly) proportional I_C fluctuations

Biassing

- Between the extremes of SAT. and cut-off for max. swing in both directions about Q-point
- A production circuit must be stable with respect to β
- Base-current bias method
 - not practical
 - Quiescent output voltage a strong function of β .
- Emitter-bias stage
 - Good stability with changes in β and temperature

Base-Current Bias

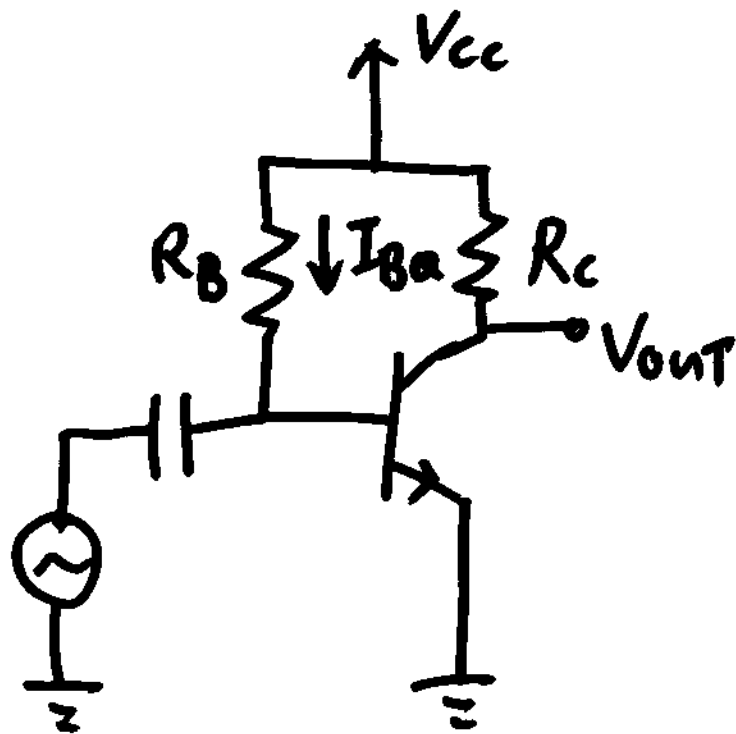

$$R_C = 5\text{k}\Omega$$


$$\beta = 120$$

$$V_{CC} = 20\text{V}$$

Find R_B ?

How about

$\beta = 60$ or 200 ?

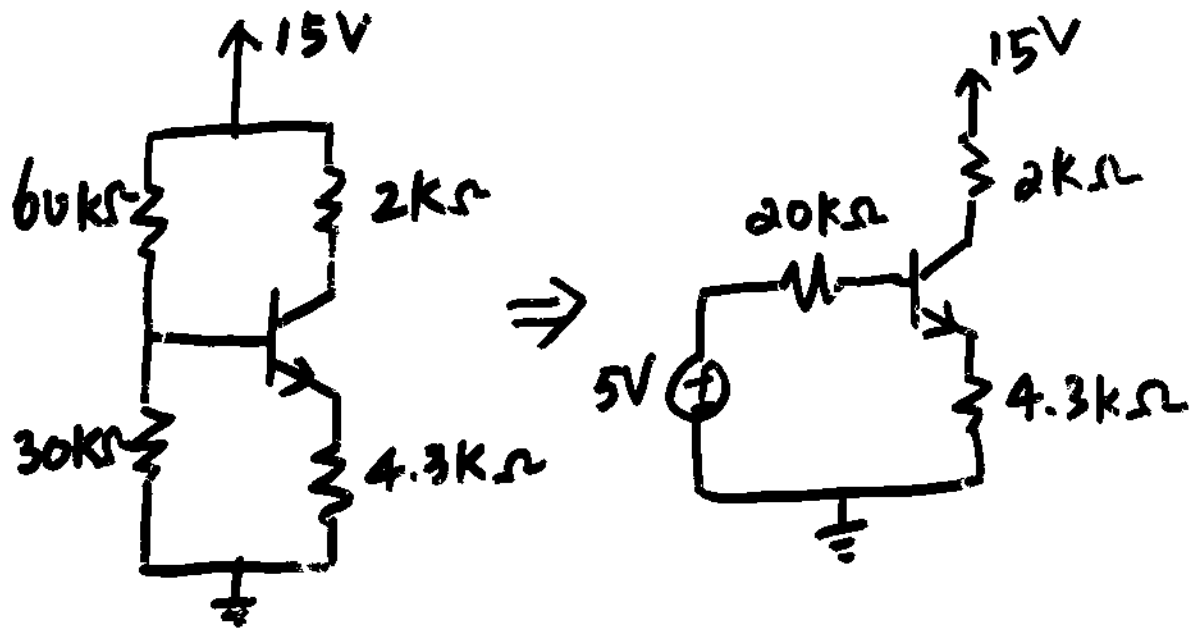

$\beta = 100$ $I_c?$

$\beta = 200$ $I_c?$

$\beta \rightarrow \infty$ $I_c?$

$$I_{BQ} = \frac{V_{TH} - V_{BE}}{R_{TH} + (1 + \beta)R_E}$$


$$V_{CQ} = V_{CC} - R_C \beta \frac{V_{TH} - V_{BE}}{R_{TH} + (1 + \beta)R_E}$$

IF $R_{TH} \ll (1 + \beta)R_E$

$$\begin{aligned} V_{CQ} &= V_{CC} - \frac{\beta R_C}{(1 + \beta)R_E} [V_{TH} - V_{BE}] \\ &= V_{CC} - \alpha \frac{R_C}{R_E} [V_{TH} - V_{BE}] \end{aligned}$$

LARGE variations in $\beta \Rightarrow 1 \sim 2\%$ variations in α .

Why stable?


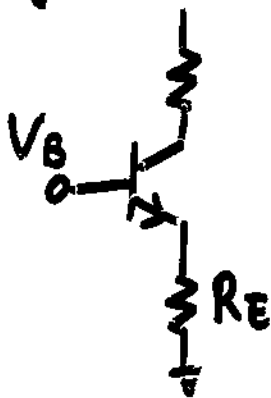


$$I_C \uparrow \Rightarrow V_E \uparrow \Rightarrow V_{BE} \downarrow \Rightarrow I_C \downarrow$$

NEGATIVE FEEDBACK

$$R_{TH} \leq 0.1 (\beta + 1) R_E$$

Emitter Bias

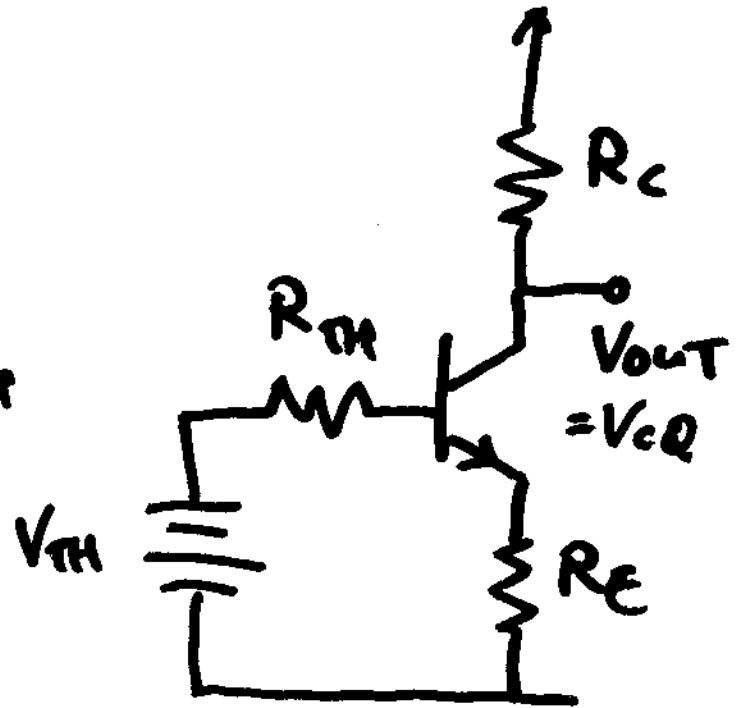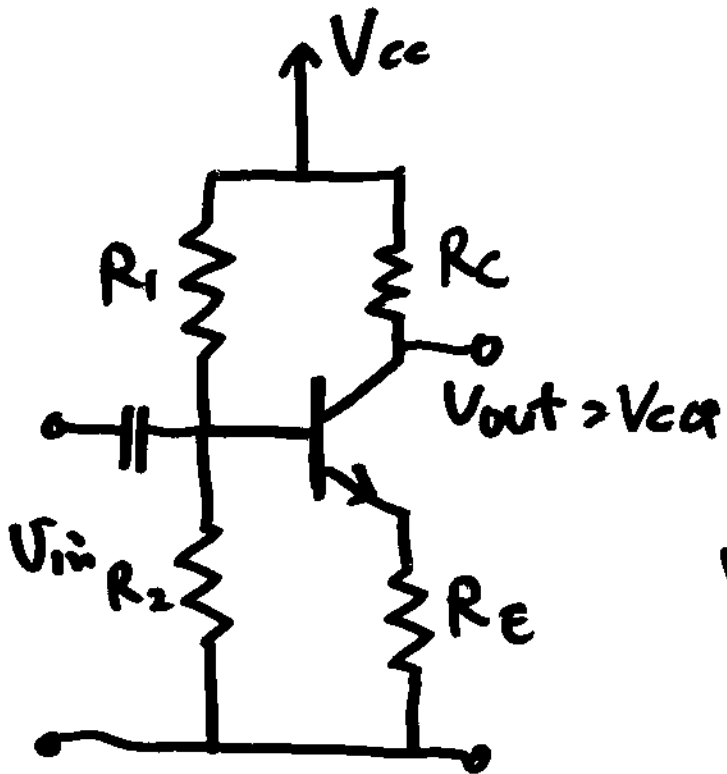

$$V_{TH} = \frac{R_2}{R_1 + R_2} V_{CC}$$



$$R_{TH} = R_1 \parallel R_2$$

$$V_{TH} = R_{TH} I_B + V_{BE} + R_E I_E$$

$$= R_{TH} I_B + V_{BE} + R_E (1 + \beta) I_B$$

$$I_{BQ} = \frac{V_{TH} - V_{BE}}{R_{TH} + (1 + \beta) R_E}$$

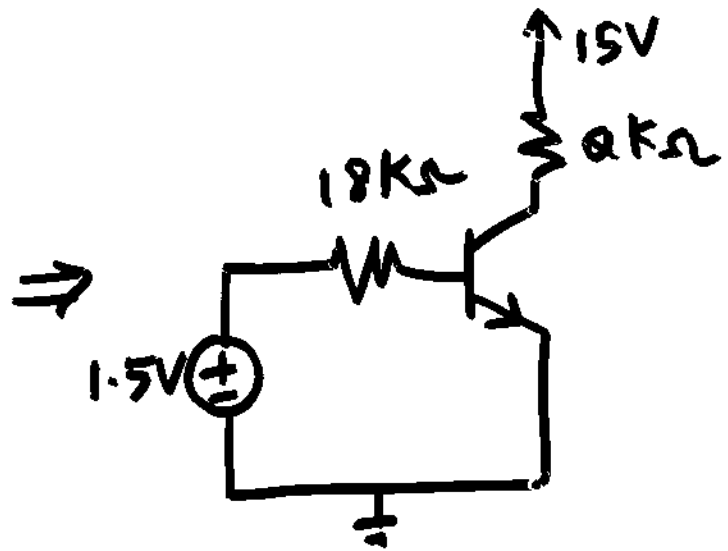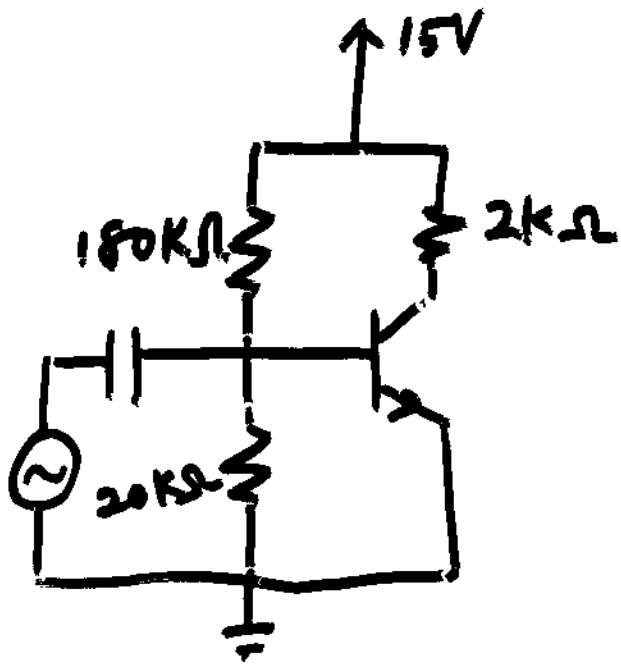$R_E = 0 \Rightarrow$ Base current bias unstable w.r.t. β



$$I_B = \frac{1.5 - 0.7}{18k\Omega} = 44 \mu A$$

$$\beta = 100 \Rightarrow$$

$$\beta = 200 \Rightarrow$$

Where is the center of active region?

$$V_{C_{MAX}} = V_{CC} \text{ (cut-off)}$$


$$V_{C_{MIN}} = \frac{R_E}{R_E + R_C} V_{CC}$$

$$V_{CQ} = \frac{V_{C_{MAX}} + V_{C_{MIN}}}{2} = \frac{V_{CC}}{2} \left(1 + \frac{R_E}{R_E + R_C} \right)$$

$$\Rightarrow V_{CE} = \frac{V_{CC}}{2}$$

Design pointers:

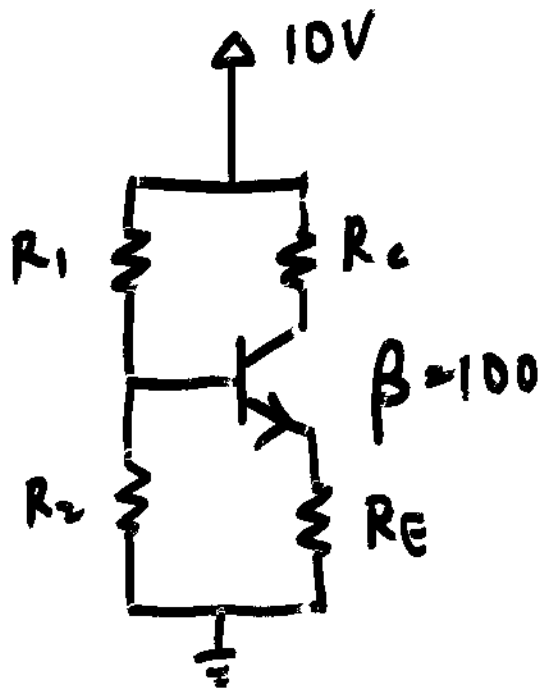- ① Choose $R_2 = 10 \sim 20 \times R_E$
- ② Choose R_E s.t. $V_{R_E} = V_{BE(ON)}$



$$I_c = 1\text{mA}$$