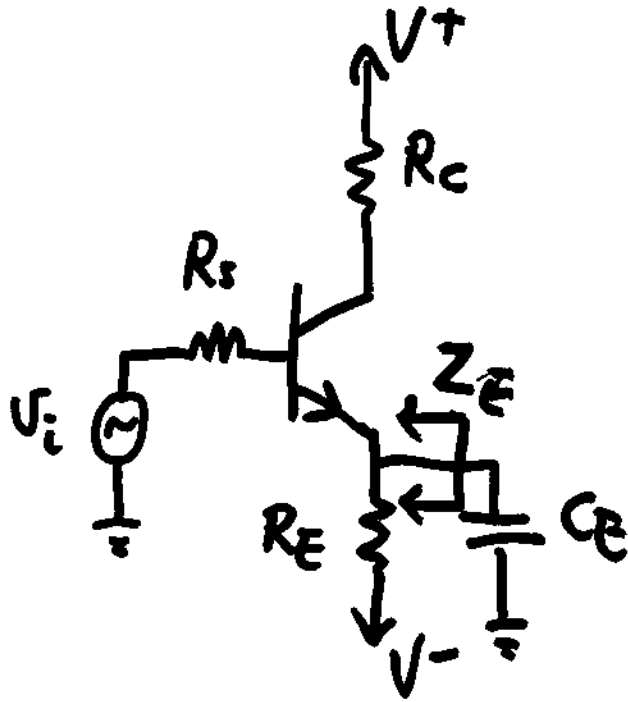


By-pass Capacitor

$$A_v = \frac{-g_m r_{\pi} R_c}{R_s + r_{\pi} + (1 + \beta) R_E}$$

$$\frac{1 + j\omega R_E C_E}{1 + \frac{j\omega R_E (R_s + r_{\pi}) C_E}{R_s + r_{\pi} + (1 + \beta) R_E}}$$



$$= \frac{-g_m r_{\pi} R_c}{R_s + r_{\pi} + (1 + \beta) R_E}$$

$$\frac{1 + j\omega \tau_A}{1 + j\omega \tau_B}$$


$$\tau_A = R_E C_E$$

$$\tau_B = Z_E C_E$$

$$\tau_A > \tau_B$$

$$\omega \rightarrow 0, \quad A_{v, \omega \rightarrow 0} = \frac{-g_m r_{\pi} R_c}{R_s + r_{\pi} + (1 + \beta) R_E}$$
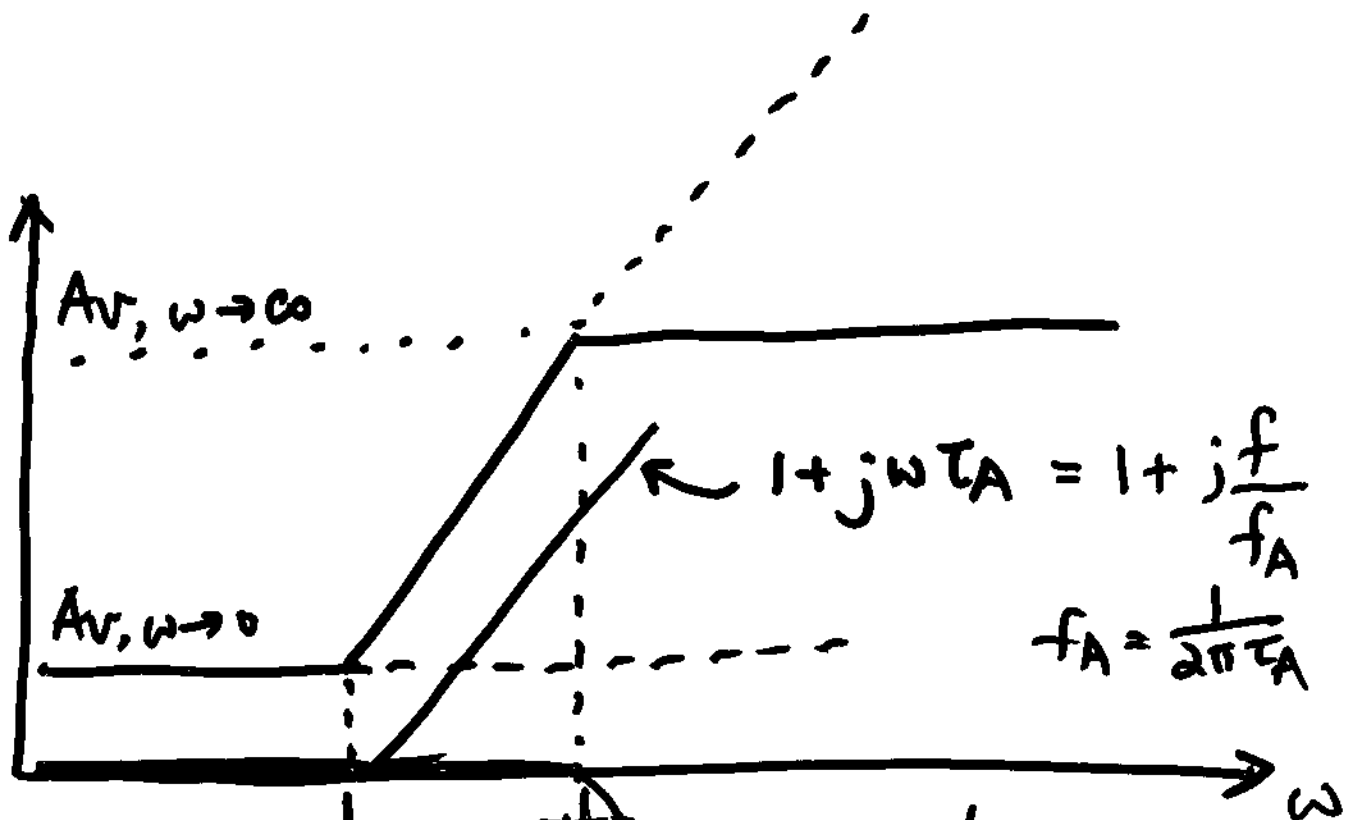
$$\omega \rightarrow \infty, \quad A_{v, \omega \rightarrow \infty} = \frac{-g_m r_{\pi} R_c}{R_s + r_{\pi}}$$



$$1 + j\omega\tau_A = 1 + j\frac{f}{f_A}$$

$$f_A = \frac{1}{2\pi\tau_A}$$

$$\frac{1}{1 + j\omega\tau_B}$$

$$= \frac{1}{1 + j\frac{f}{f_B}}$$

$$f_B = \frac{1}{2\pi\tau_B}$$