
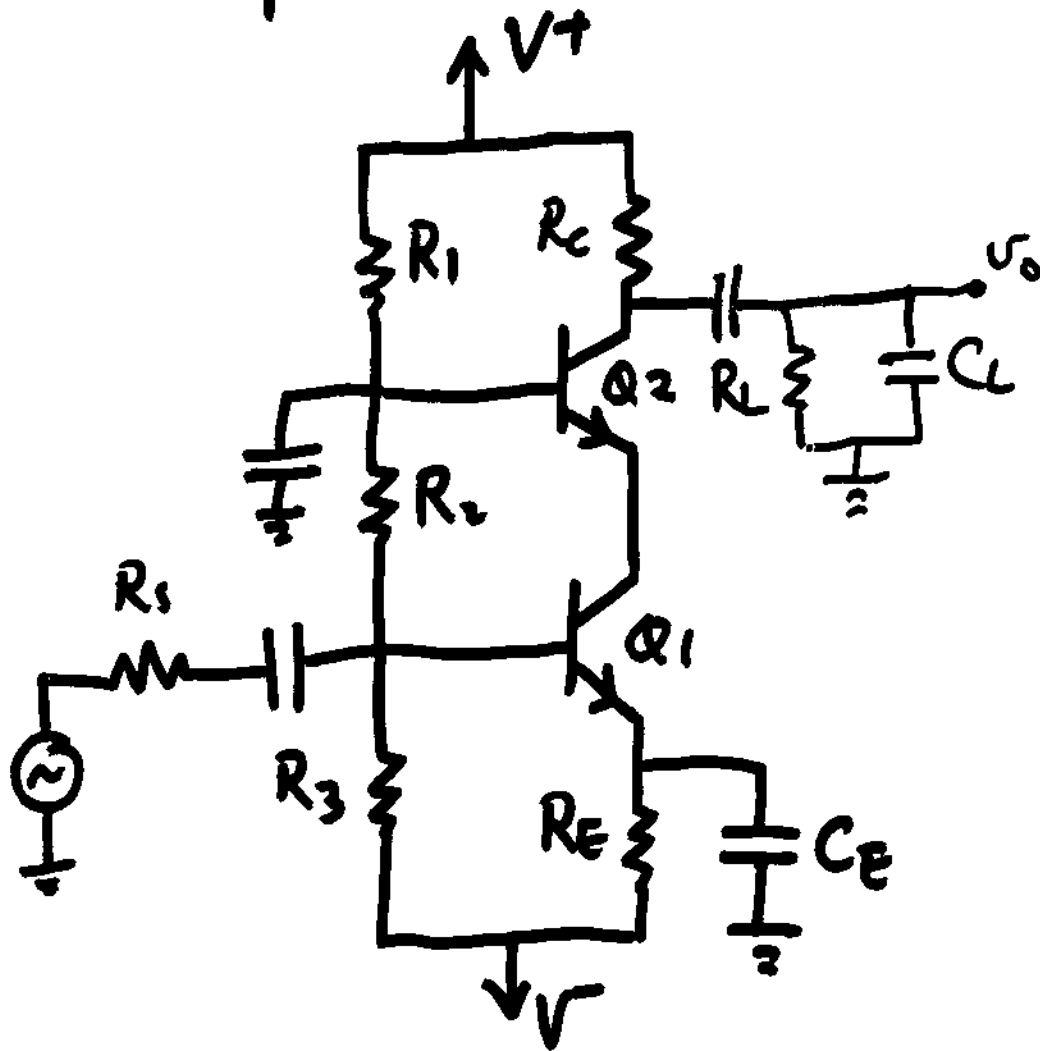


CE-CB Amplifier (Cascode)

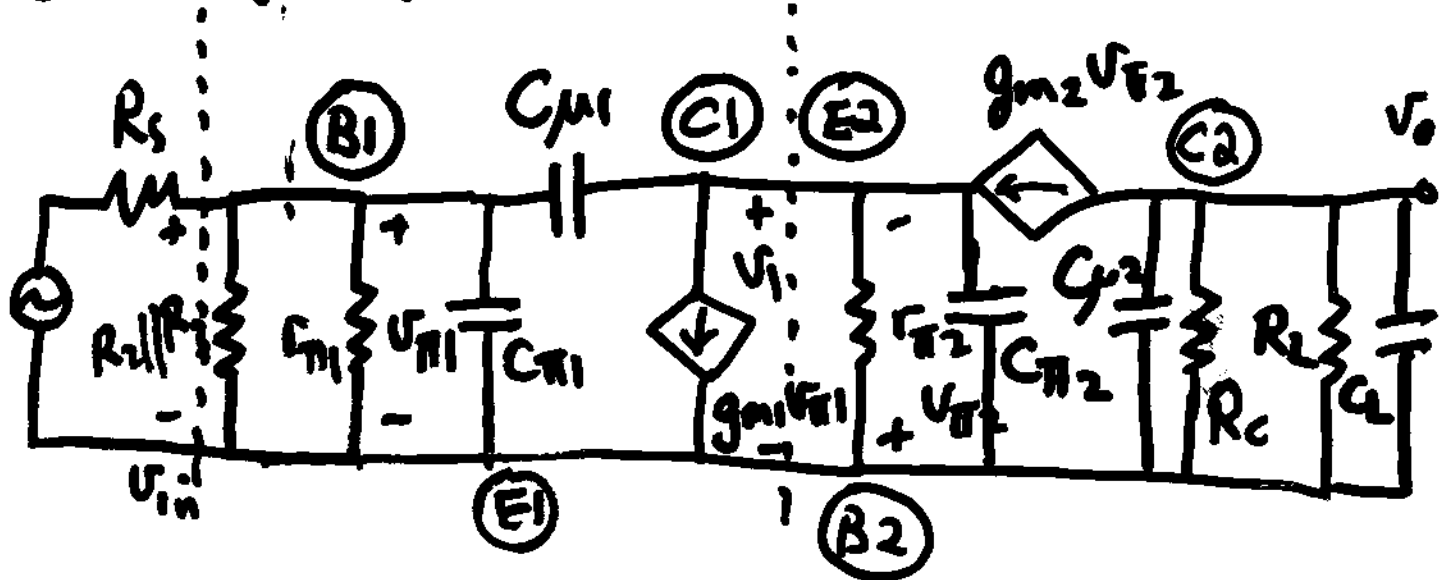

High-frequency equiv. ckt



Miller Effect

$$A_{v_i} = \frac{V_i}{V_{in}}$$

$$= -g_{m1} \frac{r_{\pi 2}}{\beta_2 + 1}$$


If $\beta_1 = \beta_2$, $I_{C1} \cong I_{C2}$, $I_{B1} \cong I_{B2}$

$g_{m1} \cong g_{m2}$, $r_{\pi 1} \cong r_{\pi 2}$

$$A_{v_i} \cong -\frac{\beta}{\beta + 1}$$

insignificant
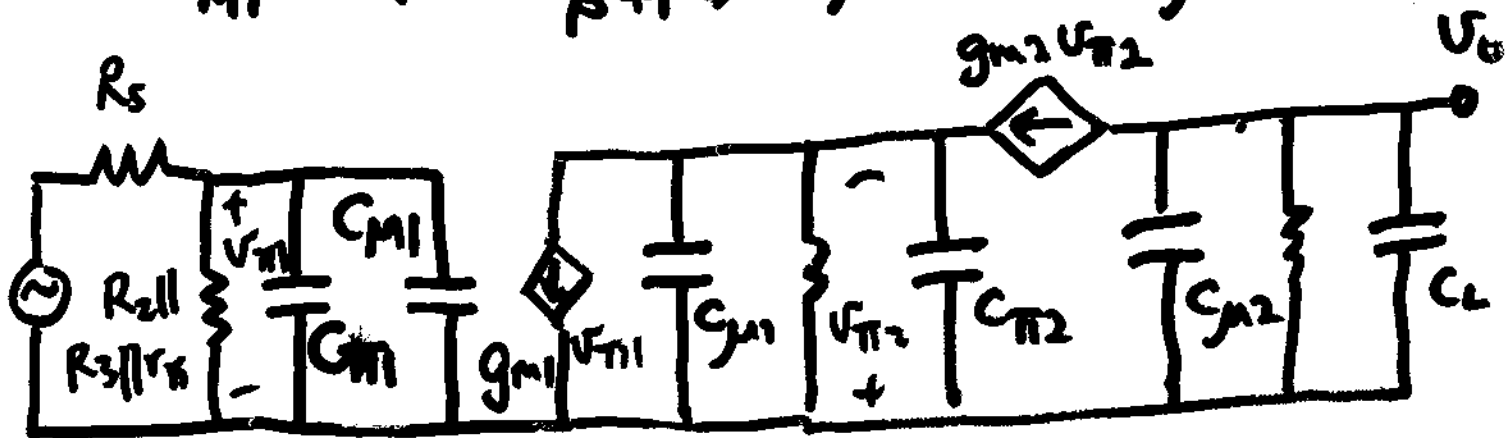
$$C_{M1} = \left(1 - \left(-\frac{\beta}{\beta + 1}\right)\right) C_{\mu 1} \cong 2 C_{\mu 1}$$



$$R_{\pi 1} = R_s \parallel R_2 \parallel R_3 \parallel r_{\pi 1}$$

$$R_{\mu 1} = (R_s \parallel R_2 \parallel R_3 \parallel r_{\pi 1}) \left(1 + g_{m1} \frac{r_{\pi 2}}{\beta + 1} \right) + \frac{r_{\pi 2}}{\beta + 1}$$


$$R_{\pi 2} = \frac{r_{\pi 2}}{\beta + 1}$$

$$R_{\mu 2} = R_c \parallel R_L$$

$$R_{cL} = R_c \parallel R_L$$

$$\omega_H \approx \frac{1}{\tau_{\pi 1} + \tau_{\mu 1} + \tau_{\pi 2} + \tau_{\mu 2} + \tau_{cL}}$$

Cascode Example

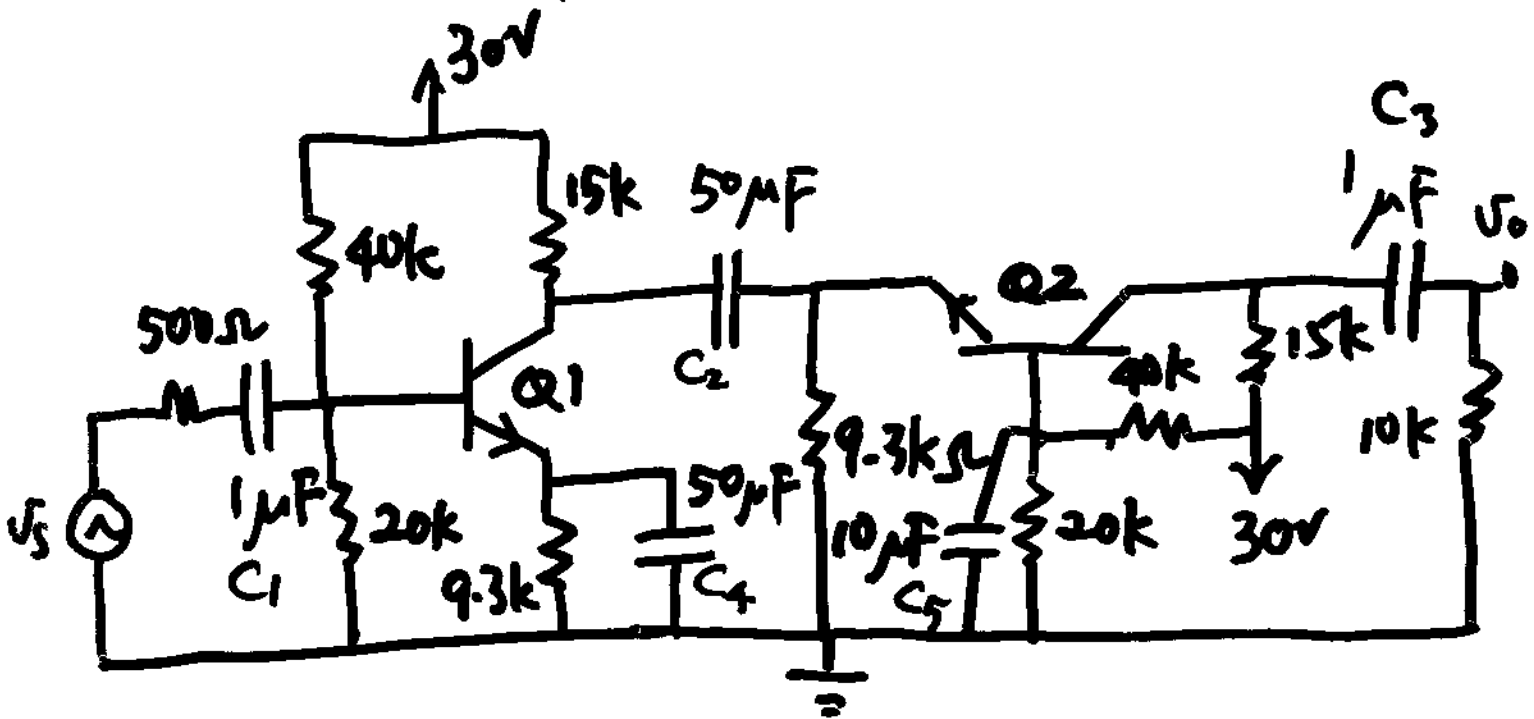


$\beta = 150$, $V_{BE(ON)} = 0.7V$
 $f_T = 500MHz$ @ $I_C = 2mA$
 $C_{\mu} = 0.3pF$ @ $V_{CB} = 5V$

Note: The two stages are identical

DC analysis : $I_{C1} \approx I_{B1} = 1mA$
 $V_{CB} = 5V$

AC analysis : $g_m = 38.5 mA/V$
 $r_{\pi} = \frac{\beta}{g_m} = 3.9k\Omega$

Mid-frequency Analysis

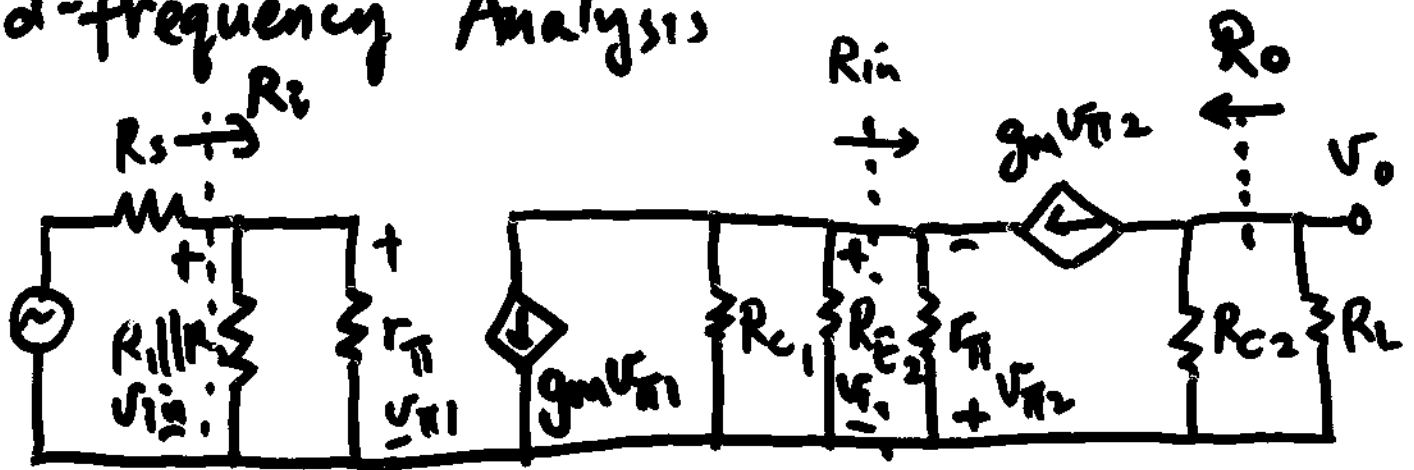

$$A_{v_1} = \frac{v_1}{v_{in}} = -g_m (R_{c1} \parallel R_{E2} \parallel \frac{r_{\pi}}{\beta+1})$$

$$= -0.99 \text{ V/V}$$

$$A_{v_2} = \frac{v_o}{v_1} = +g_m (R_{c2} \parallel R_L)$$

$$= +231 \text{ V/V}$$

$$A_v = \frac{v_o}{v_{in}} = -229$$

$$R_i = R_1 \parallel R_2 \parallel r_{\pi} = 3 \text{ k}\Omega$$

$$R_o = R_{c2} = 15 \text{ k}\Omega$$

Low Frequency :

$$R_{C1,eq} = R_s + R_1 \parallel R_2 \parallel r_{\pi} \quad O(k\Omega)$$

$$R_{C2,eq} = R_{C1} + R_{E2} \parallel \frac{r_{\pi}}{\beta+1} \quad O(k\Omega)$$

$$R_{C3,eq} = R_{C2} + R_L \quad O(k\Omega)$$

$$R_{C4,eq} = R_{E1} \parallel \frac{r_{\pi} + R_1 \parallel R_2 \parallel R_s}{\beta+1} \quad O(10\Omega)$$

$$R_{C5,eq} = R_1 \parallel R_2 \parallel [r_{\pi} + (\beta+1)R_{E2} \parallel R_{C1}] \quad O(k\Omega)$$

$R_{C4,eq}$ dominates

$$\omega_L \approx \frac{1}{R_{C4,eq} C_4} \approx \frac{1}{30\Omega \times 50\mu F}$$

$$\approx 667 \text{ rad/s}$$

$$\approx 105 \text{ Hz}$$

High Frequency:

Calculate for C_{π} first

$$f_T = 500 \text{ MHz} @ I_C = 2 \text{ mA}$$

$$\text{Assume } f_T \propto I_C \Rightarrow f_T = 250 \text{ MHz} @ I_C = 1 \text{ mA}$$

$$f_T = \frac{g_m}{2\pi(C_{\pi} + C_{\mu})}$$

$$C_{\pi} = \frac{g_m}{2\pi f_T} - C_{\mu}$$

$$\approx 24.2 \text{ pF}$$

$$R_{\pi 1, eq} = (R_s \parallel R_1 \parallel R_2 \parallel r_{\pi})$$

$$= 430 \Omega$$

$$\tau_{\pi 1} = R_{\pi 1, eq} C_{\pi 1} = 10.4 \text{ ns}$$

$$R_{\pi 2, eq} = R_{C1} \parallel R_{E2} \parallel \left(\frac{r_{\pi}}{\beta + 1} \right)$$

$$= 26 \Omega$$

$$\tau_{\pi 2} = 0.63 \text{ ns}$$

$$R_{\mu 1, eq} = (R_s \parallel R_1 \parallel R_2 \parallel r_{\pi}) \left(1 + g_m (R_{C1} \parallel R_{E2} \parallel \frac{r_{\pi}}{\beta + 1}) \right)$$

$$+ (R_{C1} \parallel R_{E2} \parallel \frac{r_{\pi}}{\beta + 1})$$

$$= 886 \Omega$$

$$\tau_{\mu 1} = 0.27 \text{ ns} \leftarrow \text{does not dominate}$$

$$R_{\mu 2, eq} = R_{C2} \parallel R_L = 6 \text{ k}$$

$$\tau_{\mu 2} = 1.8 \text{ ns}$$

$$\frac{1}{\Sigma \tau} < \omega_H < \frac{1}{\tau_{\pi 1}}$$

$$12.1 \text{ MHz} < f_H < 15.3 \text{ MHz}$$