
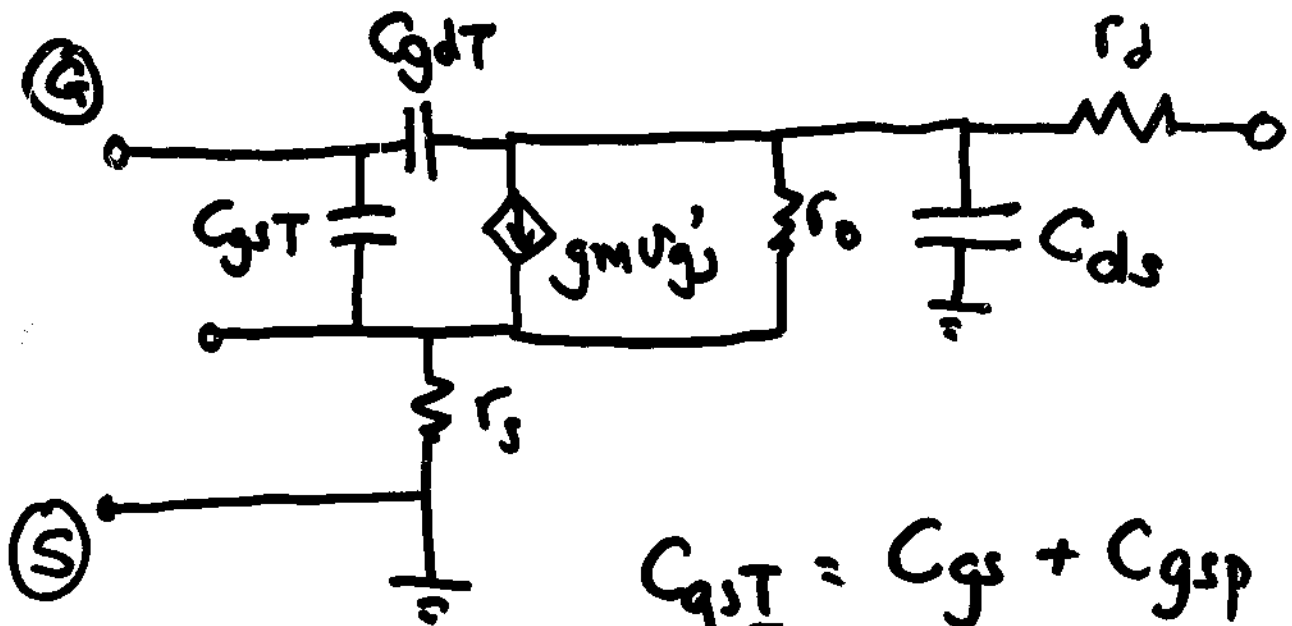


High Frequency MOSFET Transistor Model

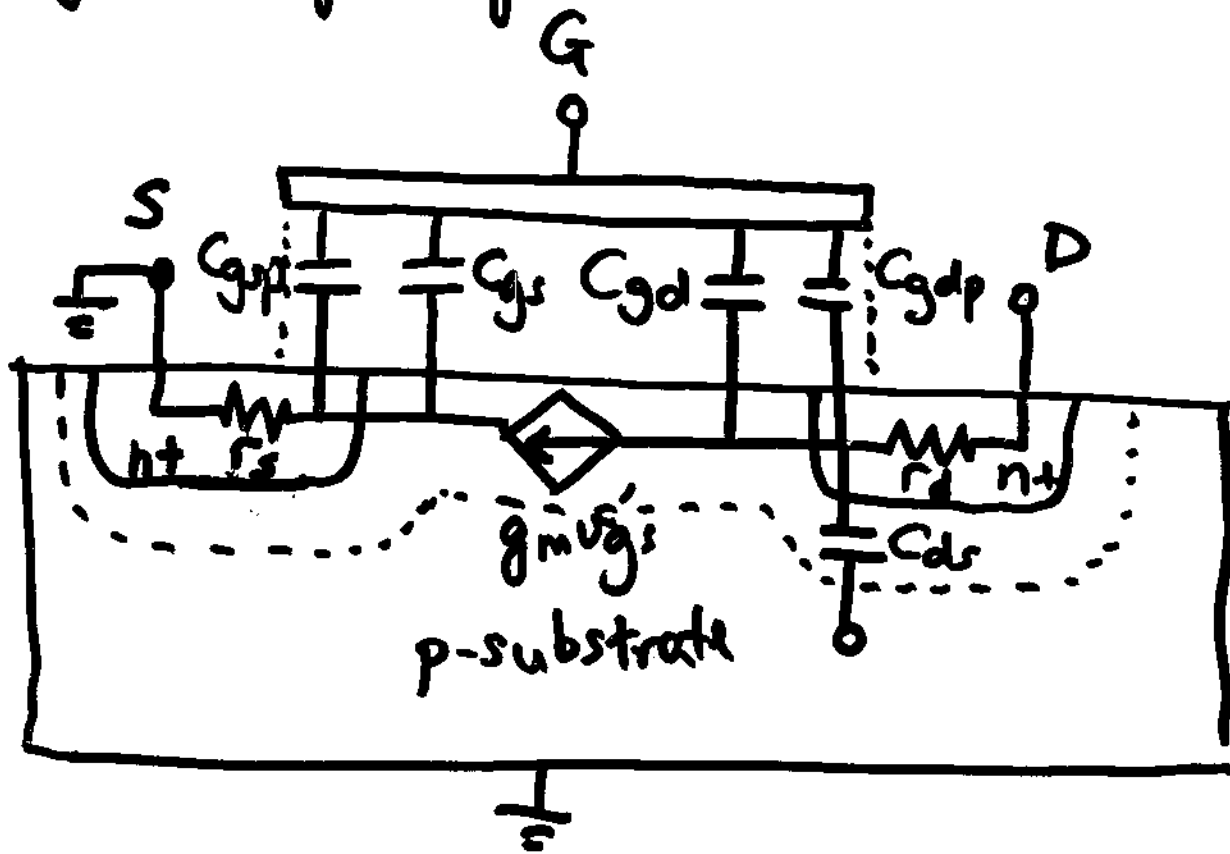

$$C_{gsT} = C_{gs} + C_{gsp}$$

$$C_{gdT} = C_{gd} + C_{gdp}$$

$$\approx C_{gdp}$$

will drop
subscript T
later on

Capacitances:

① Gate a inversion layer

$$C_{gs} \cong C_{gd} \cong \left(\frac{1}{2}\right) WL C_{ox} \quad \text{Non-sat}$$

$$C_{gs} \cong \frac{2}{3} WL C_{ox} \quad \text{SAT}$$

* $C_{gd} = 0$ (inversion layer disappears)

$$C_{gb} = WL C_{ox} \quad \begin{array}{l} \text{cut-off} \\ \text{[TOX in spice]} \end{array}$$

② Overlap capacitance

$$C_{gsp} = C_{gdp} = C_{ox} \underbrace{LD}_\downarrow W$$

[overlap in spice]

[CGSO & CGDO in spice]

③ Junction capacitance

Drain is R.B wrt substrate

[CBD in spice]

Resistances


1. r_d : Drain resistance

silicon resistance

$\sim 10 \Omega$ (R_D in $\text{spi}u$)

2. r_s : Similar to r_d (R_S in $\text{spi}u$)

Unity-gain bandwidth (Cut-off freq.)

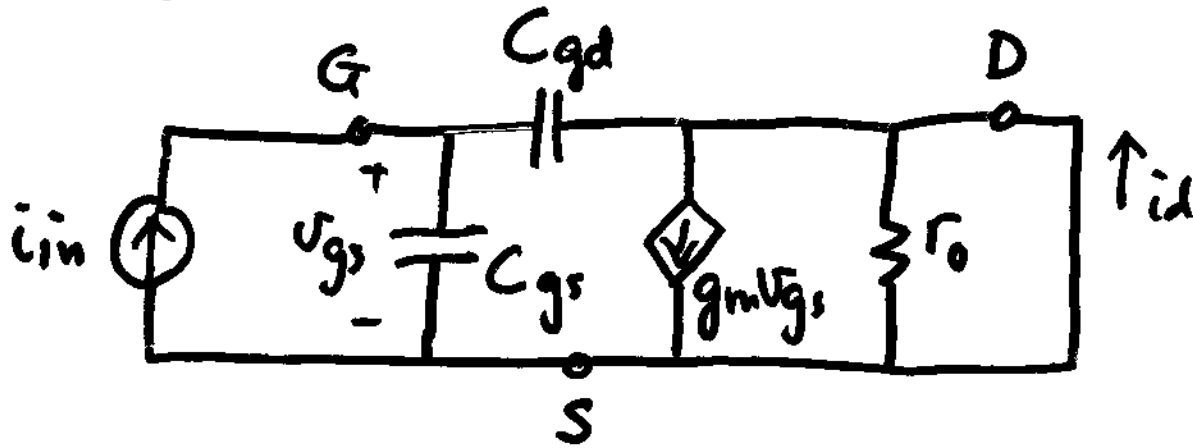

(Analogous to BJT with $\beta \rightarrow \infty$, $r_{\pi} \rightarrow \infty$)


$$\omega_{T, BJT} = \frac{g_m}{C_{\pi} + C_{\mu}} \quad \left(\frac{\beta}{r_{\pi}} \rightarrow g_m \right)$$

$$i_{in} \cdot \frac{1}{j\omega(C_{gs} + C_{gd})} = v_{gs}$$


$$i_d = g_m \frac{i_{in}}{j\omega(C_{gs} + C_{gd})}$$

Current gain $\frac{i_d}{i_{in}} = \frac{g_m}{j\omega(C_{gs} + C_{gd})}$

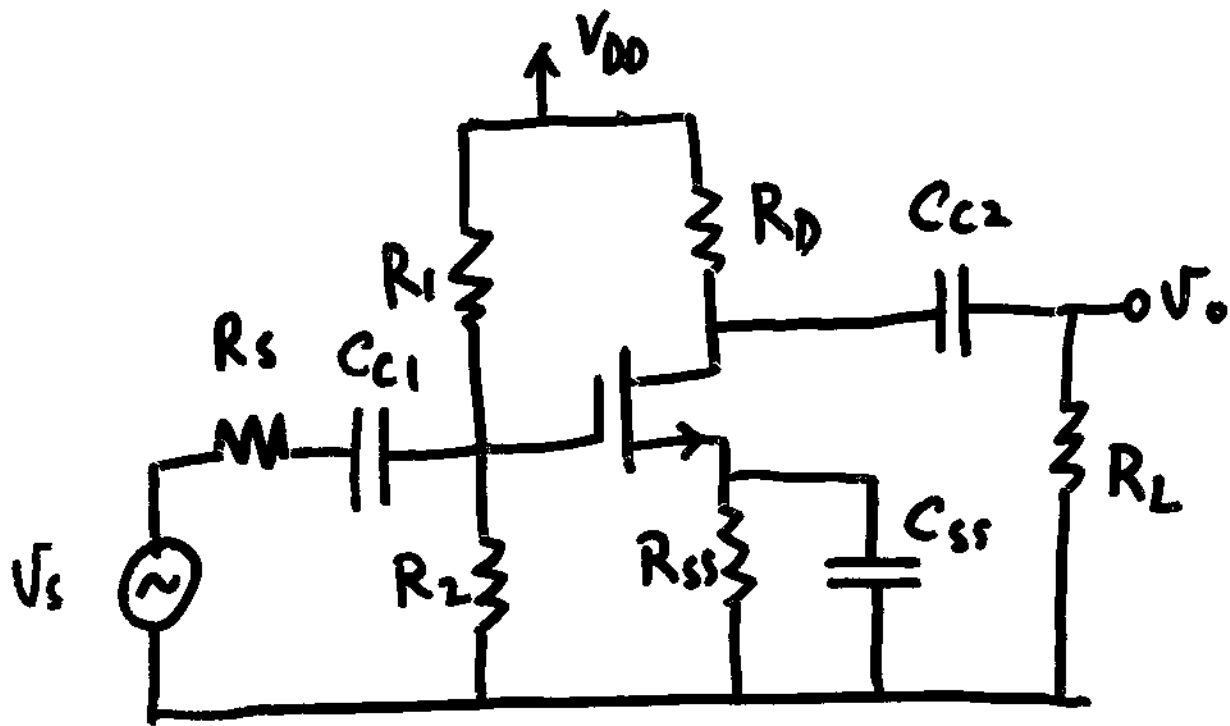Unity-gain bandwidth, $\omega_T = \frac{g_m}{C_{gs} + C_{gd}}$



High frequency model

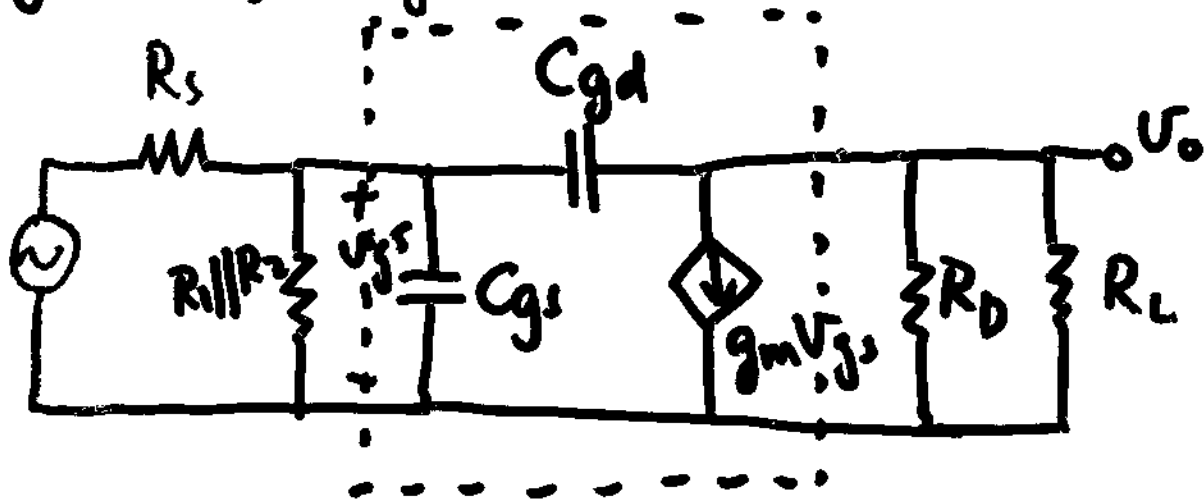


Similar to BJT with $r_{\pi} = \infty$

$$C_{\pi} = C_{gs}$$

$$C_{\mu} = C_{gd}$$

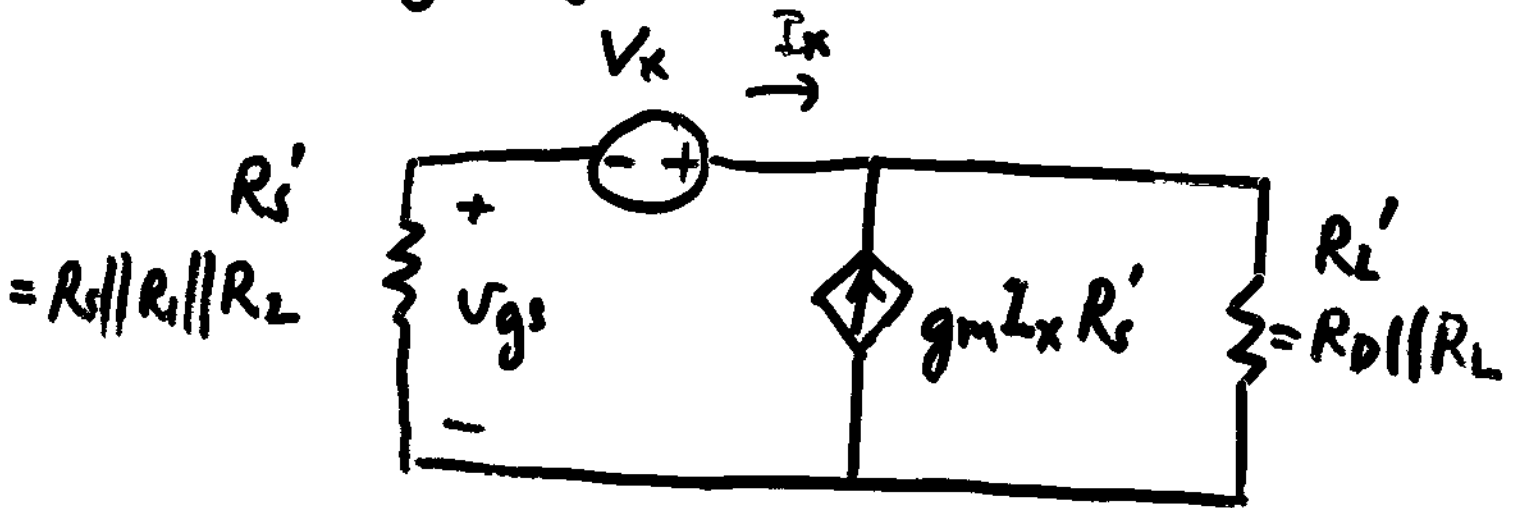R_{gd} : Thevenin Equiv. Resistance seen by C_{gd}



$$V_x = [I_x + g_m I_x R_s'] R_L' + I_x R_s'$$

$$R_{gd} = \frac{V_x}{I_x} = (1 + g_m R_s') R_L' + R_s'$$

$$= R_s' (1 + g_m R_L') + R_L'$$

$$\tau_{gd} = R_{gd} C_{gd} = R_s' (1 + g_m R_L') C_{gd} + R_L' C_{gd}$$

$$(1 - A_{v_i}) C_{gd} = C_M$$

$$R_{gs} = R_s \parallel R_1 \parallel R_2$$

$$\omega_H \approx \frac{1}{\tau_{gs} + \tau_{gd}}$$

$$\tau_{gs} = (R_s \parallel R_1 \parallel R_2) C_{gs}$$