
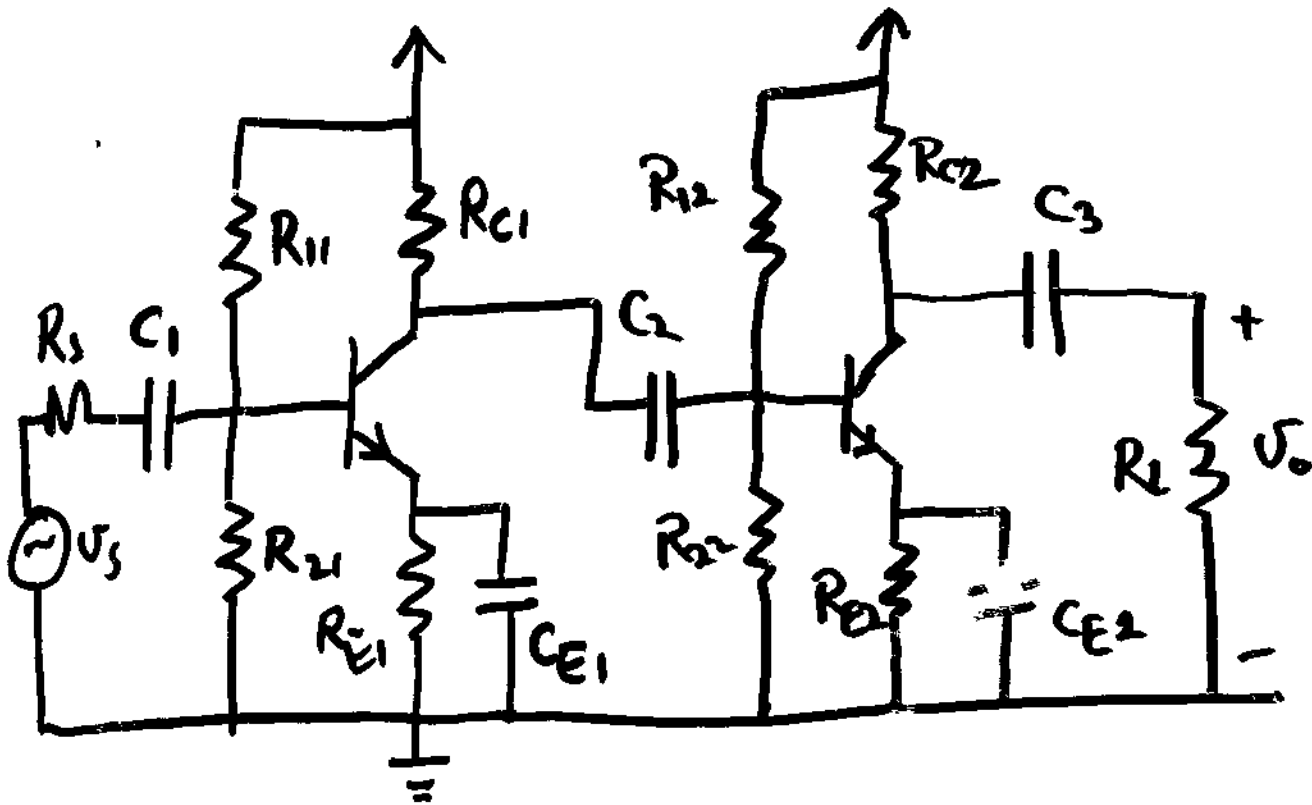


CE-CE Amplifier

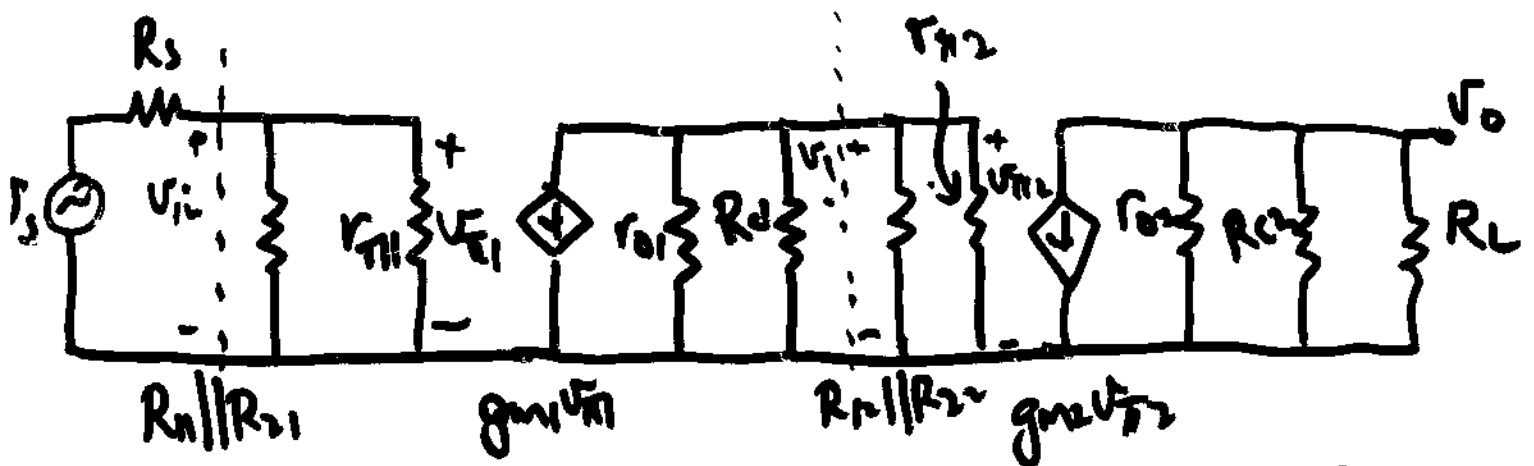

Midband Model




$$A_{v1} = \frac{v_{\pi 1}}{v_{\pi 1in}} = -g_{m1} (r_{O1} \parallel R_{C1} \parallel R_{12} \parallel R_{22} \parallel r_{\pi 2})$$

$$A_{v2} = \frac{v_o}{v_{\pi 2}} = -g_{m2} (r_{O2} \parallel R_{C2} \parallel R_L)$$

$$A_{vS} = \frac{v_o}{v_s} = \frac{R_N \parallel R_{21} \parallel r_{\pi 1}}{R_N \parallel R_{21} \parallel r_{\pi 1} + R_S} A_{v1} \cdot A_{v2}$$

Low Frequency Model

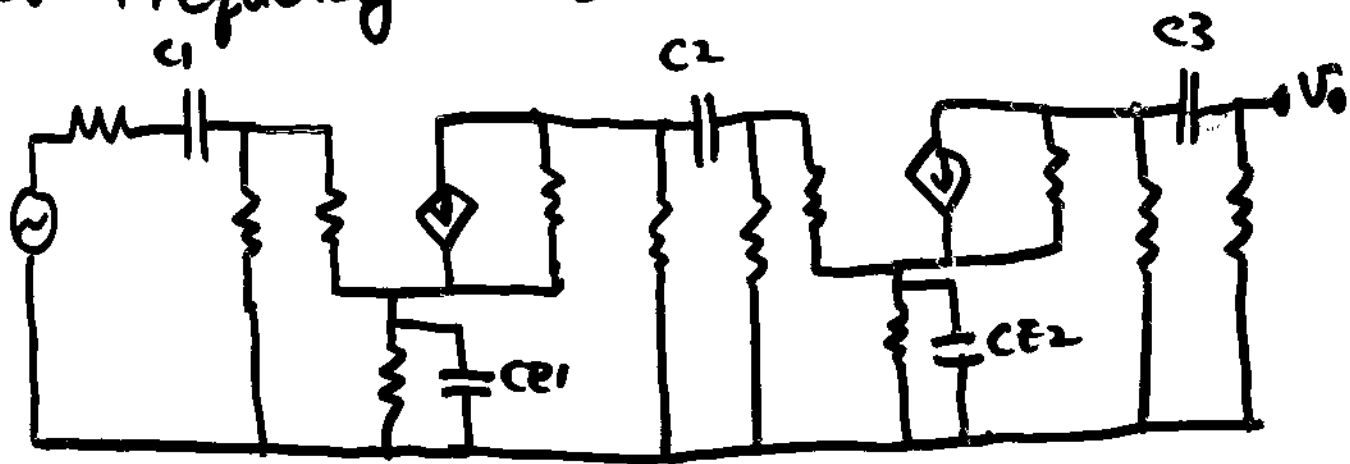

$$R_{c1, eq} = R_S + R_{B1} \parallel R_{B21} \parallel r_{\pi 1}$$


$$R_{c2, eq} = R_{C1} \parallel r_{o1} + R_{E2} \parallel (R_{B22} \parallel r_{\pi 2})$$

$$R_{c3, eq} = R_L + r_{o2} \parallel R_{E2}$$

$$R_{cE1, eq} = R_{E1} \parallel \left. \frac{r_{\pi 1} + R_S \parallel R_{B11} \parallel R_{B21}}{\beta_1 + 1} \right\} \quad \left. \begin{array}{l} \text{(Assume } r_{o1} = \infty) \\ r_{o2} = \infty \end{array} \right\}$$

$$R_{cE2, eq} = R_{E2} \parallel \left. \frac{r_{\pi 2} + R_{C2} \parallel R_{B22} \parallel R_{L}}{\beta_2 + 1} \right\} \rightarrow \text{The other corner defined by } R_{E1} C_{E1} \text{ or } R_{E2} C_{E2}$$

High Frequency Model

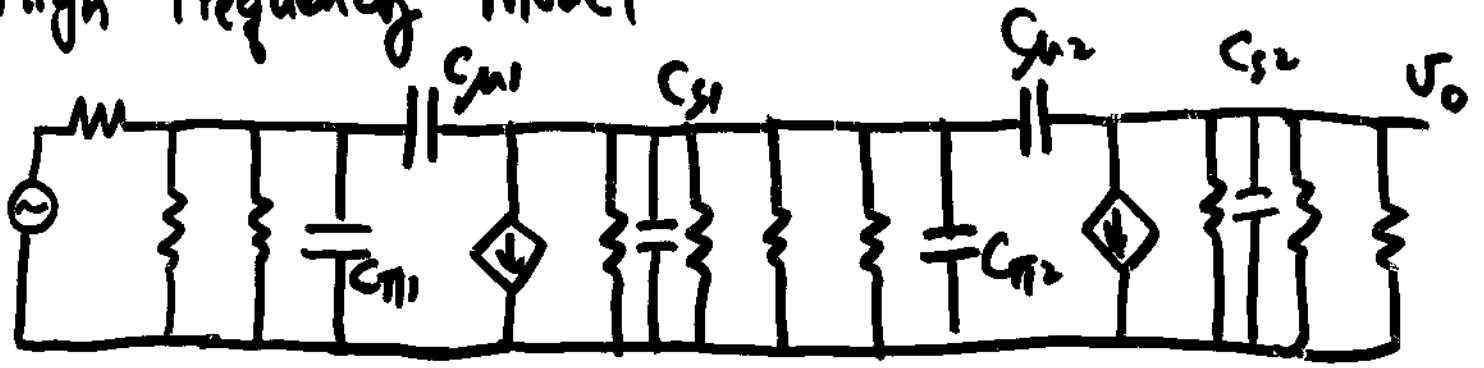

$$R_{\pi 1, eq} = R_s \parallel R_{i1} \parallel R_{e1} \parallel r_{\pi 1}$$

$$R_{\pi 2, eq} = r_{o1} \parallel R_{c1} \parallel R_{i2} \parallel R_{e2} \parallel r_{\pi 2}$$


$$R_{cs1, eq} = R_{\pi 2, eq}$$

$$R_{cs2, eq} = R_{c2} \parallel R_L \parallel r_{o2}$$



$$R_{\mu 1, eq} = R_{\pi 1, eq} \times (1 - A_{v1}) + R_{cs1, eq}$$

$$R_{\mu 2, eq} = R_{\pi 2, eq} \times (1 - A_{v2}) + R_{cs2, eq}$$

Active loads

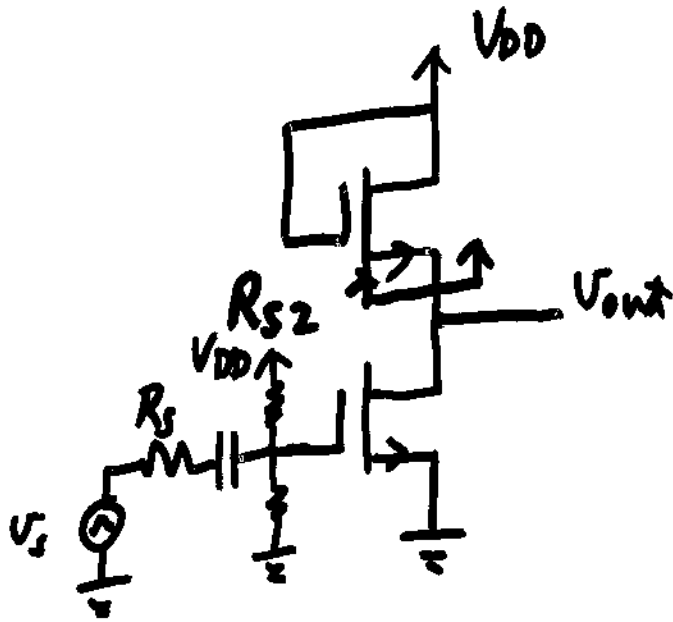


Equiv. ckt

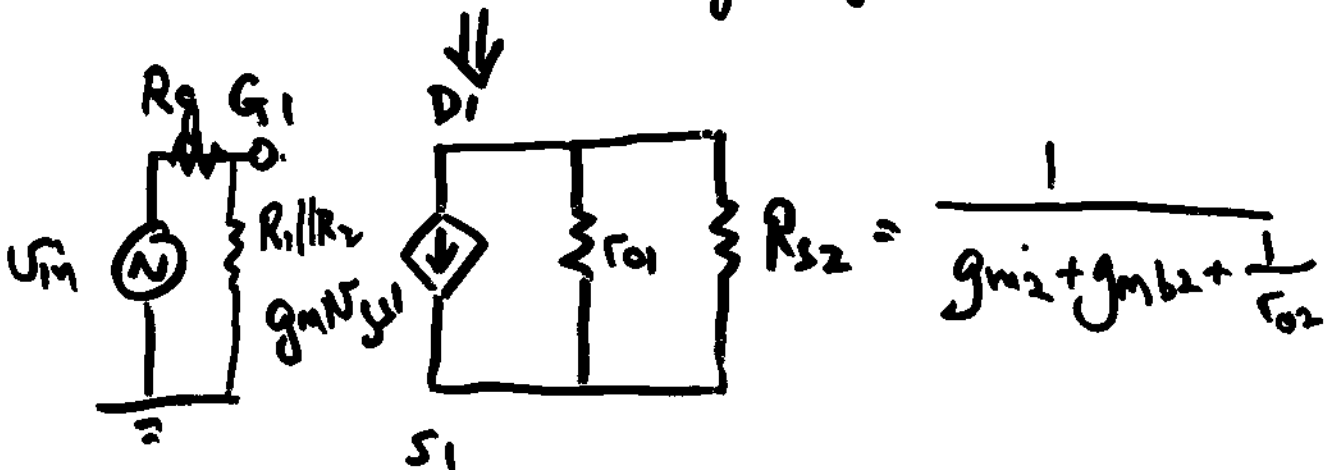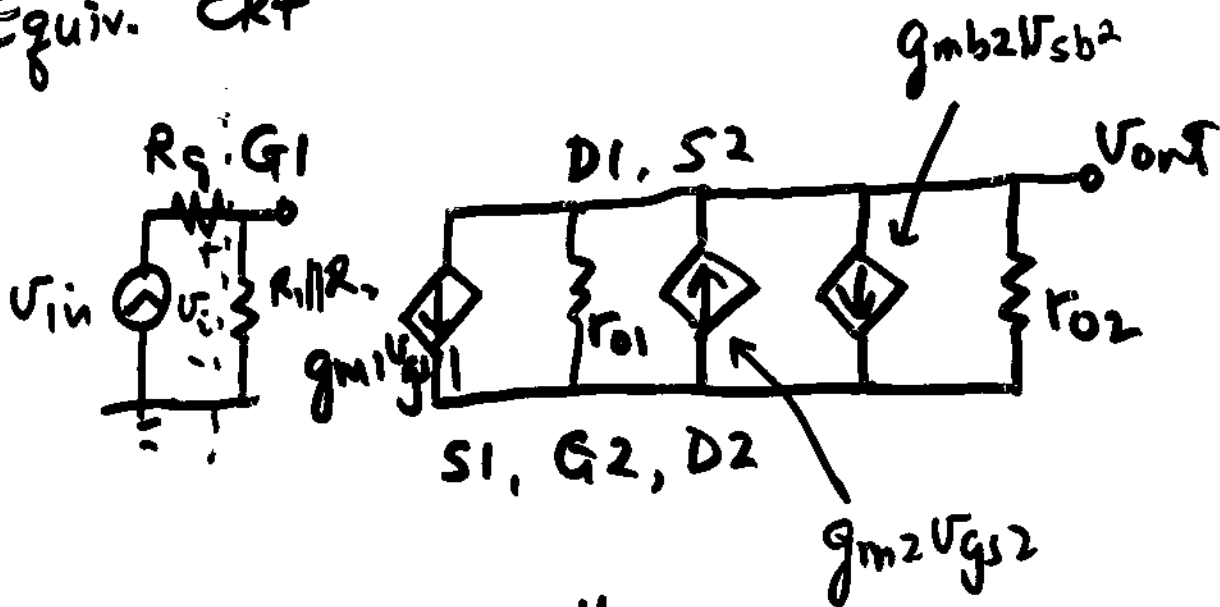

$$\begin{aligned} \frac{v_o}{v_i} &= A_{MB} = -g_{m1} (\tau_{o1} \parallel R_{s2}) \\ &= \frac{-g_{m1}}{g_{m2} + g_{mb2} + \frac{1}{\tau_{o1}} + \frac{1}{\tau_{o2}}} \\ &\approx \frac{-g_{m1}}{g_{m2}} \end{aligned}$$

High Frequency Model


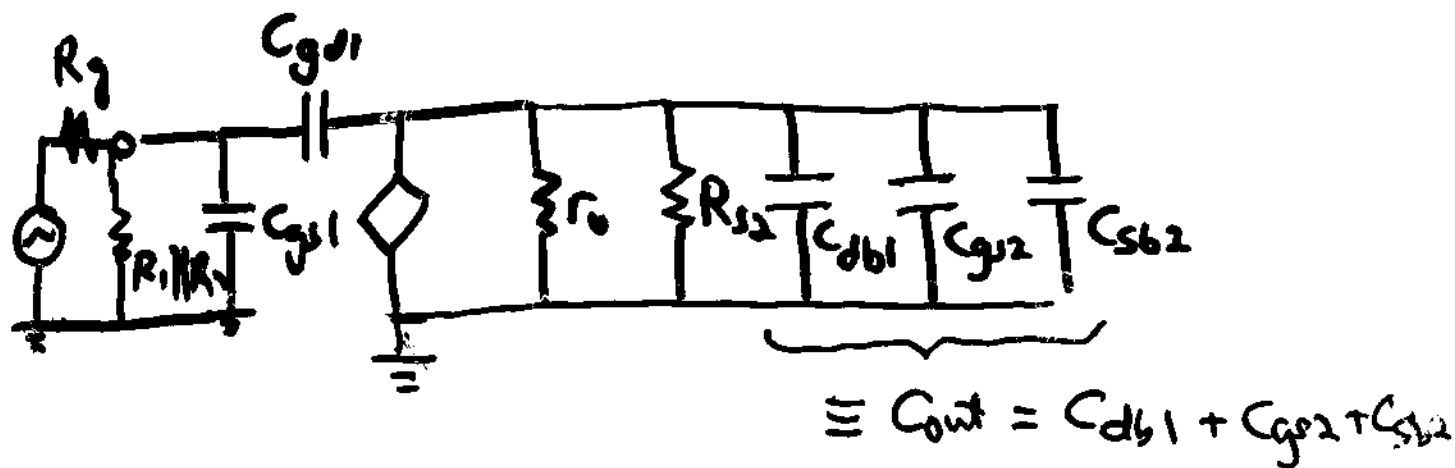


$$R_{gs1, eq} = R_g \parallel R_1 \parallel R_2$$

$$R_{gd1, eq} = R_{gs1, eq} (1 - A_{MB}) + r_o \parallel R_{s2}$$

$$R_{out, eq} = r_o \parallel R_{s2}$$


Current Mirror Load

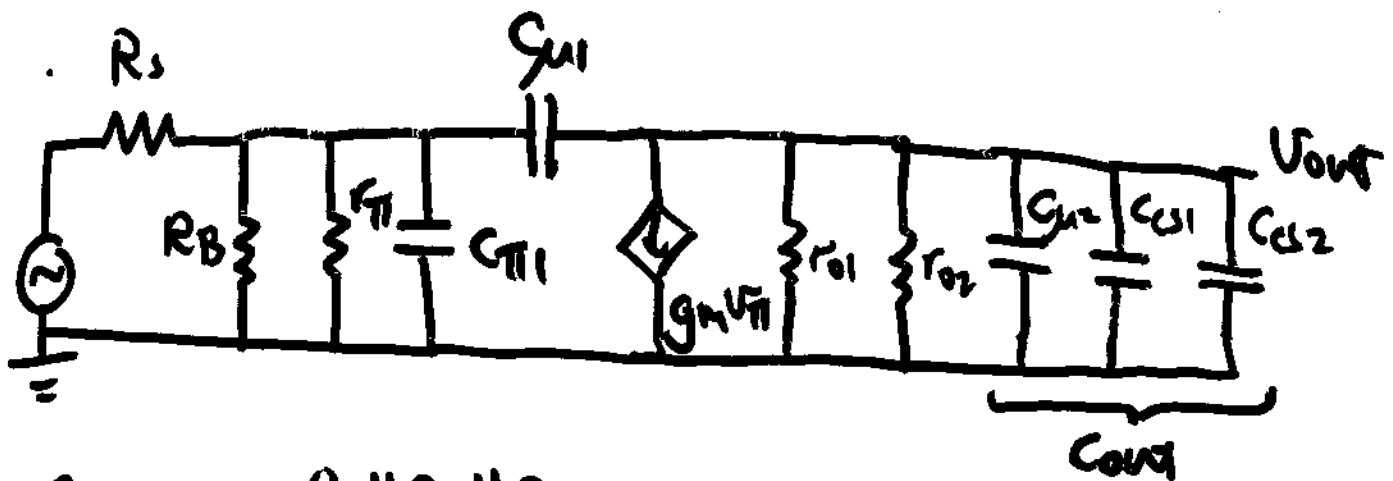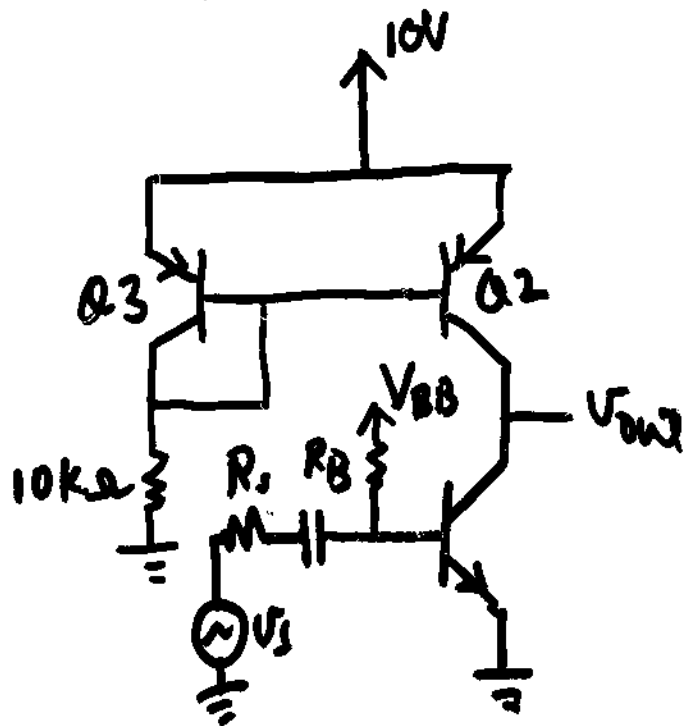

$$R_{\pi,eq} = R_S \parallel R_B \parallel r_{\pi}$$

$$R_{M1,eq} = R_{\pi,eq} (1 - g_m(r_{o1} \parallel r_{o2})) + r_{o1} \parallel r_{o2}$$

$$R_{out,eq} = r_{o1} \parallel r_{o2}$$

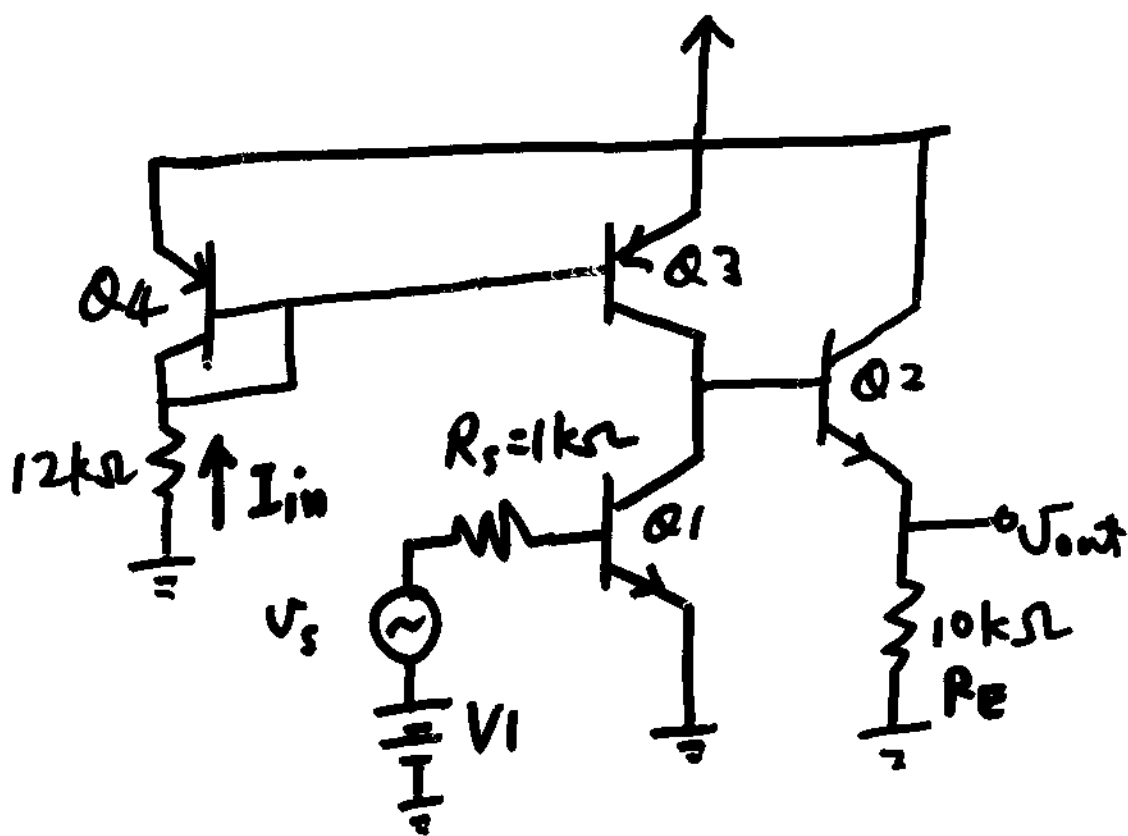

$$\beta = 80$$

$$|V_{BE(ON)}| = 0.7V$$

$$|V_A| = 62V$$

$$C_{\mu} = 2pF$$

$$C_{\pi} = 20pF$$

$$C_{es} = 2pF$$

$$V_{out,DC} = 4V$$

DC solution

$$I_{C3} \approx I_{C2} \approx \frac{\beta}{\beta+2} I_{in}$$

$$= \frac{80}{80+2} \frac{8-0.7}{12 \text{ k}\Omega} = 0.59 \text{ mA}$$

$$r_{\pi 1} = 3.57 \text{ k}\Omega$$

$$g_{m1} = 22.7 \text{ mA/V}$$

$$r_{o1} = r_{o3} = \frac{V_A}{I_C} = 105 \text{ k}\Omega$$

$$V_{OUT, DC} = 4 \text{ V}$$


$$I_{E2} = 0.4 \text{ mA}$$

$$r_{\pi 2} = 802 \Omega$$

$$g_{m2} = 15.2 \text{ mA/V}$$

$$r_{o2} = 157 \text{ k}\Omega$$

Midband Model

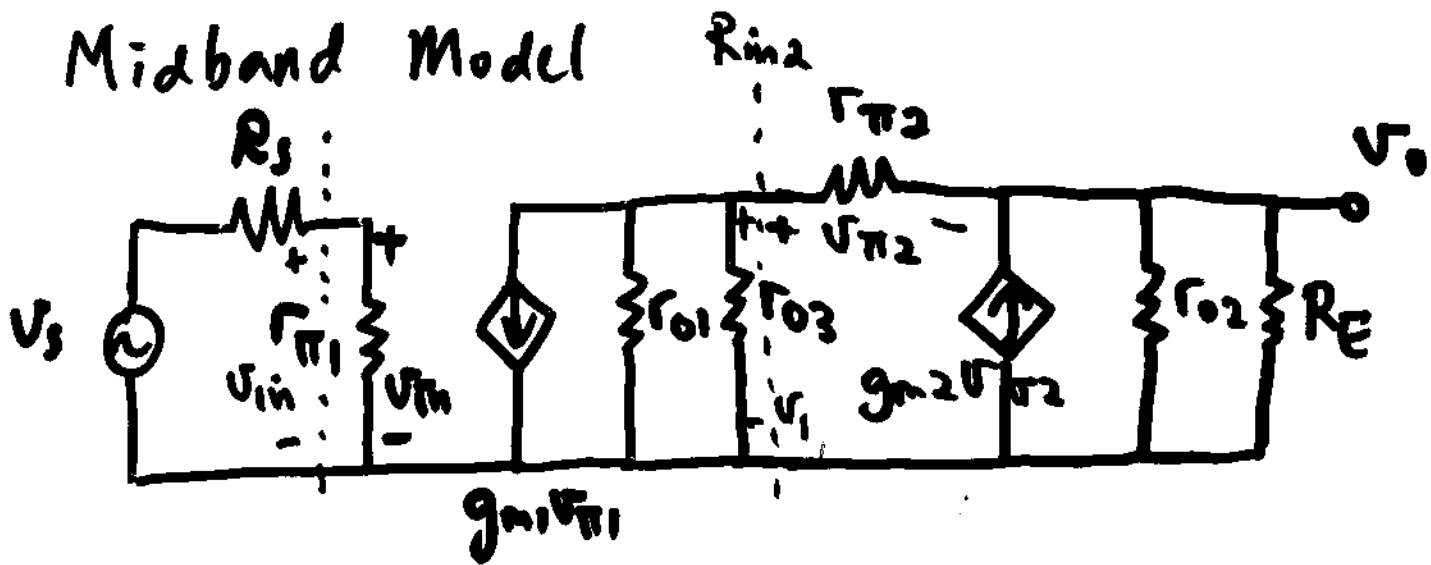

$$R_{in2} = r_{\pi} + (r_{o2} \parallel R_E)(\beta + 1)$$

$$\cong 810 \text{ k}\Omega$$

$$v_i = -g_{m1} v_{\pi 1} (r_{o1} \parallel r_{o3} \parallel R_{in2})$$

$$A_{v1} = \frac{v_i}{v_{in}} = -g_{m1} (r_{o1} \parallel r_{o3} \parallel R_{in2})$$


$$v_o = \frac{r_{o2} \parallel R_E}{r_{o2} \parallel R_E + \frac{r_{\pi 2}}{\beta + 1}} v_i$$

$$A_{v2} = \frac{v_o}{v_i} = \frac{r_{o2} \parallel R_E}{r_{o2} \parallel R_E + \frac{r_{\pi 2}}{\beta + 1}}$$

$$A_{vs} = \frac{v_o}{v_s} = \frac{r_{\pi 1}}{R_s + r_{\pi 1}} \cdot A_{v1} \cdot A_{v2}$$

$$= -858 \text{ V/V}$$

High-Frequency Model

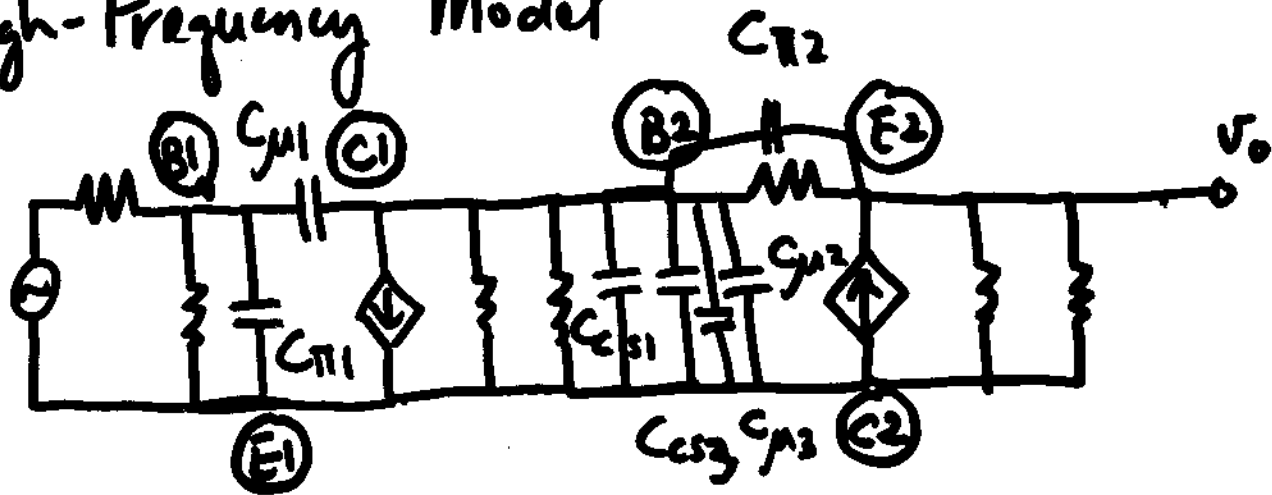

$$C_{in} = C_{\pi 1} + (1 - A_{v1}) C_{\mu 1}$$

$$= 20 + 1106 \times 2 = 2232 \text{ pF}$$

$$R_{in,eq} = R_s \parallel r_{\pi 1} = 781 \Omega$$

$$\tau_{in} = 1.74 \mu\text{s}$$

$$C_{out} = C_{es1} + C_{es3} + C_{\mu 1} + C_{\mu 2} + C_{\mu 3} = 10 \text{ pF} \approx 71 \text{ kHz}$$

$$R_{out,eq} = r_{o1} \parallel r_{o3} \parallel R_{in2} = 49.3 \text{ k}\Omega$$

$$\tau_{out} = 0.49 \mu\text{s}$$

$$\tau_H = \tau_{in} + \tau_{out} + \tau_{\pi 2}$$


$$f_H = \frac{1}{2\pi \tau_H}$$

$$C_{\pi 2} = 20 \text{ pF}$$


$$R_{\pi 2,eq} = r_{\pi 2} \parallel \frac{R'_s + R'_L}{1 + g_{m2} R'_L}$$

$$= 802 \parallel \frac{52.5 \text{ k}\Omega + 9.4 \text{ k}\Omega}{1 + 15.2 \times 9.4 \text{ k}\Omega}$$

$$= 280 \Omega$$

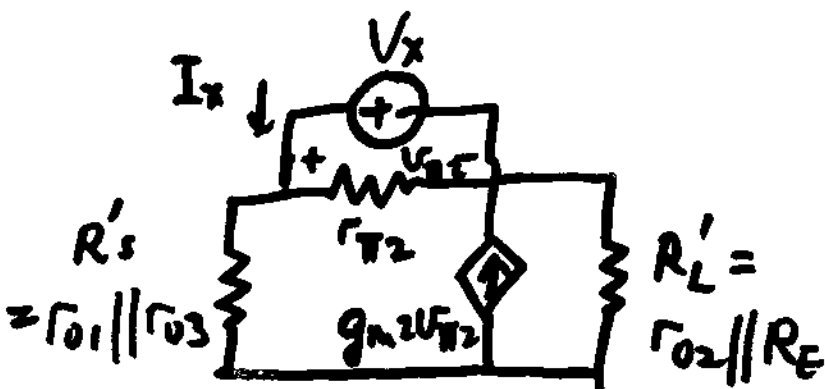

$$\tau_{\pi 2} = 5 \text{ ps}$$

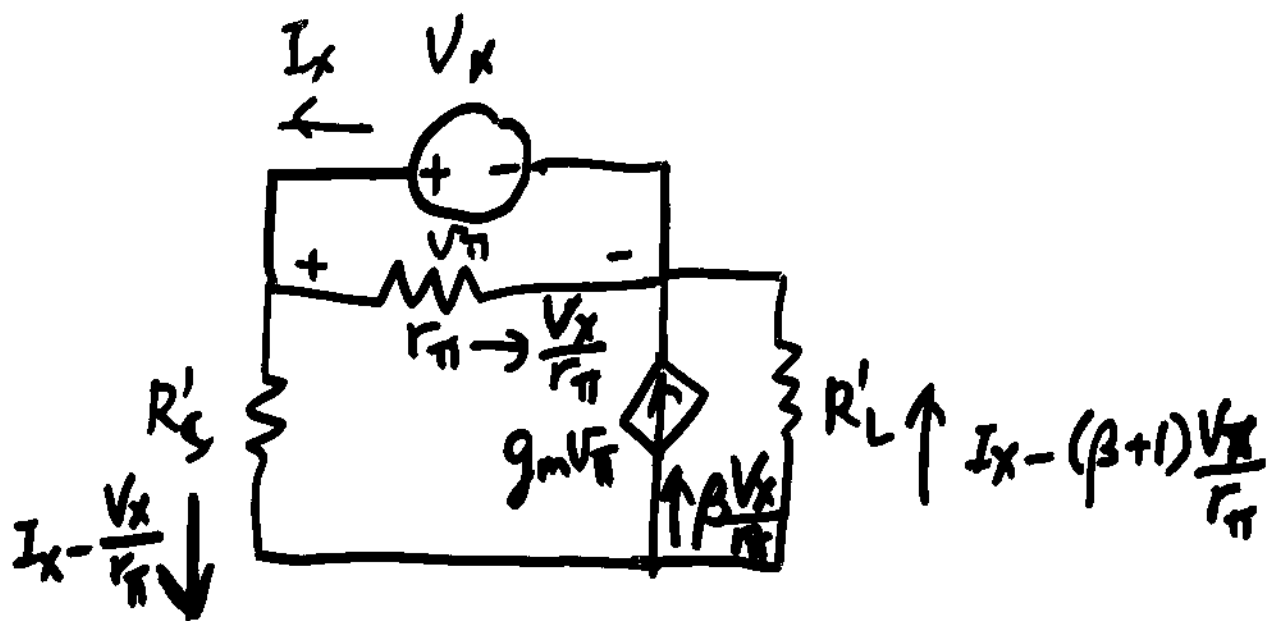

$$V_x = \left(I_x - \frac{V_x}{r_{\pi}} \right) R'_s + \left(I_x - (\beta+1) \frac{V_x}{r_{\pi}} \right) R'_L$$

$$V_x + \frac{V_x}{r_{\pi}} R'_s + (\beta+1) \frac{V_x}{r_{\pi}} R'_L = (R'_s + R'_L) I_x$$

$$\frac{I_x}{V_x} = \frac{1}{R'_s + R'_L} + \frac{1}{r_{\pi}} + \frac{g_m R'_L}{R'_s + R'_L}$$

$$= \frac{1}{r_{\pi}} + \frac{1 + g_m R'_L}{R'_s + R'_L}$$

$$\frac{V_x}{I_x} = r_{\pi} \parallel \frac{R'_s + R'_L}{1 + g_m R'_L} = R_{\pi, eq}$$