

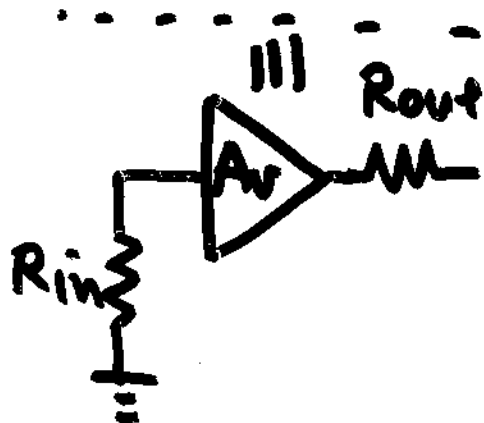


# Multistage Amplifiers

Basic Amp:

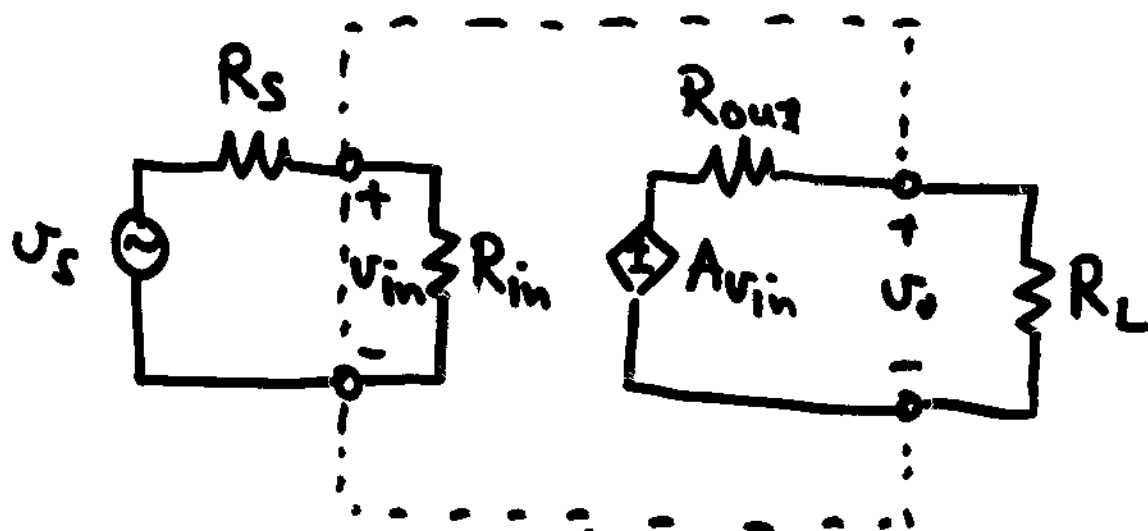

Three-stage Amplifier

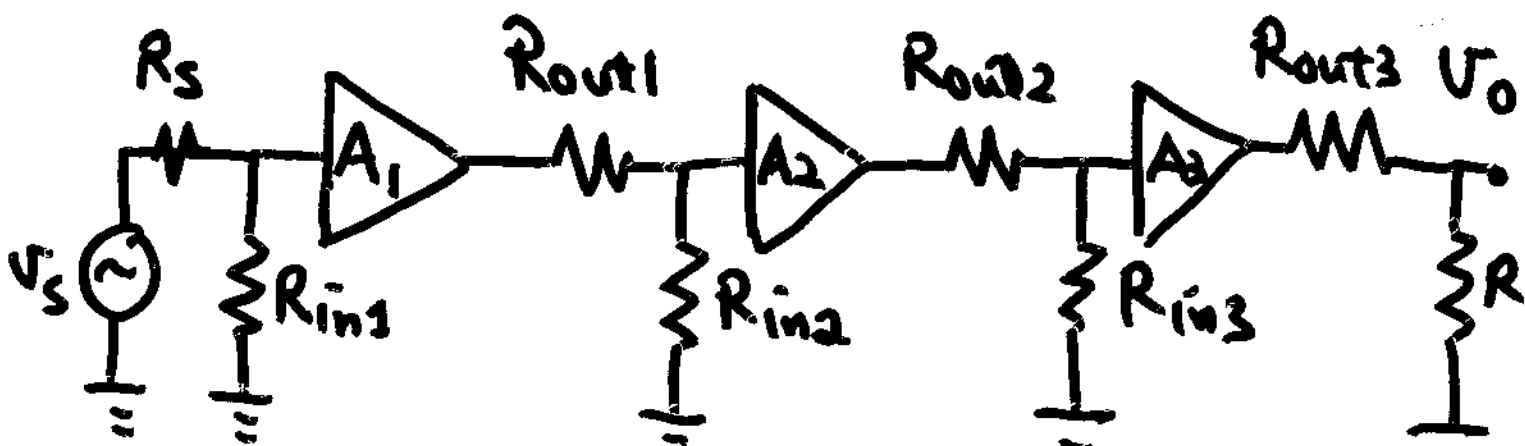

$$A_{V_s} = A_1 \cdot A_2 \cdot A_3 \cdot \frac{R_{in1}}{R_{in1} + R_s} \cdot \frac{R_{in2}}{R_{in2} + R_{out1}} \cdot \frac{R_{in3}}{R_{in3} + R_{out2}} \cdot \frac{R_L}{R_L + R_{out3}}$$

$$A_{V_s} = \frac{V_o}{V_s}$$

$$= \frac{V_{in1}}{V_s} \cdot \frac{A_1 V_{in1}}{V_{in1}} \cdot \frac{V_{out1}}{A_1 V_{in1}} \cdot \frac{A_2 V_{out1}}{V_{out1}} \cdot \frac{V_{out2}}{A_2 V_{out1}}$$

$$\frac{A_3 V_{out2}}{V_{out2}} \cdot \frac{V_o}{A_3 V_{out2}}$$

$$= \frac{R_{in1}}{R_{in1} + R_s} \cdot A_1 \cdot \frac{R_{in2}}{R_{in2} + R_{out1}} \cdot A_2 \cdot$$

$$\frac{R_{in3}}{R_{in3} + R_{out2}} \cdot A_3 \cdot \frac{R_L}{R_L + R_{out3}}$$

$$R_{in}(\text{overall}) = R_{in1}$$

$$R_{out}(\text{overall}) = R_{out3}$$

$$A_{V_s}(\text{overall}) = A_{V_{s1}} \times A_{V_{s2}} \times A_{V_{s3}}$$


CASCADE

# CE-CE Cascade Example

$A_v$  ? [Huge :  $-100 \cdot -100 = +10,000$ ]

$R_{in}$  ? [few  $k\Omega$ ] [ $r_{\pi 1} \parallel R_1 \parallel R_2$ ]

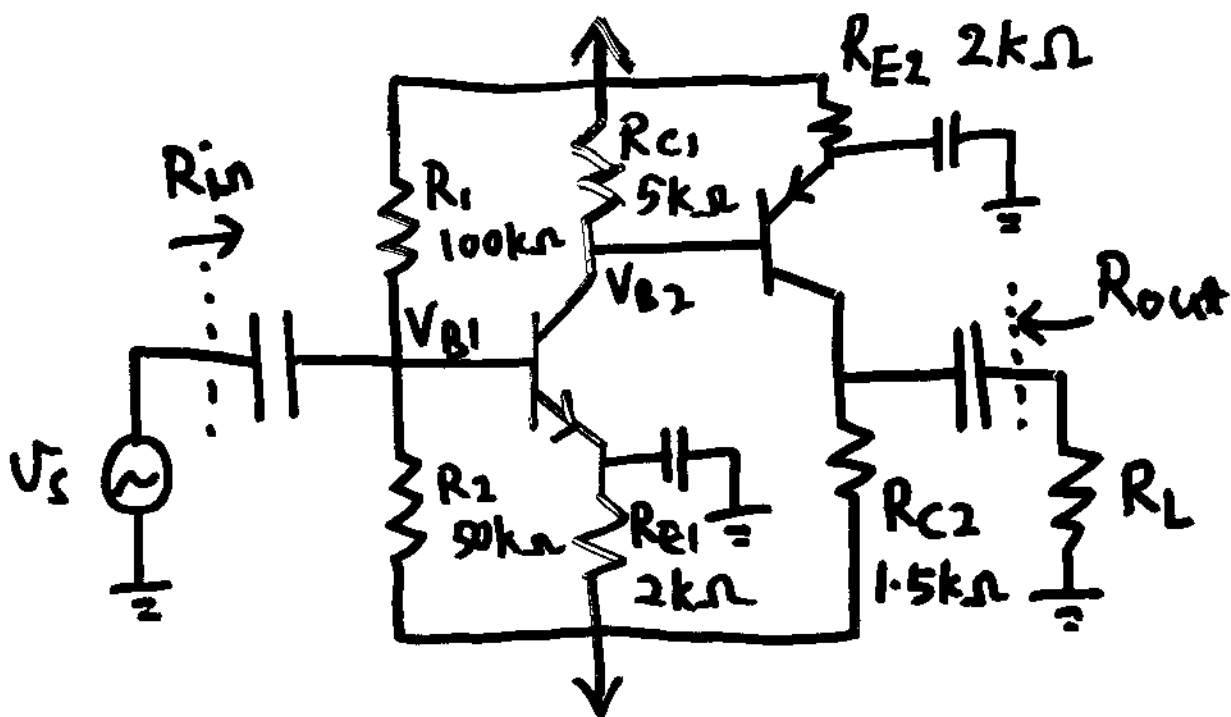$R_{out}$  ? [few  $k\Omega$ ] [ $R_{C2} \parallel r_{o2}$ ]



$$\beta = 100$$

$$V_A = \infty$$

$$I_{B1} = \frac{V_{TH} - 0.7}{R_{TH} + (\beta + 1)R_E}$$

$$= 11.2 \mu A$$

$$I_{C1} = 1.12 \text{ mA}$$

$$I_{E1} = 1.13 \text{ mA}$$

$$r_{\pi 1} = \frac{.026 \text{ V}}{11.2 \mu A}$$

$$= 2.32 \text{ k}\Omega$$

$$g_{m1} = \frac{1.12 \text{ mA}}{.026 \text{ V}}$$

$$= 43.1 \text{ mA/V}$$

KVL:

$$I_{E2} \cdot 2 \text{ k}\Omega + 0.7 \text{ V} + (I_{C1} - I_{B2}) 5 \text{ k}\Omega = 0$$

$$101 I_{B2} \cdot 2 \text{ k}\Omega + 0.7 \text{ V} + (1.12 \text{ mA} - I_{B2}) 5 \text{ k}\Omega = 0$$

$$I_{B2} = 23.7 \mu A$$

$$I_{C2} = 2.37 \text{ mA}$$

$$I_{E2} = 2.39 \text{ mA}$$


$$r_{\pi 2} = \frac{.026 \text{ V}}{23.7 \mu A}$$

$$= 1.10 \text{ k}\Omega$$

$$g_{m2} = \frac{2.37 \text{ mA}}{.026 \text{ V}}$$

$$= 91.2 \text{ mA/V}$$

## a.c. equivalent ckt

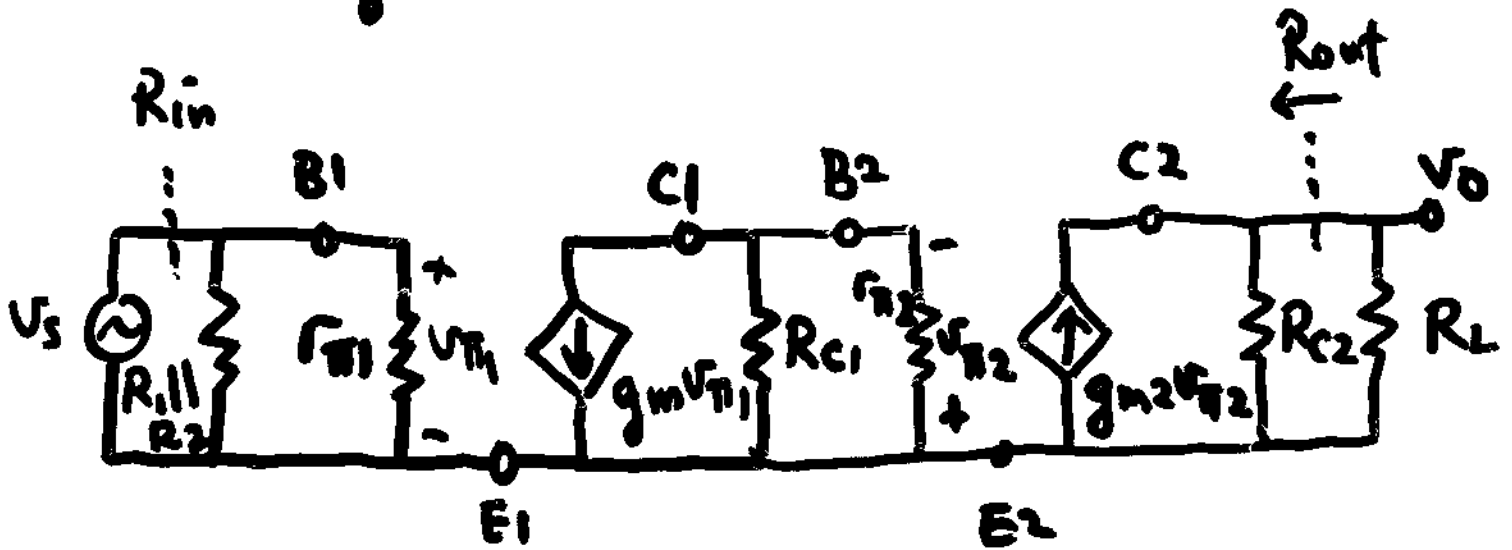

$$A_{v1} = \frac{v(B2)}{v_s}, \quad A_{v2} = \frac{v_o}{v(B2)}$$

$$v(B2) = -g_{m1} v_s (R_{c1} \parallel r_{\pi 2})$$

$$A_{v1} = -g_{m1} (R_{c1} \parallel r_{\pi 2})$$

$$v_o = -g_{m2} v(B2) (R_{c2} \parallel R_L)$$

$$A_{v2} = -g_{m2} (R_{c2} \parallel R_L)$$

$$A_{v_s} = A_{v1} \cdot A_{v2} = g_{m1} \cdot g_{m2} (R_{c1} \parallel r_{\pi 2}) (R_{c2} \parallel R_L)$$

$$= 43.1 \times 91.2 \times 0.90 \times 1.15$$

$$= 4668 \text{ V/V}$$

$$R_{in} = 2.32 \text{ k}\Omega \parallel 50 \text{ k}\Omega \parallel 100 \text{ k}\Omega = 2.17 \text{ k}\Omega$$


$$R_{out} < R_{c2} = 1.5 \text{ k}\Omega$$

# CASCODE Example : CE-CB


$A_v$  (Huge :  $-100 \cdot +100 = -10,000$ )

$R_{in}$  (few  $k\Omega$ )  $[\Gamma_{\pi 1} \parallel R_1 \parallel R_2]$

$R_{out}$  (few  $k\Omega$ )  $[R_{C2}]$

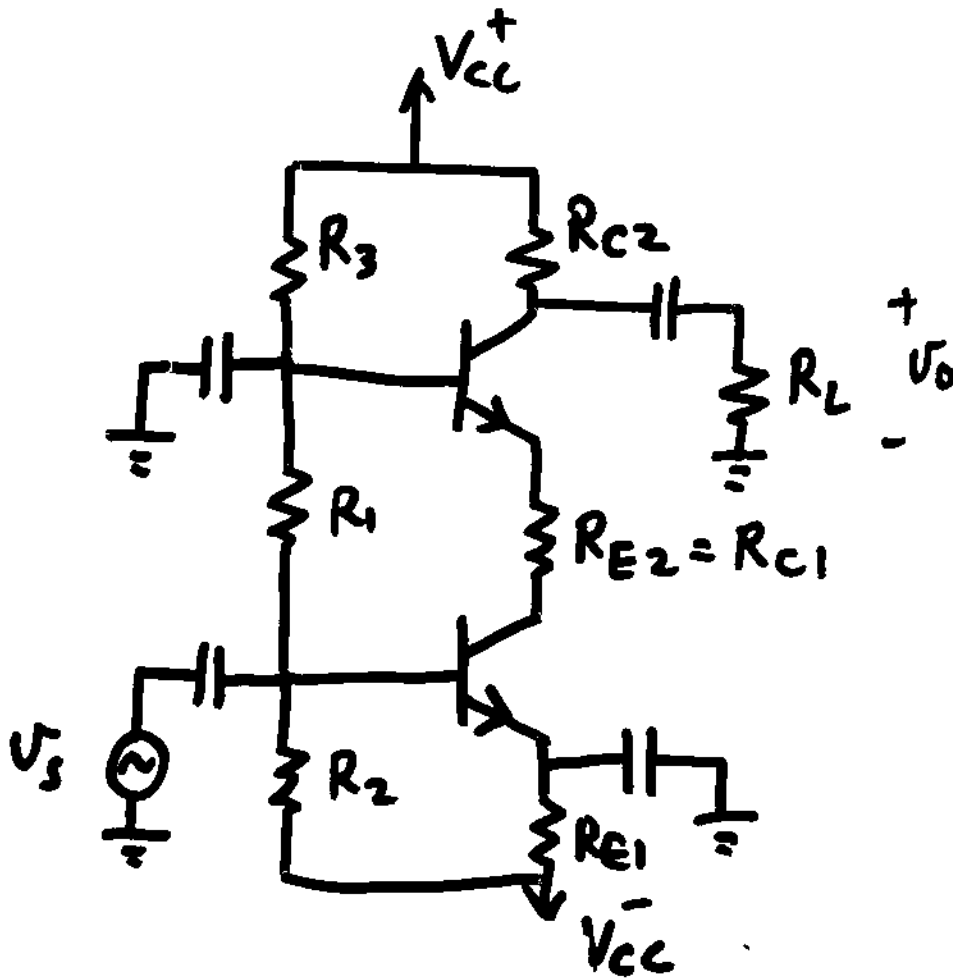

a.c. equivalent ckt

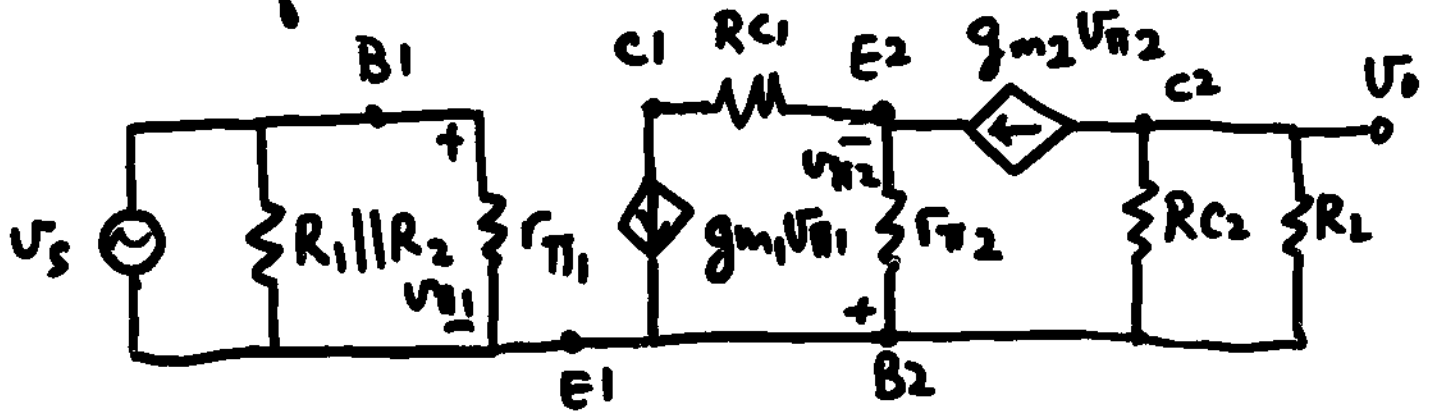

$$g_{m1} v_{\pi 1} = g_{m2} v_{\pi 2} + \frac{v_{\pi 2}}{r_{\pi 2}}$$

$$v_{\pi 2} = g_{m1} v_{\pi 1} / \left( g_{m2} + \frac{1}{r_{\pi 2}} \right)$$

$$= g_{m1} v_{\pi 1} \frac{r_{\pi 2}}{\beta_2 + 1}$$

$$v_o = -g_{m2} g_{m1} v_{\pi 1} \frac{r_{\pi 2}}{\beta_2 + 1} (R_{C2} \parallel R_L)$$


$$A_{v_s} = -g_{m1} g_{m2} \frac{r_{\pi 2}}{\beta_2 + 1} (R_{C2} \parallel R_L)$$

$$\approx -g_{m1} (R_{C2} \parallel R_L)$$


$$R_{in} = r_{\pi 1} \parallel R_1 \parallel R_2$$

$$R_{out} = R_{C2}$$

# CC-CE Darlington

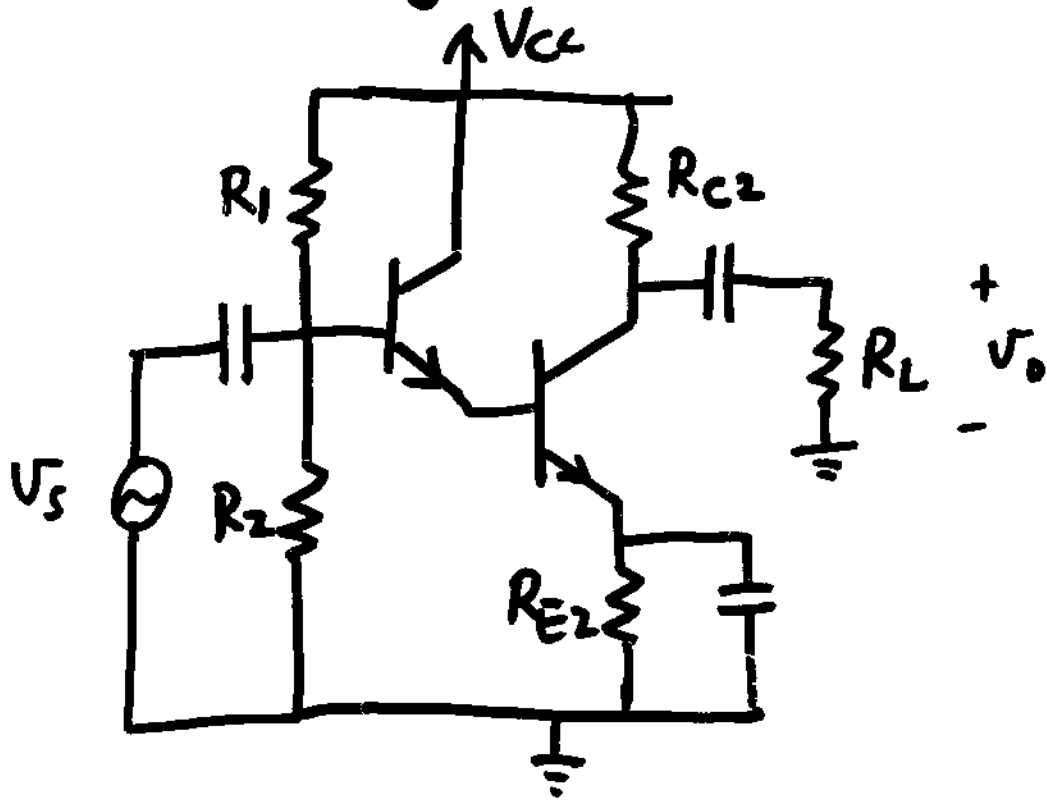

a.c. equivalent ckt

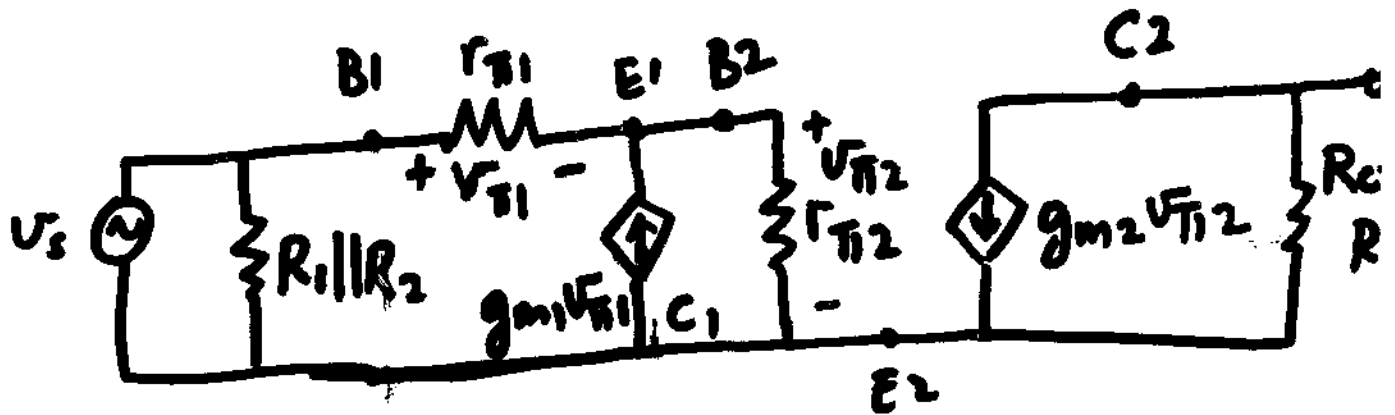

$$V_S = V_{\pi 1} + V_{\pi 2}$$

$$= V_{\pi 1} + \left( g_{m1} V_{\pi 1} + \frac{V_{\pi 1}}{r_{\pi 1}} \right) r_{\pi 2}$$

$$V_{\pi 2} = \left( g_{m1} V_{\pi 1} + \frac{V_{\pi 1}}{r_{\pi 1}} \right) r_{\pi 2}$$

$$A_{V_S} = \frac{V_{\pi 2}}{V_S} = \frac{(\beta_1 + 1) r_{\pi 2}}{r_{\pi 1} + (\beta_1 + 1) r_{\pi 2}}$$

$$V_o = -g_{m2} V_{\pi 2} (R_{C2} \parallel R_L)$$

$$A_{V_2} = -g_{m2} (R_{C2} \parallel R_L)$$

$$A_{V_S} = \frac{V_o}{V_S} = \frac{(\beta_1 + 1) r_{\pi 2}}{r_{\pi 1} + (\beta_1 + 1) r_{\pi 2}} \left[ -g_{m2} (R_{C2} \parallel R_L) \right]$$

$$R_{in} (\text{base 1}) = r_{\pi 1} + (\beta_1 + 1) r_{\pi 2}$$

HIGH IMPEDANCE