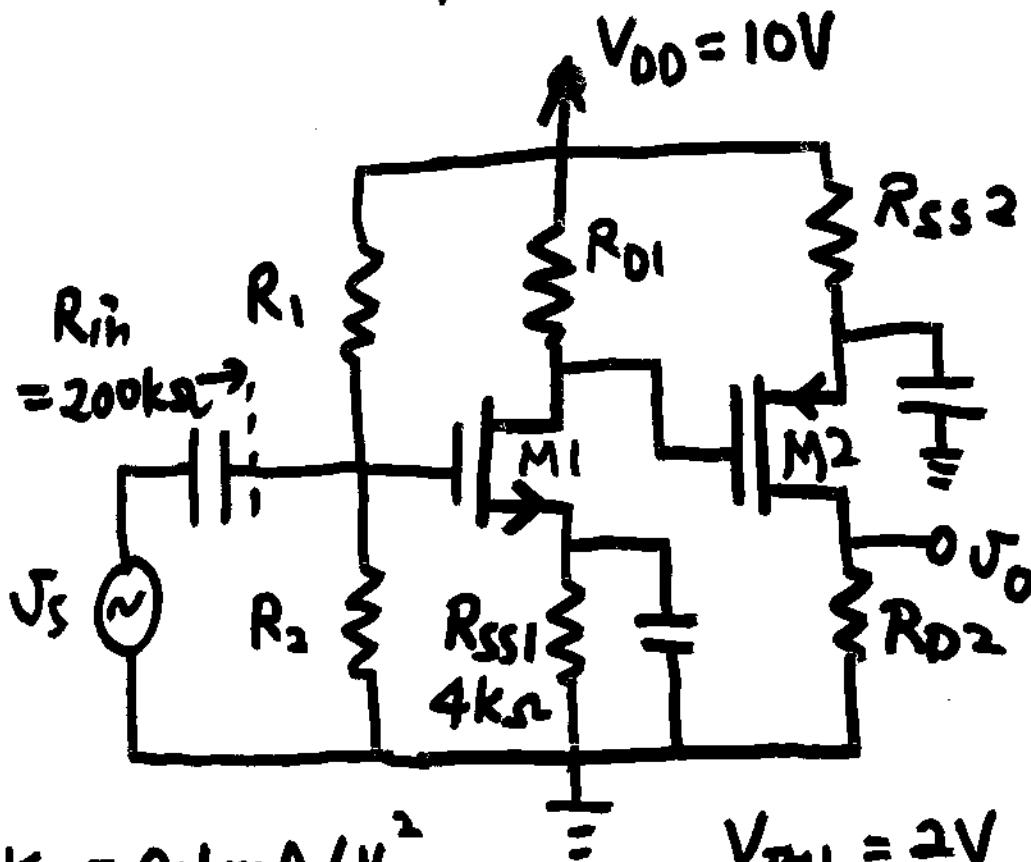


# MOS Multistage Amplifiers

- (1) Determine DC operating pt ( $I_{DQ}, V_{DSQ}$ )
- (2) Calculate small signal parameters  
 $g_m, r_o$
- (3) Draw small signal ckt
- (4) Calculate  $A_v, A_i, R_{in}, R_{out}$

## CS-CS example



$$K_1 = 0.1 \text{ mA/V}^2$$

$$V_{TH1} = 2V$$

$$\lambda_1 = \lambda_2 = 1$$

$$K_2 = 1.0 \text{ mA/V}^2$$

$$V_{TH2} = -2V$$

Design spec:  $I_{D1} = 0.4 \text{ mA}, I_{D2} = 2 \text{ mA}, V_{DS1} = 4V, V_{DS2} = 5V$

$$I_{D1} = 0.4 \text{ mA}$$

For M1

$$V_{DS1} = 4 \text{ V}$$

$$R_{SS1} = 4 \text{ k}\Omega$$

$$V_{DD} = I_{D1} R_{D1} + V_{DS1} + I_{D1} R_{SS1}$$

$$R_{D1} = \frac{V_{DD} - V_{DS1} - I_{D1} R_{SS1}}{I_{D1}}$$

$$= 11 \text{ k}\Omega$$

$$I_{D1} = k_1 [V_{GS1} - V_{TH1}]^2$$

$$\Rightarrow V_{GS1} = \sqrt{I_{D1}/k_1} + V_{TH1}$$

$$= 4 \text{ V}$$

$$V_{G1} = V_{S1} + V_{GS1} = I_{D1} R_{SS1} + V_{GS1}$$

$$= 5.6 \text{ V}$$

$$R_{in} = R_1 \parallel R_2 = 200 \text{ k}\Omega$$

$$V_{G1} = V_{DD} \frac{R_2}{R_1 + R_2} = V_{DD} \frac{R_{in}}{R_1}$$

$$\Rightarrow R_1 = \frac{V_{DD}}{V_{G1}} R_{in} = 357 \text{ k}\Omega$$

$$R_2 = \frac{R_1}{R_1/R_{in} - 1} = 455 \text{ k}\Omega$$

$$V_{G2} = V_{DD} - I_{D1} R_{D1} = 5.6 \text{ V} \quad \text{For M2}$$

$$V_{GS2} = -\sqrt{\frac{I_{D2}}{K_2}} + V_{TH2} = -3.41 \text{ V}$$

$$V_{S2} = V_{G2} - V_{GS2} = 9.01 \text{ V}$$

$$\Rightarrow R_{SS2} = \frac{V_{DD} - V_{S2}}{I_{D2}} = 495 \Omega$$

$$R_{DS} = \frac{V_{DD} - I_{D2} R_{SS2} - V_{SD2}}{I_{D2}}$$


$$= 2 \text{ k}\Omega$$

# Small signal parameters

$$g_{m1} = 2\sqrt{K_1 I_{D1}} = 0.4 \text{ mA/V}$$

$$g_{m2} = 2\sqrt{K_2 I_{D2}} = 2.8 \text{ mA/V}$$

# Small signal ckt

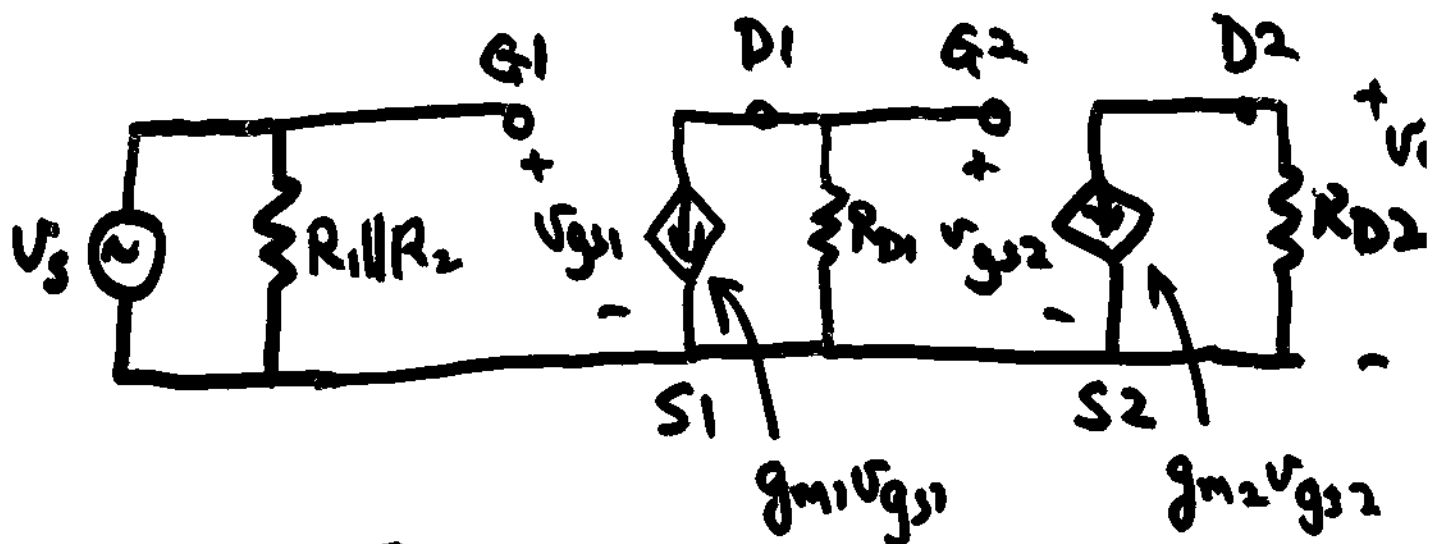


$$A_{v1} = \frac{v_{gs2}}{v_s}$$
$$= -g_{m1} R_{D1} = -4.4 \text{ V/V}$$


$$A_{v2} = \frac{v_o}{v_{gs2}} = -g_{m2} R_{D2} = -5.6 \text{ V/V}$$

$$A_{v3} = A_{v1} \times A_{v2} = 24.6$$

# Cascode CS-CG

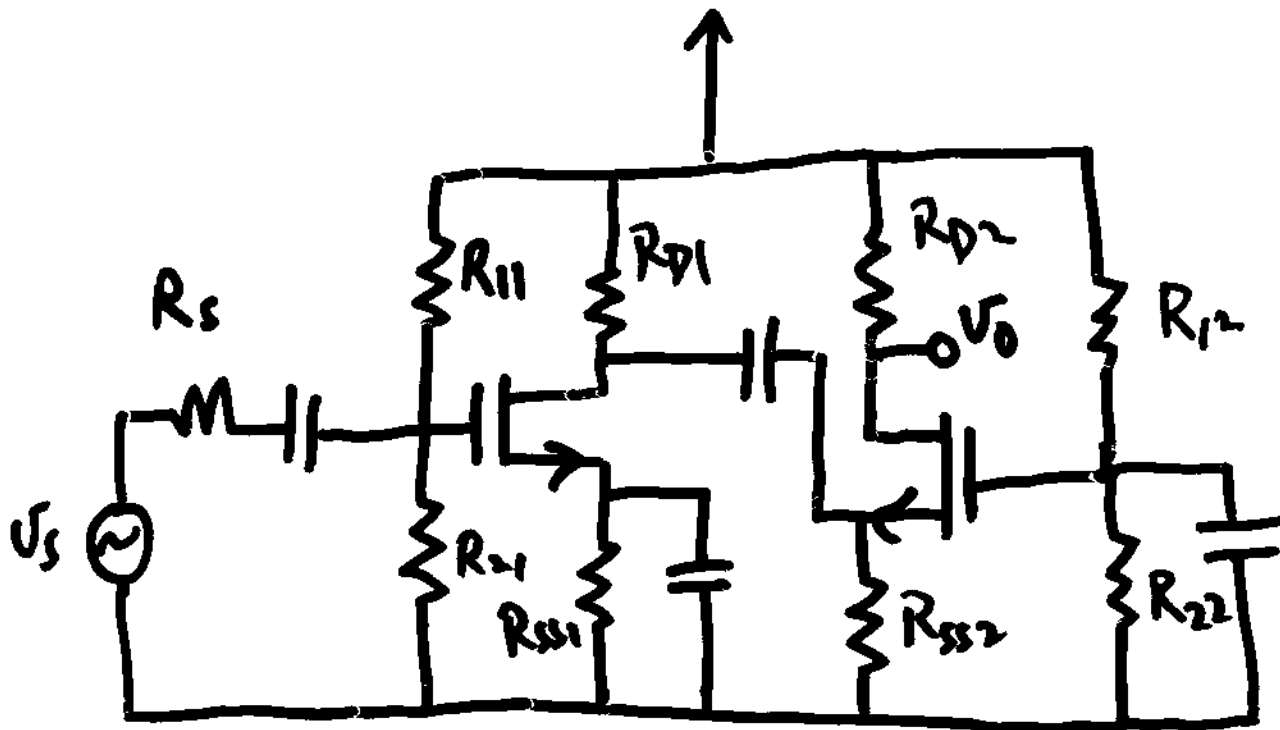

small-signal ckt

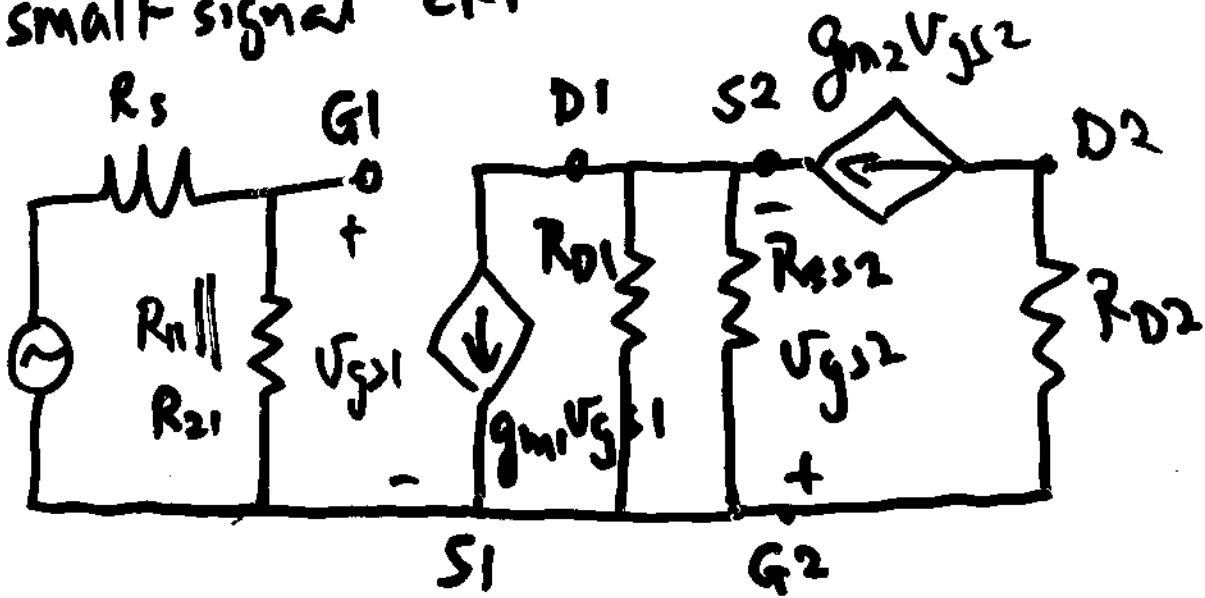

$$g_{m2}V_{gs2} + \frac{V_{gs2}}{R_{D1} \parallel R_{SS2}} = g_{m1}V_{gs1}$$

$$V_{gs2} = \frac{g_{m1} V_{gs1}}{g_{m2} + \frac{1}{R_{D1} \parallel R_{SS2}}}$$

$$= \frac{(R_{D1} \parallel R_{SS2}) g_{m1} V_{gs1}}{1 + g_{m2} (R_{D1} \parallel R_{SS2})}$$

$$V_o = -g_{m2} V_{gs2} R_{D2}$$

$$V_{gs1} = \frac{R_{11} \parallel R_{21}}{R_s + R_{11} \parallel R_{21}} V_s$$

$$A_{V_s} = \frac{V_o}{V_s} = -g_{m1} g_{m2} \frac{(R_{D1} \parallel R_{SS2})}{1 + g_{m2} (R_{D1} \parallel R_{SS2})}$$

$$\frac{R_{11} \parallel R_{21}}{R_s + R_{11} \parallel R_{21}} \cdot R_{D2}$$

$$\approx -g_{m1} R_{D2}$$