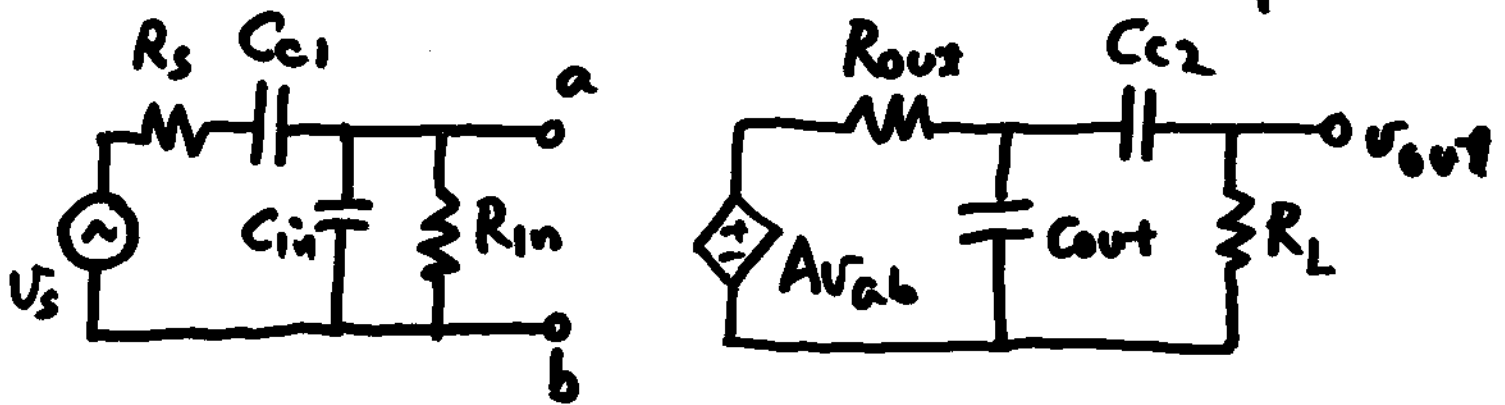


A Model for a Non-ideal Amp.




C_{c1} & C_{c2} large, μF

C_{in} & C_{out} , parasitic capacitors
very small, pF


R_{in} : BJT $\text{k}\Omega$
MOSFET $\text{M}\Omega$

R_{out} : $\Omega \sim \text{k}\Omega$

MIDBAND MODEL

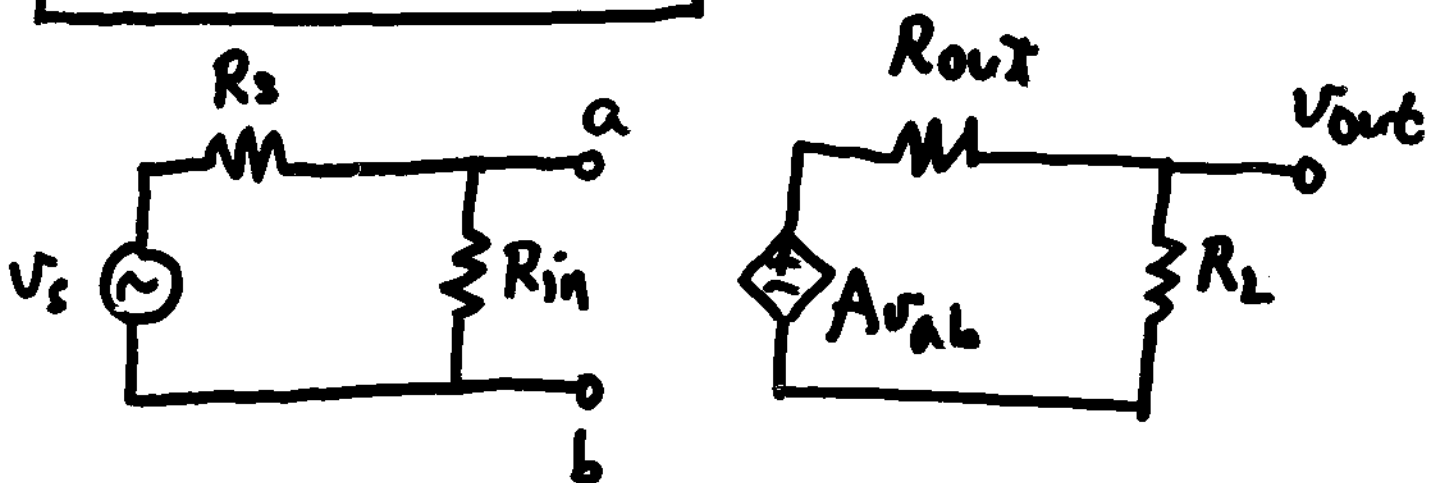

LOW FREQUENCY MODEL

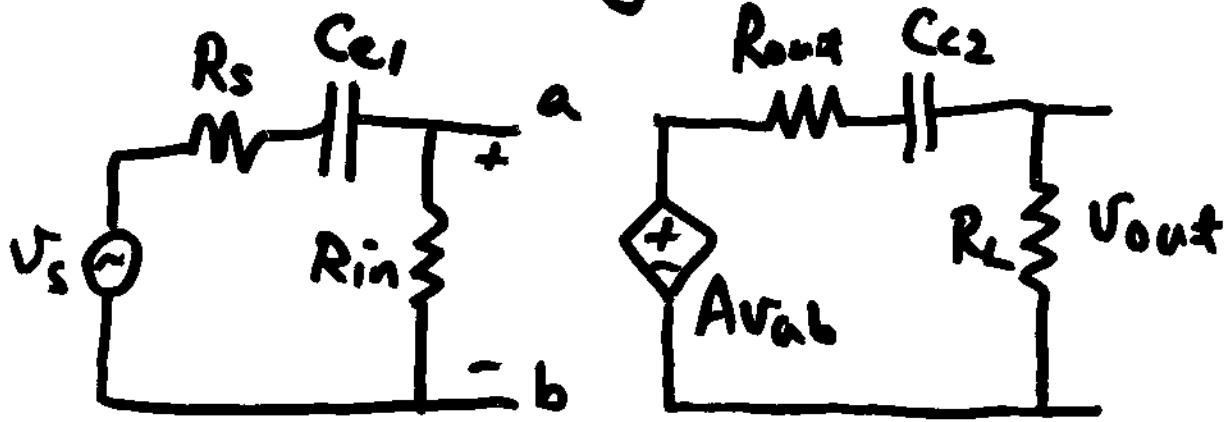


$$\omega \downarrow \Rightarrow \frac{1}{j\omega C} \uparrow$$

$$\Rightarrow V_{ab} \downarrow$$

$$\Rightarrow V_{out} \downarrow$$

Low-frequency fall
of voltage gain
High-pass filter

Example : Single-pole circuit

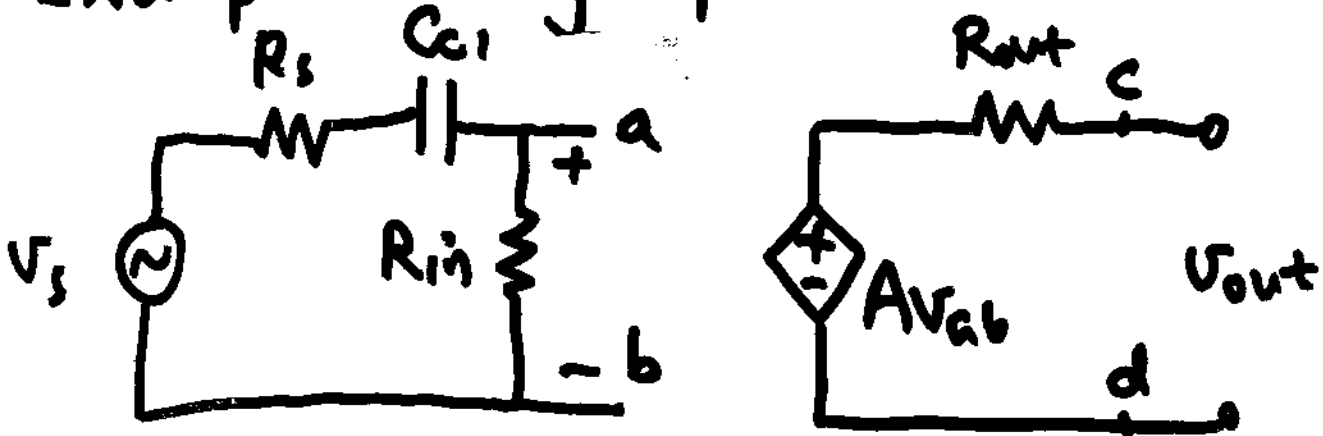

Single-pole circuit


$$A_{V_s} = \frac{V_{out}}{V_s} = \frac{V_{ab}}{V_s} \times A$$

$$\frac{V_{ab}}{V_s} = \frac{R_{in}}{R_{in} + R_s + 1/j\omega C_{c1}}$$


$$A_{V_s} = \frac{R_{in} (j\omega C_{c1})}{1 + j\omega C_{c1} (R_{in} + R_s)} A$$

$$= \frac{R_{in}}{R_{in} + R_s} \cdot A \cdot \frac{1}{1 - j/2\pi f C_{c1} (R_{in} + R_s)}$$
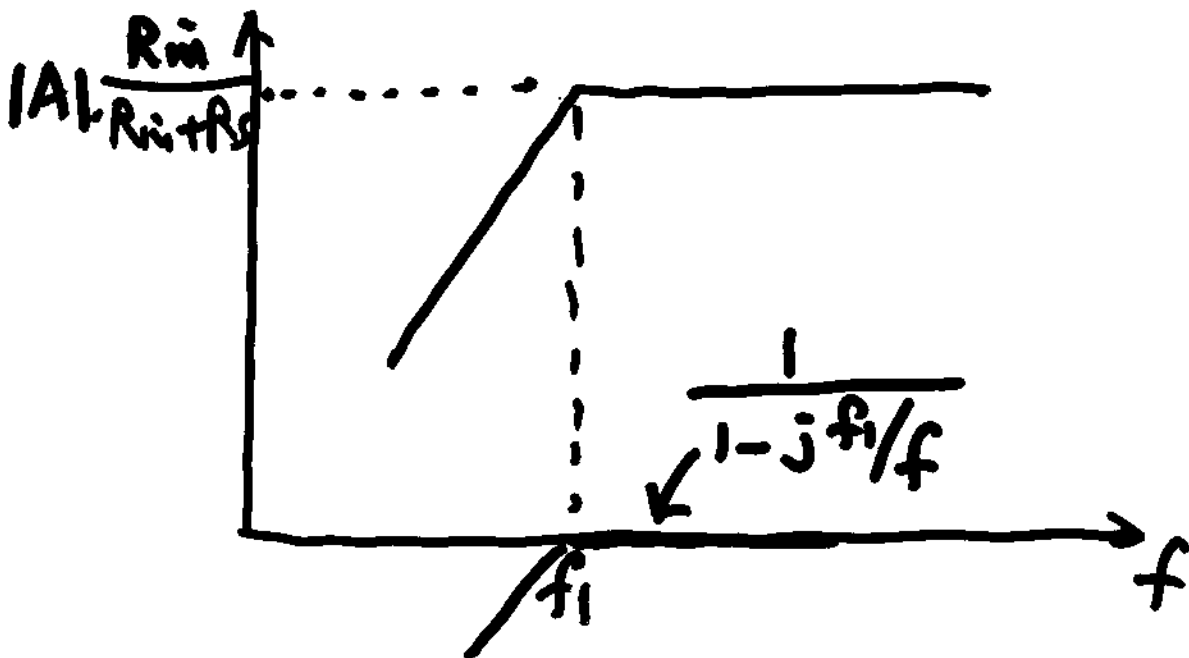
$$\text{Let } f_1 = \frac{1}{2\pi C_{c1} (R_{in} + R_s)}$$



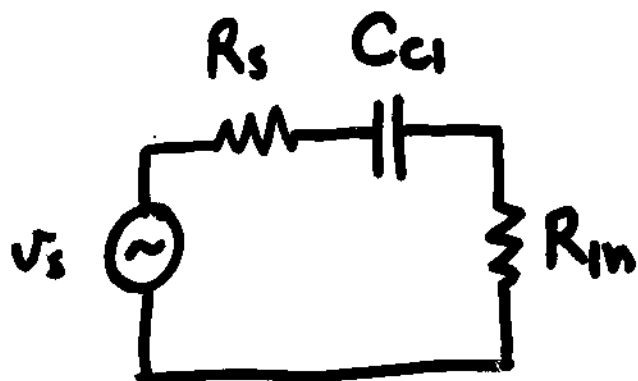$\tau_s = C_{c1} (R_{in} + R_s) :$ open-circuit time constant
 C_{in} is open



Thevenin equi. impedance seen by C_{c1}
($R_s + R_{in}$)

$$\omega_1 = 2\pi f_1 = \frac{1}{\tau_s} = \frac{1}{C_{c1}(R_{in} + R_s)}$$

Double-pole circuit

$$\tau_{s1} = C_{c1}(R_{in} + R_s)$$

$$\tau'_{s1} = C_{c2}(R_{out} + R_L)$$

$$A_{vs} = \frac{R_{in}}{R_{in} + R_s} A \frac{R_L}{R_L + R_{out}} \times$$

$$\frac{1}{1 - \frac{j}{2\pi f \tau_{s1}}} \cdot \frac{1}{1 - \frac{j}{2\pi f \tau'_{s1}}}$$

$$f_1 = \frac{1}{2\pi \tau_{s1}} = \frac{1}{2\pi (R_{in} + R_s) C_{c1}}$$

$$f'_1 = \frac{1}{2\pi \tau'_{s1}} = \frac{1}{2\pi (R_L + R_{out}) C_{c2}}$$

Where is the lower corner frequency

$$Eg \quad A = 22 \text{ V/V}$$

$$R_{in} = 10 \text{ k}\Omega, \quad R_{out} = 325 \Omega$$

$$R_s = 600 \Omega, \quad R_L = 1 \text{ k}\Omega$$

$$C_{c1} = 10 \mu\text{F}, \quad C_{c2} = 40 \mu\text{F}$$

(a) Midband gain.

$$A_{MB} = \frac{10}{10 + .6} \cdot 22 \cdot \frac{1}{1 + .325} = 15.7 \text{ V/V}$$

(b) Lower corner frequency due to C_{c1}

$$f_1 = \frac{1}{2\pi C_{c1} (R_{in} + R_s)} = 1.50 \text{ Hz}$$

(c) Lower corner frequency due to C_{c2}

$$f'_1 = \frac{1}{2\pi C_{c2} (R_L + R_{out})} = 3.00 \text{ Hz}$$

(d) Overall gain as a function of frequency,

$$A_{v_s} = 15.7 \times \frac{1}{1 - j \frac{1.50}{f}} \times \frac{1}{1 - j \frac{3.00}{f}}$$

Overall Lower Corner Frequency


$$\left[1 + \left(\frac{f_1}{f_L}\right)^2\right] \left[1 + \left(\frac{f_1'}{f_L}\right)^2\right] = 2$$

$$f_L^4 - (f_1^2 + f_1'^2)f_L^2 - (f_1^2 f_1'^2) = 0$$

Eg.

$$\begin{aligned} f_1 &= 1.50 \text{ Hz} \\ f_1' &= 3.00 \text{ Hz} \\ f_L &= 3.58 \text{ Hz} \end{aligned}$$
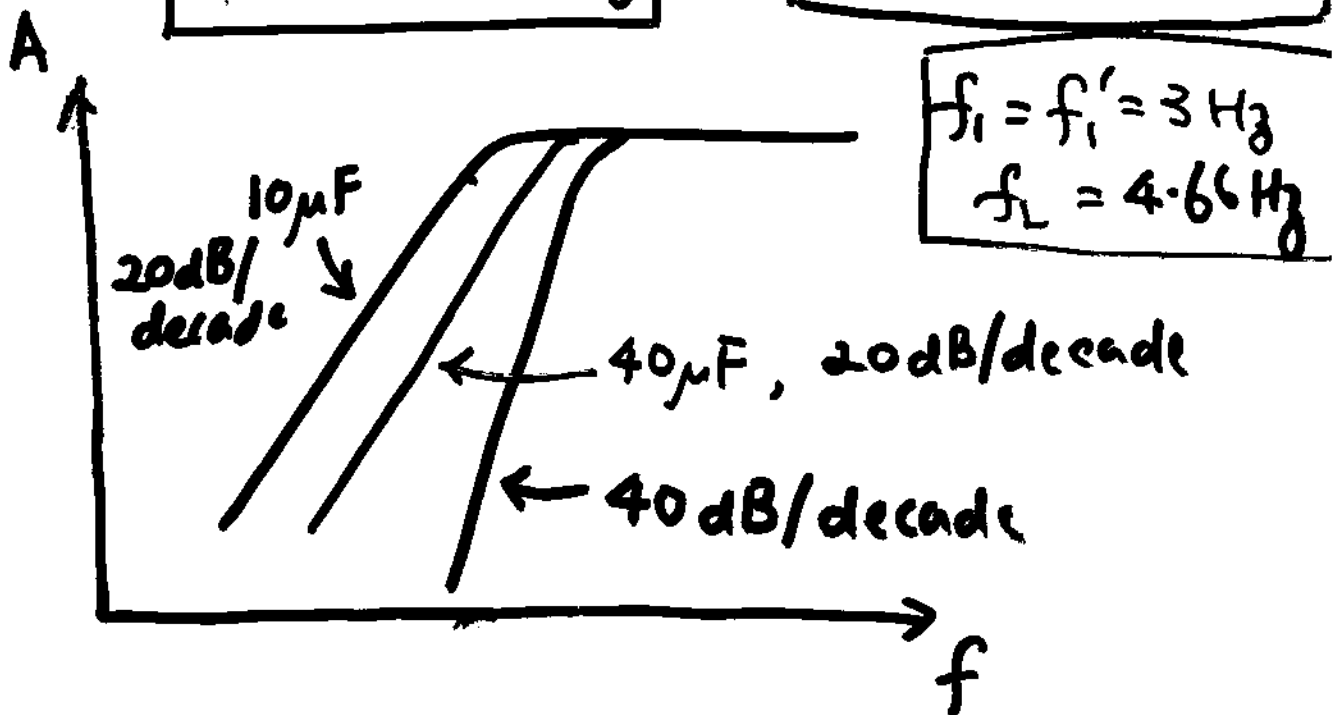
$$\begin{aligned} f_1 &= 1.50 \text{ Hz} \\ f_1' &= 30.0 \text{ Hz} \\ f_L &= 30.07 \text{ Hz} \end{aligned}$$



Approximation for f_L

1. For each C_c ,

Determine R_{eff} seen by C_c
assuming that other C_c 's are
shorted

Calculate $R_{eff} \cdot C_c = \tau_i$

2. Approximate $\omega_L = \frac{1}{\tau_1} + \frac{1}{\tau_2} + \dots$

> true lower corner freq


Note:

1. Works well when there exists
a ^{single} dominant τ_i

2. Otherwise, pick the ^{dominant} ~~closest~~ τ_i 's, ^{that} ~~are~~ ^{are} ~~close~~
solve $\left[1 + \left(\frac{f_1}{f_{min}}\right)^2\right] \dots \left[1 + \left(\frac{f_1^{(n)}}{f_{min}}\right)^2\right] = 2$

$f_{min} = \frac{1}{2\pi \tau_{min}}$, use τ_{min} & remaining
 τ_j 's to approx ω_L

CE Example

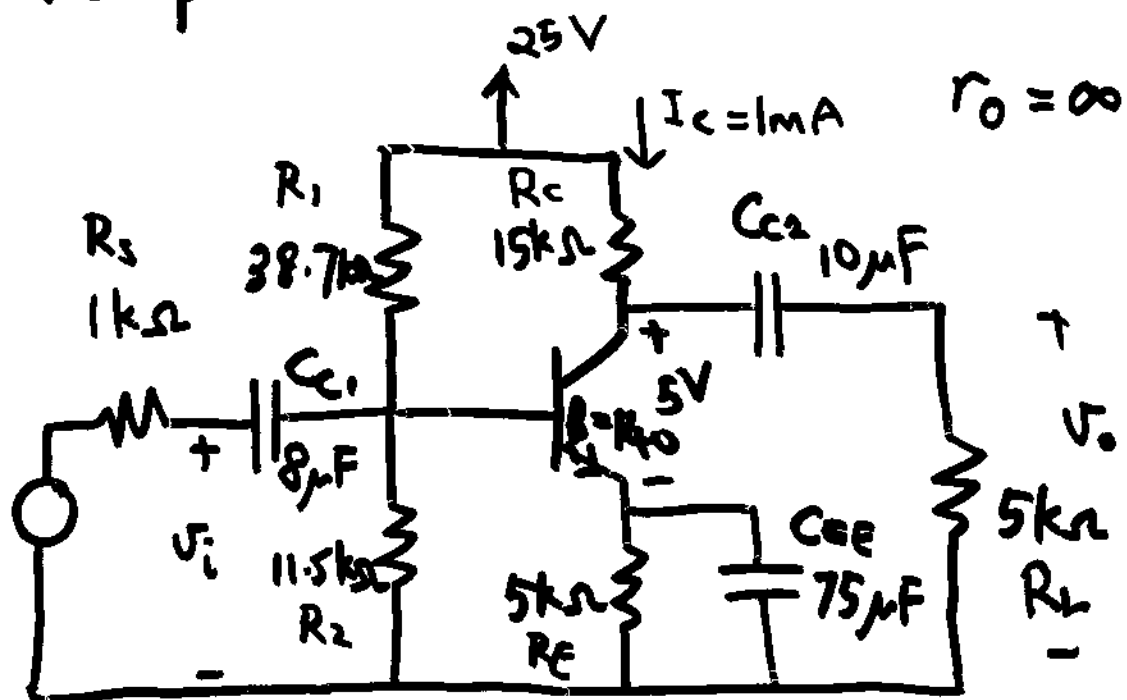

$$C_{c1}: R_{\text{eff},c1} = R_s + R_1 \parallel R_2 \parallel r_{\pi}$$

$$\tau_{s,c1} = [R_s + R_1 \parallel R_2 \parallel r_{\pi}] C_{c1}$$

$$= 28.6 \text{ ms}$$

$$f_{1,c1} = 5.6 \text{ Hz}$$

$$C_{c2}: R_{\text{eff},c2} = R_o + R_L$$

$$\tau_{s,c2} = 0.2 \text{ s}$$


$$f_{1,c2} = 0.8 \text{ Hz}$$

$$C_E: R_{\text{eff},CE} = R_E \parallel \frac{r_{\pi} + R_1 \parallel R_2 \parallel R_s}{\beta + 1}$$

$$\tau_{s,CE} = 2.5 \text{ ms}$$

$$f_{1,CE} = 63 \text{ Hz} \quad \boxed{63 \text{ Hz} < f_L < 69.4 \text{ Hz}}$$

CB Amplifier Design

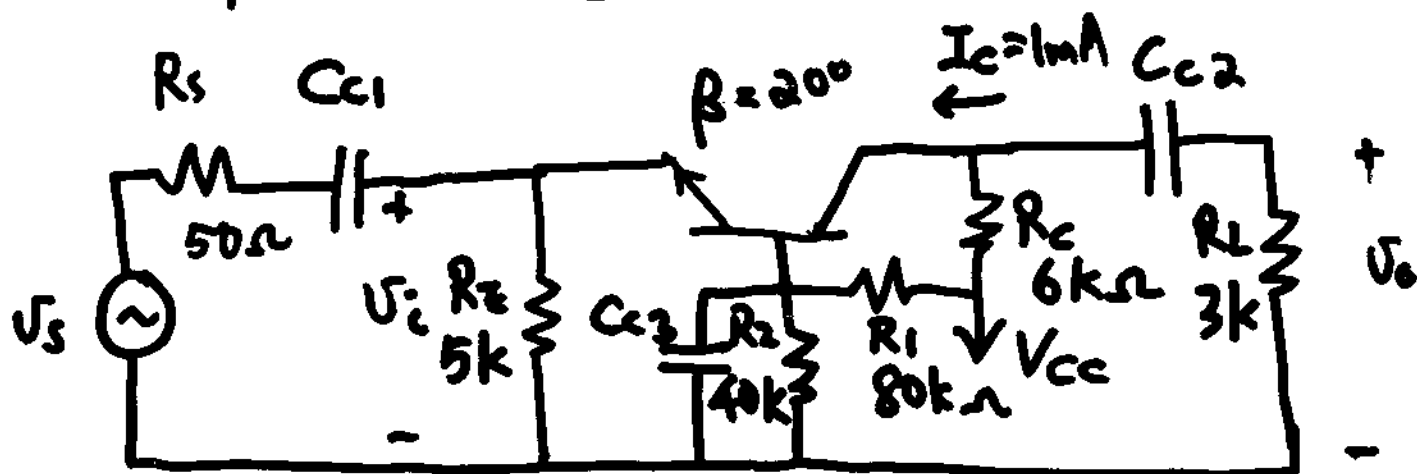

$$g_m = 38.5 \text{ mA/V}$$

$$r_o = \infty$$

$$r_{\pi} = 5.2 \text{ k}\Omega$$

Want $f_L = 10 \text{ Hz}$.

$$\tau_{s,c1} = [R_s + R_E \parallel \frac{r_{\pi}}{\beta+1}] C_{c1}$$

$$\tau_{s,c2} = [R_L + R_C] C_{c2}$$

$$\tau_{s,c3} = [R_1 \parallel R_2 \parallel (r_{\pi} + (\beta+1)(R_s \parallel R_E))] C_{c3}$$

Which will be smallest?

$$\tau_{s,c1} \approx (R_s + \frac{r_{\pi}}{201}) C_{c1} = 76 C_{c1}$$

$$\tau_{s,c2} = 9000 C_{c2}$$

$$\tau_{s,c3} \approx (R_1 \parallel R_2 \parallel r_{\pi} + (\beta+1)R_s) C_{c3} \approx 9600 C_{c3}$$

if $C_{c1} = C_{c2} = C_{c3}$

$\tau_{s,c1}$ is smallest

$$\text{Pick } 2\pi \cdot 10 = \frac{1}{76 C_{c1}}$$

$$\Rightarrow C_{c1} = 209 \mu\text{F}$$

Pick C_{c2}, C_{c3} st. $\tau_{s,c2}, \tau_{s,c3} \gg \tau_{s,c1}$

$$2\pi \cdot 1 = \frac{1}{9000 C_{c2}}$$

$$\Rightarrow C_{c2} = 18 \mu\text{F}$$

$$2\pi \cdot 1 = \frac{1}{9600 C_{c3}}$$

$$\Rightarrow C_{c3} = 17 \mu\text{F}$$

