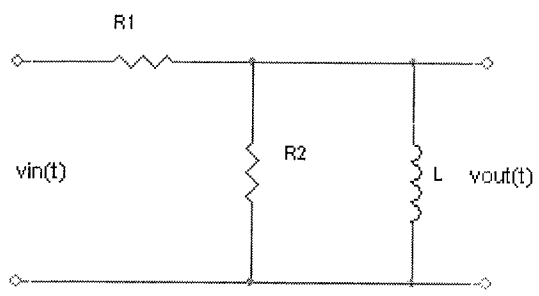


Consider the circuit below. Find:

- a) The filter type
- b) The value of the maximum voltage gain
- c) The 3-dB bandwidth



- a) Inductor is short @ low frequencies, so a high-pass circuit
- b) By inspection, Maximum gain will occur @ $\omega = \infty$,

$$H(s) = \frac{\frac{1}{\frac{1}{R_2} + \frac{1}{sL}}}{R_1 + \frac{1}{\frac{1}{R_2} + \frac{1}{sL}}} = \frac{\frac{R_2 s L}{R_2 + sL}}{R_1 + \frac{R_2 s L}{R_2 + sL}} = \frac{R_2 s L}{R_1 R_2 + R_1 s L + R_2 s L}$$

$$= \frac{s (R_2 L)}{s (R_1 L + R_2 L) + R_1 R_2} = \frac{s \left(\frac{R_2}{R_1 + R_2} \right)}{s + \frac{R_1 R_2}{(R_1 + R_2) L}}$$

$H_{max} = s(\infty) = \frac{R_2}{R_1 + R_2} = \text{v divider } R_2 \text{ \& } R_1, \text{ which is what we would expect.}$

c. $H(\omega_c) = \frac{R_2}{\sqrt{2}(R_1 + R_2)} = \frac{|j\omega_c \frac{R_2}{R_1 + R_2}|}{|j\omega_c + \frac{(R_1 R_2)}{(R_1 + R_2)} \frac{1}{L}|} = \frac{\omega_c \frac{R_2}{R_1 + R_2}}{\sqrt{\omega_c^2 + \left(\frac{R_1 R_2}{L} \right)^2}} = \frac{R_2}{\sqrt{2}(R_1 + R_2)}$

$$\frac{1}{\sqrt{2}} = \frac{\omega_c}{\sqrt{\omega_c^2 + \left(\frac{R_1 R_2}{L} \right)^2}} \Rightarrow \frac{1}{2\omega_c^2} = \frac{1}{\omega_c^2 + \left(\frac{R_1 R_2}{L} \right)^2}$$

$$2\omega_c^2 - \omega_c^2 = \omega_c^2 = \left(\frac{R_1 R_2}{L} \right)^2$$

$$\omega_c = \frac{R_1 R_2}{L}$$

Very similar to the R/L we are familiar with, except these 2 R's are in ||. Food for thought!