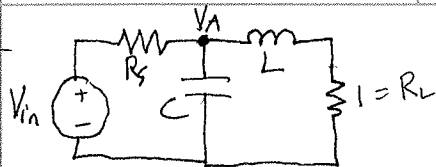


L17



a.

$$H(s) = \frac{V_A}{V_{in}} \cdot \frac{V_{out}}{V_A} = \frac{V_{out}}{V_{in}}$$

$$\frac{V_A}{V_{in}} = V_{\text{divider}} \rightarrow \frac{\frac{1}{sC} \parallel (sL+1)}{\frac{1}{sC} \parallel (sL+1) + R_s} V_{in} = \frac{\frac{1}{sC + \frac{1}{sL+1}}}{R_s + \frac{1}{sC + \frac{1}{sL+1}}} V_{in} = \frac{1}{sR_s C + \frac{R_s}{Ls+1} + 1}$$

$$\frac{V_{out}}{V_A} = \frac{V_{\text{divider}_2}}{sL+1} = \frac{1}{sL+1}$$

$$\frac{V_{out}}{V_{in}} = \frac{1}{(sL+1)(sR_s C + \frac{R_s}{Ls+1} + 1)} = \frac{1}{s^2 R_s C L + s R_s C + R_s + sL + 1}$$

$$= \frac{\frac{1}{R_s L C}}{s^2 + s \left[\frac{R_s C + L}{R_s L C} \right] + \frac{R_s + 1}{R_s L C}} = \frac{\frac{1}{R_s L C}}{s^2 + s \left[\frac{1}{L} + \frac{1}{R_s C} \right] + \frac{1 + 1/R_s}{L C}} \quad \checkmark$$

b. From table 21.1, 2nd order LP butterworth is of form:

$$s^2 + \sqrt{2}s + 1$$

Therefore $\frac{1}{L} + \frac{1}{R_s C} = \sqrt{2}$ & $\frac{1 + 1/R_s}{L C} = 1$ where $R_s = 2$

Solving, we get a quadratic equation with

Solution 1

$$C \cong 1.67 \text{ F}$$

$$L \cong 0.90 \text{ H}$$

Solution 2

$$C \cong 0.45 \text{ F}$$

$$L \cong 3.33 \text{ H}$$

c. $R_L = 2 \text{ k}\Omega$ $BW = 5 \text{ kHz}$ (From solution #2)

$$K_m = 2 \text{ k}$$

$$K_f = 5 \text{ k}$$

$$R_{s \text{ new}} = 4 \text{ k}$$

$$R_{L \text{ new}} = 2 \text{ k}$$

$$L_{\text{new}} = 1800 \text{ H}$$

$$C_{\text{new}} = 835 \mu\text{F}$$

$$BW_{\text{new}} = BW_{\text{old}} = 1 \text{ Hz}$$

$$\Rightarrow$$

$$\begin{aligned} R_{s \text{ final}} &= R_{s \text{ new}} \\ R_{L \text{ final}} &= R_{L \text{ new}} \\ L_{\text{final}} &= 0.36 \text{ H} \\ C_{\text{final}} &= 167 \text{ nF} \end{aligned}$$

$$BW_{\text{final}} = BW_{\text{old}} \cdot 5000 = \boxed{5 \text{ kHz}}$$