

# ECE 202 - Linear Circuit Analysis II

Exam 2 Solutions

October 30, 2008

## Solution 1

$$\begin{aligned}V_{out}(t) &= V_{in}(t) * h(t) \\&= 30 \sin[\pi(60t + 1)] * 2\delta\left(t - \frac{1}{40}\right) \\&= 60 \sin\left[\pi\left\{60\left(t - \frac{1}{40}\right) + 1\right\}\right] \\&= 60 \sin\left[\pi\left(60t - \frac{1}{2}\right)\right] \\&= 60 \sin\left[60\pi t - \frac{\pi}{2}\right] = -60 \cos(60\pi t)\end{aligned}$$

Hence (3) is the correct answer

## Solution 2

A 40 dB/decade fall from 100 implies the term,

$$\frac{1}{1 + \left(\frac{s}{100}\right)^2}$$

Similarly, the flat portion from 1000 to 100000 implies the term,

$$1 + \left(\frac{s}{1000}\right)^2$$

A 20 dB/decade rise from  $10^5$  implies the term,

$$1 + \frac{s}{10^5}$$

Finally the flat portion from  $10^7$  implies the term,

$$\frac{1}{1 + \frac{s}{10^7}}$$

To account for the start at 80 dB, we must have a constant term equal to  $10^{80/20} = 10^4$ . The gain function can therefore be written as,

$$H(s) = 10^4 \frac{\left[1 + \left(\frac{s}{1000}\right)^2\right] \left(1 + \frac{s}{10^5}\right)}{\left[1 + \left(\frac{s}{100}\right)^2\right] \left(1 + \frac{s}{10^7}\right)}$$

Hence (8) is the correct answer

### Solution 3

$$\begin{aligned}V_{in}(t) &= 10u(t) \\h(t) &= 3[u(t-3) - u(t-6)] + 8[u(t-6) - u(t-9)] \\&= 3u(t-3) + 5u(t-6) - 8u(t-9) \\I_{out}(t) &= V_{in}(t) * h(t) \\&= V_{in}^{(1)}(t) * h^{(-1)}(t) \text{ (convolution algebra)} \\&= 10\delta(t) * [3r(t-3) + 5r(t-6) - 8r(t-9)] \\&= 30r(t-3) + 50r(t-6) - 80r(t-9)\end{aligned}$$

Hence (5) is the correct answer

### Solution 4

From the frequency response plot,

$$\begin{aligned}Q &= \frac{\omega_m}{B_\omega} \\&= \frac{\omega_m}{\omega_2 - \omega_1} \\&= \frac{65k}{80k - 50k} = 13/6\end{aligned}$$

Hence (6) is the correct answer

### Solution 5

$$\begin{aligned}y(t) &= 3u(t) * h(t) \\&= \int_{-\infty}^{\infty} h(\tau)3u(t-\tau) d\tau \\&= 3 \int_{-\infty}^t h(\tau) d\tau \\ \Rightarrow y(6) &= 3 \int_{-\infty}^6 h(\tau) d\tau \\&= 3 \left[ (4 \times 4) + \frac{1}{2} \times 2 \times (4+2) \right] = 66\end{aligned}$$

Hence (7) is the correct answer

### Solution 6

Source transformation on the left side using Norton and Thevenin theorems respectively results in the circuit shown in Figure 1. Again, transformation using Norton theorem results in a parallel RLC circuit shown in Figure 2 for which all results are well known.

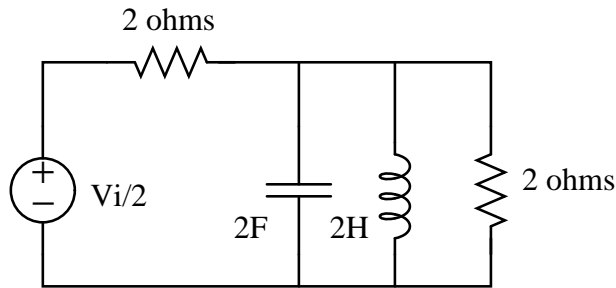


Figure 1: Source transformation

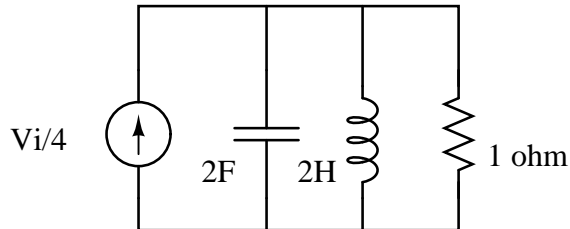


Figure 2: Parallel RLC circuit

Thus,

$$Q = R\sqrt{\frac{C}{L}} = 1$$

$$B_\omega = \frac{1}{RC} = 0.5 \text{ rad/s}$$

Hence (4) is the correct answer

## Solution 7

Here  $\omega = 0.5$ , thus the parallel RLC combination resonates at this frequency. The equivalent circuit is reduced to the one shown in Figure 3 (remember that there is a parasitic resistance  $R_p$  of the order of kilo ohms associated with the capacitor, that is how we get RLC in parallel),

The voltages at the inverting and non-inverting terminals of an ideal op-amp are equal. Thus,

$$V_+ = V_-$$

$$V_s = V_o \frac{R_p}{R_p + 1}$$

$$\approx V_o$$

$$\text{or } V_o = V_s = 2 \sin(0.5t + 30^\circ)$$

Hence (5) is the correct answer

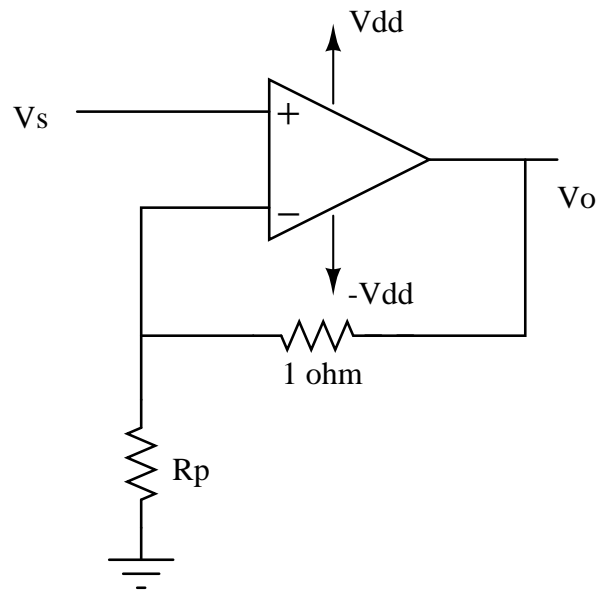


Figure 3: Simplified circuit

### Solution 8

$$\begin{aligned}
 H(s) &= -\frac{2s + 3}{s^2 + 2s + 7} \\
 H(j2) &= -\frac{4j + 3}{-4 + 4j + 7} \\
 &= -1 = 1\angle 180^\circ \\
 \mathbf{V}_s &= 3\angle 45^\circ \\
 \Rightarrow |\mathbf{V}_{out}| &= |\mathbf{V}_s| |H(j2)| = 3 \\
 \angle \mathbf{V}_{out} &= \angle \mathbf{V}_s + \angle H(j2) = 225^\circ
 \end{aligned}$$

Hence (2) is the correct answer

### Solution 9

$$\begin{aligned}
 v_{out}(t) &= 2h(t) - h(t - 1) + 3h(t - 2) \\
 \Rightarrow v_{out}(2.5) &= 2h(2.5) - h(1.5) + 3h(0.5) \\
 &= 0 - (2 - 1.5) + 3 = 2.5
 \end{aligned}$$

Hence (4) is the correct answer

### Solution 10

$$\begin{aligned}
 \mathbf{I} &= \frac{20\angle 0^\circ}{2} = 10\angle 0^\circ \\
 V_L(j\omega_r) &= j\omega_r L \mathbf{I} \\
 \Rightarrow |V_L(j\omega_r)| &= \omega_r L |\mathbf{I}| \\
 &= \frac{1}{\sqrt{LC}} L |\mathbf{I}| \\
 &= \sqrt{\frac{L}{C}} |\mathbf{I}| = 2 \times 10 = 20
 \end{aligned}$$

Hence (3) is the correct answer

## Solution 11

$$\begin{aligned}H(s) &= K \frac{s}{s^2 + 2\sigma_p s + \omega_p^2} \\&= K \frac{s}{s^2 + \left(\frac{\omega_p}{Q_p}\right) s + \omega_p^2} \\&= 10 \frac{s}{(s + 3 - 4j)(s + 3 + 4j)} \\&= 10 \frac{s}{(s + 3)^2 + 16} \\&= 10 \frac{s}{s^2 + 6s + 25} \\ \Rightarrow \omega_p &= 5 \\ Q_p &= 5/6\end{aligned}$$

Hence (1) is the correct answer