

ECE 202 Summer 2009

Exam 2

7/13/09


Problem	Score
1	/25
2	/25
3	/25
4	/25
Total	/100

Question 1: (25 Points)

In the circuit below,

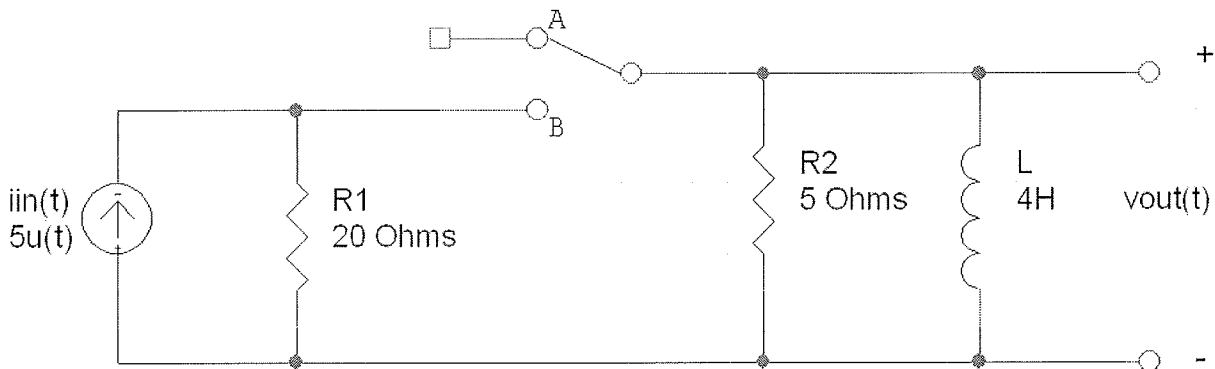
- 1) The switch has been in **position A** for a long time. ($t < 0$)
- 2) Then, it switches to **position B** for 2 seconds. ($0 \leq t < 2$)
- 3) Finally, it switches back to **position A**. ($2 \leq t$)

What is the voltage across the inductor at $t=6$?



@ $t < 0$, $i_L = 0$; $i_L(0^-) = 0A$

Region 1: Position B

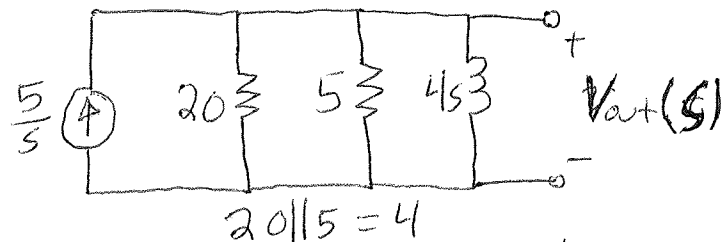

Current division:
$$I_L = I_{in} \cdot \frac{\frac{1}{4s}}{\frac{1}{4} + \frac{1}{4s}} = \frac{5}{s(s+1)}$$

Partial fractions
$$\frac{5}{s(s+1)} = \frac{A}{s} + \frac{B}{s+1}$$
@ $s=1 \Rightarrow B=-5$
@ $s=0 \Rightarrow A=5$


$0 \leq t < 2$
$$i_L(t) = 5u(t) - 5e^{-t}u(t)$$

$$i_L(2^-) = 5(1 - e^{-2})$$

Region 2: $2 \leq t$ $t' = t - 2$

Circuit starts @ $t' = 0$

Position A

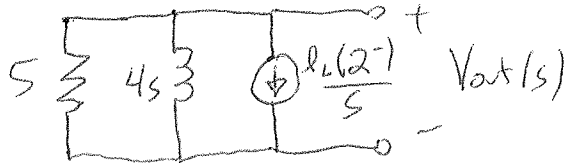

Want: $V_{out}(t)$ @ $t = 6$

$$\begin{aligned} V_{out} &= -\frac{l_L(2^-)}{s} \cdot \frac{1}{\frac{1}{4s} + \frac{1}{5}} \\ &= -l_L(2^-) \cdot \frac{1}{s} \cdot \frac{5s}{s + \frac{5}{4}} \\ &= -5 l_L(2^-) \cdot \frac{1}{s + \frac{5}{4}} \end{aligned}$$

$$v_{out}(t) = -5 l_L(2^-) e^{-\frac{5}{4}t'} u(t')$$

$$v_{out}(6) = -5(1 - e^{-2}) \cdot 5 \cdot e^{-\frac{5}{4}(6-2)} u(6-2)$$


$$v_{out}(6) = 25(e^{-2} - 1)e^{-5}$$

Question 2: (25 Points)

Given the graph below with $|H(j1)| = 10$ and a DC phase of 0° .

- 1) Find $H(s)$
- 2) Find Magnitude and Phase of $H(s)$ at $\omega=2$

$$\angle K = 0^\circ$$

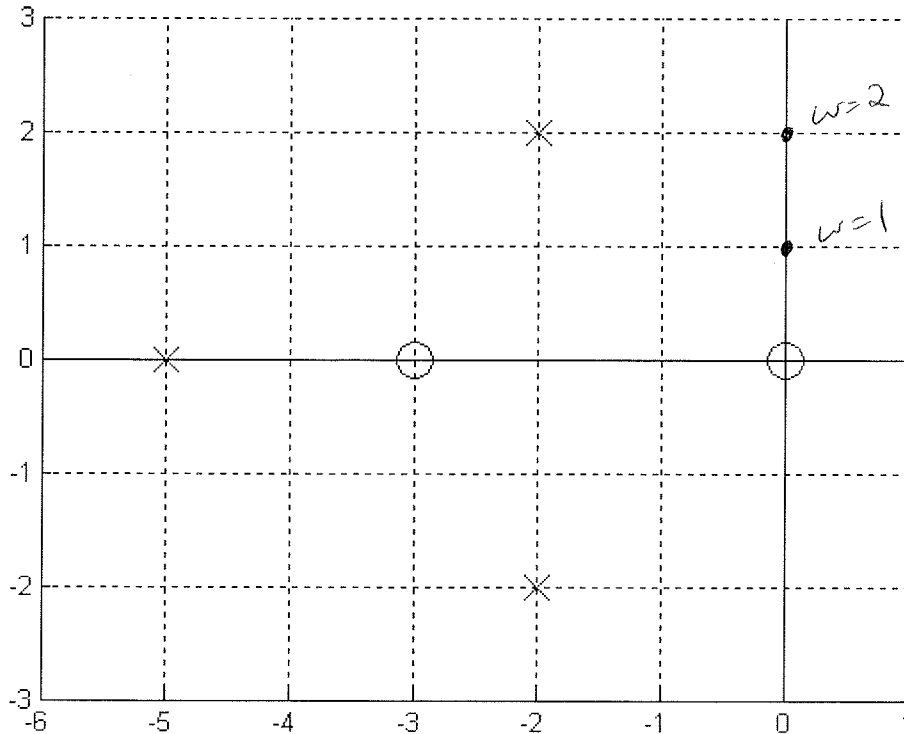

$$H(s) = K \frac{s(s+3)}{(s+5)(s^2+4s+8)}$$

Need to find $|K|$

$$H(j1) = 10 = \frac{|K| \cdot 1 \cdot \sqrt{10}}{\sqrt{26} \cdot \sqrt{5} \cdot \sqrt{13}} \Rightarrow |K| = 130$$

$$H(s) = 130 \frac{s(s+3)}{(s+5)(s^2+4s+8)}$$

$$|H(j2)| = \frac{130 \cdot 2 \cdot \sqrt{13}}{2 \cdot \sqrt{20} \cdot \sqrt{29}} = 65 \sqrt{\frac{13}{145}}$$

$$\angle H(j2) = 0^\circ + 90^\circ + \arctan\left(\frac{2}{3}\right) - \arctan\left(\frac{4}{2}\right) - 0^\circ - \arctan\left(\frac{2}{5}\right) \approx 38.5^\circ$$


Question 3: (25 Points)

For the circuit below, find $v_{out}(t)$, given that

$$v_{in}(t) = 120\cos(5t + 30^\circ)$$

$$Z_1 = \frac{1}{\frac{s}{20} + \frac{1}{s+5}}$$

$$= \frac{20(s+5)}{s^2 + 5s + 20}$$

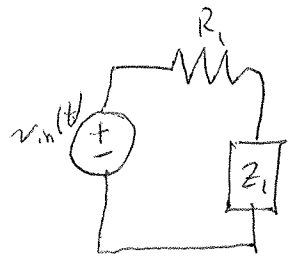

V divider

$$V_{out}(s) = V_{in}(s) \cdot \frac{\frac{20(s+5)}{s^2 + 5s + 20}}{20 + \frac{20(s+5)}{s^2 + 5s + 20}}$$


$$\frac{V_{out}(s)}{V_{in}(s)} = H(s) = \frac{s+5}{s^2 + 5s + 20 + s+5} = \frac{s+5}{s^2 + 6s + 25}$$

$$H(j5) = \frac{5 + j5}{-25 + j30 + 25} = \frac{5\sqrt{2} \angle 45^\circ}{30 \angle 90^\circ}$$



$$H(j5) = \frac{\sqrt{2}}{6} \angle -45^\circ$$

$$v_{out}(t) = 120 \cdot \frac{\sqrt{2}}{6} \cdot \cos(5t + 30^\circ - 45^\circ)$$

$$v_{out}(t) = 20\sqrt{2} \cos(5t - 15^\circ)$$

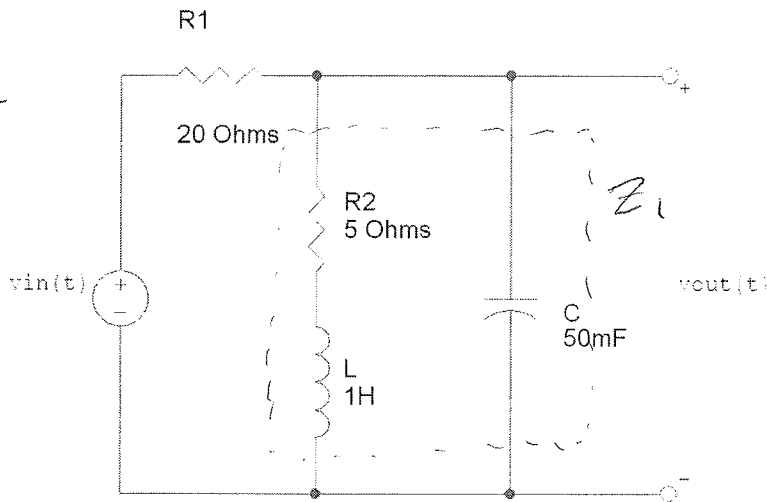

Question 4: (25 Points)

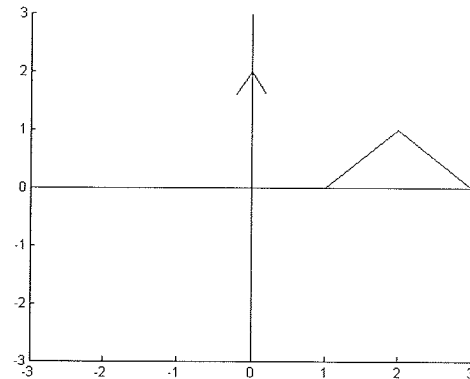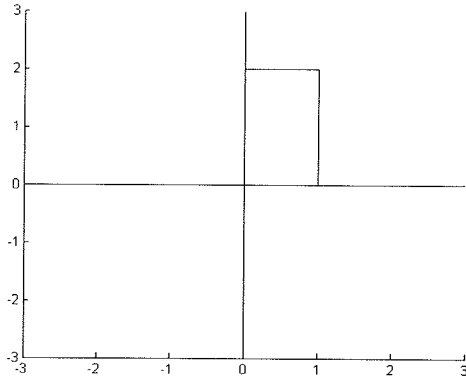Find: $f(t) * g(t)$ 

$$f(t) = 2u(t) - 2u(t-1) \quad g(t) = 2\delta(t) + r(t-1) - 2r(t-2) + r(t-3)$$

Region 0 $t \leq 0$ 0

Region 1 $0 \leq t \leq 1$ 4

Region 2 $1 \leq t \leq 2$

$$\int_1^t 2(t-1) dt = t^2 - 2t \Big|_1^t = t^2 - 2t + 1$$

Region 3 $2 \leq t \leq 3$

Two parts:


$$\int_{t-1}^2 2(t-1) dt + \int_2^t 2(3-t) dt$$

$$(t^2 - 2t) \Big|_{t-1}^2 + [-t^2 + 6t]_2^t$$

$$4 - 4 - [(t-1)^2 - 2(t-1)] - t^2 + 6t + 4 - 12$$

$$- [t^2 - 2t + 1 - 2t + 2] - t^2 + 6t - 8$$

$$\boxed{-2t^2 + 10t - 11}$$

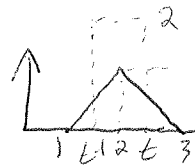

Region 4 $3 \leq t \leq 4$

$$\int_{t-1}^3 2(3-t) dt = -t^2 + 6t \Big|_{t-1}^3$$

$$-9 + 18 - [-(t-1)^2 + 6(t-1)]$$

$$9 - [-(t^2 - 2t + 1) + 6t - 6]$$

$$9 - [-t^2 + 2t - 1 + 6t - 6]$$

$$\boxed{t^2 - 8t + 16}$$

Region 5

$$t \geq 4$$

$$\boxed{0}$$

Laplace Transform Pairs

Item Number	$f(t)$	$\mathcal{L}\{f(t)\}=F(s)$
1	$K\delta(t)$	K
2	$Ku(t)$ or K	$\frac{K}{s}$
3	rt	$\frac{1}{s^2}$
4	$t^n u(t)$	$\frac{n!}{s^{n+1}}$
5	$e^{-at}u(t)$	$\frac{1}{s+a}$
6	$te^{-at}u(t)$	$\frac{1}{(s+a)^2}$
7	$t^n e^{-at}u(t)$	$\frac{n!}{(s+a)^{n+1}}$
8	$\sin(\omega t)u(t)$	$\frac{\omega}{s^2 + \omega^2}$
9	$\cos(\omega t)u(t)$	$\frac{s}{s^2 + \omega^2}$
10	$e^{-at} \sin(\omega t)u(t)$	$\frac{\omega}{(s+a)^2 + \omega^2}$
11	$e^{-at} \cos(\omega t)u(t)$	$\frac{s+a}{(s+a)^2 + \omega^2}$
12	$t \sin(\omega t)u(t)$	$\frac{2\omega s}{(s^2 + \omega^2)^2}$
13	$t \cos(\omega t)u(t)$	$\frac{s^2 - \omega^2}{(s^2 + \omega^2)^2}$
14	$\sin(\omega t + \varphi)u(t)$	$\frac{s \sin \varphi + \omega \cos \varphi}{s^2 + \omega^2}$
15	$\cos(\omega t + \varphi)u(t)$	$\frac{s \cos \varphi - \omega \sin \varphi}{s^2 + \omega^2}$
16	$e^{-at}[\sin(\omega t) - \omega t \cos(\omega t)]u(t)$	$\frac{2\omega^3}{[(s+a)^2 + \omega^2]^2}$
17	$te^{-at} \sin(\omega t)u(t)$	$2\omega \frac{s+a}{[(s+a)^2 + \omega^2]^2}$
18	$e^{-at} \left[C_1 \cos(\omega t) + \left(\frac{C_2 - C_1 a}{\omega} \right) \sin(\omega t) \right] u(t)$	$\frac{C_1 s + C_2}{(s+a)^2 + \omega^2}$
19	$2\sqrt{A^2 + B^2} e^{-at} \cos \left[\omega t - \tan^{-1} \left(\frac{B}{A} \right) \right] u(t)$	$\frac{A + jB}{s + a + j\omega} + \frac{A - jB}{s + a - j\omega}$
20	$2\sqrt{A^2 + B^2} t e^{-at} \cos \left[\omega t - \tan^{-1} \left(\frac{B}{A} \right) \right] u(t)$	$\frac{A + jB}{(s + a + j\omega)^2} + \frac{A - jB}{(s + a - j\omega)^2}$

Laplace Properties

Property	$f(t)$	$\mathcal{L}\{f(t)\}=F(s)$
Linearity	$a_1f_1(t) + a_2f_2(t)$	$a_1F(s) + a_2F_2(s)$
Time Shift	$f(t - T)u(t - T)$	$e^{-sT}F(s)$
Multiplication by t	$tf(t)u(t)$	$-\frac{d}{ds}F(s)$
Multiplication by t^n	$t^n f(t)$	$(-1)^n \frac{d^n F(s)}{ds^n}$
Frequency Shift	$e^{-at}f(t)$	$F(s + a)$
Time Differentiation	$\frac{d}{dt}f(t)$	$sF(s) - f(0^-)$
Second-order Differentiation	$\frac{d^2 f(t)}{dt^2}$	$s^2 F(s) - sf(0^-) - f^{(1)}(0^-)$
n th-order Differentiation	$\frac{d^n f(t)}{dt^n}$	$s^n F(s) - s^{n-1}f(0^-) - s^{n-2}f^{(1)}(0^-) - \dots - f^{(n-1)}(0^-)$
Time Integration	(a) $\int_{-\infty}^t f(q)dq$ (b) $\int_{0^-}^t f(q)dq$	$\frac{F(s)}{s} + \frac{\int_{-\infty}^{0^-} f(q)dq}{s}$ $\frac{F(s)}{s}$
Time or Frequency Scaling	$f(at)$	$\frac{1}{a}F\left(\frac{s}{a}\right)$