

ECE 202 Summer 2009

Exam 3


7/24/09

Problem	Score
1	/25
2	/25
3	/25
4	/25
Total	/100

Question 1: (25 Points)

For the circuit below, find:

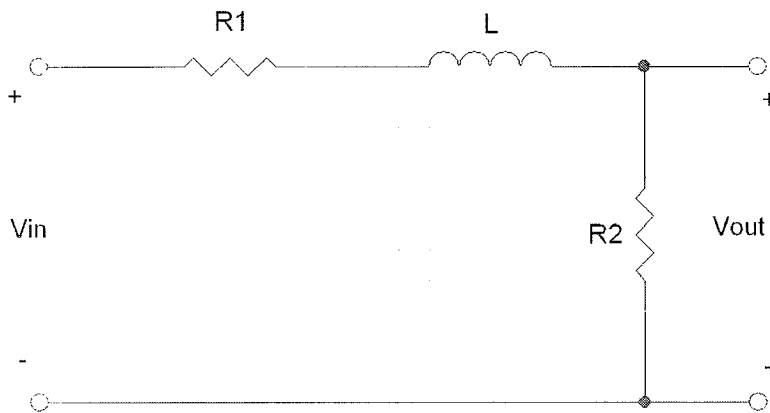- 1) The filter classification (High-pass, Low-pass, Band-pass, or Band-reject)
Why?
- 2) Find H_{\max}
- 3) Find the cutoff frequency/frequencies



1) Low-Pass filter. The inductor is a short at low frequencies, and an open @ high frequencies. Therefore, low frequencies will be passed to the output, and high frequencies will be suppressed.

2) H_{\max} occurs @ $s=0$, and the inductor is a short

$$\therefore \text{V divider } H_{\max} = \frac{R_2}{R_1 + R_2}$$

$$3) H(s) = \frac{R_2}{R_1 + R_2 + sL}$$

$$@ \omega_c \Rightarrow |H(j\omega_c)| = \frac{H_{\max}}{\sqrt{2}} = \frac{|R_2|}{|R_1 + R_2 + j\omega_c L|}$$

$$\frac{R_2}{\sqrt{2}(R_1 + R_2)} = \frac{R_2}{|R_1 + R_2 + j\omega_c L|}$$

$$\frac{R_2}{\sqrt{2} (R_1 + R_2)} = \frac{R_2}{|R_1 + R_2 + j\omega_c L|}$$

$$\sqrt{2} \frac{(R_1 + R_2)}{R_2} = \frac{|R_1 + R_2 + j\omega_c L|}{R_2}$$

$$\sqrt{2} \frac{(R_1 + R_2)}{R_2} = \frac{\sqrt{(R_1 + R_2)^2 + \omega_c^2 L^2}}{R_2}$$

$$2 \frac{(R_1 + R_2)^2}{R_2^2} = \frac{(R_1 + R_2)^2}{R_2^2} + \frac{\omega_c^2 L^2}{R_2^2}$$

$$\frac{(R_1 + R_2)^2}{\cancel{R_2^2}} = \frac{\omega_c^2 L^2}{\cancel{R_2^2}}$$

$$\frac{(R_1 + R_2)^2}{L^2} = \omega_c^2$$


$$\boxed{\omega_c = \frac{R_1 + R_2}{L}}$$

Question 2: (25 Points)

For the circuit below,

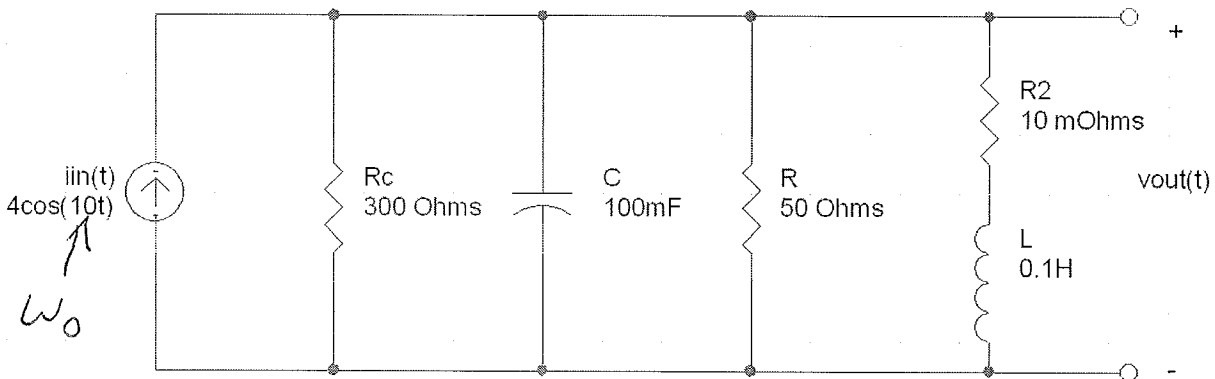- 1) Find the BW
- 2) Find H_{\max}

Hint: Using Q_{coil} formulas (located on back of exam), transform R_2 and L as done in class, then combine the three resistances into R_{eq} to get $H(s)$ for a parallel RLC circuit.




$$Q_{\text{coil}} = Q_L = \frac{\omega_0 L}{R_s} = \frac{10 \cdot 0.1}{10\text{m}} = 100$$

$Q > 6$, therefore,

$$\hat{L} = L = 0.1 \text{ H} \quad \& \quad \hat{R}_L = Q_L^2 R_2 = 100 \Omega$$

$$R_{\text{eq}} = R_c \parallel \hat{R}_L \parallel R = \underline{30 \Omega}$$

New circuit:

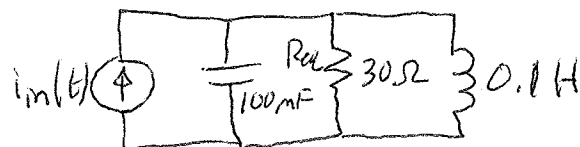

$$H(s) = \frac{s/C}{s^2 + \frac{1}{R_{\text{eq}}}s + \frac{1}{LC}} \quad H_m = \frac{|K|}{2\sigma_p} = \frac{\frac{1}{C}}{\frac{1}{R_{\text{eq}}C}} = R_{\text{eq}} = \boxed{30}$$

$$\text{BW} = 2\sigma_p = \frac{1}{R_{\text{eq}}C} = \frac{1}{30 \cdot 0.1} = \boxed{\frac{1}{3} \text{ rad}}$$

Question 3: (25 Points)

For the two-pole Sallen-Key Low-Pass Normalized Butterworth-type filter below, **prove that this is a Normalized Butterworth low-pass filter** find new component values to **make $\omega_c = 1\text{M rad/s}$ and $C_1=C_2 = 1\text{nF}$** . Remember, A Normalized Butterworth filter has a cutoff frequency of 1 rad/s, and its two-pole form is $s^2 + \sqrt{2}s + 1$.

The transfer function of the circuit is:

$$H(s) = \frac{K}{R_1 R_2 C_1 C_2} \frac{1}{s^2 + \left(\frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} + \frac{1-K}{R_2 C_2} \right) s + \frac{1}{R_1 R_2 C_1 C_2}}$$


Where:

$$K = \frac{R_a + R_b}{R_a}$$

Given:

$$R_1 = 10\sqrt{2}; R_2 = 20\sqrt{2}; C_1 = \frac{1}{20}F; C_2 = \frac{1}{20}F; R_a = R_b$$

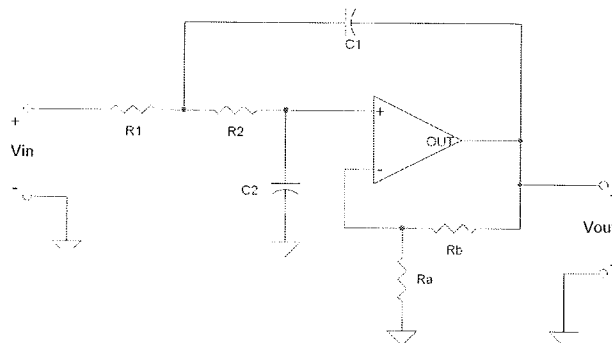Hint: In other words, use the given formulas and the Normalized Butterworth equation to prove that it is a Butterworth function. Then, use frequency and magnitude scaling to get the correct new component values.



Proof:

$$s^2 + \sqrt{2}s + 1 = s^2 + \left(\frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} + \frac{1-K}{R_2 C_2} \right) s + \frac{1}{R_1 R_2 C_1 C_2}$$

if $R_a = R_b$

$$\sqrt{2} = \left(\frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} + \frac{1-K}{R_2 C_2} \right)$$

$$1 = \frac{1}{R_1 R_2 C_1 C_2}$$

$$K = \frac{R_a + R_b}{R_a} = \frac{2R_a}{R_a} = 2$$

$$\sqrt{2} = \left(\frac{1}{10\sqrt{2} \cdot \frac{1}{20}} + \frac{1}{20\sqrt{2} \cdot \frac{1}{20}} - \frac{1}{20\sqrt{2} \cdot \frac{1}{20}} \right)$$

$$1 = \frac{1}{10\sqrt{2} \cdot 20\sqrt{2} \cdot \frac{1}{20} \cdot \frac{1}{20}}$$

$$\sqrt{2} = \frac{1}{10\sqrt{2} \cdot \frac{1}{20}} \Rightarrow 2 = \frac{1}{10 \cdot \frac{1}{20}} = 2 \quad \checkmark$$

$$1 = \frac{1}{\frac{10 \cdot 2}{20}} = 1 \quad \checkmark$$

First, we frequency scale from 1 rad/s to 1 Mrad/s

$$K_f = 1 \times 10^6$$

$$C_{\text{new}} = C_{2\text{new}} = \frac{C_{1,2\text{old}}}{1 \times 10^6} = \frac{1}{20} \times 10^{-6} \text{F} = 50 \text{nF}$$


Next, we use magnitude scaling

$$\sqrt{\frac{C_{1,2\text{old}}}{K_m}} = 1 \text{nF} \Rightarrow K_m = 50, \quad \boxed{C_1 = C_2 = 1 \text{nF}}$$

$$R_{1\text{old}} \cdot K_m = R_{1\text{new}} = 50 \cdot 10\sqrt{2} = \boxed{500\sqrt{2} \Omega}$$

$$R_{2\text{old}} \cdot K_m = R_{2\text{new}} = 50 \cdot 20\sqrt{2} = 1000\sqrt{2} \Omega = \boxed{\sqrt{2} \text{k}\Omega}$$

Question 4: (25 Points)

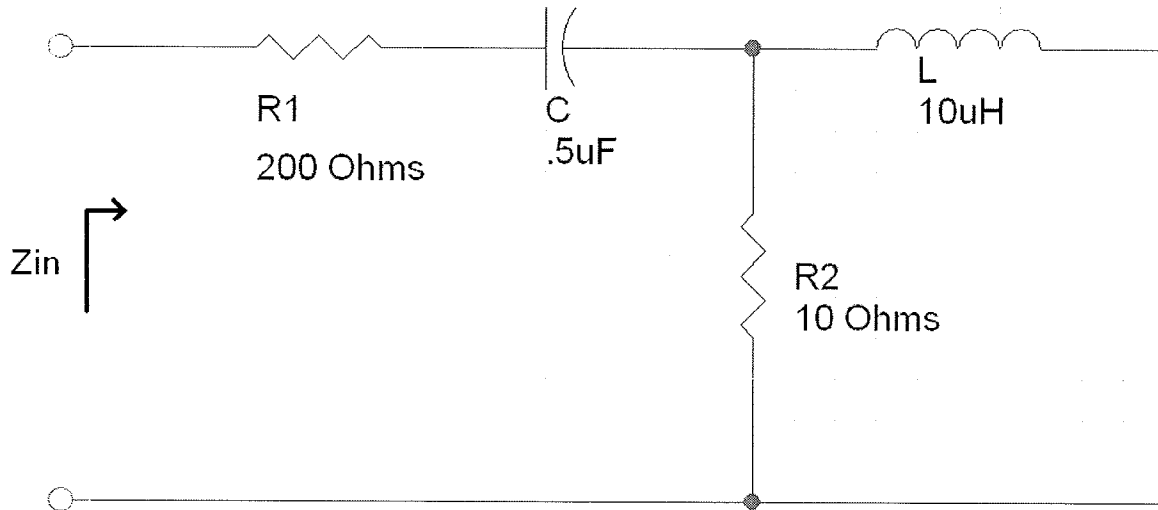Find the resonant frequency of Z_{in} 

$$Z_{in} = R_1 + \frac{1}{j\omega C} + \frac{1}{\frac{1}{R_2} + \frac{1}{j\omega L}} = R_1 - \frac{j}{\omega C} + \frac{jR_2\omega L}{j\omega L + R_2} \cdot \frac{R_2 - j\omega L}{R_2 - j\omega L}$$

$$Z_{in}(j\omega) = R_1 - \frac{j}{\omega C} + \frac{jR_2^2\omega L + R_2\omega^2 L^2}{R_2^2 + \omega^2 L^2}$$

$$= R_1 + \frac{R_2\omega^2 L^2}{R_2^2 + \omega^2 L^2} + j \left[\frac{R_2^2\omega L}{R_2^2 + \omega^2 L^2} - \frac{1}{\omega C} \right]$$

$$\text{@ } \omega_r, \quad Z_{in} = R_e + j \cdot 0$$

$$\therefore \frac{1}{\omega_r C} = \frac{R_2^2\omega_r L}{R_2^2 + \omega_r^2 L^2}$$

$$\omega_r^2 R_2^2 L C = R_2^2 + \omega_r^2 L^2$$

$$\omega_r^2 [R_2^2 L C - L^2] = R_2^2$$

$$\omega_r = \sqrt{\frac{R_2^2}{R_2^2 L C - L^2}} = \sqrt{\frac{100}{100 \cdot 5e^{-10} - 1e^{-10}}} = \sqrt{\frac{100}{5e^{-10} - 1e^{-10}}} = \sqrt{\frac{100}{4e^{-10}}}$$











$$= \frac{10}{\sqrt{4e^{-10}}} = \frac{10}{2e^{-5}} = 5e^5 = \boxed{500,000 \text{ rad/s}}$$

Laplace Transform Pairs

Item Number	$f(t)$	$\mathcal{L}\{f(t)\}=F(s)$
1	$K\delta(t)$	K
2	$Ku(t)$ or K	$\frac{K}{s}$
3	rt	$\frac{1}{s^2}$
4	$t^n u(t)$	$\frac{n!}{s^{n+1}}$
5	$e^{-at}u(t)$	$\frac{1}{s+a}$
6	$te^{-at}u(t)$	$\frac{1}{(s+a)^2}$
7	$t^n e^{-at}u(t)$	$\frac{n!}{(s+a)^{n+1}}$
8	$\sin(\omega t)u(t)$	$\frac{\omega}{s^2 + \omega^2}$
9	$\cos(\omega t)u(t)$	$\frac{s}{s^2 + \omega^2}$
10	$e^{-at} \sin(\omega t)u(t)$	$\frac{\omega}{(s+a)^2 + \omega^2}$
11	$e^{-at} \cos(\omega t)u(t)$	$\frac{s+a}{(s+a)^2 + \omega^2}$
12	$t \sin(\omega t)u(t)$	$\frac{2\omega s}{(s^2 + \omega^2)^2}$
13	$t \cos(\omega t)u(t)$	$\frac{s^2 - \omega^2}{(s^2 + \omega^2)^2}$
14	$\sin(\omega t + \varphi)u(t)$	$\frac{s \sin \varphi + \omega \cos \varphi}{s^2 + \omega^2}$
15	$\cos(\omega t + \varphi)u(t)$	$\frac{s \cos \varphi - \omega \sin \varphi}{s^2 + \omega^2}$
16	$e^{-at}[\sin(\omega t) - \omega t \cos(\omega t)]u(t)$	$\frac{2\omega^3}{[(s+a)^2 + \omega^2]^2}$
17	$te^{-at} \sin(\omega t)u(t)$	$2\omega \frac{s+a}{[(s+a)^2 + \omega^2]^2}$
18	$e^{-at} \left[C_1 \cos(\omega t) + \left(\frac{C_2 - C_1 a}{\omega} \right) \sin(\omega t) \right] u(t)$	$\frac{C_1 s + C_2}{(s+a)^2 + \omega^2}$
19	$2\sqrt{A^2 + B^2} e^{-at} \cos \left[\omega t - \tan^{-1} \left(\frac{B}{A} \right) \right] u(t)$	$\frac{A + jB}{s + a + j\omega} + \frac{A - jB}{s + a - j\omega}$
20	$2\sqrt{A^2 + B^2} t e^{-at} \cos \left[\omega t - \tan^{-1} \left(\frac{B}{A} \right) \right] u(t)$	$\frac{A + jB}{(s + a + j\omega)^2} + \frac{A - jB}{(s + a - j\omega)^2}$

Laplace Properties

Property	$f(t)$	$\mathcal{L}\{f(t)\}=F(s)$
Linearity	$a_1f_1(t) + a_2f_2(t)$	$a_1F(s) + a_2F_2(s)$
Time Shift	$f(t - T)u(t - T)$	$e^{-sT}F(s)$
Multiplication by t	$tf(t)u(t)$	$-\frac{d}{ds}F(s)$
Multiplication by t^n	$t^n f(t)$	$(-1)^n \frac{d^n F(s)}{ds^n}$
Frequency Shift	$e^{-at}f(t)$	$F(s + a)$
Time Differentiation	$\frac{d}{dt}f(t)$	$sF(s) - f(0^-)$
Second-order Differentiation	$\frac{d^2 f(t)}{dt^2}$	$s^2 F(s) - sf(0^-) - f^{(1)}(0^-)$
n th-order Differentiation	$\frac{d^n f(t)}{dt^n}$	$s^n F(s) - s^{n-1}f(0^-) - s^{n-2}f^{(1)}(0^-) - \dots - f^{(n-1)}(0^-)$
Time Integration	(a) $\int_{-\infty}^t f(q)dq$ (b) $\int_{0^-}^t f(q)dq$	$\frac{F(s)}{s} + \frac{\int_{-\infty}^{0^-} f(q)dq}{s}$ $\frac{F(s)}{s}$
Time or Frequency Scaling	$f(at)$	$\frac{1}{a}F\left(\frac{s}{a}\right)$

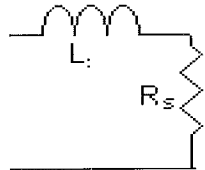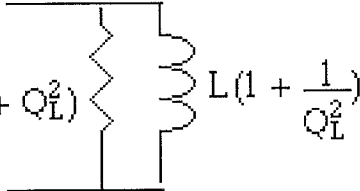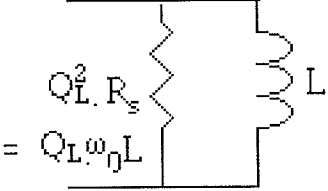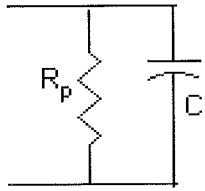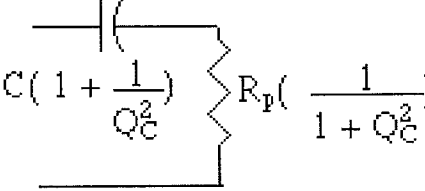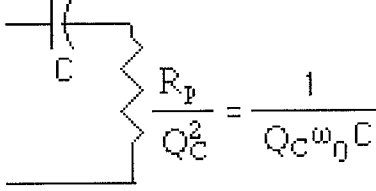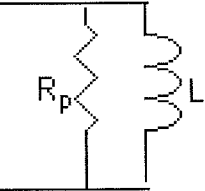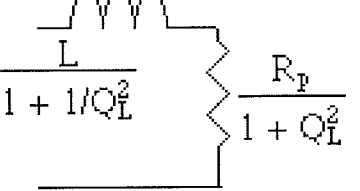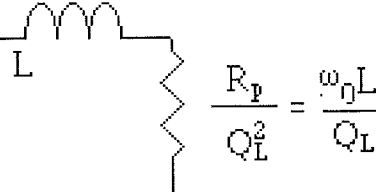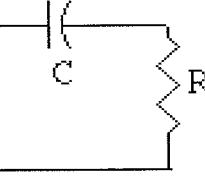Original Circuit	Exact Equivalent Circuit at ω_0	Approximate Equivalent circuit, for high Q, ($Q_L > 6$ and $Q_C > 6$) and ω within $(1 \pm 0.05)\omega_0$
 <p>$Q_L(\omega_0) = \frac{\omega_0 L}{R_s}$</p>		
 <p>$Q_c(\omega_0) = \omega_0 R_p C$</p>		
 <p>$Q_L(\omega_0) = \frac{R_p}{\omega_0 L}$</p>		
 <p>$Q_C(\omega_0) = \frac{1}{\omega_0 R_s C}$</p>	