

ECE 202 - Linear Circuit Analysis II

Final Exam Solutions

December 19, 2008

Solution 1

Breaking $F(s)$ into partial fractions,

$$\begin{aligned} F(s) &= \frac{4s^2 - 9}{s(s-9)} \\ &= 4 + \frac{1}{s} + \frac{35}{s-9} \\ \Rightarrow f(t) &= 4\delta(t) + [1 + 35e^{9t}]u(t) \\ \Rightarrow A &= 9 \end{aligned}$$


Hence (3) is the correct answer.

Solution 2

$$\begin{aligned} f(t) &= 3[u(t) - u(t-1)] - 2[u(t-1) - u(t-2)] \\ &= 3u(t) - 5u(t-1) + 2u(t-2) \\ \Rightarrow F(s) &= \frac{3}{s} - \frac{5e^{-s}}{s} + \frac{2e^{-2s}}{s} \end{aligned}$$

Hence (1) is the correct answer.

Solution 3

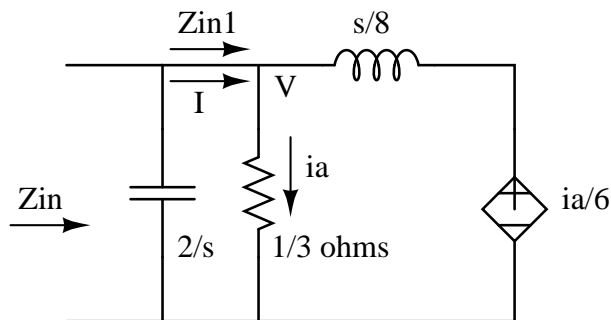

Consider the impedance Z_{in1} looking right at the node with voltage V . We can then write,

$$\begin{aligned} V &= \frac{i_a}{3} \\ -(I - i_a)\frac{s}{8} - \frac{i_a}{6} + \frac{i_a}{3} &= 0 \end{aligned}$$

$$\begin{aligned}
I &= \frac{i_a}{3} \left(3 + \frac{4}{s} \right) = V \left(3 + \frac{4}{s} \right) \\
\Rightarrow Z_{in1} &= \frac{V}{I} = \frac{s}{3s+4} \\
\Rightarrow Z_{in} &= (2/s) \parallel Z_{in1} \\
&= \frac{2s}{s^2 + 6s + 8}
\end{aligned}$$

Hence (3) is the correct answer.

Solution 4

Transfer function is given by the standard expression,

$$\begin{aligned}
H(s) &= \frac{V_{out}(s)}{V_{in}(s)} = -\frac{Z_2}{Z_1} \\
Z_2 &= (2/s) \parallel 1 \\
&= \frac{2}{s+2} \\
Z_1 &= 1 + (1/s) \\
&= \frac{s+1}{s} \\
\Rightarrow H(s) &= -\frac{2s}{(s+1)(s+2)}
\end{aligned}$$

Hence (4) is the correct answer.

Solution 5

Using voltage division,

$$\begin{aligned}
H(s) = \frac{V_o}{V_i} &= \frac{\frac{1}{s}}{\frac{1}{s} + s + 2} \\
&= \frac{1}{s^2 + 2s + 1} \\
&= \frac{1}{(s+1)^2} \\
\Rightarrow h(t) &= te^{-t}u(t)
\end{aligned}$$

Hence (5) is the correct answer.

Solution 6

$$\begin{aligned}
v_i(t) &= 2[u(t) - u(t-1)] \\
V_i(s) &= 2(1 - e^{-s})\frac{1}{s} \\
V_o(s) = H(s)V_i(s) &= \frac{2(1 - e^{-s})}{s(s+1)^2} \\
&= 2(1 - e^{-s}) \left[\frac{1}{s} - \frac{1}{(s+1)^2} - \frac{1}{s+1} \right] \\
\Rightarrow v_o(t) &= [2 - 2te^{-t} - 2e^{-t}]u(t) - [2 - 2(t-1)e^{-(t-1)} - 2e^{-(t-1)}]u(t-1)
\end{aligned}$$

Hence (4) is the correct answer.

Solution 7

The equivalent impedance of the LC combination at $\omega=0.5$ is zero. Thus voltage at the inverting terminal of the op-amp is v_o . By virtual ground principle of ideal op-amp,

$$v_o(t) = v_s(t) = 2 \sin(0.5t + 30^\circ)$$

Hence (5) is the correct answer.

Solution 8

When the switch is closed, $v_5(t) = v_3(t) = v_2(t)$. Thus applying principle of conservation of charge,

$$\begin{aligned} v_5(t) &= \frac{5 \times 8}{5 + 3 + 2} \\ &= 4 \end{aligned}$$

Hence (4) is the correct answer.

Solution 9


Here common mistake is to forget converting the circuit from time domain to s-domain and keeping the voltage source as 2 instead of $(2/s)$. Analyzing the equivalent circuit in s-domain, and applying voltage division,

$$\begin{aligned} V_{out} &= \frac{2}{s} \left(\frac{\frac{4}{s}}{\frac{4}{s} + \frac{s}{2} + 3} \right) \\ &= \frac{16}{s(s+2)(s+4)} \end{aligned}$$

Hence (1) is the correct answer.

Solution 10

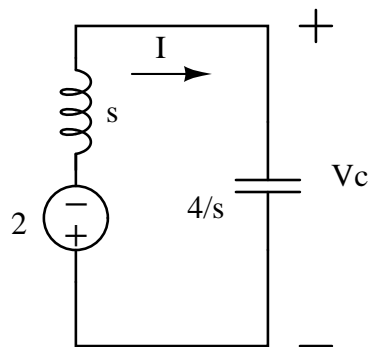Just before $t=0$ the circuit is in steady state and the inductor acts as a short, while the capacitor is open. Thus initial current through the inductor $= 4/2 = 2$ A. The circuit thus looks as follows for $t > 0$:-




Applying KVL around the loop,

$$\begin{aligned}
 I &= \frac{sV_c}{4} \\
 V_c + Is + 2 &= 0 \\
 V_c \left(1 + \frac{s^2}{4}\right) + 2 &= 0 \\
 V_c &= -\frac{8}{s^2 + 4} \\
 &= -4 \left(\frac{2}{s^2 + 4}\right) \\
 \Rightarrow v_c(t) &= -4 \sin(2t)u(t)
 \end{aligned}$$

Hence (5) is the correct answer.

Solution 11

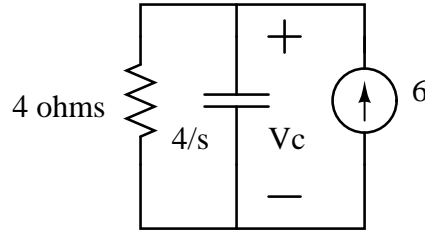Just before $t=0$, the capacitor is charged to an initial voltage of 24V. The equivalent s-domain circuit for *zero input response* is as shown below. Clearly, V_c is given by,



$$\begin{aligned}
 V_c &= 6(4 \parallel 4/s) \\
 &= \frac{24}{s + 1} \\
 \Rightarrow v_c(t) &= 24e^{-t}u(t)
 \end{aligned}$$

Hence (6) is the correct answer.

Solution 12

The equivalent admittance between the two terminals is given by,

$$\begin{aligned}
 Y_{eq}(s) &= Cs + \left(\frac{s^2 + 6}{s} + 1\right)^{-1} \\
 &= Cs + \frac{s}{s^2 + s + 6} \\
 &= s \left(C + \frac{1}{s^2 + s + 6}\right) \\
 Y_{eq}(j3) &= j3 \left(C + \frac{1}{-3 + 3j}\right) \\
 &= j3 \left(C + \frac{-1 - j}{6}\right)
 \end{aligned}$$

Clearly, for resonance, $Y_{eq}(j3)$ should be real, which is possible if $C=1/6$. Hence (2) is the correct answer.

Solution 13

Applying KVL to the s-domain equivalent circuit,

$$\begin{aligned} V_s - I_L(R + Ls) - \frac{(\beta + 1)I_L}{Cs} &= 0 \\ \Rightarrow \frac{V_s}{I_L} &= R + Ls + \frac{(\beta + 1)}{Cs} \\ \Rightarrow Y_{eq}(s) &= \left[R + Ls + \frac{(\beta + 1)}{Cs} \right]^{-1} \end{aligned}$$

Clearly, the circuit is resonant when,

$$\begin{aligned} \omega_r^2 LC &= (\beta + 1) \\ \text{or } \omega_r &= \sqrt{\frac{\beta + 1}{LC}} \end{aligned}$$


Hence (6) is the correct answer.

Solution 14

$$\begin{aligned} K_m &= \frac{50}{0.05} = 1000 \\ \omega_{old} &= \frac{1}{\sqrt{0.5 \times 8}} = 0.5 \\ K_f &= \frac{\omega_{new}}{\omega_{old}} = 100/0.5 = 200 \\ \Rightarrow C_{new} &= \frac{C_{old}}{K_m K_f} \\ &= \frac{8}{1000 \times 200} = 40 \mu F \end{aligned}$$

Hence (2) is the correct answer.

Solution 15

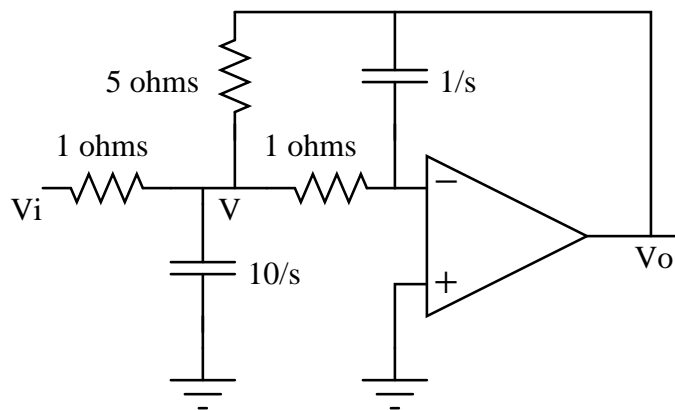

The following KCL node equations can be written,

$$(V_i - V) + (0 - V) + \left(-\frac{sV}{10}\right) + \left(\frac{V_o - V}{5}\right) = 0$$

$$sV_o = -V$$

Eliminating V from the above equations, we get,

$$\frac{V_o}{V_i} = \frac{-10}{s^2 + 22s + 2}$$

This is clearly the transfer function of a low pass filter with a DC gain(s=0) of -10/2=-5. Hence (2) is the correct answer.

Solution 16

Let input voltage be V and input current be I from the top. Here care has to be taken to write the proper sign for drop due to mutual inductance. We can write, using KVL and dot convention,

$$\begin{aligned} V - 5I - 3sI + (2sI) - \frac{I}{6s} - 5sI + (2sI) &= 0 \\ \Rightarrow Z_{in}(s) = \frac{V}{I} &= 5 + 4s + (6/s) \end{aligned}$$

Hence (5) is the correct answer.

Solution 17

Using convolution algebra,

$$\begin{aligned} f(t) * h(t) &= f^1(t) * h^{-1}(t) \\ &= 3\delta(t) * h^{-1}(t) \\ &= 3h^{-1}(t) \\ &= 3 \int_{-\infty}^t t^2 [u(t) - u(t-2)] dt \\ &= \begin{cases} 0, & t < 0 \\ t^3, & 0 \leq t \leq 2 \\ 8, & t \geq 2 \end{cases} \end{aligned}$$

Hence (1) is the correct answer.

Solution 18

Again, using convolution algebra,

$$\begin{aligned} f(t) * h(t) &= f^{-1}(t) * h^1(t) \\ &= f^{-1}(t) * 2\delta(t) \\ &= 2f^{-1}(t) \\ &= 2 \int_{-\infty}^t f(\tau) d\tau \\ &= \begin{cases} 0, & t < 0 \\ 6t, & 0 \leq t < 2 \\ 24 - 6t, & 2 \leq t < 4 \\ 0, & t \geq 4 \end{cases} \end{aligned}$$

Hence (4) is the correct answer.


Solution 19

We know,

$$h_{11} = \frac{V_1}{I_1} \Big|_{V_2=0}$$

$$h_{22} = \frac{I_2}{V_2} \Big|_{I_1=0}$$

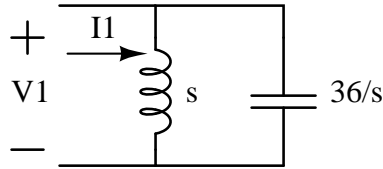For finding h_{11} , we short circuit the output side and reflect the secondary impedance on the primary side. The reflected impedance becomes $a^2 Z_s = (9 \times 4/s) = 36/s$. Thus we get the following circuit,




$$h_{11} = \frac{V_1}{I_1}$$

$$= \frac{s(36/s)}{s + 36/s}$$

$$= \frac{36s}{s^2 + 36}$$

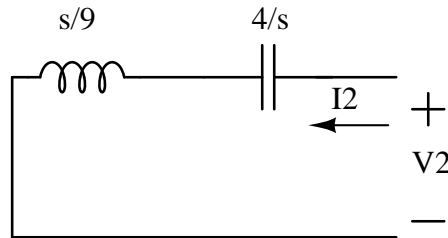Similarly, for finding h_{22} , we open circuit the input side and reflect the primary impedance on the secondary side. The reflected impedance becomes $(1/a^2)Z_p = (1/9 \times s) = s/9$. Thus we get the following circuit,



$$h_{22} = \frac{I_2}{V_2}$$

$$= \left(\frac{s}{9} + \frac{4}{s} \right)^{-1}$$

$$= \frac{9s}{s^2 + 36}$$

Hence (2) is the correct answer.

Solution 20

Note that when we short the input side, the voltage appearing on the primary side of the ideal transformer becomes $1 \Omega \times I_1 = I_1$. Also, from the ideal transformer relation, $I_1/V_2 = n$. Thus,

$$\begin{aligned}
 t_{12} &= \left. \frac{V_2}{I_1} \right|_{V_1=0} \\
 &= \frac{1}{n}
 \end{aligned}$$

Hence (3) is the correct answer.

Solution 21

$$\begin{aligned}
 [T] &= [T_A][T_B] \\
 &= \begin{pmatrix} 1 & 2 \\ 1 & 2 \end{pmatrix} \begin{pmatrix} 1+s & s \\ 1 & 1 \end{pmatrix} \\
 &= \begin{pmatrix} 3+s & s+2 \\ 3+s & s+2 \end{pmatrix}
 \end{aligned}$$

Hence (6) is the correct answer.

Solution 22

If we keep reflecting the load impedance Z_L from the right to the left most side, we will get the reflected load impedance Z_r as,

$$\begin{aligned}
 Z_r &= [(N_1/N_2)^2(N_3/N_4)^2(N_5/N_6)^2]Z_L \\
 &= [(2/3)^2(2/2)^2(6/2)^2]Z_L \\
 &= 4Z_L
 \end{aligned}$$

Now, using *Maximum Power Transfer* theorem,

$$\begin{aligned}
 4Z_L &= 12 \\
 \Rightarrow Z_L &= 3 \Omega
 \end{aligned}$$

Hence (3) is the correct answer.

Wish you all the best for your final grade ☺