

## ECE 202 Summer 2009

## Final Exam

8/5/09

Problem	Score	Maximum
0	Averages 5 / 0	5
1	22.8 / 35	31
2	13.6 / 30	26
3	16.1 / 35	35
4	17.9 / 30	30
5	14.6 / 35	32
6	14.1 / 35	35
Total	109 / 200	156


**Question 1: (5 Extra Credit Points)**

To get you started, here is a free problem. There will be NO partial credit.

For the circuit below,  $V_{\text{out}} = \underline{5\text{ V}}$

$$R_1 = R_2 = 5\Omega$$

$$V_{\text{in}} = 10\text{ V}$$

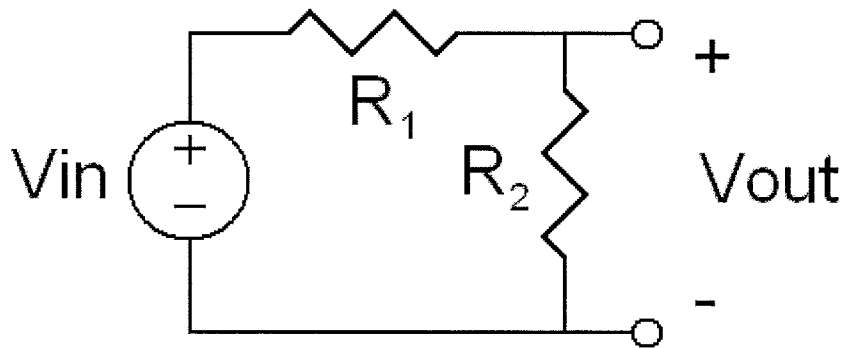



## Question 1: (35 Points)

For the circuit below, find:


- 1)  $v_{out}(0)$  by the initial value theorem
- 2)  $v_{out}(\infty)$  by the final value theorem
- 3)  $v_{out}(t)$  given that  $v_{in}(t) = 2e^{-2t}$

$$R = 5\Omega$$

$$L = 1H$$

$$C = 1/4 F$$
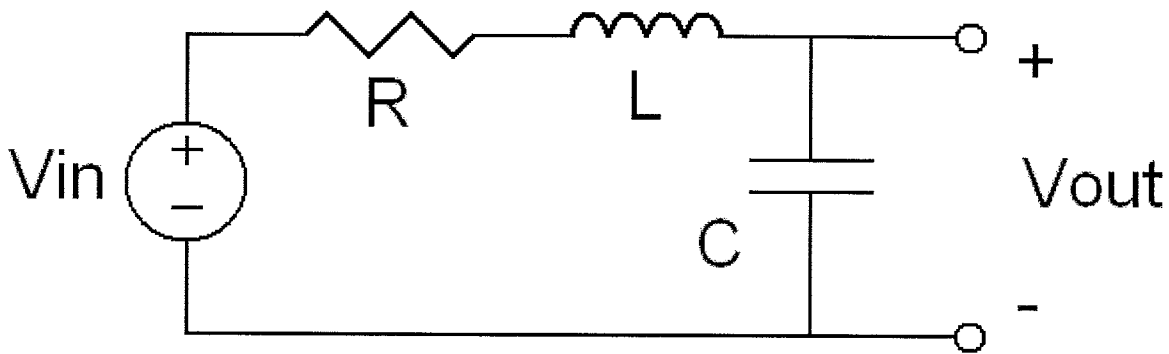
$$\mathcal{L}\{v_{in}(t)\} = \frac{2}{s+2}$$



$$H(s) = \frac{\frac{1}{sC}}{sL + R + \frac{1}{sC}} = \frac{\frac{1}{LC}}{s^2 + \frac{R}{L}s + \frac{1}{LC}} = \frac{4}{s^2 + 5s + 4} = \frac{4}{(s+1)(s+4)}$$

$$V_{out}(s) = \mathcal{L}\{v_{in}(t)\} \cdot \frac{4}{(s+1)(s+4)} = \frac{8}{(s+1)(s+2)(s+4)}$$

$$1) \text{ Initial value: } v(0^-) = \lim_{s \rightarrow \infty} sF(s) = \lim_{s \rightarrow \infty} \left[ \frac{8s}{(s+1)(s+2)(s+4)} \right] = \boxed{0}$$

$$2) \text{ Final Value: } v(\infty) = \lim_{s \rightarrow 0} sF(s) = \lim_{s \rightarrow 0} \left[ \frac{8s}{(s+1)(s+2)(s+4)} \right] = \boxed{0}$$

$$3) V_{out}(s) \Rightarrow \frac{A}{s+1} + \frac{B}{s+2} + \frac{C}{s+4} \Rightarrow 8 = A(s+2)(s+4) + B(s+1)(s+4) + C(s+1)(s+2)$$

$$\begin{aligned} @ s = -1, & \quad A = 8/3 \\ @ s = -2, & \quad B = -4 \\ @ s = -4, & \quad C = 4/3 \end{aligned}$$



$$v_{out}(t) = \mathcal{L}^{-1}\left\{ \frac{8/3}{s+1} + \frac{-4}{s+2} + \frac{4/3}{s+4} \right\} = \boxed{\left( \frac{8}{3}e^{-t} - 4e^{-2t} + \frac{4}{3}e^{-4t} \right) u(t)}$$



Question 2: (30 Points)

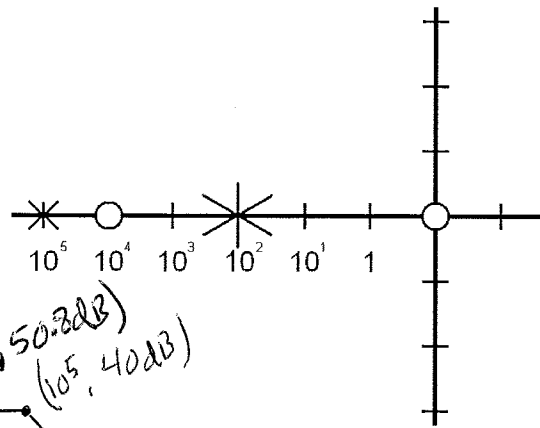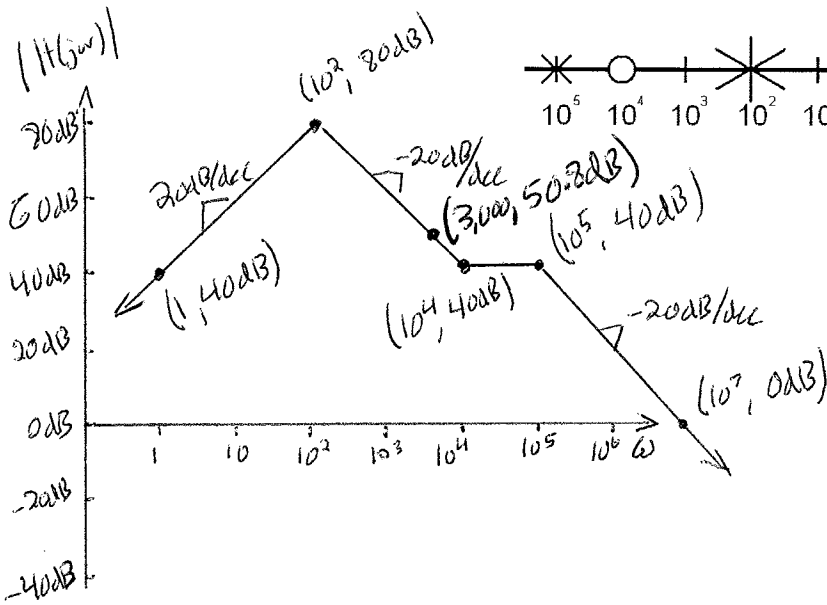- (a) For the pole-zero diagram below, draw out a bode diagram for the magnitude and frequency of  $H(s)$ . On your diagram, label each point of interest (i.e. change of slope or zero crossing) with its magnitude and frequency. Assume  $K = 100 + j0$ .
- (b) Find the exact magnitude (in dB) and phase of  $H(s)$  at  $\omega = 3,000$  rad/s. Label it on your plot. If your plot shows a different value, I will not take off extra. This will probably require a calculator.


Note: There is a double pole (two different poles) at  $\omega = 100$  rad/s.



$$H(s) = 100 \frac{s(\frac{s}{10^4} + 1)}{(\frac{s}{100} + 1)^2 (\frac{s}{10^5} + 1)}$$

$$H(j3000) = 347 \angle -71^\circ$$

$$|H(j3000)| = 50.8 \text{ dB}$$

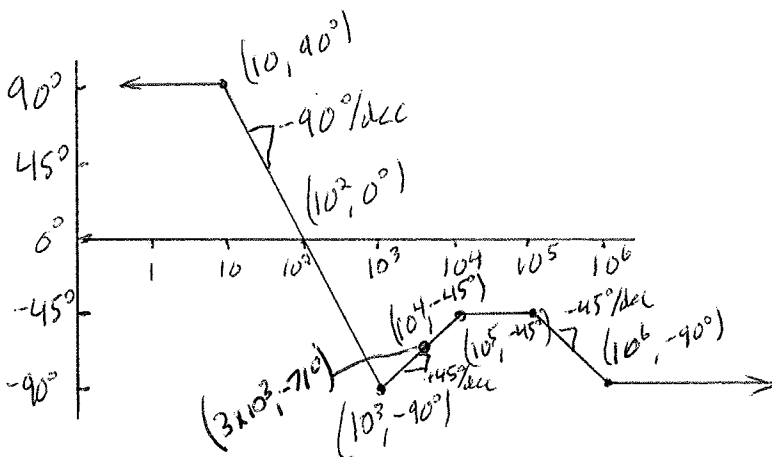



## Question 3: (35 Points)

Find:

$f(t)$

$h(t)$

$$[r(t) + 2r(t-2) - 4r(t-3)] * [\cos(t)[u(t) - u(t-4\pi)]]$$

$$f(t) * h(t) = \frac{\partial^2 f(t)}{\partial t^2} * \iint h(t) dt dt$$

$$\frac{\partial f(t)}{\partial t} = u(t) + 2u(t-2) - 4u(t-3)$$

$$\frac{\partial^2 f(t)}{\partial t} = \delta(t) + 2\delta(t-2) - 4\delta(t-3)$$

$$\begin{aligned} \int h dt &= \int_{-\infty}^t \cos(t) u(t) dt - \int_{-\infty}^t \cos(t) u(t-4\pi) dt \\ &= u(t) \int_0^t \cos(t) dt - u(t-4\pi) \int_{4\pi}^t \cos(t) dt \\ &= u(t) [\sin(t)]_0^t - u(t-4\pi) [\sin(t)]_{4\pi}^t \\ &= u(t) \sin(t) - u(t-4\pi) \sin(t) \end{aligned}$$

$$\begin{aligned} \iint h dt dt &= \int_{-\infty}^t \sin(t) u(t) dt - \int_{-\infty}^t \sin(t) u(t-4\pi) dt \\ &= u(t) \int_0^t \sin(t) dt - u(t-4\pi) \int_{4\pi}^t \sin(t) dt \\ &= u(t) [-\cos(t)]_0^t - u(t-4\pi) [-\cos(t)]_{4\pi}^t \end{aligned}$$

$$k(t) \equiv \iint h dt dt = u(t) [1 - \cos(t)] - u(t-4\pi) [1 - \cos(t)]$$

$$f * h = k(t) + 2k(t-2) - 4k(t-3)$$

$$\begin{aligned} &= u(t) [1 - \cos(t)] - u(t-4\pi) [1 - \cos(t)] \\ &\quad + 2u(t-2) [1 - \cos(t-2)] - 2u(t-2-4\pi) [1 - \cos(t-2)] \\ &\quad - 4u(t-3) [1 - \cos(t-3)] + 4u(t-3-4\pi) [1 - \cos(t-3)] \end{aligned}$$



## Question 4: (30 Points)

Find  $H(s)$  and put it in its simplified form. Simplified form means that the highest power of 's' in the denominator has a coefficient of 1, and there are no sub-fractions with 's' in the denominator. This does **not** mean you have to do partial fractions.


$$R_1 = 1\Omega$$

$$R_2 = 2\Omega$$

$$L_1 = 3H$$

$$L_2 = 6H$$

$$M = 4H$$

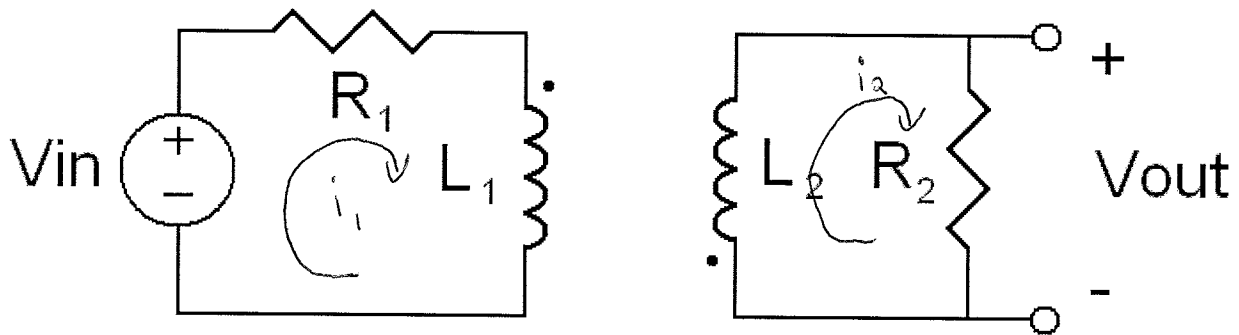

$$V_{in} = i_1 R_1 + i_1 s L_1 + i_2 s M \quad -V_{out} = i_2 s L_2 + i_1 s M \quad V_{out} = i_2 R_2$$

$$V_{in} = i_1 (s L_1 + R_1) + i_2 (s M) \quad i_1 = -\frac{(V_{out} + i_2 s L_2)}{s M} \quad i_2 = \frac{V_{out}}{R_2}$$

$$V_{in} = \frac{-V_{out} - i_2 s L_2}{s M} (s L_1 + R_1) + i_2 s M$$

$$V_{in} = \frac{-V_{out} - \frac{V_{out} s L_2}{R_2}}{s M} (s L_1 + R_1) + \frac{V_{out} s M}{R_2}$$

$$\frac{V_{out}}{V_{in}} = H(s) = \frac{1}{\frac{(-1 - \frac{s L_2}{R_2}) (s L_1 + R_1) + \frac{s M}{R_2}}{s M}} = \frac{s M R_2}{(-R_2 - s L_2)(s L_1 + R_1) + s^2 M^2}$$


$$H(s) = \frac{-s M R_2}{s^2 [L_1 L_2 - M^2] + s [L_1 R_2 + L_2 R_1] + R_1 R_2} = \frac{-s M R_2}{s^2 + s \left[ \frac{L_1 R_2 + L_2 R_1}{L_1 L_2 - M^2} \right] + \frac{R_1 R_2}{L_1 L_2 - M^2}}$$

$$= \frac{-8s}{s^2 + s \left[ \frac{6+6}{2} \right] + \frac{2}{2}} = \boxed{\frac{-4s}{s^2 + 6s + 1}}$$


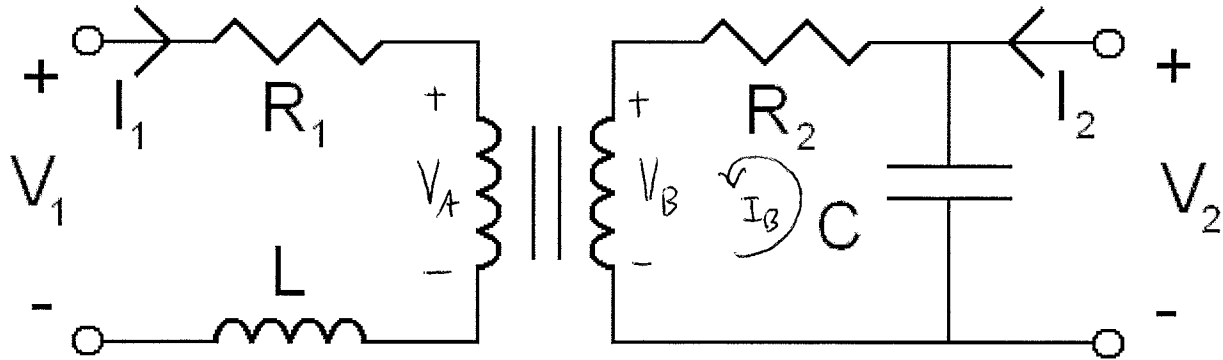
## Question 5: (35 Points)

Find the four z-parameters of the two-port circuit below.



$$V_1 = I_1 R_1 + V_A + sL I_1$$

$$a V_A = V_B$$

$$\frac{-I_1}{a} = I_B$$

$$V_2 = \frac{I_2 - I_B}{sC}$$

$$V_2 = \frac{I_2 + \frac{I_1}{a}}{sC} = \frac{I_2}{sC} + \frac{I_1}{a sC}$$

Need to find  $V_A$ 

$$I_B \text{ loop eqn } \Rightarrow 0 = -V_B - I_B R_2 + V_2$$

$$V_B + I_B R_2 = V_2$$

$$\rightarrow a V_A + \frac{-I_1}{a} R_2 = \frac{I_2}{sC} + \frac{I_1}{a sC}$$

$$V_A = \frac{I_1}{a^2} R_2 + \frac{I_1}{a^2 sC} + \frac{I_2}{a sC}$$

$$V_1 = I_1 R_1 + \frac{I_1}{a^2} R_2 + \frac{I_1}{a^2 sC} + \frac{I_2}{a sC} + sL I_1$$

$$V_1 = I_1 \left[ R_1 + sL + \frac{R_2}{a^2} + \frac{1}{a^2 sC} \right] + I_2 \frac{1}{a sC}$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} R_1 + sL + \frac{R_2}{a^2} + \frac{1}{a^2 sC} & \frac{1}{a sC} \\ \frac{1}{a sC} & \frac{1}{sC} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$



## Question 6: (35 Points)


Find the admittance parameters of the circuit below.

$$R_1 = 1/12 \Omega$$

$$R_2 = 1 \Omega$$

$$C = 6F$$

$$L = 1/2H$$

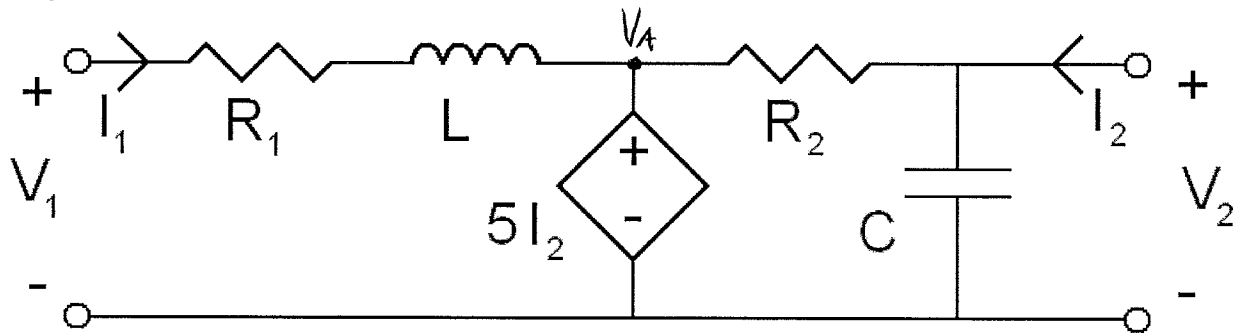Admittance  $\rightarrow$  Nodal Equations

$$\text{@ } V_A \Rightarrow V_A = 5I_2$$

$$\text{@ Port 1} \quad I_1 = \frac{V_1 - 5I_2}{R_1 + sL}$$

$$I_1 = \frac{V_1 - 5(V_2(s + \frac{1}{6}))}{R_1 + sL}$$

$$I_1 = \frac{V_1 - V_2 5(s + \frac{1}{6})}{\frac{1}{12} + \frac{s}{2}}$$

$$I_1 = \frac{2V_1}{s + \frac{1}{6}} - 10V_2 \frac{s + \frac{1}{6}}{s + \frac{1}{6}}$$

$$= V_1 \frac{2}{s + \frac{1}{6}} - V_2 10$$

$$\text{@ Port 2} \quad I_2 = V_2 sC + \frac{V_2 - 5I_2}{R_2}$$

$$I_2 \left(1 + \frac{5}{R_2}\right) = V_2 \left(sC + \frac{1}{R_2}\right)$$

$$I_2 = V_2 \frac{sC + \frac{1}{R_2}}{1 + \frac{5}{R_2}}$$

$$I_2 = V_2 \frac{6s + 1}{1 + 5} = V_2 \left(s + \frac{1}{6}\right)$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} \frac{2}{s + \frac{1}{6}} & -10 \\ 0 & s + \frac{1}{6} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

















## Laplace Transform Pairs

Item Number	$f(t)$	$\mathcal{L}\{f(t)\}=F(s)$
1	$K\delta(t)$	$K$
2	$Ku(t)$ or $K$	$\frac{K}{s}$
3	$r(t)$	$\frac{1}{s^2}$
4	$t^n u(t)$	$\frac{n!}{s^{n+1}}$
5	$e^{-at} u(t)$	$\frac{1}{s+a}$
6	$te^{-at} u(t)$	$\frac{1}{(s+a)^2}$
7	$t^n e^{-at} u(t)$	$\frac{n!}{(s+a)^{n+1}}$
8	$\sin(\omega t) u(t)$	$\frac{\omega}{s^2 + \omega^2}$
9	$\cos(\omega t) u(t)$	$\frac{s}{s^2 + \omega^2}$
10	$e^{-at} \sin(\omega t) u(t)$	$\frac{\omega}{(s+a)^2 + \omega^2}$
11	$e^{-at} \cos(\omega t) u(t)$	$\frac{s+a}{(s+a)^2 + \omega^2}$
12	$t \sin(\omega t) u(t)$	$\frac{2\omega s}{(s^2 + \omega^2)^2}$
13	$t \cos(\omega t) u(t)$	$\frac{s^2 - \omega^2}{(s^2 + \omega^2)^2}$
14	$\sin(\omega t + \varphi) u(t)$	$\frac{s \sin \varphi + \omega \cos \varphi}{s^2 + \omega^2}$
15	$\cos(\omega t + \varphi) u(t)$	$\frac{s \cos \varphi - \omega \sin \varphi}{s^2 + \omega^2}$
16	$e^{-at} [\sin(\omega t) - \omega t \cos(\omega t)] u(t)$	$\frac{2\omega^3}{[(s+a)^2 + \omega^2]^2}$
17	$te^{-at} \sin(\omega t) u(t)$	$2\omega \frac{s+a}{[(s+a)^2 + \omega^2]^2}$
18	$e^{-at} \left[ C_1 \cos(\omega t) + \left( \frac{C_2 - C_1 a}{\omega} \right) \sin(\omega t) \right] u(t)$	$\frac{C_1 s + C_2}{(s+a)^2 + \omega^2}$
19	$2\sqrt{A^2 + B^2} e^{-at} \cos \left[ \omega t - \tan^{-1} \left( \frac{B}{A} \right) \right] u(t)$	$\frac{A + jB}{s + a + j\omega} + \frac{A - jB}{s + a - j\omega}$
20	$2\sqrt{A^2 + B^2} t e^{-at} \cos \left[ \omega t - \tan^{-1} \left( \frac{B}{A} \right) \right] u(t)$	$\frac{A + jB}{(s + a + j\omega)^2} + \frac{A - jB}{(s + a - j\omega)^2}$

## Laplace Properties

Property	$f(t)$	$\mathcal{L}\{f(t)\}=F(s)$
Linearity	$a_1f_1(t) + a_2f_2(t)$	$a_1F(s) + a_2F_2(s)$
Time Shift	$f(t - T)u(t - T)$	$e^{-sT}F(s)$
Multiplication by t	$tf(t)u(t)$	$-\frac{d}{ds}F(s)$
Multiplication by $t^n$	$t^n f(t)$	$(-1)^n \frac{d^n F(s)}{ds^n}$
Frequency Shift	$e^{-at}f(t)$	$F(s + a)$
Time Differentiation	$\frac{d}{dt}f(t)$	$sF(s) - f(0^-)$
Second-order Differentiation	$\frac{d^2f(t)}{dt^2}$	$s^2F(s) - sf(0^-) - f^{(1)}(0^-)$
$n$ th-order Differentiation	$\frac{d^n f(t)}{dt^n}$	$s^n F(s) - s^{n-1}f(0^-) - s^{n-2}f^{(1)}(0^-) - \dots - f^{(n-1)}(0^-)$
Time Integration	(a) $\int_{-\infty}^t f(q)dq$ (b) $\int_{0^-}^t f(q)dq$	$\frac{F(s)}{s} + \frac{\int_{-\infty}^{0^-} f(q)dq}{s}$ $\frac{F(s)}{s}$
Time or Frequency Scaling	$f(at)$	$\frac{1}{a}F\left(\frac{s}{a}\right)$

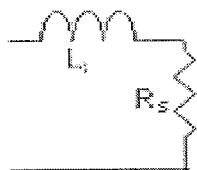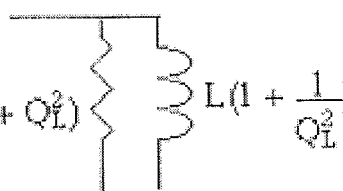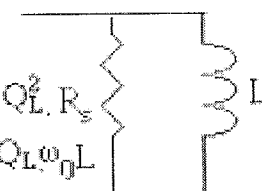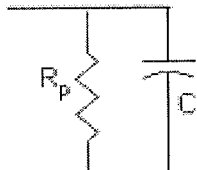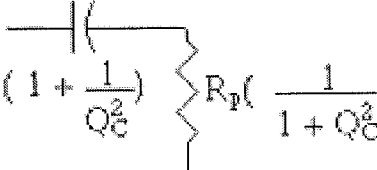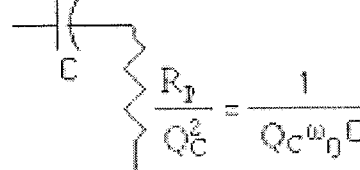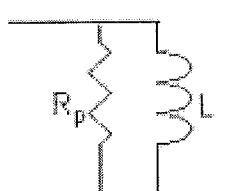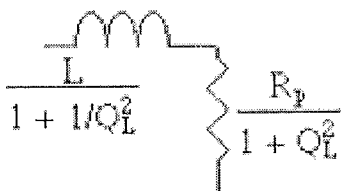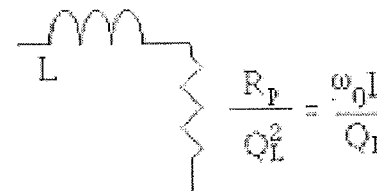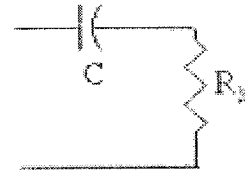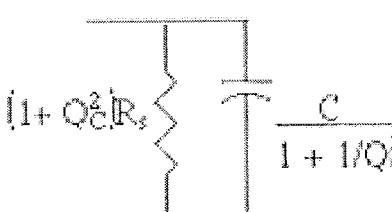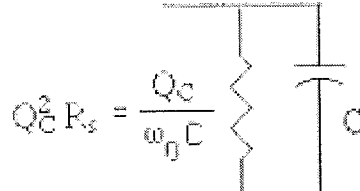Original Circuit	Exact Equivalent Circuit at $\omega_0$	Approximate Equivalent circuit, for high Q, ( $Q_L > 6$ and $Q_C > 6$ ) and $\omega$ within $(1 \pm 0.05)\omega_0$
 <p><math>Q_L(\omega_0) = \frac{\omega_0 L}{R_s}</math></p>		 <p><math>= Q_L \omega_0 L</math></p>
 <p><math>Q_C(\omega_0) = \omega_0 R_p C</math></p>		 <p><math>= \frac{1}{Q_C \omega_0 C}</math></p>
 <p><math>Q_L(\omega_0) = \frac{R_p}{\omega_0 L}</math></p>		 <p><math>= \frac{\omega_0 L}{Q_L}</math></p>
 <p><math>Q_C(\omega_0) = \frac{1}{\omega_0 R_s C}</math></p>		 <p><math>Q_C^2 R_s = \frac{Q_C}{\omega_0 C}</math></p>

