

# ECE 202 - Linear Circuit Analysis II

Purdue University, Spring 2009

## Homework Set 5 Solutions

### Solution 49

(a)

$$\left(\frac{\omega_s}{\omega_p}\right)^{2n} \geq \frac{10^{0.1A_{min}} - 1}{10^{0.1A_{max}} - 1}$$

```
>> wp=2*pi*550;
>> ws=2*pi*2200;
>> n=3;
>> Amax=0.75;
>> Amin=1;
>> limit=((ws/wp)^(2*n))*((10^(0.1*Amax))-1)
```

```
limit =
```

```
772.1051
```

```
>> while(((10^(0.1*Amin))-1)<=limit)
Amin=Amin+1;
end
>> Amin=Amin-1
```

```
Amin =
```

```
28
```

(b)

```
>> fp=550; fs=2200; Amax=0.75; Amin=28;
>> n=buttord(fp, fs, Amax, Amin, 's')
```

```
n =  
  
    3  
  
>> fcmin=fp/((10^(0.1*Amax)-1)^(1/(2*n)))  
  
fcmin =  
  
    726.3455  
  
>> fcmax=fs/((10^(0.1*Amin)-1)^(1/(2*n)))  
  
fcmax =  
  
    751.3994  
  
>> wcmin=2*pi*fcmin  
  
wcmin =  
  
    4.5638e+003  
  
>> wcmax=2*pi*fcmax  
  
wcmax =  
  
    4.7212e+003
```

(c)

```
>> [z, p, k]=buttap(n)
```

```
z =
```

```
    []
```

```
p =
```

```
-0.5000 + 0.8660i  
-0.5000 - 0.8660i  
-1.0000
```

```
k =
```

```
1.0000
```

```
>> abs(p)
```

```
ans =
```

```
1.0000
```

```
1.0000
```

```
1.0000
```

Thus poles lie on the unit circle.

(d)

```
>> firstorder=poly(p(3))
```

```
firstorder =
```

```
1 1
```

```
>> secondorder=poly(p(1:2))
```

```
secondorder =
```

```
1.0000 1.0000 1.0000
```

(e)

```
>> wc=wcmin;
```

```
>> fc=fcmin;
```

```
>> znew=z*wc
```

```

znew =

[]

>> pnew=p*wc

pnew =

1.0e+003 *

-2.2819 + 3.9523i
-2.2819 - 3.9523i
-4.5638

```

```
>> knew=k*wc^n
```

```
knew =

9.5054e+010
```

```
>> abs(pnew)
```

```
ans =

1.0e+003 *


4.5638
4.5638
4.5638
```

Thus poles lie on a circle about origin.


(f)

$$\begin{aligned}
 -20 \log_{10} |H_{3dB NLP}(j1)| &= 3.0103 \text{ dB} \\
 -20 \log_{10} |H_{3dB NLP}\left(j \frac{\omega_s}{\omega_p}\right)| &= 36.1247 \text{ dB}
 \end{aligned}$$

(g)

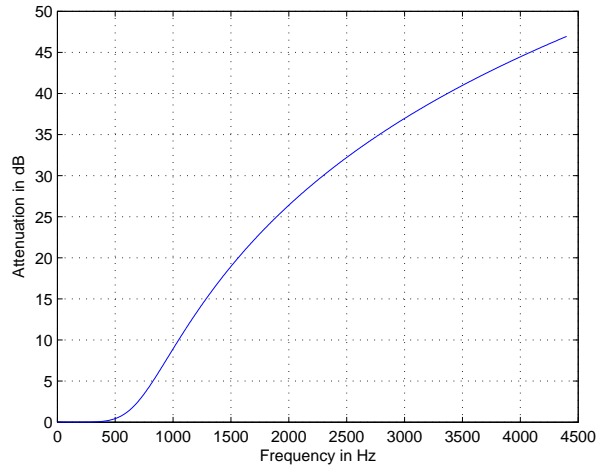

(h)

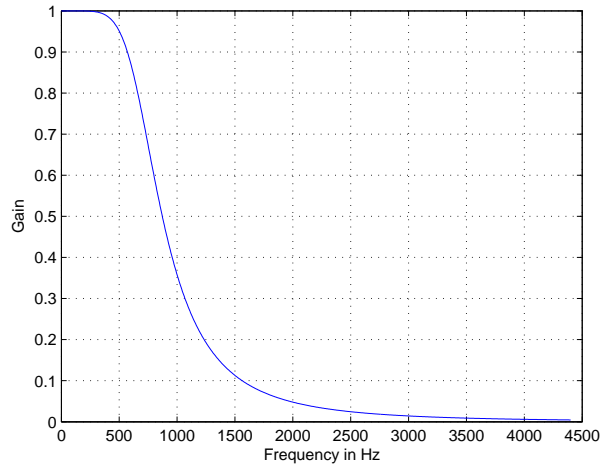

At  $f_s = 2200 \text{ Hz}$ , the attenuation is 28.88 dB, which is greater than  $A_{min} = 28 \text{ dB}$ . At  $f_p = 550 \text{ Hz}$ , the attenuation is 0.75 dB, which is equal to  $A_{max} = 0.75 \text{ dB}$ . Thus filter response meets the given brickwall specifications.

## Solution 50

(a)

$$\begin{aligned}
 n &\geq \frac{\log_{10} \left( \sqrt{\frac{10^{0.1A_{min}} - 1}{10^{0.1A_{max}} - 1}} \right)}{\log_{10} \left( \frac{\omega_s}{\omega_p} \right)} \\
 \Rightarrow n &\geq 1.8508 \\
 \Rightarrow n &= 2 \\
 \Rightarrow H_{3dB\text{BNLP}} &= \frac{1}{s^2 + \sqrt{2}s + 1} \\
 \omega_{c,min} &= \frac{\omega_p}{(10^{0.1A_{max}} - 1)^{\frac{1}{2n}}} \\
 &= 3592.4 \text{ rad/s} \\
 \omega_{c,max} &= \frac{\omega_s}{(10^{0.1A_{min}} - 1)^{\frac{1}{2n}}} \\
 &= 3983.8 \text{ rad/s}
 \end{aligned}$$

(b)

(i)

$$\begin{aligned}
 H(s) &= \frac{1}{s^2 LC + sCR_s + 1} \\
 &= \frac{1/LC}{s^2 + sR_s/L + 1/LC}
 \end{aligned}$$

(ii)

Realization:  $L=0.707 \text{ H}$ ,  $C=1.414 \text{ F}$ ,  $R_s = 1 \text{ } \Omega$

(c)

$$\begin{aligned}
 K_f &= \omega_{c,min} \\
 &= 3592.4 \\
 \Rightarrow K_m &= \frac{C}{K_f C_{final}} \\
 &= 3.9361 \times 10^4 \\
 \Rightarrow L_{final} &= \frac{LK_m}{K_f} \\
 &= 7.7464 \text{ H}
 \end{aligned}$$

$$\begin{aligned}\Rightarrow R_{final} &= K_m R \\ &= 39.361 \text{ k}\Omega\end{aligned}$$

## Solution 51

(a)

$$\begin{aligned}H_1(s) &= \frac{R_L || 1/C_1 s}{(R_L || 1/C_1 s) + Ls} \\ &= \frac{1}{LC_1} \frac{1}{s^2 + s/R_L C_1 + 1/LC_1} \\ H_2(s) = -\frac{Y_{in}(s)}{Y_{out}(s)} &= -\frac{G_1}{C_2 s + G_2} \\ &= -\frac{1}{R_1 C_2} \frac{1}{s + 1/R_2 C_2} \\ H(s) &= H_1(s) H_2(s)\end{aligned}$$

(b)

Realization:  $R_1 = R_2 = R_L = 1 \Omega$ ,  $L = 1 H$ ,  $C_1 = 1 F$ ,  $C_2 = 1 F$

(c)

$$\begin{aligned}K_f &= 4.5638k \\ K_{m1} &= 20k \\ K_{m2} &= 100 \\ \Rightarrow R_{2,new} &= 20 \text{ k}\Omega \\ \Rightarrow C_{1,new} &= \frac{C_1}{K_{m2} K_f} \\ &= 2.19 \mu F \\ \Rightarrow C_{2,new} &= \frac{C_2}{K_{m1} K_f} \\ &= 10.96 \text{ nF} \\ \Rightarrow L_{new} &= \frac{L K_{m2}}{K_f} \\ &= 0.0219 H\end{aligned}$$

Two separate magnitude scale factors are needed because the transfer function is realized as two sections, a second order section followed by an active first

order section. So the two sections can be magnitude scaled separately. Thus the second order section is magnitude scaled by  $K_{m2}$  and the first order by  $K_{m1}$ .

## Solution 52

(a)

The following KCL equations can be written,

$$\begin{aligned} V_{in} - V_1 + \frac{V_{out} - V_1}{Ls} &= V_1 C_1 s \\ \Rightarrow V_1 \left( 1 + C_1 s + \frac{1}{Ls} \right) &= V_{in} + \frac{V_{out}}{Ls} \\ \frac{V_1 - V_{out}}{Ls} &= V_{out}(1 + C_2 s) \\ \Rightarrow V_1 &= V_{out}[Ls(1 + C_2 s) + 1] \end{aligned}$$

Eliminating  $V_1$  from the above equations,

$$\begin{aligned} V_{out} \left[ \left\{ 1 + C_1 s + \frac{1}{Ls} \right\} \{ 1 + Ls(1 + C_2 s) \} - \frac{1}{Ls} \right] &= V_{in} \\ \Rightarrow \frac{V_{out}}{V_{in}} &= \frac{1}{s^3 LC_1 C_2 + s^2 (C_1 + C_2)L + s(C_1 + C_2 + L) + 2} \\ H_{cir}(s) = \frac{V_{out}(s)}{V_{in}(s)} &= \frac{\frac{1}{LC_1 C_2}}{s^3 + \frac{C_1 + C_2}{C_1 C_2} s^2 + \frac{C_1 + C_2 + L}{LC_1 C_2} s + \frac{2}{LC_1 C_2}} \end{aligned}$$

(b)

$$\begin{aligned} H_{3dB NLP}(s) &= \frac{K}{s^3 + 2s^2 + 2s + 1} \\ \Rightarrow \frac{C_1 + C_2}{C_1 C_2} &= 2 \\ LC_1 C_2 &= 2 \\ \frac{C_1 + C_2 + L}{LC_1 C_2} &= 2 \\ \Rightarrow C_1 = C_2 &= 1 F \\ L &= 2 H \end{aligned}$$

(c)

$$\begin{aligned}K_f &= 4.5638k \\ \Rightarrow K_m &= \frac{C_2}{C_{2final}K_f} \\ &= 21.912k \\ \Rightarrow C_{1final} &= 10 \text{ nF} \\ L_{final} &= \frac{LK_m}{K_f} \\ &= 9.6025 \text{ H}\end{aligned}$$

(d)

The frequency response can be verified in SPICE. The circuit schematic and the simulated response are shown below.

