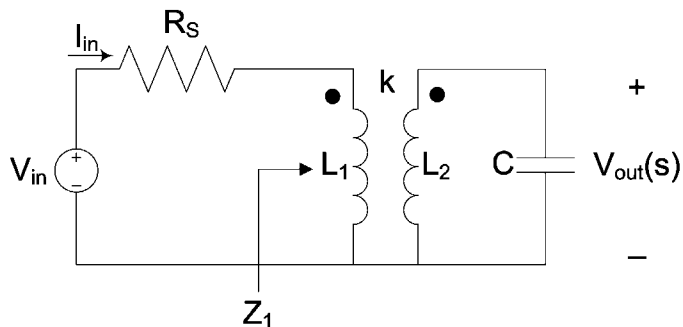


ECE 202 LINEAR CIRCUIT ANALYSIS II (SP'09)


Homework #18 Solution (69-72)

Problem 69




$$R_s = 0.1\Omega, L_1 = 2\text{H}, L_2 = 1\text{H}, C = 0.02\text{F}, \omega_r = 10\text{rad/sec}$$

T-equivalent circuit

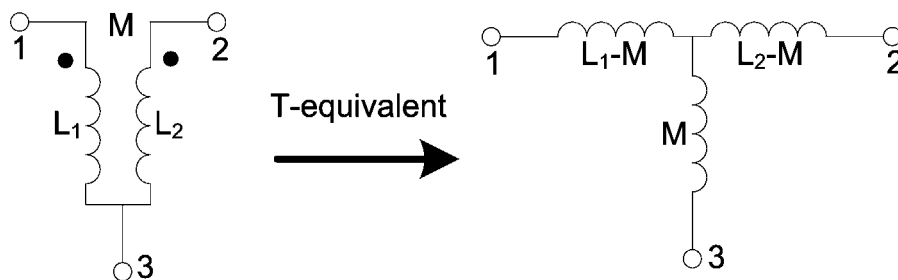

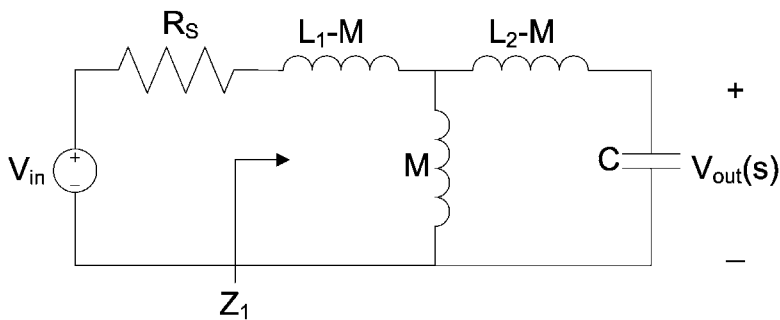Using T-equivalent circuit, the circuit can be redrawn as



(a) Find k

Given the resonant frequency value we will get an expression for the resonant frequency and find the value for k . To find the expression for the resonant frequency we need to compute either $Z_{in}(s)$ or $Y_{in}(s)$. We can use both the original circuit and T-equivalent circuit to compute Z_{in} . Here, we will show both ways.

From the original circuit drawing,

Define I_2 as the current flowing into the dotted terminal of L_2 and we can write the loop equations as following:

$$\text{Loop1 : } V_{in} = (R_s + L_1s)I_{in} + (Ms)I_2 \quad (69.1)$$

$$\text{Loop2 : } 0 = (Ms)I_{in} + \left(L_2s + \frac{1}{Cs}\right)I_2 \quad (69.2)$$

Since $Z_{in} = \frac{V_{in}}{I_{in}}$ we can simply divide both (eq.69.1) and (eq.69.2) by I_{in} . Then

$$\text{Loop1 : } \frac{V_{in}}{I_{in}} = (R_s + L_1s) + (Ms)\frac{I_2}{I_{in}} \quad (69.3)$$

$$\text{Loop2 : } 0 = (Ms) + \left(L_2s + \frac{1}{Cs}\right)\frac{I_2}{I_{in}} \quad (69.4)$$

From (eq.69.4) we get $\frac{I_2}{I_{in}} = -\frac{Ms}{\frac{1}{Cs} + L_2s}$. Substituting into (eq.69.3) gives

$$Z_{in}(s) = \frac{V_{in}}{I_{in}} = R_s + L_1s - \frac{M^2Cs^3}{1 + L_2Cs^2}$$

$$Z_{in}(j\omega) = R_s + j\omega L_1 + j\omega \frac{M^2C\omega^2}{1 - L_2C\omega^2}$$

$$\text{Im}[Z_{in}(j\omega)] = j\omega \left(L_1 + \frac{M^2C\omega^2}{1 - L_2C\omega^2} \right)$$

At resonant frequency, $\text{Im}[Z_{in}(j\omega_r)] = 0$.

$$0 = L_1 + \frac{M^2C\omega_r^2}{1 - L_2C\omega_r^2}$$

$$0 = 2 + \frac{M^2(0.02)(10^2)}{1 - (1)(0.02)(10^2)}$$

$$\Rightarrow M = 1$$

From the circuit drawing with T-equivalent inductors,

$$\begin{aligned}
 Z_1(s) &= (L_1 - M)s + \left(Ms \parallel \left((L_2 - M)s + \frac{1}{Cs} \right) \right) \\
 &= (L_1 - M)s + \frac{(Ms) \left((L_2 - M)s + \frac{1}{Cs} \right)}{Ms + (L_2 - M)s + \frac{1}{Cs}} \\
 &= (L_1 - M)s + \frac{Ms((L_2 - M)Cs^2 + 1)}{L_2Cs^2 + 1} \\
 Z_1(j\omega) &= j\omega(L_1 - M) + \frac{j\omega M(1 - (L_2 - M)C\omega^2)}{1 - L_2C\omega^2}
 \end{aligned}$$

At resonant frequency, $Im[Z(j\omega_r)] = 0$

$$j\omega \left[(L_1 - M) + \frac{M(1 - (L_2 - M)C\omega_r^2)}{1 - L_2C\omega_r^2} \right] = 0$$


Plugging in $L_1 = 2H$, $L_2 = 1H$, $C = 0.02F$, and $\omega_r = 10r/s$,

$$\begin{aligned}
 (2 - M) + \frac{M(1 - 2(1 - M))}{1 - 2} &= 0 \\
 (2 - M) - M(2M - 1) &= 0 \\
 \boxed{M = 1} \\
 \Rightarrow k = \frac{M}{\sqrt{L_1L_2}} = \frac{1}{\sqrt{2}} &= \boxed{0.707}
 \end{aligned}$$

(b) $H(s) = \frac{V_{out}(s)}{I_{in}(s)}$ and poles and zeros

From section (a) we found that $M = 1H$ and $L_2 - M = 0$ which corresponds to zero impedance \rightarrow short circuit.


From the right figure we find

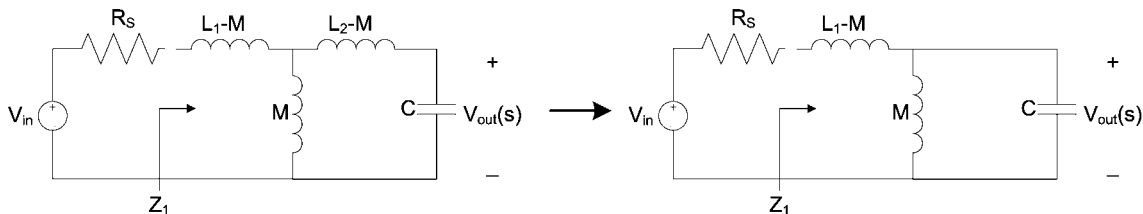


```
poles=roots(den)
% poles =
%
%   -0.0250 + 9.9998i
%   -0.0250 - 9.9998i
%   -0.0500
firstorder=poly(poles(3))
% firstorder =
%
%   1.0000   0.0500
secondorder=poly(poles(1:2))
% secondorder =
%
%   1.0000   0.0500  99.9975
wm=sqrt(secondorder(3))
% wm =
%
%   9.9999
w=linspace(1,20,1000);
h=freqs(num,den,w);
plot(w,abs(h),'linewidth',2); grid on;
xlabel('\omega [rad/s]'); ylabel('|H(j\omega)|');
```

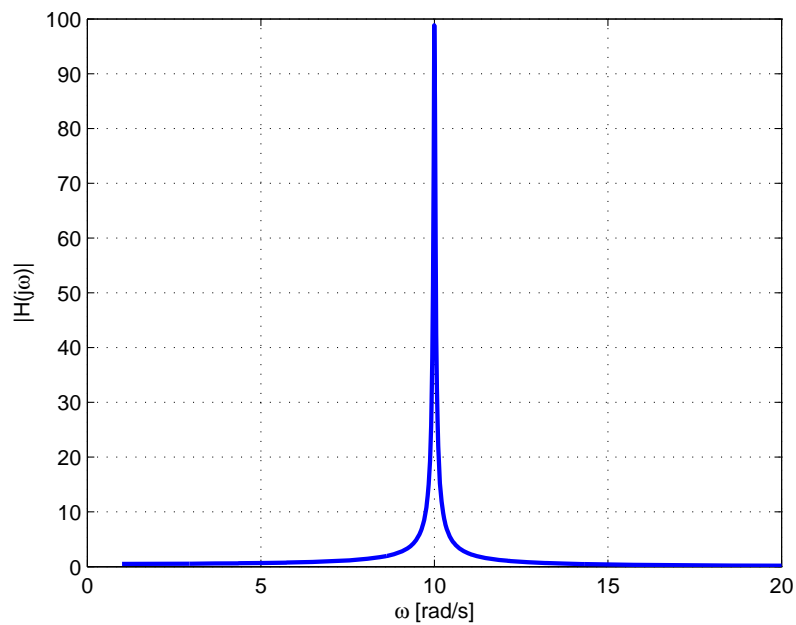(c) MATLAB plot

The MATLAB code in part (b) generates the plot from which we see a bandpass characteristic behavior.



(d) ω_m , B_w , Q , H_m , ω_1 and ω_2

From the MATLAB code in part (b),

$$\begin{aligned} H(s) &= H_1(s)H_2(s) = \frac{50s}{s^3 + 0.1s^2 + 100s + 5} \\ &= \left(\frac{10}{s + 0.05} \right) \left(\frac{5s}{s^2 + 0.05s + 99.9975} \right) \end{aligned}$$

$$\omega_m \approx \sqrt{99.9975} = 9.9999 \approx \boxed{10[\text{rad/s}]}$$


$$B_w \approx \boxed{0.05[\text{rad/s}]}$$

$$Q = \frac{\omega_m}{B_w} = \frac{10}{0.05} = \boxed{200}$$

$$H_m \approx \frac{5}{0.05} = \boxed{100[\text{V/V}]}$$

$$\omega_1 \approx \omega_m - \frac{B_w}{2} = \boxed{9.975[\text{rad/s}]}$$

$$\omega_2 \approx \omega_m + \frac{B_w}{2} = \boxed{10.025[\text{rad/s}]}$$

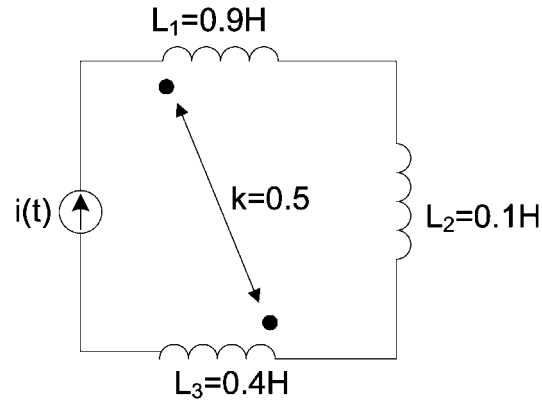Problem 70 Maximum Instantaneous stored energy

$$i(t) = 2\sqrt{2} \cos(100t + 35^\circ) \text{ A}$$


$$k = \frac{M}{\sqrt{L_1 L_2}} \Rightarrow M = k\sqrt{L_1 L_2} = 0.3$$

$$\begin{aligned} Z_{eq} &= s(L_1 + L_2 + 2M + L_3) \\ \Rightarrow L_{eq} &= L_1 + L_2 + 2M + L_3 \\ &= 0.9 + 0.4 + 2(0.3) + 0.1 \\ &= 2\text{H} \end{aligned}$$

$$I_{max} = 2\sqrt{2}$$

$$\begin{aligned} W_{max} &= \frac{1}{2} L_{eq} I_{max}^2 \\ &= \frac{1}{2} (2) (2\sqrt{2})^2 \\ &= \boxed{8\text{J}} \end{aligned}$$


Problem 71

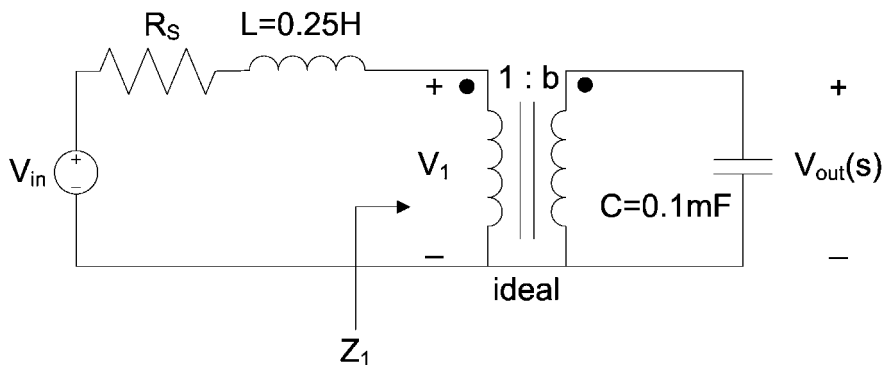

$$\text{where } Z_1 = \left(\frac{1}{b}\right)^2 \frac{1}{Cs} = \frac{1}{(b^2C)s}$$

(a) Transfer function

Using impedance transformation property,

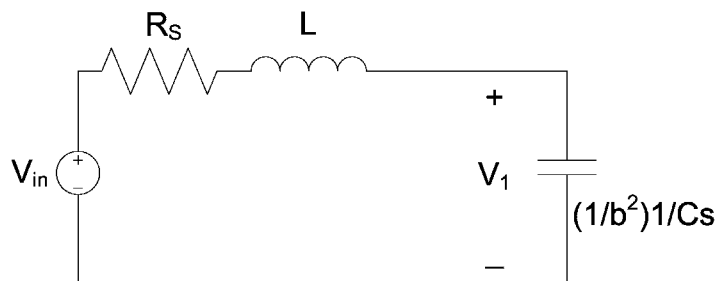

$$V_1 = \frac{1}{R_s + Ls + \frac{1}{b^2Cs}} V_{in}$$

$$V_1 = \frac{1}{b} V_{out}$$

Combining the above two equations,


```

yimpulse=ilaplace(H);
pretty(simplify(ilaplace(H)))
%
%      10000  1/2
%      ----- 51   exp(- 2/5 t) sin(14/5 51  t)
%      357
%
%Step response
ystep=ilaplace(H/s);
pretty(simplify(ilaplace(H*(1/s))))
%
%      10 - 10 exp(- 2/5 t) cos(14/5 51  t)
%
%      10  1/2
%      - ---- 51   exp(- 2/5 t) sin(14/5 51  t)
%      357
%
wp=abs(poles(1))
% wp =
%
%      20.0000
sigmag=abs(real(poles(1)))
% sigmag =
%
%      0.4000
Q=wp/(2*sigmag)
% Q =
%
%      25.0000
w=linspace(1,40,1000);
h=freqs(num,den,w);
plot(w,abs(h),'linewidth',2); grid on;
xlabel('\omega [rad/s]'); ylabel('|H(j\omega)|');

```

(b) Impulse and Step response

The impulse and step responses are easily calculated using MATLAB command *ilaplace*. From the above MATLAB code we found that the impulse and step responses are:

$$\text{Impulse Response} = \boxed{200e^{-0.4t} \sin(20t)u(t)}$$

$$\text{Step Response} = \boxed{[10 - 9.9960e^{-0.4t} \cos(20t) - 0.1999e^{-0.4t} \sin(20t)]u(t)}$$


(c) ω_p , Q_p , ω_m , B_w , $\omega_{1,2}$

$$p_{1,2} = \sigma_p \pm j\omega_d = 0.4 \pm j19.9960$$


For ω_p and Q_p the subscript p refers to the poles.

$$\begin{aligned}\omega_p = \omega_d &= \boxed{19.9960} \\ Q_p &= \frac{\omega_p}{2\sigma_p} = \frac{19.9960}{2(0.4)} \approx \boxed{25} \\ \omega_m &\approx \omega_p = \boxed{20[\text{rad/s}]} \\ \omega_{m,exact} &= \omega_p \sqrt{1 - \frac{1}{2Q_p^2}} = (20) \sqrt{1 - \frac{1}{2(25)^2}} = 19.9840[\text{rad/s}] \\ B_w &= 2\sigma_p = \frac{\omega_p}{Q_p} = \boxed{0.8[\text{rad/s}]} \\ \omega_1 &\approx \omega_m - \frac{B_w}{2} = \boxed{19.6[\text{rad/s}]} \\ \omega_2 &\approx \omega_m + \frac{B_w}{2} = \boxed{20.4[\text{rad/s}]}\end{aligned}$$

The MATLAB code in part(a) produces a figure below:

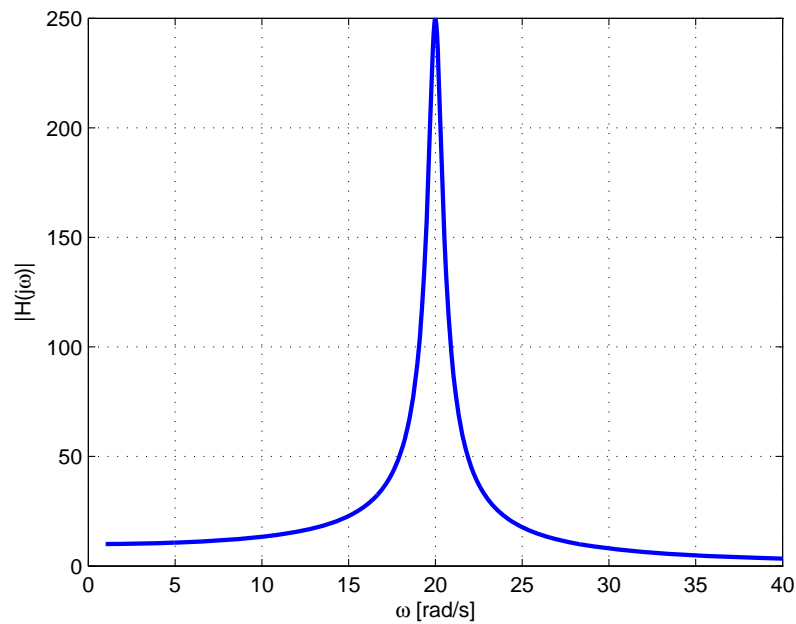

Problem 72

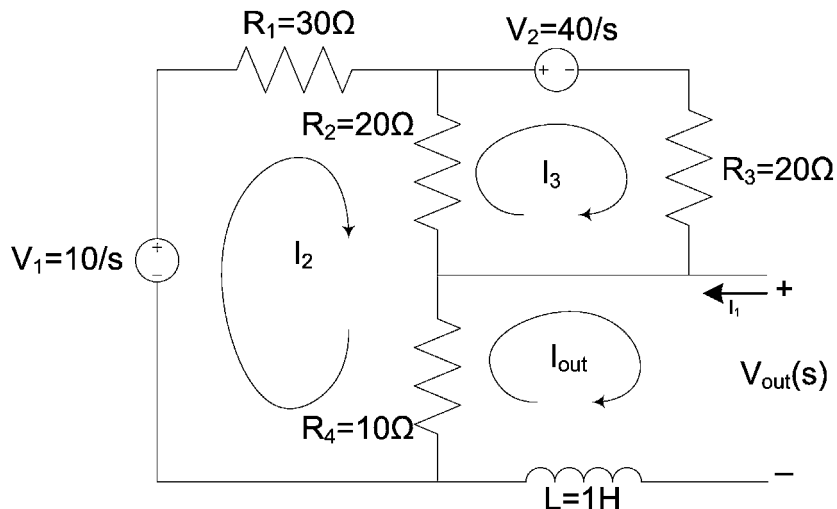

(a) Thevenin equivalent using Matrix partitioning

Writing loop equations,

$$\text{Loop1 : } 0 = -\frac{10}{s} + 30I_2 + 20(I_2 - I_3) + 10(I_2 - I_{out})$$

$$\text{Loop2 : } 0 = \frac{40}{s} + 20I_3 + 20(I_3 - I_2)$$

$$\text{Loop3 : } 0 = V_{out} + sI_{out} + 10(I_{out} - I_2)$$

$$I_1 = -I_{out}$$

Simplifying and writing into a matrix form,

$$\begin{bmatrix} 10/s \\ 40/s \\ V_{out} \end{bmatrix} = \begin{bmatrix} 60 & -20 & -10 \\ 20 & -40 & 0 \\ 10 & 0 & -(s+10) \end{bmatrix} \begin{bmatrix} I_2 \\ I_3 \\ I_{out} \end{bmatrix}$$

$$\begin{bmatrix} 10/s \\ 40/s \\ V_{out} \end{bmatrix} = \begin{bmatrix} W_{11} & W_{12} \\ W_{21} & W_{22} \end{bmatrix} \begin{bmatrix} I_2 \\ I_3 \\ I_{out} \end{bmatrix}$$

Writing out the equations,

$$V_{out} = W_{21} \begin{bmatrix} I_2 \\ I_3 \end{bmatrix} + W_{22} I_{out} \quad (\text{eq72.1})$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = W_{11} \begin{bmatrix} I_2 \\ I_3 \end{bmatrix} + W_{12} I_{out} \quad (\text{eq72.2})$$

From (eq72.2) we will find the expression for $\begin{bmatrix} I_2 \\ I_3 \end{bmatrix}$ and substitute it back to (eq72.1)

$$\begin{aligned} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} &= W_{11} \begin{bmatrix} I_2 \\ I_3 \end{bmatrix} + W_{12} I_{out} & (\text{eq72.2}) \\ \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} - W_{12} I_{out} &= W_{11} \begin{bmatrix} I_2 \\ I_3 \end{bmatrix} \\ W_{11}^{-1} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} - W_{11}^{-1} W_{12} I_{out} &= \begin{bmatrix} I_2 \\ I_3 \end{bmatrix} \end{aligned}$$

$$\Rightarrow \begin{bmatrix} I_2 \\ I_3 \end{bmatrix} = W_{11}^{-1} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} - W_{11}^{-1} W_{12} I_{out} \quad (\text{eq72.3})$$

Now substituting (eq72.3) into (eq.72.1),

$$\begin{aligned} V_{out} &= W_{21} \begin{bmatrix} I_2 \\ I_3 \end{bmatrix} + W_{22} I_{out} \\ V_{out} &= W_{21} \left(W_{11}^{-1} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} - W_{11}^{-1} W_{12} I_{out} \right) + W_{22} I_{out} \\ &= W_{21} W_{11}^{-1} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} - W_{21} W_{11}^{-1} W_{12} I_{out} + W_{22} I_{out} \\ &= W_{21} W_{11}^{-1} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} + (W_{22} - W_{21} W_{11}^{-1} W_{12}) I_{out} \\ &= \underbrace{W_{21} W_{11}^{-1} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}}_{V_{oc}} + \underbrace{(W_{21} W_{11}^{-1} W_{12} - W_{22}) I_1}_{Z_{th}} \end{aligned}$$

$$\begin{aligned}
V_{oc} &= W_{21} W_{11}^{-1} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = [10 \quad 0] \begin{bmatrix} 60 & -20 \\ 20 & -40 \end{bmatrix}^{-1} \begin{bmatrix} 10/s \\ 40/s \end{bmatrix} \\
&= [10 \quad 0] \frac{1}{(60)(-40) - (-20)(20)} \begin{bmatrix} -40 & 20 \\ -20 & 60 \end{bmatrix} \begin{bmatrix} 10/s \\ 40/s \end{bmatrix} \\
&= -\frac{1}{2000} [10 \quad 0] \begin{bmatrix} -40 & 20 \\ -20 & 60 \end{bmatrix} \begin{bmatrix} 10/s \\ 40/s \end{bmatrix} \\
&= -\frac{1}{2000} [10(-40) + 0(-20) \quad 10(20) + 0(60)] \begin{bmatrix} 10/s \\ 40/s \end{bmatrix} \\
&= -\frac{1}{2000} [-400 \quad 200] \begin{bmatrix} 10/s \\ 40/s \end{bmatrix} \\
&= -\frac{1}{2000} (-400(10/s) + 200(40/s)) \\
&= -\frac{1}{2000} (8000/s) \\
&= -\frac{2}{s}
\end{aligned}$$

$$\begin{aligned}
Z_{th} &= W_{21} W_{11}^{-1} W_{12} - W_{22} = [10 \quad 0] \begin{bmatrix} 60 & -20 \\ 20 & -40 \end{bmatrix}^{-1} \begin{bmatrix} -10 \\ 0 \end{bmatrix} - [-(s+10)] \\
&= -\frac{1}{2000} [10 \quad 0] \begin{bmatrix} -40 & 20 \\ -20 & 60 \end{bmatrix} \begin{bmatrix} -10 \\ 0 \end{bmatrix} + (s+10) \\
&= -\frac{1}{2000} [-400 \quad 200] \begin{bmatrix} -10 \\ 0 \end{bmatrix} + (s+10) \\
&= -\frac{1}{2000} (-4000) + (s+10) \\
&= s+8
\end{aligned}$$

Using MATLAB to compute V_{oc} and Z_{th} ,

```

syms s I2 I3 Iout V1 V2 Vout Voc Zth
b=[10/s;40/s;Vout];
x=[I2;I3;Iout];
A=[60 -20 -10; 20 -40 0; 10 0 -(s+10)];
W11=[60 -20; 20 -40];
W12=[-10;0];
W21=[10 0];
W22=[-(s+10)];

```

```

Voc=W21*inv(W11) * [10/s;40/s]
% Voc =
%
% -2/s
Zth=W21*inv(W11) *W12-W22
% Zth =
%
% 8+s


```

$$V_{oc} = -\frac{2}{s}$$

$$Z_{th} = s + 8$$

(b)

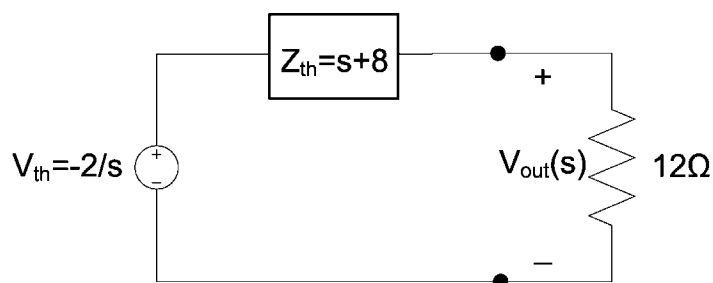When 12Ω resistor is connected to the output, the circuit becomes:



Simply using voltage division,

$$\begin{aligned}
 V_{out} &= \frac{12}{(s + 8) + 12} V_{th} \\
 &= \frac{12}{s + 20} \left(-\frac{2}{s} \right) \\
 &= \frac{-24}{s(s + 20)}
 \end{aligned}$$

Using *ilaplace* command in MATLAB,

$$v_{out}(t) = -1.2(1 - e^{-20t})u(t)$$