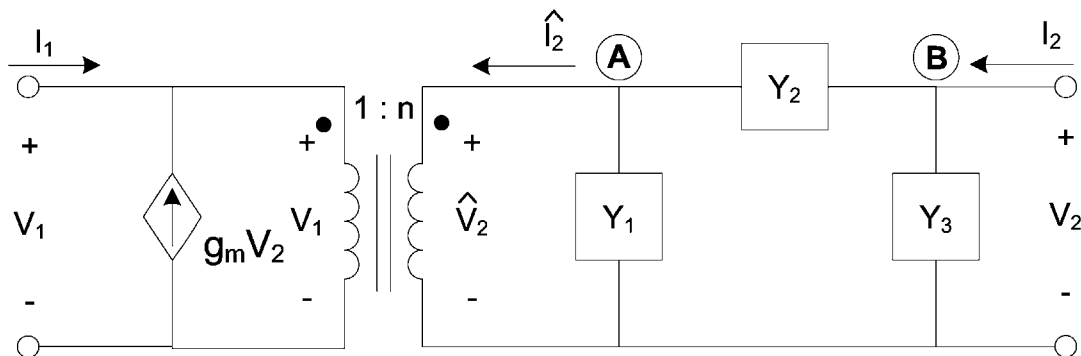


ECE 202 LINEAR CIRCUIT ANALYSIS II (SP'09)

Homework #19 Solution (73-76)

Problem 73



$$g_m = 2\text{S} , n = 2 , Y_1 = Y_2 = 0.2 \text{ S} , Y_3 = 0.5\text{s S}$$

(a) Find Y-parameters

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \underbrace{\begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix}}_{[Y]} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

To find Y-parameters we need to express I_1 and I_2 in terms of V_1 and V_2 . We will do this by writing node equations at nodes A and B as indicated in the diagram.

$$\text{node A:} \quad 0 = \hat{I}_2 + \hat{V}_2 Y_1 + (\hat{V}_2 - V_2) Y_2 \tag{73.1}$$

$$\text{node B:} \quad 0 = -I_2 + V_2 Y_3 + (V_2 - \hat{V}_2) Y_2 \tag{73.2}$$

Using voltage relationship of ideal transformer we get

$$\hat{V}_2 = nV_1 \tag{73.3}$$

$$\hat{I}_2 = -\frac{1}{n} \hat{I}_1 = -\frac{1}{n} (I_1 + g_m V_2) \tag{73.4}$$

Substituting \hat{V}_2 and \hat{I}_1 into (eq.73.1) and (eq.73.2),

$$0 = -\frac{1}{n} (I_1 + g_m V_2) + (nV_1) Y_1 + (nV_1 - V_2) Y_2 \quad \Rightarrow \quad I_1 = (n^2(Y_1 + Y_2))V_1 + (-g_m - nY_2)V_2$$

$$0 = -I_2 + V_2 Y_3 + (V_2 - nV_1) Y_2 \quad \Rightarrow \quad I_2 = (-nY_2)V_1 + (Y_2 + Y_3)V_2$$

Writing into a matrix form,

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} n^2(Y_1 + Y_2) & -(g_m + nY_2) \\ -nY_2 & Y_2 + Y_3 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

Plugging in the given values, we get

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 1.6 & -2.4 \\ -0.4 & 0.2 + 0.5s \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$


(b) Z-parameters

Z-parameter is simply the inverse of Y-parameter.

$$\begin{aligned} [I] &= [Y][V] \\ [Y]^{-1}[I] &= [V] \\ \Rightarrow [Z] &= [Y]^{-1} \\ &= \begin{bmatrix} 1.6 & -2.4 \\ -0.4 & 0.2 + 0.5s \end{bmatrix}^{-1} \\ &= \frac{1}{(1.6)(0.2 + 0.5s) - (-2.4)(-0.4)} \begin{bmatrix} 0.2 + 0.5s & 2.4 \\ 0.4 & 1.6 \end{bmatrix} \\ &= \frac{1}{s - 0.8} \begin{bmatrix} 0.625s + 0.25 & 3 \\ 0.5 & 2 \end{bmatrix} [\Omega] \end{aligned}$$

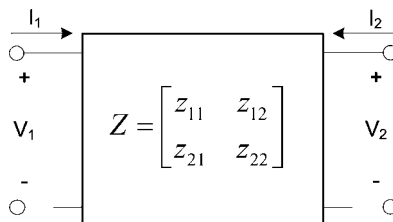(c) impulse response $v_2(t)$


Before any connection the matrix equation is:



$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

When port 1 is connected to a current source and port 2 is connected to a $R_L = 10\Omega$ resistor, our matrix equations changes in the following way:

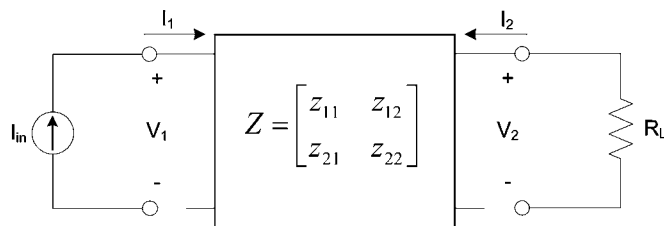Since $I_1 = I_{in}(s) = 1$ and $I_2 = -V_2 Y_L$,



$$\begin{aligned} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} &= \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} \\ \Rightarrow \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} &= \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} 1 \\ -V_2/R_L \end{bmatrix} \end{aligned}$$

Writing out the second equation,

$$\begin{aligned} V_2 &= z_{21} - z_{22} \frac{V_2}{R_L} \\ V_2 + z_{22} \frac{V_2}{R_L} &= z_{21} \\ V_2 &= \frac{z_{21} R_L}{z_{22} + R_L} \\ &= \frac{1/2}{s - 0.8} (10) \\ &= \frac{2}{s - 0.8} + 10 \\ &= \frac{5/2}{5s - 3} = \frac{1/2}{s - 3/5} \\ v_2(t) &= \boxed{0.5e^{+0.6t} u(t) [\text{V}]} \end{aligned}$$


MATLAB codes

```

syms s I1 I2 V1 V2 y11 y12 y21 y22 Y Z z11 z12 z21 z22
gm=2; n=2; Y1=0.2; Y2=Y1; Y3=0.5*s;
y11=n^2*(Y1+Y2);
y12=-(gm+n*Y2);
y21=-n*Y2;
y22=Y2+Y3;
Y=[y11 y12;y21 y22]
% pretty(simplify(Y))
%
%               [8/5          -12/5   ]
%               [                ]
%               [-2/5    1/5 + 1/2 s]
Z=inv(Y);
z11=Z(1,1); z12=Z(1,2); z21=Z(2,1); z22=Z(2,2);
RL=10;
V2=RL*z21/(z22+RL)
%
%               1
%               -----
%               5/2  -3 + 5 s
%

```

Problem 74

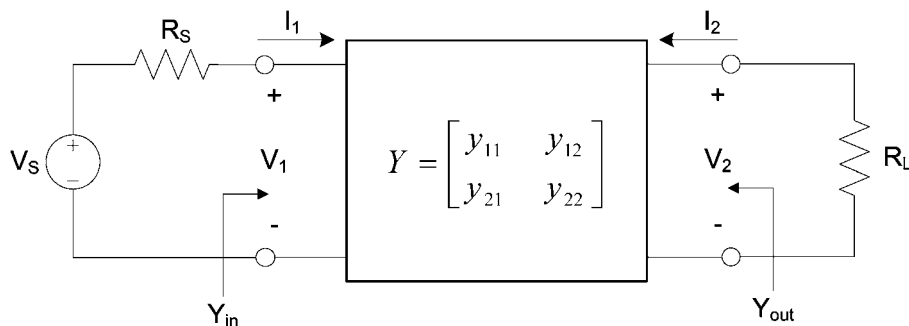


$$R_s = 1\Omega, y_{21} = -1S, y_{12} = 0.75S, y_{22} = 0.25S, R_L = 8\Omega, \frac{V_1}{V_s} = \frac{2}{s+6}$$

(a) y_{11}

$$\begin{aligned} \frac{V_1}{V_s} &= \frac{Z_{in}}{Z_{in} + Z_s} = \frac{Y_s}{Y_{in} + Y_s} = \frac{2}{s+6} \\ \Rightarrow Y_s(s+6) &= 2(Y_{in} + Y_s) \\ Y_{in}(s) &= \frac{s+4}{2} Y_s = \frac{s+4}{2} \end{aligned}$$

Input and Output Immittance

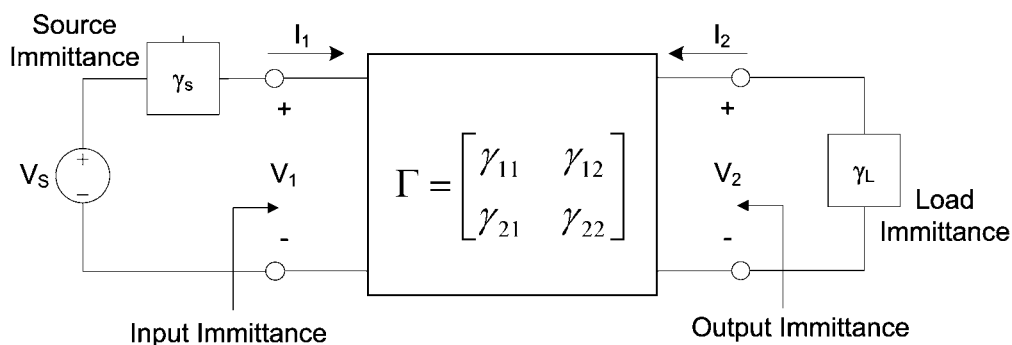

$$\begin{aligned} \text{Input immittance} &= \gamma_{11} - \frac{\gamma_{12}\gamma_{21}}{\gamma_{22} + (\text{load immittance})} \\ \text{Output immittance} &= \gamma_{22} - \frac{\gamma_{12}\gamma_{21}}{\gamma_{11} + (\text{source immittance})} \end{aligned}$$

Using above formula,

$$\begin{aligned}
 Y_{in}(s) &= y_{11} - \frac{y_{12}y_{21}}{y_{22} + Y_L} \\
 y_{11} &= Y_{in}(s) + \frac{y_{12}y_{21}}{y_{22} + Y_L} \\
 y_{11} &= \frac{s+4}{2} + \frac{(0.75)(-1)}{0.25 + 1/8} \\
 &= \boxed{\frac{s}{2} [\text{S}]}
 \end{aligned}$$

(b) Y_{out}

$$\begin{aligned}
 Y_{out} &= y_{22} - \frac{y_{12}y_{21}}{y_{11} + Y_s} \\
 &= (0.25) - \frac{(0.75)(-1)}{s/2 + 1} \\
 &= \boxed{\frac{1s + 8}{4s + 2} [\text{S}]}
 \end{aligned}$$

(c) Voltage Gain $G_v = \frac{V_2}{V_s}$

$$\begin{aligned}
 G_v &= \frac{V_2}{V_s} = \frac{V_2}{V_1} \frac{V_1}{V_s} \\
 &= \left(\frac{Y_s}{Y_{in} + Y_s} \right) \left(\frac{-y_{21}}{y_{22} + Y_L} \right) \\
 &= \boxed{\frac{16/3}{s + 6}}
 \end{aligned}$$

(d) Power $p_L(t)$ absorbed by R_L

$$\text{Given } v_s(t) = 30u(t) \text{ V, } V_s(s) = 30/s$$

$$\begin{aligned}
 G_v &= \frac{V_2}{V_s} \Rightarrow V_2 = G_v V_s \\
 &= \frac{16/3 \cdot 30}{s + 6} \\
 &= \frac{160}{s(s + 6)} \\
 \Rightarrow v_2(t) &= \frac{80}{3} (1 - e^{-6t}) \text{ [V]} \\
 p_L(t) &= \frac{(v_2(t))^2}{R_L} = \frac{1}{8} \left(\frac{80}{3} (1 - e^{-6t}) \right)^2 \\
 &= \boxed{\frac{800}{9} (1 - e^{-6t})^2 \text{ [W]}}
 \end{aligned}$$


MATLAB code

```

syms s I1 I2 V1 V2 y11 y12 y21 y22 Y Yin Ys Yout Gv
Rs=1; Ys=1/Rs; y21=-1; y12=0.75; y22=0.25; RL=8; YL=1/RL;
Vs=30/s;
Yin=(s+4)/2;
y11=Yin+y12*y21/(y22+YL)
% 1/2*s
Yout=y22-(y12*y21)/(y11+Ys)
%
%          s + 8
%          1/4 -----
%          s + 2
Gv=(Ys/(Ys+Yin))*(-y21/(y22+YL))
%
%          1
%          16/3 -----
%          6 + s
V2=Gv*Vs
%
%          160
%          -----
%          (6 + s) s

```

Problem 75 Admittance Parameters

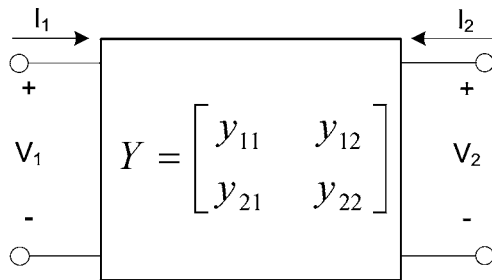

$$y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0}$$

$$y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0}$$

$$y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0}$$

$$y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0}$$


(a) Y-parameters

Short-ckt port-2 $\Rightarrow V_2 = 0$

Given

$$v_1(t) = (1 - e^{-4t})u(t) \quad \Rightarrow V_1(s) = \frac{1}{s(s+4)}$$
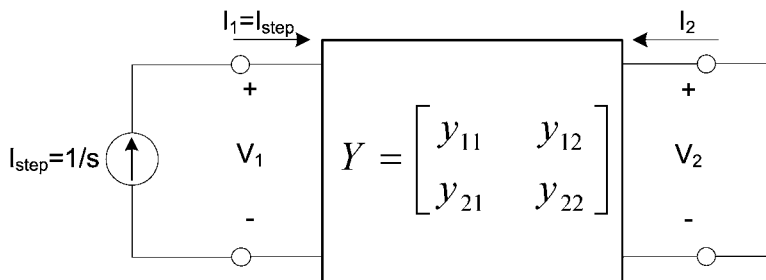
$$v_2(t) = -e^{-3t}u(t) \quad \Rightarrow V_2(s) = -\frac{1}{s+3}$$



$$y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0} = -\frac{1}{s+3} \frac{s(s+4)}{4} = \boxed{-\frac{1}{4} \frac{s(s+4)}{s+3}} [S]$$


$$y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} = \left(\frac{1}{s} \right) \frac{s(s+4)}{4} = \boxed{\frac{1}{4}(s+4)} [S]$$

1Ω resistor at port 2

Given

$$v_1(t) = (1 - e^{-4t} + te^{-4t})u(t) \quad \Rightarrow V_1(s) = \frac{5s + 6}{s(s+4)^2}$$
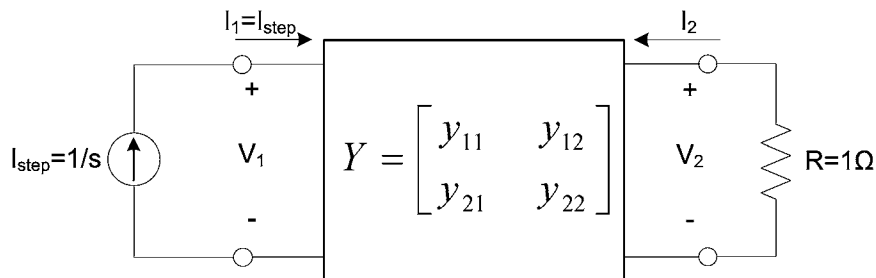
$$v_2(t) = -e^{-7t}u(t) \quad \Rightarrow V_2(s) = -\frac{1}{s+7}$$



$$\begin{bmatrix} I_1 \\ -V_2 Y_L \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$\begin{bmatrix} I_1 \\ 0 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} + Y_L \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \tag{75.1}$$

$$I_1 = y_{11}V_1 + y_{12}V_2 \tag{75.2}$$

$$0 = y_{21}V_1 + (y_{22} + Y_L)V_2 \tag{75.3}$$

Rearranging (eq.75.2) we get

$$y_{12} = \frac{I_1 - y_{11}V_1}{V_2}$$

$$= \frac{\frac{1}{s} + \left(\frac{1}{4}(s+4) \right) \left(\frac{5s+6}{s(s+4)^2} \right)}{-\frac{1}{s+7}}$$

$$= \boxed{-\frac{1}{4} \frac{s+7}{s+4}} [S]$$

and from (eq.75.3),

$$\begin{aligned} V_2 &= \frac{-y_{21}}{y_{22} + Y_L} V_1 \\ \Rightarrow y_{22} &= -Y_L - y_{21} \frac{V_1}{V_2} \\ &= \boxed{\frac{1}{4} \frac{s^2 + 23s + 64}{(s+3)(s+4)}} \text{ [S]} \end{aligned}$$

$$Y = \frac{1}{4} \begin{bmatrix} (s+4) & -\frac{s+7}{s+4} \\ -\frac{s(s+4)}{s+3} & \frac{s^2 + 23s + 64}{(s+3)(s+4)} \end{bmatrix}$$

(b) $Z_{in}(s)$

$$\begin{aligned} Y_{in}(s) &= y_{11} - \frac{y_{12}y_{21}}{y_{22} + Y_L} \\ &= \frac{s^2 + 8s + 16}{5s + 16} \\ Z_{in}(s) &= \frac{1}{Y_{in}(s)} \\ &= \boxed{\frac{5s + 16}{s^2 + 8s + 16}} \text{ [\Omega]} \end{aligned}$$

(c) Steady state magnitude of the gain

$$i_1(t) = \cos(4t)u(t) \Rightarrow I_1(s) = \frac{s}{s^2 + 16}$$

Using the Y-matrix obtained from part (a) and (eq.75.1),


$$\begin{bmatrix} \frac{s}{s^2 + 16} \\ 0 \end{bmatrix} = \frac{1}{4} \begin{bmatrix} (s+4) & -\frac{s+7}{s+4} \\ -\frac{s(s+4)}{s+3} & \frac{s^2 + 23s + 64}{(s+3)(s+4)} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$


```

%
%
%          [      2      ]
%          [ (s  + 23 s + 64) s ]
%          [1/4 -----]
%          [      2      2      ]
%          [ (s + 4) (s  + 16) ]
%
%
%          [      2      ]
%          [      s      ]
%          [ 1/4 ----- ]
%          [      2      ]
%          [      s  + 16  ]
%
V2=V(2,1);
G=V2/I(1)
%          1/4 s
%
s=i*4;
abs(1/4*s)
% ans =
%
%      1

```

Problem 76

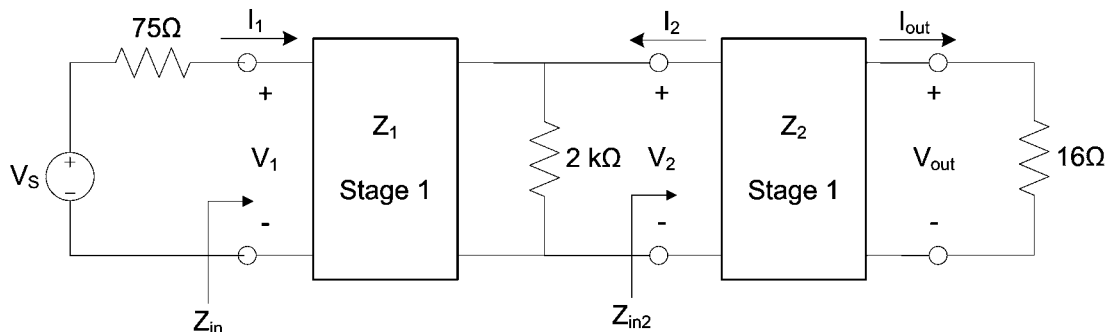


$$Z_1 = \begin{bmatrix} 2 & 0 \\ -10^3 & 20 \end{bmatrix} [\text{k}\Omega] \quad \text{and} \quad Z_2 = \begin{bmatrix} 62.582 & 1.2075 \\ 63.75 & 1.25 \end{bmatrix} [\text{k}\Omega]$$

(a) $Z_{in2}(s)$ and $Z_{in}(s)$

$$\begin{aligned} Z_{in2}(s) &= z_{2,11} - \frac{z_{2,12}z_{2,21}}{z_{2,22} + Z_L} \\ &= (62.582) - \frac{(1.2075)(63.75)}{1.25 + 0.016} \\ &= \boxed{1.7778[\text{k}\Omega]} \\ Z_{in}(s) &= z_{1,11} - \frac{z_{1,12}z_{1,21}}{z_{1,22} + (2\text{k}\Omega || Z_{in2}(s))} \\ &= (2) - \frac{(0)(-10^3)}{z_{1,22} + (2\text{k}\Omega || Z_{in2}(s))} \\ &= \boxed{2[\text{k}\Omega]} \end{aligned}$$

(b) $G_v = \frac{V_{out}}{V_s}$

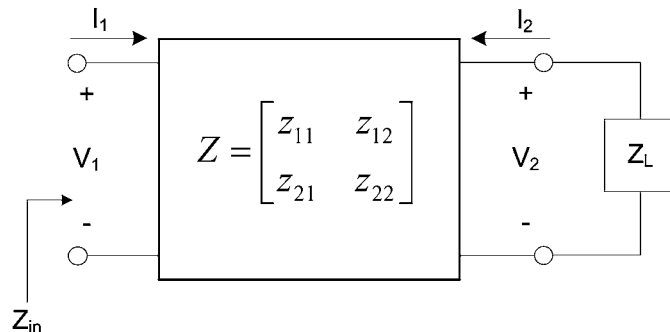


$$\begin{aligned} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} &= \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} & \text{and} & V_2 = -I_2 Z_L \\ \Rightarrow \begin{bmatrix} V_1 \\ 0 \end{bmatrix} &= \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} + Z_L \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} \\ \Rightarrow I_2 &= \frac{-z_{21}}{z_{22} + Z_L} I_1 \\ \Rightarrow V_2 &= \frac{z_{21} Z_L}{z_{22} + Z_L} I_1 \end{aligned} \tag{76.1}$$

$$\begin{aligned} G_v &= \frac{V_{out}}{V_s} = \left(\frac{V_{out}}{V_2} \right) \left(\frac{V_2}{V_1} \right) \left(\frac{V_1}{V_s} \right) \\ &= G_{v3} G_{v2} G_{v1} \\ G_{v1} &= \frac{V_1}{V_s} = \frac{Z_{in}}{Z_{in} + Z_s} = \frac{2}{2 + 0.075} = 0.9639 \\ G_{v2} &= \frac{V_2}{V_1} = \frac{V_2 I_1}{I_1 V_1} = \frac{z_{1,21}(2||Z_{in2})}{z_{1,22} + (2||Z_{in2})} \frac{1}{Z_{in}} \\ &= -22.4720 \\ G_{v3} &= \frac{V_{out}}{V_2} = \frac{V_{out} I_2}{I_2 V_2} = \frac{z_{2,21} Z_L}{z_{2,22} + Z_L} \frac{1}{Z_{in2}} \\ &= 0.4532 \\ \Rightarrow G_v &= (0.9639)(-22.4720)(0.4532) = \boxed{-9.8161} \end{aligned}$$

(c) $P_{gain} = \frac{v_{out} i_{out}}{v_1 i_1}$

$$\begin{aligned}
 P_{gain} &= \frac{v_{out} i_{out}}{v_1 i_1} = \frac{v_{out}}{v_1} \frac{i_{out}}{i_1} \\
 &= \frac{v_{out}}{v_1} \frac{v_{out}/0.016}{v_1/Z_{in}} \\
 &= (G_{v2} G_{v3})^2 \frac{2}{0.016} \\
 &= \boxed{12.965 \times 10^3}
 \end{aligned}$$

(d) Check the impedance matching

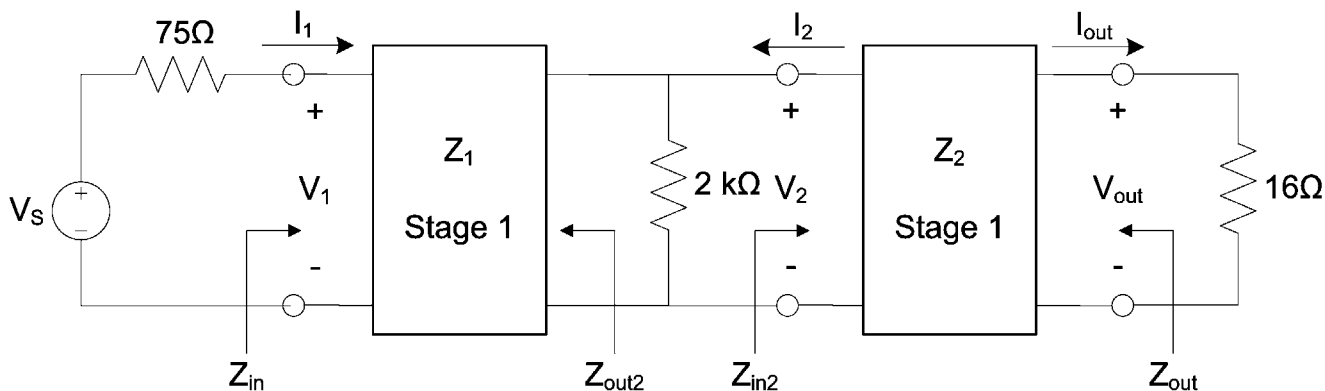

Output Impedance

$$\begin{aligned}
 Z_{out2} &= z_{1,22} - \frac{z_{1,12} z_{1,21}}{z_{1,11} + Z_s} \\
 &= 20[\text{k}\Omega] \\
 Z_{out} &= z_{2,22} - \frac{z_{2,12} z_{2,21}}{z_{2,11} + (Z_{out2} || 2)} \\
 &= \boxed{54.7[\Omega]}
 \end{aligned}$$

The load impedance is 16Ω and the output impedance is 54.7Ω. So the impedances do not match well.

MATLAB code

```

Zs=75e-3; ZL=16e-3;
Z1=[2, 0; -10^3, 20];
    z1_11=Z1(1,1);
    z1_12=Z1(1,2);
    z1_21=Z1(2,1);
    z1_22=Z1(2,2);

Z2=[62.582, 1.2075; 63.75, 1.25];
    z2_11=Z2(1,1);
    z2_12=Z2(1,2);
    z2_21=Z2(2,1);
    z2_22=Z2(2,2);

Zin2= z2_11-(z2_12*z2_21)/(z2_22+ZL)
% Zin2 =
%
%      1.7778
Zin= z1_11-(z1_12*z1_21)/(z1_22+(Zin2*2)/(Zin2+2))
% Zin =
%
%      2
Gv1=Zin/(Zin+Zs)
% Gv1 =
%
%      0.9639
Z2=(Zin2*2)/(Zin2+2);
Gv2=(z1_21*Z2)/(z1_22+Z2)/Zin
% Gv2 =
%
%     -22.4720
Gv3=(z2_21*ZL)/(z2_22+ZL)/Zin2
% Gv3 =
%
%      0.4532
Gv=Gv1*Gv2*Gv3
% Gv =
%
%     -9.8161
P=(Gv2*Gv3)^2*Zin/ZL
% P =
%
%      1.2965e+004
Zout2=z1_22-(z1_12*z1_21)/(z1_11+Zs)
% Zout2 =
%
%      20

Zout=z2_22-(z2_12*z2_21)/(z2_11+(Zout2*2)/(Zout2+2))
% Zout =
%
%      0.0547

```