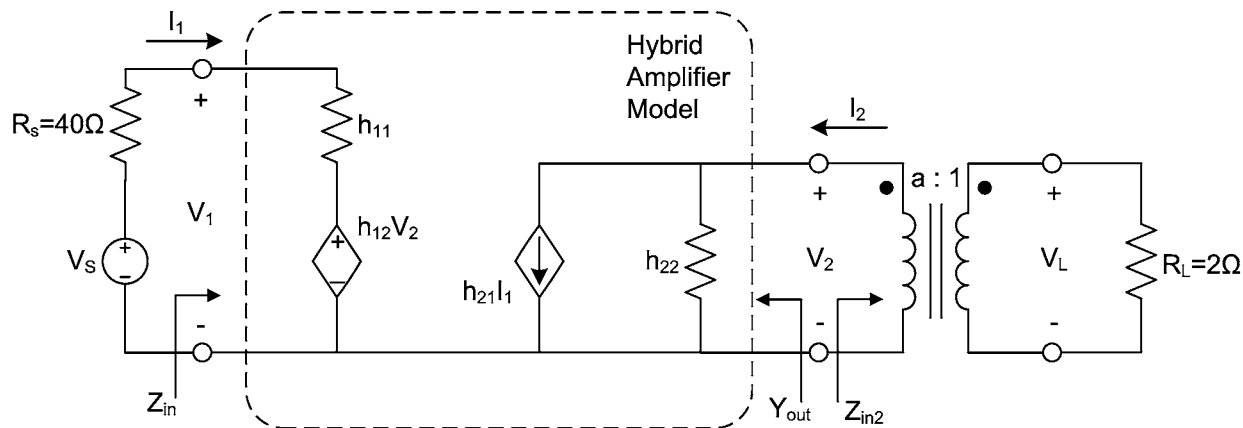


## ECE 202 LINEAR CIRCUIT ANALYSIS II (SP'09)

Homework #20 Solution (77–78)

### Problem 77–78



Amplifier Specifications:

1. When  $I_1$  is zero, the ratio  $\frac{V_1}{V_2} = 0$ , when a source is applied to port 2.
2. There must be maximum power transfer from the amplifier output to the load under the condition that  $Z_{out}(s) = 800\Omega$ .
3.  $\frac{V_1}{V_s} = \frac{25}{26}$
4. The voltage gain  $\frac{V_2}{V_1} = -100$

The two port Hybrid parameters are:

$$V_1 = h_{11}I_1 + h_{12}V_2 \tag{77.1}$$

$$I_2 = h_{21}I_1 + h_{22}V_2 \tag{77.2}$$

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} \text{ } [\Omega]$$

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0}$$

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0}$$

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0} \text{ } [S]$$

(a)  $h_{12}$ 

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0} = \boxed{0} \quad \text{From condition 1.}$$

(b)  $Y_{out}, h_{22}$ , and turn ratio  $a$ Given the condition that the value of  $Z_{out} = 800\Omega$ ,

$$Y_{out} = \frac{1}{Z_{out}} = \boxed{\frac{1}{800} = [\text{S}]}$$

$h_{22}$  is defined as  $\left. \frac{I_2}{V_2} \right|_{I_1=0}$ . When  $I_1$  is zero, the value of the dependent current source  $h_{21}I_1$  is zero and it becomes an open circuit. As a result,

$$h_{22} = Y_{out} = \boxed{\frac{1}{800} = [\text{S}]}$$

From the condition 2, we want the impedances  $Z_{out}$  and  $Z_{in2}$  to match.

$$\begin{aligned} Z_{out} &= Z_{in2} \\ &= a^2 R_L \\ \Rightarrow a &= \sqrt{\frac{Z_{out}}{R_L}} = \sqrt{\frac{800}{2}} = \boxed{20} \end{aligned}$$

(c)  $h_{11}$ Because  $h_{12} = 0$ , the dependent voltage source becomes a short circuit and  $Z_{in} = h_{11}$ . Given  $\frac{V_1}{V_s} = \frac{25}{26}$ ,

$$\begin{aligned} \frac{V_1}{V_s} &= \frac{Z_{in}}{Z_{in} + R_s} = \frac{25}{26} = \frac{h_{11}}{h_{11} + R_s} \\ \Rightarrow h_{11} &= \boxed{1\text{k}\Omega} \end{aligned}$$

(d)  $Z_{in}$ From part c) we found that  $Z_{in} = h_{11} = \boxed{1\text{k}\Omega}$ .(e)  $h_{21}$ When port 2 is connected to the load  $Z_{in2}$ , then the  $I_2$  in (eq.77.2) becomes  $-V_2 Y_{in2}$ . Then it simplifies to:

$$\begin{aligned}
 I_2 &= h_{21} I_1 + h_{22} V_2 \\
 -V_2 Y_{in2} &= h_{21} I_1 + h_{22} V_2 \\
 \Rightarrow h_{21} &= -\frac{V_2 (h_{22} + Y_{in2})}{I_1} \\
 &= -\left(\frac{V_1}{I_1}\right) \left(\frac{V_2}{V_1}\right) (h_{22} + Y_{in2}) \\
 &= -(Z_{in}) (-100) \left(\frac{1}{800} + \frac{1}{800}\right) \\
 &= \boxed{250}
 \end{aligned}$$

(f) Ratio of Power delivered to the load to the power delivered to  $R_L$ 

$$\begin{aligned}
 P_{load} &= \frac{(V_2)^2}{Z_{in2}} \\
 P_{R_L} &= \frac{(V_L)^2}{R_L} = \frac{(V_2/a)^2}{R_L} \\
 \therefore \frac{P_{load}}{P_{R_L}} &= \frac{(V_2)^2}{Z_{in2}} \frac{a^2 R_L}{(V_2)^2} = \frac{(400)(2)}{800} = \boxed{1}
 \end{aligned}$$