


ECE 202 - Linear Circuit Analysis II

Purdue University, Spring 2009

Homework Set 3 Solutions


Solution 21

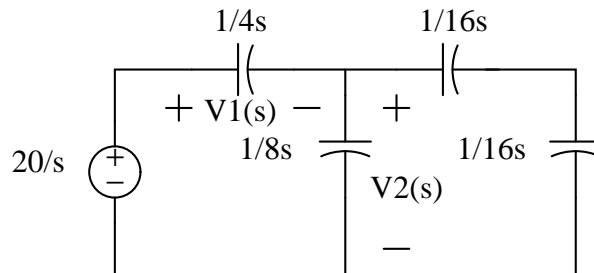When the switches are moved to position A, the circuit looks like the following:-



$$\begin{aligned}
 V_1 &= \left[\frac{20}{s} \left(\frac{1}{4s} + \frac{1}{16s} \right)^{-1} \right] \frac{1}{4s} \\
 &= \frac{16}{s} \\
 \Rightarrow v_1(t) &= 16u(t) \\
 V_2 &= \left[\frac{20}{s} \left(\frac{1}{4s} + \frac{1}{16s} \right)^{-1} \right] \frac{1}{16s} \\
 &= \frac{4}{s} \\
 \Rightarrow v_2(t) &= 4u(t) \\
 \Rightarrow v_1(0+) = v_1(2-) &= 16 \text{ V} \\
 v_2(0+) = v_2(2-) &= 4 \text{ V}
 \end{aligned}$$

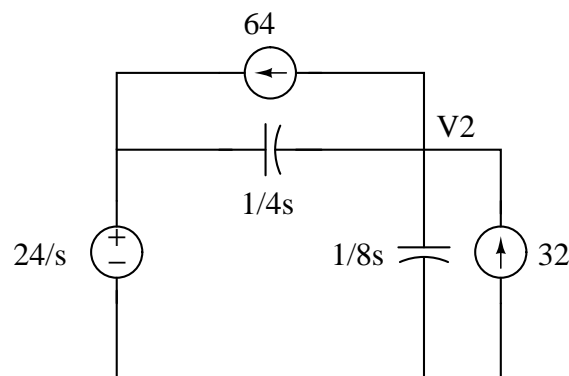At $t=2$, when the switch is moved to position B, we get the following circuit, Thus is the new time frame we have,



$$\left(\frac{24}{s} - V_2 \right) 4s + 32 = V_2(8s) + 64$$

$$\begin{aligned}\Rightarrow v_2 &= \frac{16}{3}u(t) \\ \Rightarrow v_2(2+) &= \frac{16}{3}V \\ v_1(2+) &= 24 - \frac{16}{3} = \frac{56}{3}V\end{aligned}$$

Solution 22


(a)

Before $t=0$, the circuit reaches steady state so that capacitors can be assumed to be in open circuit. Thus we get,

$$v_1(0-) = v_2(0-) = \frac{16}{2R} \times R = 8V$$

(b)

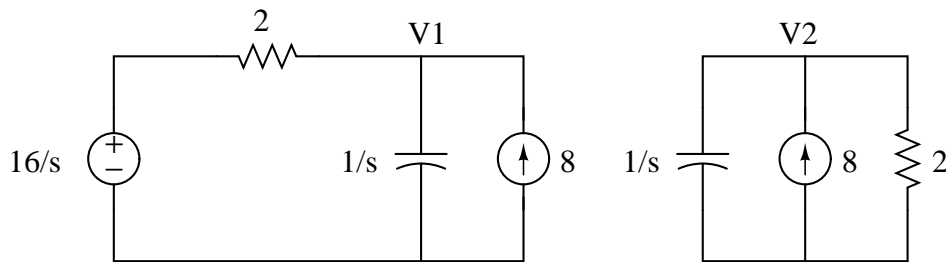After S_2 is opened the circuit looks like the following,



$$\begin{aligned}\frac{1}{2}\left(\frac{16}{s} - V_1\right) + 8 &= sV_1 \\ V_1 &= \frac{8(s+1)}{s(s+0.5)} \\ \Rightarrow v_1(t) &= [16 - 8e^{-0.5t}]u(t), \quad 0 \leq t < 1 \\ sV_2 + 0.5V_2 &= 8 \\ V_2 &= \frac{8}{s+0.5} \\ \Rightarrow v_2(t) &= 8e^{-0.5t}u(t), \quad 0 \leq t < 1 \\ \Rightarrow v_1(0+) = v_2(0+) &= 8V\end{aligned}$$

Check: The voltage across a capacitor cannot change instantaneously once it is in steady state, so our solution is correct.

(c)


See part (b)

(d)

$$\begin{aligned}v_1(1^-) &= 16 - 8e^{-0.5} = 11.1478 \text{ V} \\v_1(1^-) &= 8e^{-0.5} = 4.8522 \text{ V}\end{aligned}$$

(e)

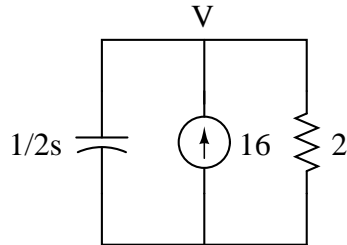Redefining the time frame when switch S_2 is closed and S_1 is opened, we get the following circuit. Parallel capacitances are clubbed together and also the current sources due to initial conditions.




$$\begin{aligned}V(2s + 0.5) &= 16 \\ \Rightarrow V &= \frac{8}{s + 0.25} \\ \Rightarrow v(t) &= 8e^{-0.25t}u(t) \\ \Rightarrow v_1(1^+) = v_2(1^+) &= 8 \text{ V}\end{aligned}$$

Thus in the original time frame,

$$v_1(t) = v_2(t) = 8e^{-0.25(t-1)}u(t-1), \quad t > 1$$

(f)

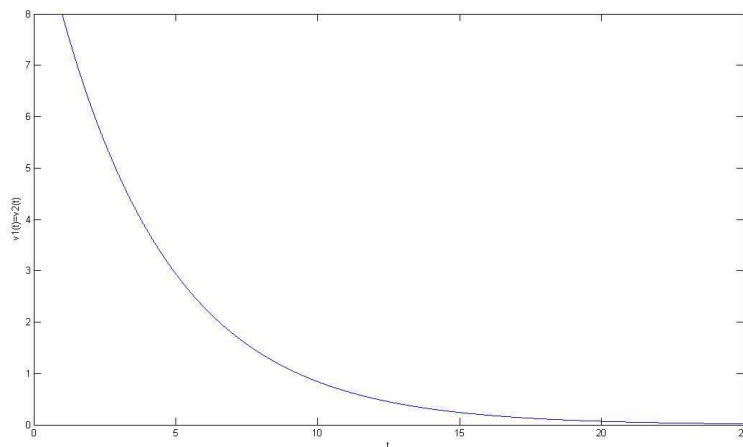

Solution 23

(a)

From the pole-zero diagram,

$$\begin{aligned}H(s) &= \frac{K(s^2 - 16)}{(s + 2)(s^2 + 16)} \\H(0) &= -10 \\ \Rightarrow K &= 20\end{aligned}$$

(b)

Impulse response is found using ¹`ilaplace` command in MATLAB,

$$h(t) = [32 \cos(4t) - 12e^{-2t} - 16 \sin(4t)]u(t)$$

(c)

$$\begin{aligned}\text{Step response} &= L^{-1}[H(s)/s] \\ &= [4 \cos(4t) + 6e^{-2t} + 8 \sin(4t) - 10]u(t)\end{aligned}$$

(d)

$$V_{zs} = \frac{200(s^2 - 16)}{(s + a)(s + 2)(s^2 + 16)}$$

To get rid of the term of the form $Ke^{-at}u(t)$ in $v_{zs}(t)$, we should get rid of the term $K/(s + a)$ in the partial fraction expansion of V_{zs} . Also, $a > 0$, so by seeing the form of V_{zs} , this is possible if $a=4$. Thus V_{zs} becomes,

$$\begin{aligned}V_{zs} &= \frac{200(s - 4)}{(s + 2)(s^2 + 16)} \\ \Rightarrow v_{zs}(t) &= [60 \cos(4t) - 60e^{-2t} + 20 \sin(4t)]u(t)\end{aligned}$$

Solution 24

(a)

The following s-domain equations can be written,

$$\begin{aligned}\frac{V_{in} - V_{out}}{R} + g_m V_{out} &= V_{out}(Cs) \\ \Rightarrow H(s) = \frac{V_{out}(s)}{V_{in}(s)} &= \frac{1}{1 + R(Cs - g_m)} \\ &= \frac{1}{s - (4g_m - 1)}\end{aligned}$$

¹Note that we will be using 'ilaplace' frequently whenever calculating inverse laplace transform

For BIBO stability, poles should be in the left half plane, which is possible if $g_m < 0.25$.

(b)

The following s-domain equations can be written,

$$\begin{aligned}\frac{V_{in} - V_{out}}{4} &= (V_{out} - r_m V_{out}) \frac{s}{4} \\ \Rightarrow H(s) = \frac{V_{out}(s)}{V_{in}(s)} &= \frac{1}{1 + s(1 - r_m)} \\ &= \frac{1/(1 - r_m)}{s + 1/(1 - r_m)}\end{aligned}$$

For BIBO stability, poles should be in the left half plane, which is possible if $r_m < 1$.