

# ECE 202 - Linear Circuit Analysis II

Purdue University, Spring 2009

## Homework Set 3 Solutions

### Solution 25 & 26


(a)

In steady state the capacitor is open circuit and the inductor is short circuit. Thus,

$$\begin{aligned} i_L(0^-) &= \frac{-25}{10+15} = -1 \text{ A} \\ v_C(0^-) &= -25 + 10 = -15 \text{ V} \end{aligned}$$

(b)

For  $t > 0$ , the circuit looks like,

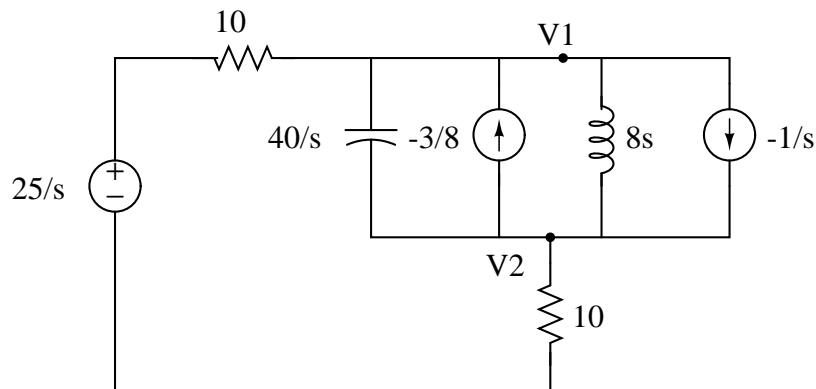

$$\begin{aligned} \frac{1}{10} \left( \frac{25}{s} - V_1 \right) - \frac{3}{8} &= (V_1 - V_2) \left( \frac{s}{40} + \frac{1}{8s} \right) - \frac{1}{s} \\ \frac{1}{10} \left( \frac{25}{s} - V_1 \right) &= \frac{V_2}{10} \end{aligned}$$

Rearranging and simplifying, we get the following matrix equation,

$$\begin{pmatrix} \frac{s}{40} + \frac{1}{8s} + \frac{1}{10} & -\left(\frac{s}{40} + \frac{1}{8s}\right) \\ 1 & 1 \end{pmatrix} \begin{pmatrix} V_1 \\ V_2 \end{pmatrix} = \begin{pmatrix} \frac{3.5}{s} - \frac{3}{8} \\ \frac{25}{s} \end{pmatrix}$$


Solving using cramer's rule,

$$\begin{aligned} V_1 &= \frac{5(2s^2 + 28s + 25)}{2s(s^2 + 2s + 5)} \\ V_2 &= \frac{5(8s^2 - 8s + 25)}{2s(s^2 + 2s + 5)} \\ \Rightarrow V_C &= V_1 - V_2 \\ &= \frac{15(6-s)}{s^2 + 2s + 5} \end{aligned}$$

$$\begin{aligned} \Rightarrow v_C(t) &= -15e^{-t}[\cos(2t) + 3.5\sin(2t)]u(t), t > 0 \\ I_L &= \frac{V_1 - V_2}{8s} - \frac{1}{s} \\ &= \frac{-(8s^2 + 31s - 50)}{8s^3 + 16s^2 + 40s} \\ \Rightarrow i_L(t) &= \frac{5}{4} - \frac{9}{4}e^{-t} \left[ \cos(2t) + \frac{11}{12}\sin(2t) \right] u(t), t > 0 \end{aligned}$$

(c)

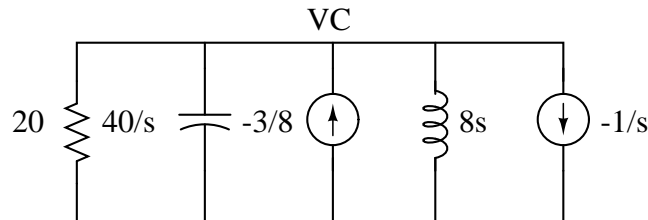
The circuit only due to initial conditions is drawn below,



$$\begin{aligned} V_{C_{zi}} &= \left( \frac{1}{s} - \frac{3}{8} \right) \left( 20 \parallel 8s \parallel \frac{40}{s} \right) \\ &= \frac{40 - 15s}{s^2 + 2s + 5} \\ \Rightarrow v_{C_{zi}}(t) &= -15e^{-t} \left[ \cos(2t) - \frac{11}{6}\sin(2t) \right] u(t) \\ \Rightarrow v_{out_{zi}}(t) &= \frac{v_{C_{zi}}(t)}{2} \\ &= \frac{-15}{2}e^{-t} \left[ \cos(2t) - \frac{11}{6}\sin(2t) \right] u(t) \end{aligned}$$

(d)

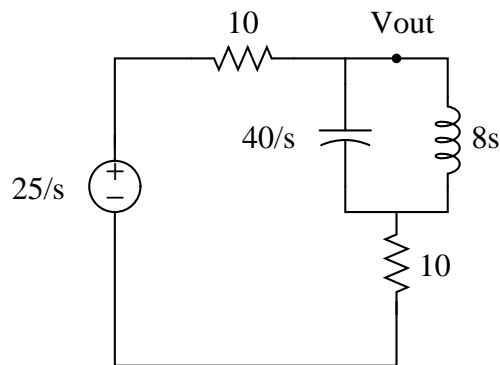The circuit with zero initial conditions is drawn below,



$$\begin{aligned} I &= \frac{25}{s} \left( \frac{40s}{s^2 + 5} + 20 \right)^{-1} \\ V_{out_{zs}} &= \frac{25}{s} - 10I \\ &= \frac{25s^2 + 100s + 125}{2s^3 + 4s^2 + 10s} \end{aligned}$$

$$\Rightarrow v_{out_{zs}}(t) = 12.5[1 + e^{-t} \sin(2t)]u(t)$$

(e)

$$\begin{aligned} v_{out_{complete}}(t) &= v_{out_{zs}}(t) + v_{out_{zi}}(t) \\ &= 12.5 + e^{-t}[26.25 \sin(2t) - 7.5 \cos(2t)]u(t) \\ \Rightarrow v_{out_{ss}}(t) &= 12.5 \\ v_{out_{tr}}(t) &= e^{-t}[26.25 \sin(2t) - 7.5 \cos(2t)]u(t) \end{aligned}$$

## Solution 27

(a)

$$\begin{aligned} H(j4) &= \frac{64j + 96}{32j + 48} \\ &= 2 \angle 0^\circ \\ \Rightarrow v_{out}(t) &= 8 \cos(4t + 45^\circ) \end{aligned}$$

(b)

Clearly,  $\omega = 3$ .

$$\begin{aligned} H(j3) &= \frac{4\sqrt{5}(-9 - 4)}{11 + 12j} \\ &= 7.1427 \angle 132.5103^\circ \\ \Rightarrow K &= \frac{25}{7.1427} = 3.5 \\ \theta &= 100 - 132.5103 = -32.5103^\circ \\ \Rightarrow v_{in}(t) &= 3.5 \cos(3t - 32.5103^\circ) \end{aligned}$$

(c)

$$\begin{aligned} H(s) = Z_{in}(s) &= (R_1 + Ls) \parallel \left( R_2 + \frac{1}{Cs} \right) \\ &= (15 + s) \parallel \left( 5 + \frac{100}{s} \right) \\ &= \frac{5(s^2 + 35s + 300)}{s^2 + 20s + 100} \\ \Rightarrow H(j10) &= 10.0778 \angle -29.7422^\circ \\ \Rightarrow v_{out}(t) &= 1007.78 \cos(10t - 29.7422^\circ) \end{aligned}$$

## Solution 28

$$Z_1 = R_1 \parallel \frac{1}{C_1 s} = \frac{R_1}{R_1 C_1 s + 1}$$

$$\begin{aligned}
Z_2 = R_2 \parallel \frac{1}{C_2 s} &= \frac{R_2}{R_2 C_2 s + 1} \\
H(s) = -\frac{Z_2}{Z_1} &= -\frac{R_2}{R_1} \left( \frac{R_1 C_1 s + 1}{R_2 C_2 s + 1} \right) \\
&= -\frac{C_1}{C_2} \left( \frac{s + 1/R_1 C_1}{s + 1/R_2 C_2} \right) \\
&= \frac{-5(s + 0.2)}{s + 4} \\
C_2 &= 1 \text{ F} \\
\Rightarrow C_1 &= 5 \text{ F} \\
R_1 &= 1 \text{ } \Omega \\
R_2 &= 0.25 \text{ } \Omega
\end{aligned}$$

(a)

$$\begin{aligned}
H(j\omega) &= \frac{-5(j\omega + 0.2)}{j\omega + 4} \\
&= \frac{-5(0.2 + j\omega)(4 - j\omega)}{16 + \omega^2} \\
&= \frac{-5(\omega^2 + 0.8 + 3.8j\omega)}{16 + \omega^2} \\
&= \rho e^{j\phi + \pi} \\
\rho &= \frac{5\sqrt{\omega^4 + 16.04\omega^2 + 0.64}}{\omega^2 + 16} \\
\phi &= \tan^{-1} \left( \frac{3.8\omega}{\omega^2 + 0.8} \right) \\
v_{in}(t) &= 2 \cos(\omega t + \frac{\pi}{2}) u(t) \\
\Rightarrow v_{out}(t) &= 2\rho \cos(\omega t + \frac{3\pi}{2} + \phi) = K \cos(\omega t + \theta) \\
\Rightarrow K &= 2\rho \\
\theta &= \frac{3\pi}{2} + \phi
\end{aligned}$$

(b)

$$\begin{aligned}
V_{in} &= \frac{2\omega}{\omega^2 + s^2} \\
V_{out} = V_{in} H(s) &= \frac{-10\omega(s + 0.2)}{(s^2 + \omega^2)(s + 4)} \\
&= \frac{A}{s + 4} + \frac{Bs + C}{s^2 + \omega^2}
\end{aligned}$$

If we solve the above partial fraction expansion,

$$\begin{aligned}
A &= \frac{38\omega}{\omega^2 + 16} \\
B &= \frac{-38\omega}{\omega^2 + 16} \\
C &= \frac{-10\omega^3 - 8\omega}{\omega^2 + 16}
\end{aligned}$$

Employing the well known expression,

$$\begin{aligned} -a \cos(\omega t) - b \sin(\omega t) &= \sqrt{a^2 + b^2} \sin(\omega t + \pi + \Theta), \quad a, b > 0 \\ &= \sqrt{a^2 + b^2} \cos\left(\omega t + \frac{3\pi}{2} + \Theta\right) \\ \Theta &= \tan^{-1}\left(\frac{a}{b}\right) \end{aligned}$$

We can get after taking inverse laplace transform,

$$v_{out}(t) = Ae^{-4t} + B \cos(\omega t) + \frac{C}{\omega} \sin(\omega t)$$

Clearly,

$$\begin{aligned} v_{out_{tr}}(t) &= Ae^{-4t} \\ &= \frac{38\omega}{\omega^2 + 16} e^{-4t} \\ v_{out_{ss}}(t) &= K \cos(\omega t + \theta) \\ K &= \sqrt{B^2 + (C/\omega)^2} \\ \theta &= \frac{3\pi}{2} + \tan^{-1}(B\omega/C) \end{aligned}$$

**(c)**

Clearly, steady state value part (a) and steady state part of (b) coincide.