

Consider the circuit below. Find:

- The filter type
- The value of the maximum voltage gain
- The 3-dB bandwidth

