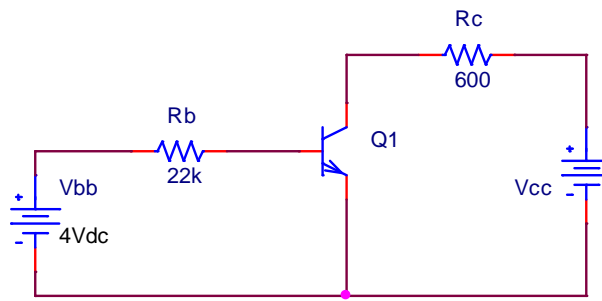


COURSE WEBSITE: <http://cobweb.ecn.purdue.edu/~ee255/>

- 1) Text problem 5.86, page 270. Assume $V_{BE} = V_0 = 0.7 \text{ V}$.
- 2) Text problem 5.87, page 270. Assume $V_{BE} = V_0 = 0.7 \text{ V}$.
- 3) Text problem 5.91, page 270. Assume $V_{BE} = V_0 = 0.7 \text{ V}$.
- 4) The transistor in the circuit shown below is modeled by $V_0 = 0.7 \text{ V}$, $\beta_{dc} = 100$, $I_{CE0} = 5 \mu\text{A}$, and $R_{sat} = 60 \Omega$. If $V_{BB} = 4 \text{ V}$, $R_B = 22 \text{ k}\Omega$, and $R_C = 600 \Omega$, find I_C and V_{CE} if V_{CC} is:

(a) 12 V

(b) 6 V



- 5) An *npn* transistor is modeled in its active region by $\beta_{dc} = 75$, $V_0 = 0.6 \text{ V}$, and $I_{CE0} = 1 \mu\text{A}$. A $1 \text{ k}\Omega$ resistor and a 9 V dc source are connected in series between the base and collector (positive source terminal to collector), and a 500Ω resistor and a 3 V dc source in series are connected between the base and emitter (negative source terminal to emitter). Find I_B , I_C , I_E , V_{BE} , and V_{CE} .
- 6) A *pnp* transistor is described by $V_0 = \frac{2}{3} \text{ V}$, $I_{CE0} = 3 \mu\text{A}$, and $\beta_{dc} = 80$. Design a circuit (using a single power supply) that will give an operating point of $|I_C| = 6 \text{ mA}$ and $|V_{CE}| = 6 \text{ V}$.
- 7) Text problem 13.49, page 742. Note: use $\frac{q}{kT} = 38.92 \text{ V}^{-1}$
- 8) Text problem 13.50, page 742. Assume an ideality constant of unity and $T = 25^\circ\text{C}$. (Note $r_o \equiv r_d$ and $V_A \gg V_{CE}$)
- 9) Text problem 13.54 (part 1), page 742. Assume an ideality constant of unity and $T = 25^\circ\text{C}$. Determine $\beta_F = \beta_{dc} \approx \beta_0$ and V_A using the values from the table.
- 10) Text problem 13.54 (part 2), page 742. Fill in the table. (Note the intrinsic voltage gain $\mu_f = g_m \times r_o$)