

Homework 1 Solutions

Problem 1 (Text 2.12)

- (a) A voltage of 5 V is applied across a 10
- μm
- long region of silicon.

What is the electric field? $|E| = \frac{\text{Voltage}}{\text{Distance}} = \frac{5\text{ V}}{10\mu\text{m}} = 5000 \frac{\text{V}}{\text{cm}}$

- (b) Suppose the maximum field allowed in silicon is
- 10^5 V/cm
- . How large a voltage can be applied to a 10
- μm
- long region of silicon?
- $V = |E| \times \text{Distance} = \left(10^5 \frac{\text{V}}{\text{cm}}\right)(10\mu\text{m}) = 100 \text{ V}$

Problem 2 (Text 2.27)

Silicon is doped with 6×10^{18} boron atoms/ cm^3 .

- (a) Is this
- n
- or
- p
- type silicon? Since boron is in group III of the periodic table, it is an acceptor
- $\Rightarrow N_A = 6 \times 10^{18}/\text{cm}^3$

Assume $N_D = 0$, since it is not specified. Therefore, the material is p -type.

- (b) What are the electron and hole concentrations at room temperature?

At room temperature, $n_i \approx 10^{10} / \text{cm}^3$ (text page 47) and $N_A = 6 \times 10^{18}/\text{cm}^3 \gg n_i$

Therefore, $p \approx 6 \times 10^{18}/\text{cm}^3$ and $n \approx \frac{n_i^2}{p} = \frac{10^{20}/\text{cm}^6}{6 \times 10^{18}/\text{cm}^3} = 16.7/\text{cm}^3$

- (c) What are the electron and hole concentrations at 200°K?

At 200°K, $n_i^2 = BT^3 e^{\frac{-E_G}{kT}} = 1.08 \times 10^{31} (200)^3 e^{\left(\frac{-1.12}{8.62 \times 10^{-5}(200)}\right)} = 5.28 \times 10^9 / \text{cm}^6$

Therefore, $p \approx 6 \times 10^{18}/\text{cm}^3$ and $n \approx \frac{n_i^2}{p} = \frac{5.28 \times 10^9 / \text{cm}^6}{6 \times 10^{18}/\text{cm}^3} = 8.80 \times 10^{-10} / \text{cm}^3$

Problem 3 (Text 2.30)

Silicon is doped with 5×10^{17} boron atoms/ cm^3 and 2×10^{17} phosphorus atoms/ cm^3 .

- (a) Is this
- n
- or
- p
- type silicon? Boron is in group III and therefore an acceptor, while phosphorus is in group V and therefore a donor.
- $N_A = 5 \times 10^{17}/\text{cm}^3$
- and
- $N_D = 2 \times 10^{17}/\text{cm}^3$
-
- Since
- $N_A > N_D$
- , the material is
- p
- type.

- (b) What are the electron and hole concentrations at room temperature?

At room temperature, $n_i \approx 10^{10} / \text{cm}^3$ and $N_A - N_D = 3 \times 10^{17} / \text{cm}^3 \gg 2n_i$

Consequently, $p \approx 3 \times 10^{17} / \text{cm}^3$ and $n = \frac{n_i^2}{p} = \frac{10^{20} / \text{cm}^6}{3 \times 10^{17} / \text{cm}^3} = 333 / \text{cm}^3$


Problem 4 (Text 3.21)

What are the values of I_S and n for the diode in the graph below? Assume $V_T = 0.025$ V.

Since $I_D = I_S \left[e^{\left(\frac{V_D}{nV_T}\right)} - 1 \right]$, pick two points; then

you will have two equations in two unknowns.

The simultaneous solution to the two equations yields $n = 1.39$ and $I_S = 3.17 \times 10^{-12}$ A = 3.17 pA.

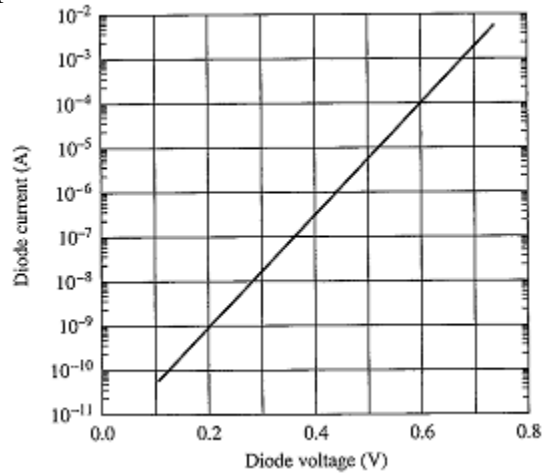

Problem 5

Based on the information in plot above, develop a D.C. diode model which will be exact at 100 μ A and very accurate in the neighborhood of 100 μ A. Show your method of solution (including calculations) and the resulting values for V_0 and R_0 .

The slope at 100 μ A is $\left. \frac{dI_D}{dV_D} \right|_Q = \left(\frac{1}{nV_T} \right) I_S e^{\left(\frac{V_D}{nV_T}\right)} = \left(\frac{1}{nV_T} \right) (I_D + I_S) \approx \frac{1}{1.39 \times 0.025 \text{ V}} (100 \mu\text{A})$

Therefore, $R_0 = \frac{34.75 \text{ mV}}{100 \mu\text{A}} = 348 \Omega$ and

$V_D = R_0 I_D + V_0 = 0.60 \text{ V} = 348 \Omega \times 0.1 \text{ mA} + V_0 \Rightarrow V_0 = 0.565 \text{ V}$

Problem 6 (Text 3.52)


A pn diode has a resistivity 2 Ω -cm on the p -type side and 0.01 Ω -cm on the n -type side. What is the value of R_S for the diode if the cross-sectional area of the diode is 0.01 cm^2 and the length of the p - and n - sides of the diode are each 250 μm ?

The series resistance R_S is the sum of the bulk resistance on the n -side, R_n , and p -side, R_p , of the junction. $R_n = \rho_n \frac{L_n}{A_n} = (0.01 \Omega\text{-cm}) \frac{0.025 \text{ cm}}{0.01 \text{ cm}^2} = 0.025 \Omega$ and

$R_p = \rho_p \frac{L_p}{A_p} = (2 \Omega\text{-cm}) \frac{0.025 \text{ cm}}{0.01 \text{ cm}^2} = 5.0 \Omega$ Therefore, $R_S = R_p + R_n = 5.03 \Omega$

Problem 7 (Text 3.56)

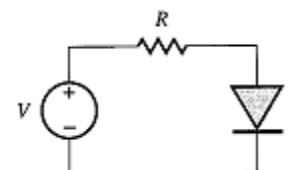
- (a) Plot the load line and find the Q -point for the diode circuit shown if $V = 5$ V and $R = 10$ k Ω . Use the i - v characteristic in Figure P3.41.



From KVL, $5 \text{ V} = (10 \text{ k}\Omega) I_D + V_D$
 Load line axis intercepts are: $V_D = 0, I_D = 0.5 \text{ mA}$
 and $V_D = 5 \text{ V}, I_D = 0$

$$Q: \{V_D = 0.5 \text{ V}, I_D = 0.45 \text{ mA}\}$$

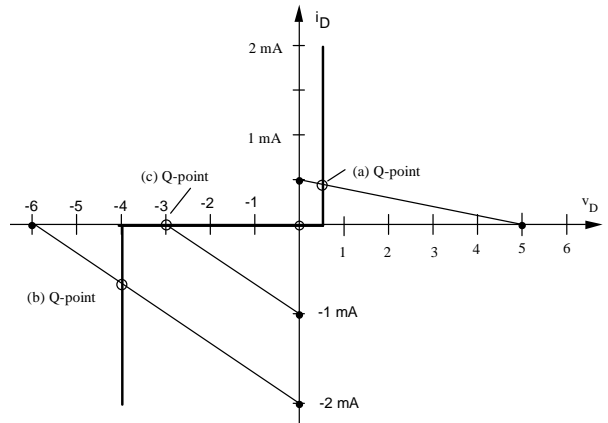- (b) Repeat for $V = -6 \text{ V}$ and $R = 3 \text{ k}\Omega$
 $Q: \{V_D = -4 \text{ V}, I_D = -0.667 \text{ mA}\}$
- (c) Repeat for $V = -3 \text{ V}$ and $R = 3 \text{ k}\Omega$
 $Q: \{V_D = -3 \text{ V}, I_D = 0 \text{ mA}\}$





Problem 8 (Text 3.66)

Find the Q -point for the diode in the circuit shown using:

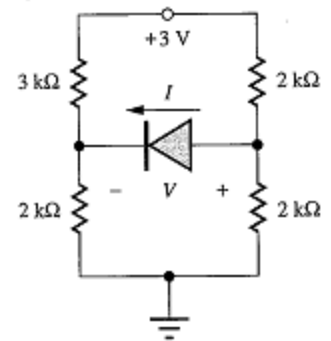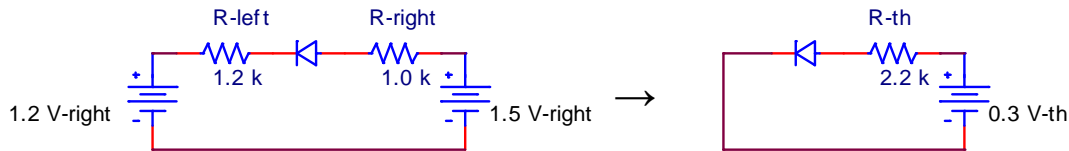- (a) the ideal diode

The diode is clearly forward biased and therefore is modeled as a short circuit.

Using Thévenin equivalent circuits we can redraw the circuit as:



Therefore, $Q: \{V_D = 0, I_D = 0.136 \text{ mA}\}$

- (b) the constant voltage model with $V_{on} = 0.6 \text{ V}$.

If we simply plug in the constant voltage model with $V_{on} = 0.6 \text{ V}$, we find that $I_D = -0.136 \text{ mA}$ which is inconsistent with our assumption that the diode is “on”. Thus the diode model must be “off”.

Consequently, $Q: \{V_D = 0.3 \text{ V}, I_D = 0\}$

- (c) Which answer do you feel is most correct? Neither are very good!

The second estimate is a bit better since 0.3 V is not sufficient to forward bias the diode into significant conduction.

Problem 9 (Text 3.69)

- (a) Find I and V in the four circuits shown using the ideal diode model.


- (a) Diode forward biased, $Q: \{V_D = 0 \text{ V}, I_D = ?\}$

$$I_D = \frac{10 \text{ V}}{16 \text{ k}\Omega} = .625 \text{ mA} \quad \therefore \quad V = 3 \text{ V} \quad \text{and} \quad I = 0.625 \text{ mA}$$

- (b) Diode forward biased $\therefore \quad V = -5 \text{ V} \quad \text{and} \quad I = 0.625 \text{ mA}$

- (c) Diode reverse biased $\therefore \quad V = -5 \text{ V} \quad \text{and} \quad I = 0$

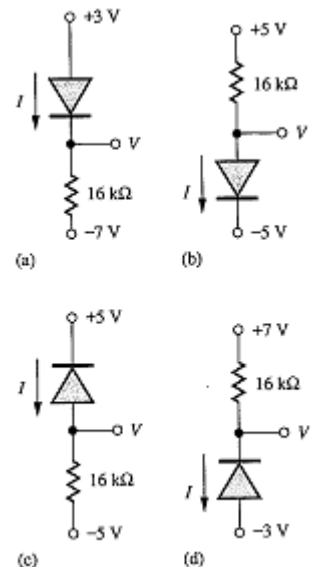- (d) Diode reverse biased $\therefore \quad V = 7 \text{ V} \quad \text{and} \quad I = 0$



(b) Repeat using the constant voltage model with $V_{on} = 0.7 \text{ V}$.

- (a) Diode forward biased, so $I_D = \frac{(10-0.7)\text{V}}{16\text{k}\Omega} = .581\text{mA}$
 $\therefore V = 2.3 \text{ V}$ and $I = 0.581 \text{ mA}$
 (b) Diode forward biased $\therefore V = -4.3 \text{ V}$ and $I = 0.581 \text{ mA}$
 (c) Diode reverse biased $\therefore V = -5 \text{ V}$ and $I = 0$
 (d) Diode reverse biased $\therefore V = 7 \text{ V}$ and $I = 0$

Problem 10

Continue the previous using a diode model with $V_0 = 0.6 \text{ V}$ and $R_0 = 200 \Omega$.

- (a) Diode forward biased, $Q: \{V_D = ?, I_D = ?\}$

$$I_D = \frac{(10-0.6)\text{V}}{(16+0.2)\text{k}\Omega} = 0.580\text{mA}$$

$$\text{and } V_D = 0.6 \text{ V} + 200\Omega \times I_D = 0.716 \text{ V}$$

$$\text{so } Q: \{V_D = 0.716 \text{ V}, I_D = 0.580 \text{ mA}\}$$

$$\text{Therefore: } V = 2.284 \text{ V} \quad \text{and} \quad I = 0.580 \text{ mA}$$

- (b) Diode forward biased $\therefore V = -4.284 \text{ V}$ and $I = 0.580 \text{ mA}$
 (c) Diode reverse biased $\therefore V = -5 \text{ V}$ and $I = 0$
 (d) Diode forward biased $\therefore V = 7 \text{ V}$ and $I = 0$

