

Problem 1 (Text 3.71)Find the Q -points for the diodes in the four circuits shown using:

(a) The ideal diode model

(a) Both diodes are forward biased

$$I_{D2} = \frac{[0 - (-9)] \text{ V}}{22 \text{ k}\Omega} = 409 \mu\text{A}$$

$$I_{D1} = 409 \mu\text{A} - \frac{(6 - 0) \text{ V}}{43 \text{ k}\Omega} = 270 \mu\text{A}$$

$$\Rightarrow Q_{D1}: \{V_{D1} = 0, I_{D1} = 270 \mu\text{A}\} \quad \text{and} \quad Q_{D2}: \{V_{D2} = 0, I_{D2} = 409 \mu\text{A}\}$$

(b) Diode D_1 is forward biased and diode D_2 is reverse biased

$$I_{D1} = \frac{(6 - 0) \text{ V}}{43 \text{ k}\Omega} = 140 \mu\text{A} \quad \text{and} \quad V_{D2} = -9 \text{ V}$$

$$\Rightarrow Q_{D1}: \{V_{D1} = 0, I_{D1} = 140 \mu\text{A}\} \quad \text{and} \quad Q_{D2}: \{V_{D2} = -9 \text{ V}, I_{D2} = 0\}$$

(c) Diode D_1 is reverse biased and diode D_2 is forward biased

$$I_{D2} = \frac{[6 - (-9)] \text{ V}}{65 \text{ k}\Omega} = 231 \mu\text{A} \quad \text{and} \quad V_{D1} = 6 \text{ V} - 43 \text{ k}\Omega \times I_{D2} = -3.92 \text{ V}$$

$$\Rightarrow Q_{D1}: \{V_{D1} = -3.92 \text{ V}, I_{D1} = 0\} \quad \text{and} \quad Q_{D2}: \{V_{D2} = 0, I_{D2} = 231 \mu\text{A}\}$$

(d) Both diodes are forward biased

$$I_{D2} = \frac{[0 - (-6)] \text{ V}}{43 \text{ k}\Omega} = 140 \mu\text{A}$$

$$I_{D1} = \frac{(9 - 0) \text{ V}}{22 \text{ k}\Omega} - 140 \mu\text{A} = 270 \mu\text{A}$$

$$\Rightarrow Q_{D1}: \{V_{D1} = 0, I_{D1} = 270 \mu\text{A}\} \quad \text{and} \quad Q_{D2}: \{V_{D2} = 0, I_{D2} = 140 \mu\text{A}\}$$

(b) The constant voltage drop model with $V_{on} = .75 \text{ V}$

(a) Both diodes are forward biased

$$I_{D2} = \frac{[-.75 - .75 - (-9)] \text{ V}}{22 \text{ k}\Omega} = 341 \mu\text{A}$$


$$I_{D1} = 341 \mu\text{A} - \frac{6 - (-.75) \text{ V}}{43 \text{ k}\Omega} = 184 \mu\text{A}$$

$$\Rightarrow Q_{D1}: \{V_{D1} = .75 \text{ V}, I_{D1} = 184 \mu\text{A}\} \quad \text{and} \quad Q_{D2}: \{V_{D2} = .75 \text{ V}, I_{D2} = 341 \mu\text{A}\}$$

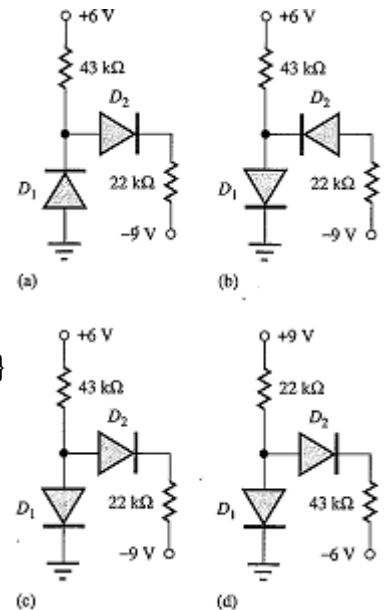(b) Diode D_1 is forward biased and diode D_2 is reverse biased

$$I_{D1} = \frac{(6 - .75) \text{ V}}{43 \text{ k}\Omega} = 122 \mu\text{A} \quad \text{and} \quad V_{D2} = -9 - .75 = -9.75 \text{ V}$$

$$\Rightarrow Q_{D1}: \{V_{D1} = .75 \text{ V}, I_{D1} = 122 \mu\text{A}\} \quad \text{and} \quad Q_{D2}: \{V_{D2} = -9.75 \text{ V}, I_{D2} = 0\}$$



(c) Diode D_1 is reverse biased and diode D_2 is forward biased

$$I_{D2} = \frac{[6 - .75 - (-9)]V}{65k\Omega} = 219\mu A \quad \text{and} \quad V_{D1} = 6V - 43k\Omega \times I_{D2} = -3.43V$$

$$\Rightarrow Q_{D1}: \{V_{D1} = -3.43V, I_{D1} = 0\} \quad \text{and} \quad Q_{D2}: \{V_{D2} = .75V, I_{D2} = 219\mu A\}$$

(d) Both diodes are forward biased

$$I_{D2} = \frac{[.75 - .75 - (-6)]V}{43k\Omega} = 140\mu A$$

$$I_{D1} = \frac{(9 - .75)V}{22k\Omega} - 140\mu A = 235\mu A$$

$$\Rightarrow Q_{D1}: \{V_{D1} = .75V, I_{D1} = 235\mu A\} \quad \text{and} \quad Q_{D2}: \{V_{D2} = .75V, I_{D2} = 140\mu A\}$$

Problem 2 (Text 3.71 cont.)

(c) A diode model containing an ideal diode, a voltage source, $V_0 = .65V$, and resistor, $R_0 = 200\Omega$.

(a) Assume both diodes are forward biased

Define the voltage at the junction of the two diodes as V_X

$$\frac{6V - V_X}{43k\Omega} = \frac{V_X + .65V}{200\Omega} + \frac{V_X - .65V - (-9V)}{22k\Omega + 200\Omega} \Rightarrow V_X = -688mV$$

$$I_{D1} = \frac{0 - .65V - V_X}{200\Omega} = 190\mu A$$

$$I_{D2} = \frac{V_X - .65V - (-9V)}{22k\Omega + 200\Omega} = \frac{7.662V}{22.2k\Omega} = 345\mu A$$

$$V_{D2} = .65V + 200\Omega \times I_{D2} = 719mV$$

The results of the calculations are consistent with our initial assumptions regarding the regions of operation; therefore,

$$\Rightarrow Q_{D1}: \{V_{D1} = .688V, I_{D1} = 190\mu A\} \quad \text{and} \quad Q_{D2}: \{V_{D2} = .719V, I_{D2} = 345\mu A\}$$

(b) Assume diode D_1 is forward biased and diode D_2 is reverse biased

$$I_{D1} = \frac{(6 - .65)V}{43k\Omega + 200\Omega} = 124\mu A \quad \text{and} \quad V_{D1} = .65V + 200\Omega \times I_{D1} = 675mV$$

$$\Rightarrow Q_{D1}: \{V_{D1} = .675V, I_{D1} = 124\mu A\} \quad \text{and} \quad Q_{D2}: \{V_{D2} = -9.68V, I_{D2} = 0\}$$

(c) Assume diode D_1 is reverse biased and diode D_2 is forward biased

$$I_{D2} = \frac{[6 - .65 - (-9)]V}{[43k + 200 + 22k]\Omega} = \frac{14.35V}{65.2k\Omega} = 220\mu A$$


$$V_{D2} = .65V + 200\Omega \times I_{D2} = 694mV$$

$$V_{D1} = 6V - 43k\Omega \times I_{D2} = -3.46V$$

$$\Rightarrow Q_{D1}: \{V_{D1} = -3.46V, I_{D1} = 0\} \quad \text{and} \quad Q_{D2}: \{V_{D2} = .694V, I_{D2} = 220\mu A\}$$

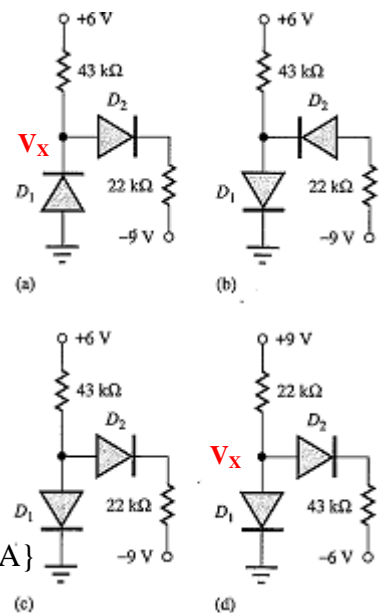(d) Assume both diodes are forward biased

Define the voltage at the junction of the two diodes as V_X



$$\frac{9V - V_X}{22k\Omega} = \frac{V_X - .65V}{200\Omega} + \frac{V_X - .65V - (-6V)}{43k\Omega + 200\Omega} \Rightarrow V_X = 697.5mV$$

$$I_{D1} = \frac{V_X - .65V}{200\Omega} = 237\mu A$$

$$I_{D2} = \frac{V_X - .65V - (-6V)}{43k\Omega + 200\Omega} = \frac{6.0475V}{43.2k\Omega} = 140\mu A$$


$$V_{D2} = .65V + 200\Omega \times I_{D2} = 678mV$$

The results of the calculations are consistent with our initial assumptions regarding the regions of operation; therefore,


$$\Rightarrow Q_{D1}: \{V_{D1} = .698V, I_{D1} = 237\mu A\} \text{ and } Q_{D2}: \{V_{D2} = .678V, I_{D2} = 140\mu A\}$$

Problem 3


Using a Zener diode with $|V_{BR}| = V_Z = 15V$ and $R_Z = 25\Omega$ in the simple voltage regulator shown below, having $V_{CC} = 30V$, calculate the load voltage, V_{Load} , when

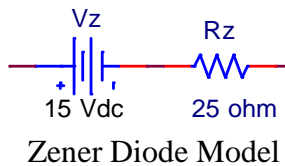

$V_{CC} = 30\text{ Volts}$

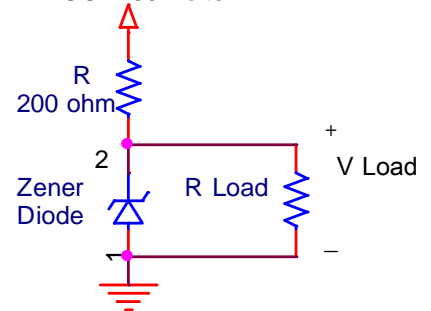

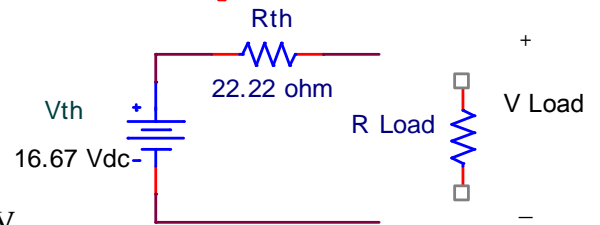Construct the Thévenin equivalent circuit



- (a) $I_{Load} = 0$ $V_{Load} = V_{OC} = V_{TH} = 16.67V$
- (b) $I_{Load} = 1\text{ mA}$ $V_{Load} = 16.67 - 22.22(0.001) = 16.65V$
- (c) $I_{Load} = 10\text{ mA}$ $V_{Load} = 16.67 - 22.22(0.010) = 16.45V$
- (d) $I_{Load} = 70\text{ mA}$ $V_{Load} = 16.67 - 22.22(0.070) = 15.11V$

- (e) What is the maximum possible current that can be drawn by the load before the Zener diode stops providing any regulation?

When the output voltage drops to 15 Volts, no current will be flowing through the Zener diode. If more current is drawn the Zener diode will appear to be an open circuit.

$$V_{Load} = 16.67 - 22.22(I_{max}) = 15.00V \rightarrow I_{max} = 75\text{ mA}$$

- (f) If the 30 V supply, V_{CC} , has a ripple, $\Delta V_{CC} = 0.1V$, what is the ripple seen at the load when 50 mA is being drawn?

When $I_{Load} = 50 \text{ mA}$, $V_{Load} = 16.67 - 22.22(0.050) = 15.56 \text{ V}$
 Therefore $R_{Load} = 15.56/0.05 = 311 \Omega$

$$\Delta v_{Load} = \frac{R_Z \parallel R_{Load}}{R_Z \parallel R_{Load} + R} \times \Delta v_{CC} = \frac{25 \parallel 311}{25 \parallel 311 + 200} \times 0.1 = \frac{23.14}{223.14} \times 0.1 = 0.104 \times 0.1 = 0.01 \text{ V}$$

Problem 4 (Text 3.91)

The half-wave rectifier shown below is operating at a frequency of 60 Hz, and the rms value of the transformer voltage is 6.3 V.

- (a) What is the value of the dc output voltage, V_O , if the diode voltage drop is 1 V and assuming that $R = \infty$?

$$V_{dc} = -(V_P - V_0) = -(6.3\sqrt{2} - 1.0) \text{ V} = -7.91 \text{ V}$$

- (b) What is the minimum value of C required to ensure that the ripple voltage is less than 0.25 V if $R = 50 \Omega$?

$$V_r \approx \frac{V_{max} \times T}{R \times C} \Rightarrow C \approx \frac{7.91}{.25 \times 50 \times 60} = 10.5 \text{ mF}$$

- (c) What is the *minimum* PIV rating of the diode in this circuit?

$$PIV \geq 2 \times V_P - V_D = 2 \times 6.3\sqrt{2} - 1 = 16.82 \text{ V}$$

- (d) What is the surge current when the power is first applied?

$$I_{surge} = \omega \times C \times V_P = 2\pi \times 0.0105 \times 6.3\sqrt{2} = 35.3 \text{ A}$$

- (e) What is the *peak* amplitude of the repetitive current in the diode?


During the time interval ΔT the output voltage rises from $(V_{max} - V_r)$ to (V_{max})

$$V_P \cos(-\omega \Delta T) = V_P - V_r \text{ expanding } \cos(x) = 1 - \frac{x^2}{2!} + \dots \text{ yields } \frac{(\omega \Delta T)^2}{2} = \frac{V_r}{V_P}$$

$$\Delta T = \frac{1}{\omega} \sqrt{\frac{2V_r}{V_P}} = \frac{1}{2\pi \times 60} \sqrt{\frac{2 \times 0.25}{6.3\sqrt{2}}} = 0.628 \text{ ms}$$


$$I_P \approx I_{dc} \frac{2T}{\Delta T} \text{ where } I_{dc} = \frac{V_P - V_{on} - 0.5V_r}{R} = \frac{7.91 - 1.25}{50} = 158 \text{ mA}$$
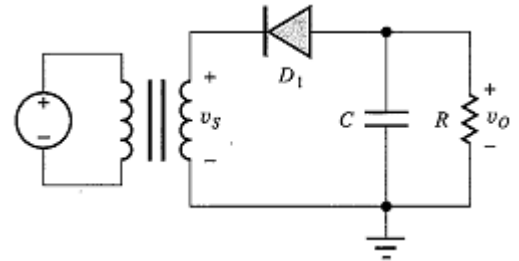
$$\text{Therefore } I_P = .158 \times \frac{2k}{60 \times .628} = 8.28 \text{ A}$$



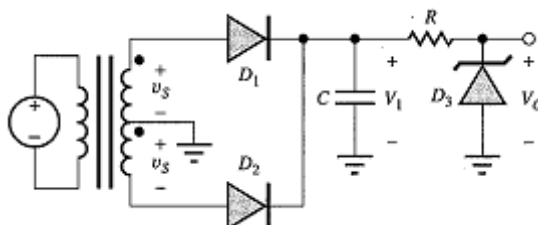Problem 5 (Text 3.95)

For the Zener regulated power supply shown below the rms value of v_s is 15 V, the operating frequency is 60 Hz, $R = 100 \Omega$, $C = 1000 \mu\text{F}$, the on-voltage of diodes D_1 and D_2 is .75 V, and the Zener voltage of diode D_3 is 15 V.



(a) What is the type of rectifier used in this power supply circuit?

Full-wave rectifier.

(b) What is the dc voltage V_1 ?

$$V_{1(\max)} = 15\sqrt{2} - .75 = 20.463 \text{ V}$$

$$V_{1(\min)} = (V_{1(\max)} - 15)e^{\frac{-T}{RC}} + 15 \approx (V_{1(\max)} - 15V) \left(1 - \frac{T}{RC}\right) + 15 \text{ V}$$

$$V_{1(\min)} = 5.463 \left(1 - \frac{1}{120 \times 100 \times .001}\right) + 15 = 5.463(1 - .0833) + 15 = 20.008 \text{ V}$$

$$V_{dc} = \frac{V_{1(\max)} + V_{1(\min)}}{2} = 20.24 \text{ V}$$

(c) What is the dc output voltage V_O ? 15 V


(d) What is the magnitude of the ripple voltage at V_1 ?

$$V_r = V_{1(\max)} - V_{1(\min)} = 0.455 \text{ V}$$

(e) What is the minimum PIV rating for the rectifier diodes?

$$\text{PIV} \geq 2 \times V_p - V_D = 2 \times 15\sqrt{2} - .75 = 41.7 \text{ V}$$


(f) Draw a new version of the circuit that will produce an output voltage of -15 V .

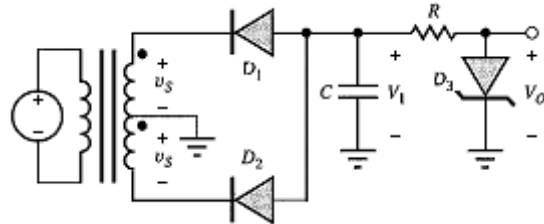


Problem 6

A diode is represented by a dc model with $V_0 = 0.60 \text{ V}$ and $R_0 = 10 \Omega$, and an ac model having $r = 2 \Omega$. If the diode is in parallel with a 50Ω resistor and this combination is in series with a 1Ω resistor and a voltage source, $v_s = 8 + 0.1 \cos(1000t)$ volts, find the total voltage across the diode as a function of time. Assume that the source is connected such that it provides forward bias to the diode.

Consider the D.C. bias first

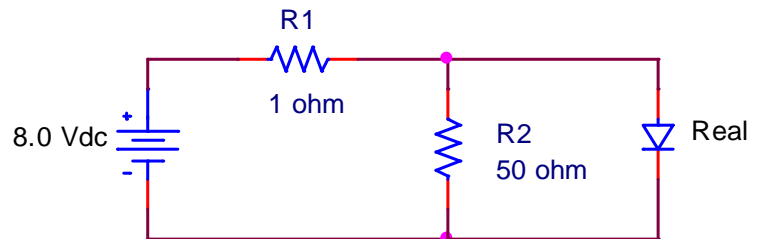

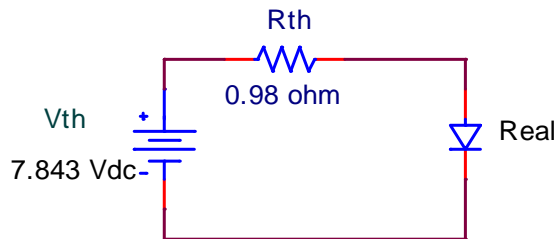Thévenin equivalent: $R_{th} = 50 \parallel 1 = \frac{50}{51} = .98 \Omega$ and $V_{th} = \frac{50}{51}(8) = \frac{400}{51} = 7.843 \text{ V}$




D.C. Analysis of the operating point using the given model

$$I_D = \frac{V_{th} - 0.6 \text{ V}}{R_{th} + 10 \Omega} = \frac{7.843 - 0.6}{0.98 + 10} = \frac{7.243}{10.98} = 650 \text{ mA}$$

$$V_D = (10 \Omega)I_D + 0.6 \text{ V} = 10 \times 1.211 + 0.6 = 7.20 \text{ V}$$

Next consider the A.C. Analysis

A.C. Equivalent circuit

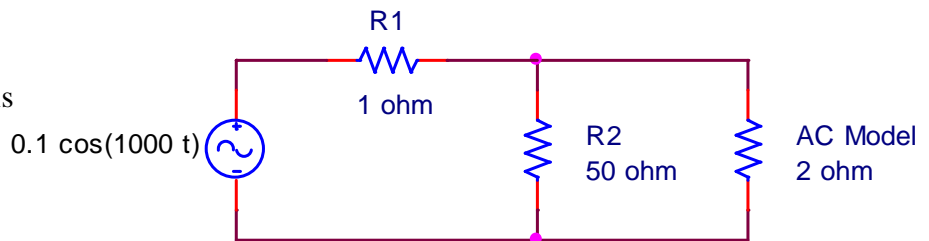

$$50 \Omega \parallel 2 \Omega = \frac{100}{52} = 1.923 \Omega$$

Therefore, $v_d = \frac{1.923}{1+1.923} [0.1 \cos(1000t)] = 0.0658 \cos(1000t)$

Combining the D.C. solution (Operating Point, Q) and the A.C. solution yields the total solution

$$v_D = V_D + v_d = 7.20 + 0.0658 \cos(1000t)$$

Problem 7

For each of the following statements, determine whether it applies to (normal) active-region operation, of an *nnp* transistor, a *pnnp* transistor, both, or neither.

- (a) $V_{EB} = 0.6 \text{ V}$ PNP
- (b) $I_C > I_E$ NPN (Since $I_C < 0$ for PNP)
- (c) $|I_C| > |I_E|$ Neither (Since $|I_E| = |I_C| + |I_B|$)
- (d) $I_E > I_B$ PNP (Since $I_E < 0$ for NPN)
- (e) $V_{CE} > V_{CB}$ NPN
- (f) $|V_{CE}| > |V_{CB}|$ Both

Problem 8

The active region model for an *npn* transistor contains $V_0 = 0.55 \text{ V}$, $\beta_{dc} = 125$, and $I_{CE0} = 2 \mu\text{A}$. Find I_C when

(a) $I_B = 200 \mu\text{A}$

$$I_C = \beta I_B + I_{CE0} = 125(0.2) + 0.002 \text{ mA} = 25.002 \text{ mA}$$


(b) $|I_E| = 3 \text{ mA}$

$$I_B + I_C = -I_E = |I_E| = 3 \text{ mA}$$

$$I_C = \beta I_B + I_{CE0} = 125(3 - I_C) + 0.002 \quad \Rightarrow \quad I_C = 2.976 \text{ mA}$$

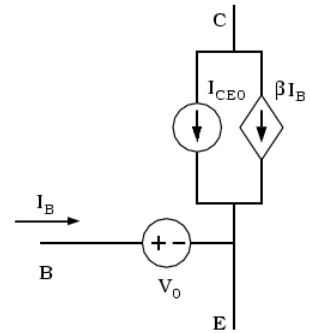(c) Find V_{BE} when $I_C = 2 \text{ mA}$

$$V_{BE} = V_0 = 0.55 \text{ V} \quad (\text{given})$$



Problem 9 (Text 5.82)


(a) Find the Q -point for the circuit shown below. Assume that $\beta_F = 50$ and $V_{BE} = 0.7 \text{ V}$.

$$V_{TH} = \frac{36 \text{ k}\Omega}{(68 \text{ k} + 36 \text{ k})\Omega} \times 10 \text{ V} = 3.462 \text{ V} \quad \text{and} \quad R_{TH} = 36 \text{ k} \parallel 68 \text{ k}\Omega = 23.54 \text{ k}\Omega$$

$$V_{TH} = R_{TH} \times I_B + V_{BE} + R_E \times (I_C + I_B) \quad \Rightarrow \quad I_B = \frac{V_{TH} - V_{BE}}{R_{TH} + (\beta + 1)R_E}$$

$$I_B = \frac{2.762}{23.54 \text{ k} + (51)33 \text{ k}} = 1.618 \mu\text{A} \quad \therefore I_C = \beta_F I_B = 80.9 \mu\text{A}$$

and $V_{CE} = V_{CC} - I_C R_C - |I_E| R_E = 3.80 \text{ V}$

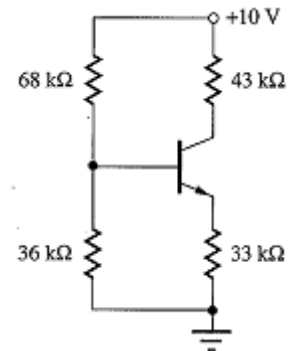

(b) Repeat the calculation if all of the resistor values are decreased by a factor of 5.

$$V_{TH} \text{ is unchanged and } R_{TH}(\text{new}) = 0.2 \times R_{TH}(\text{old}) = 4.708 \text{ k}\Omega \quad \Rightarrow \quad I_B(\text{new}) = 5 \times I_B(\text{old}) = 8.09 \mu\text{A}$$

$$I_C(\text{new}) = 5 \times I_C(\text{old}) = 405 \mu\text{A} \quad \text{and} \quad V_{CE} \text{ is unchanged, } V_{CE} = 3.80 \text{ V}$$


Problem 10 (Text 5.82)

(c) Repeat (a) of text problem 5.82 for the second circuit shown.

$$V_{TH} = \frac{68 \text{ k}\Omega}{(68 \text{ k} + 36 \text{ k})\Omega} \times 10 \text{ V} = 6.538 \text{ V} \quad \text{and} \quad R_{TH} = 36 \text{ k} \parallel 68 \text{ k}\Omega = 23.54 \text{ k}\Omega$$

$$V_{TH} = R_{TH} \times I_B - 0.7 \text{ V} + R_E \times (I_C + I_B) + 10 \text{ V} \quad \Rightarrow \quad -I_B = \frac{10 \text{ V} - V_{TH} - 0.7 \text{ V}}{R_{TH} + (\beta + 1)R_E}$$
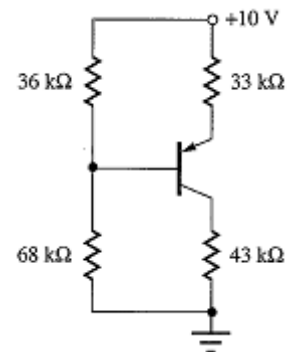
$$I_B = \frac{-2.762}{23.54 \text{ k} + (51)33 \text{ k}} = -1.618 \mu\text{A} \quad \therefore I_C = -80.9 \mu\text{A} \quad \text{and} \quad V_{CE} = -3.80 \text{ V}$$



(d) Repeat (b) of text problem 5.83 for the second circuit shown.

$$V_{TH} \text{ is unchanged and } R_{TH}(\text{new}) = 0.2 \times R_{TH}(\text{old}) = 4.708 \text{ k}\Omega \quad \Rightarrow \quad I_B(\text{new}) = 5 \times I_B(\text{old}) = -8.09 \mu\text{A}$$

$$I_C(\text{new}) = 5 \times I_C(\text{old}) = -405 \mu\text{A} \quad \text{and} \quad V_{CE} \text{ is unchanged, } V_{CE} = -3.80 \text{ V}$$