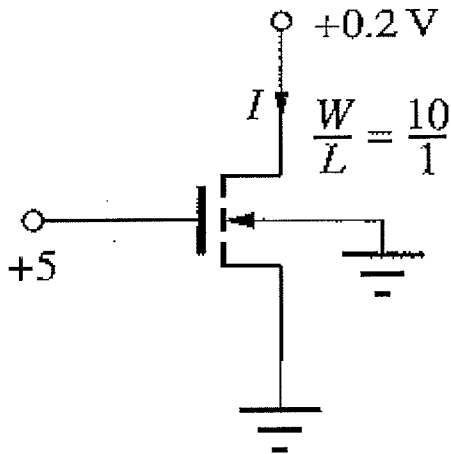




1) For the circuit shown below what is  $I_D$ ? Assume  $\lambda=0$ ,  $V_{TN}=0.7V$ , and  $K'_N=100\mu A/V^2$



NMOS in enhancement  
mode  
 $V_t = +ve$

(1) 0.84mA  
(5) 1.68mA

(2) 9.24mA  
(6) None of the above

(3) 0.084mA

(4) 0mA

$V_{gs} > V_t \Rightarrow$  transistor is ON

$$V_{ds} < V_{gs} - V_t$$

$$0.2 < 5 - 0.7$$


So triode or linear region.

$$\begin{aligned} I_D &= K_n \left( V_{gs} - V_t - \frac{V_{ds}}{2} \right) V_{ds} \\ &= 100\mu \left( 5 - 0.7 - 0.1 \right) 0.2 \\ &= 100\mu \times 4.2 \times 0.2 \\ &= 84\mu \\ &= 0.084\text{mA} \end{aligned}$$

So Ans (1)

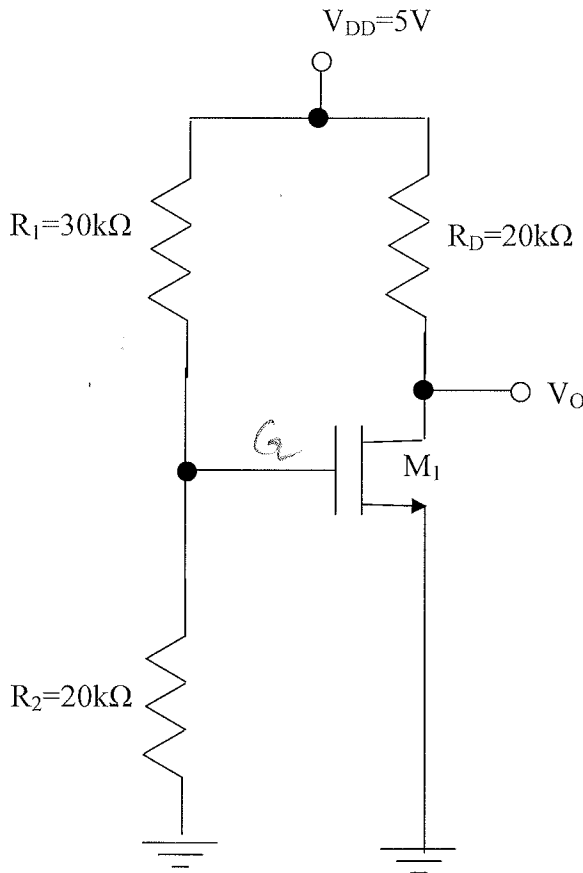2) For the MOS circuit shown below,  $V_o = ?$

$\lambda = 0, V_{TN} = 1V, K_N = 0.2 \text{ mA/V}^2$



$V_{G2} = \frac{5}{50} \times 20k$   
 $= 2 \text{ Volt}$

$V_{GS} = 2$

$V_t = 1$

- (1) 4V
- (2) 2.5V
- (3) 2V
- (4) 3.5V
- (5) 3V
- (6) None of the above


Let's assume in saturation as  $V_{GS} - V_t = 1 \text{ Volt}$  & supply is 5V (though it depends upon  $R_D$ ). But I guess its good start.

$I_D = \frac{K_N}{2} (V_{GS} - V_t)^2 = \frac{0.2 \text{ mA}}{2} (1)^2 = \underline{0.1 \text{ mA}}$

drop in  $R_D \Rightarrow 20k \times 0.1 \text{ mA} = 2 \text{ Volt}$

So  $V_o = 3 \text{ Volt}$  check  $V_{DS} = (3) > V_{GS} - V_t (1)$   
 So Ans (5)

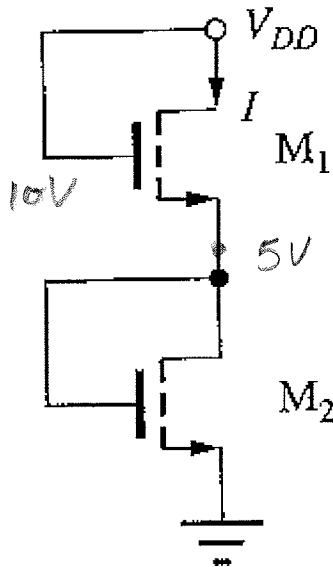- 3) Find the current  $I$  in the circuit below if  $V_{DD}=10V$  and  $\lambda=0$ . Both transistors have  $W/L=10/1$ ,  $V_{TN}=0.75V$ , and  $K'_N=100\mu A/V^2$



If we ignore body effect &  $\lambda=0$  which we will do,  $V_{drop}$  across both the transistors will be same. mid point will be

$$\frac{V_{DD}}{2} = 5$$

This is true b'coz  $W/L$  of both of them are same.

- (1) 18mA      (2) 0.9mA      (3) 9.03mA      (4) 42mA  
 (5) 0mA since gates are tied to drains (transistors are off)  
 (6) None of the above

diode connected transistor is always in saturation as  $(V_{ds} > V_{gs} - V_t \text{ always})$


$$I = \frac{10 \times 100 \mu}{2} (5 - 0.75)^2$$

$$= \frac{100 \mu \times (4.25)^2 \times 10}{2}$$

$$= 9030 \mu = 9.03 \text{ mA}$$

Ans (3)

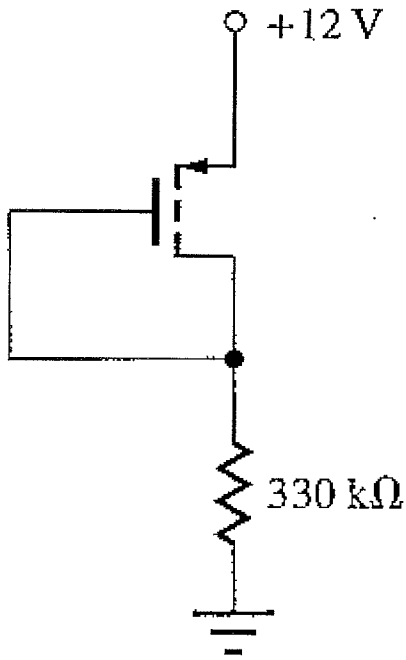- 4) What is the value of  $V_{GS}$  for the circuit shown below? Assume  $\lambda=0$ ,  $V_{TP}=-1V$ ,  $W/L=10/1$ , and  $K'_p=40\mu A/V^2$



transistor is always ON  
& always in saturation

$$|V_{DS}| \geq |V_{GS} - V_{TP}| \geq 0$$

$$i_D = \frac{10 \times 40 \mu A}{2} (V_{SG} + V_{TP})^2$$

$$i_D = 200 \mu A (12 - V_G - 1)^2$$

$$\frac{V_G}{330k} = i_D$$

- (1) 0V                      (2) -1.4V                      (3) 12V                      (4) -0.7V  
(5) 1.4V                      (6) None of the above

$$\text{So } \frac{V_G}{330k} = 200 \mu A (11 - V_G)^2$$

$$V_G = 330k \times 200 \mu A (11 - V_G)^2$$


$$V_G = 66 (11 - V_G)^2$$

$$V_G \approx 10.56 V$$

$$V_{GS} \approx -1.4 V$$

So Ans (2)

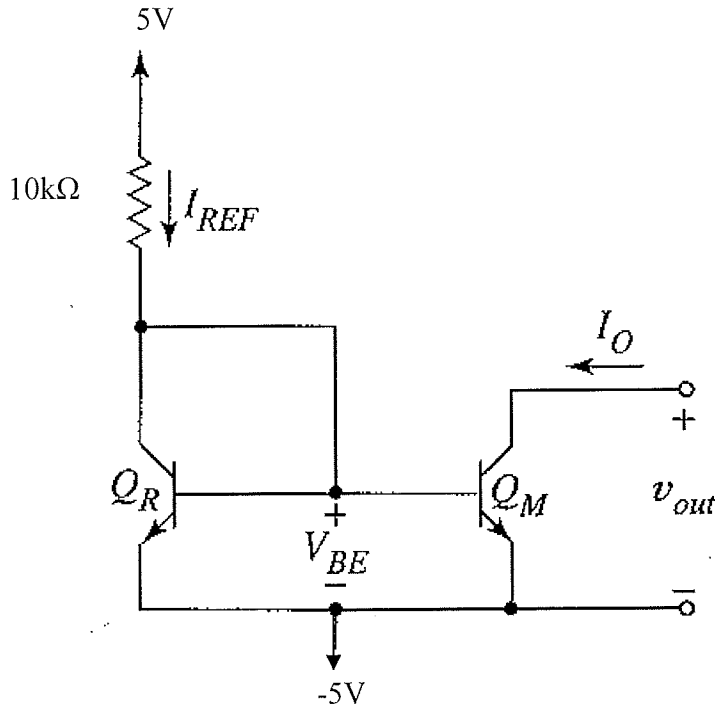- 5) What is the value of output current for the current mirror shown below? Assume  $\beta = \infty$ ,  $V_{BE(ON)} = 0.7V$ ,  $V_A = \infty$



- (1) 0.93mA      (2) 0.43mA      (3) 1.07mA      (4) 5.07mA  
 (5) 0mA since emitters are connected together  
 (6) None of the above

$V_A = \infty \Rightarrow$  current will match exactly.

$$I_O = I_{ref}$$

$$5 - I_{ref} \times 10k - 0.7 = -5$$


$$I_{ref} = \frac{10 - 0.7}{10k}$$

$$= \frac{9.3}{10k}$$

$$= 0.93m$$

So ans (1)

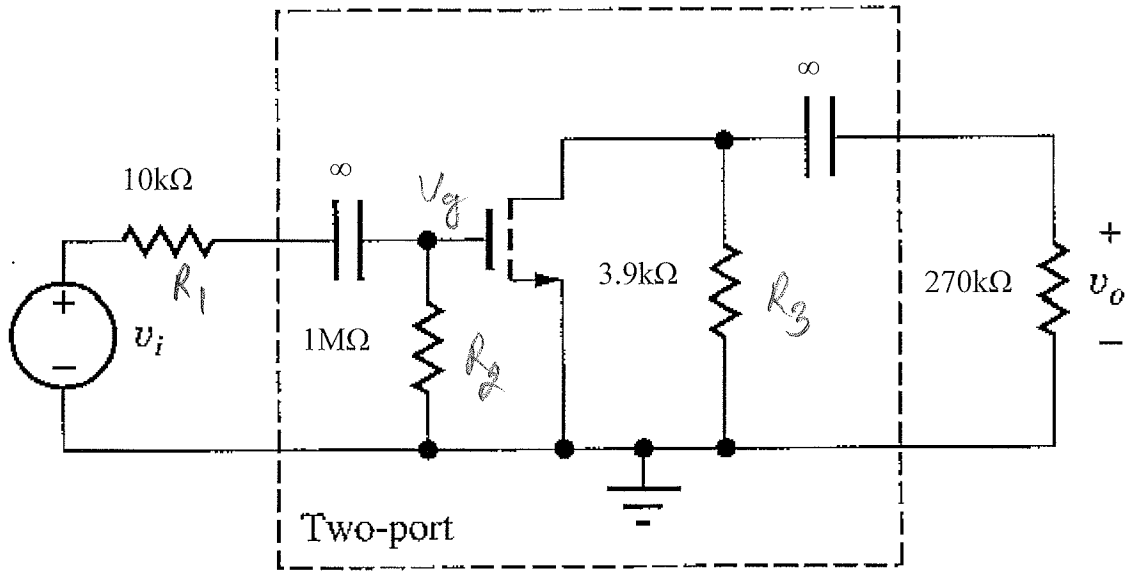- 6) What is the voltage gain ( $v_o/v_i$ ) for the common source amplifier whose ac equivalent circuit is shown below? Assume the MOSFET Q points are (2mA, 7.5V),  $K_n=1\text{mA/V}^2$ , and  $\lambda=0$



- (1) -7.8      (2) -7.61      (3) -540      (4) -25  
 (5) gain is zero since we ignored the channel length modulation  
 (6) None of the above

$$g_m = \frac{2I_D}{V_{GS} - V_{th}}$$

$$\approx \sqrt{2K_n I_D}$$

$$= \sqrt{4\text{mA} \times 1\text{M}}$$

$$= \underline{2\text{mA/V}}$$

there is gain in two stages

- (i) from  $v_i$  to  $V_g$       (ii) from  $V_g$  to  $v_o$

$$\Downarrow$$

$$\frac{R_2}{R_1 + R_2} = \frac{1\text{M}}{1\text{M} + 10\text{k}}$$

$$= .99$$

$$\Downarrow$$

$$-g_m \times R_3 \parallel R_L = -g_m \times 3.9\text{k} \parallel 270\text{k}$$

$$= -2\text{m} \times$$

$$= \underline{-7.68}$$


lolol

$$\underline{\underline{-7.6}}$$

so (2)

7) What is the input and output impedances for the common emitter amplifier whose ac equivalent circuit is shown below? Assume the BJT Q points are  $(2\mu A, 1.5V)$ ,  $\beta=50$ ,  $V_A=50V$ ,  $V_T=25mV$ , and  $V_{BE(ON)}=0.7V$ .

$$r_o = \frac{V_A}{I_C}$$

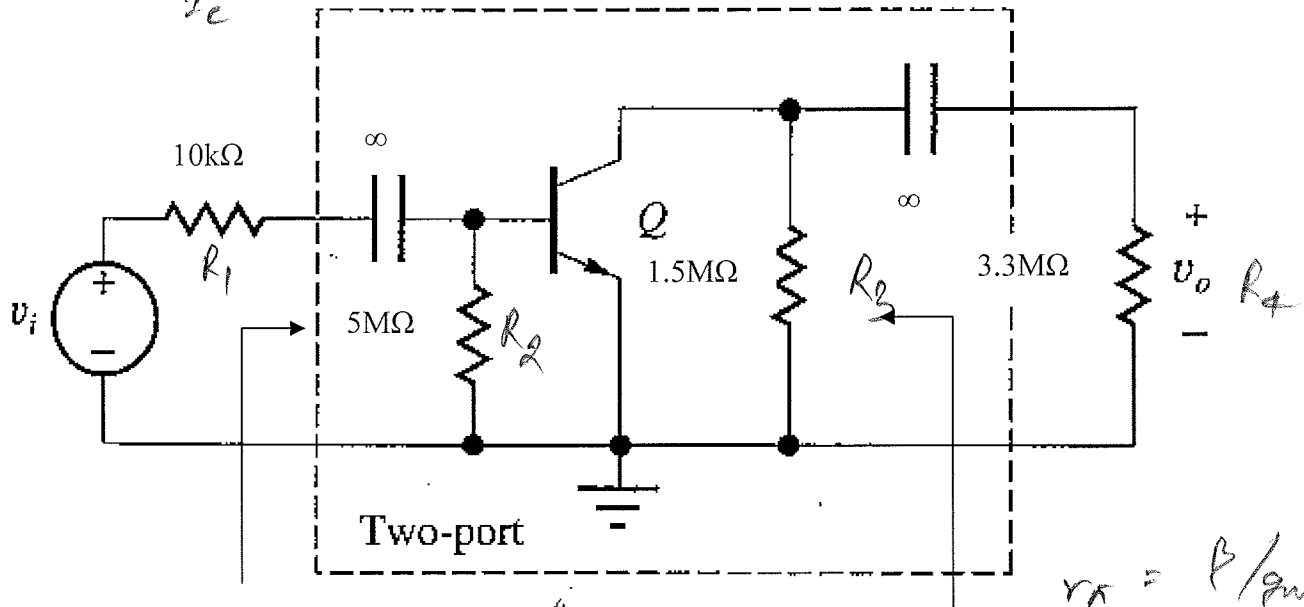

$$g_m = \frac{I_C}{V_T} = \frac{2\mu A}{25m} = \frac{200 \times 10^{-5}}{25} = 8 \times 10^{-5} \text{ A/V}$$

$$r_\pi = \frac{\beta}{g_m} = \frac{50}{8 \times 10^{-5}} = 0.625M$$

- (1)  $R_{in}=555k\Omega, R_{out}=1.5M\Omega$
- (2)  $R_{in}=5M\Omega, R_{out}=1.41M\Omega$
- (3)  $R_{in}=555k\Omega, R_{out}=25M\Omega$
- (4)  $R_{in}=625k\Omega, R_{out}=1.41M\Omega$
- (5)  $R_{in}=555k\Omega, R_{out}=1.41M\Omega$
- (6) None of the above

$$R_{in} = R_2 \parallel r_\pi = 5m \parallel 0.625M$$

$$R_{in} = \underline{\underline{555k}}$$


$$R_{out} = R_3 \parallel r_o = 1.5M \parallel 2.5 \times 10^7 = \underline{\underline{1.41M}}$$

Ans 5



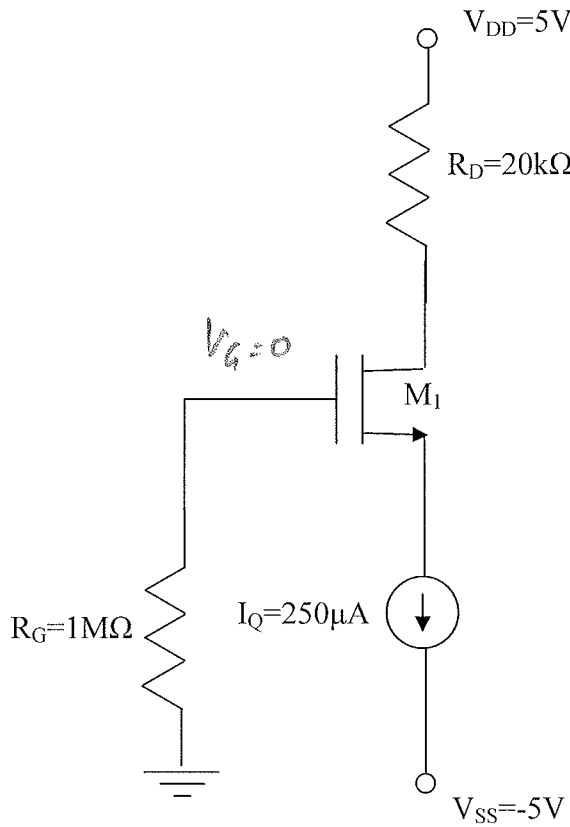8) For the MOS circuit shown below, what is the  $V_{DS}$ ?

$V_{TN}=1V, K'_N=80 \mu A/V^2, (W/L)=3, \lambda=0$



let's assume  $T_{trans}$  is in saturation.

$$I_D = \frac{K'_N W}{L} \frac{(V_{GS} - V_{TE})^2}{2}$$

$$= \frac{80 \mu A}{V^2} \times 3 \frac{(-V_S - 1)^2}{2}$$

$$I_D = 120 \mu A (V_S + 1)^2$$

$$250 \mu A = 120 \mu A (V_S + 1)^2$$

$$V_S = -2.94 \text{ Volt}$$

other solution is dropped b'coz in that case transistor is off.

- (1) 2.44V
- (2) 0V
- (3) 2V
- (4) 2.56V
- (5) 5V
- (6) None of the above

$$V_D = 5 - 20k \times 250 \mu A$$

$$= 5 - 20 \times 25 \times 5$$


$$= 0$$

$$V_{DS} = 2.94 \text{ Volt}$$

(1)

9) For the circuit shown below (Common emitter amplifier) the voltage gain and input impedance are? Assume  $V_{BE(ON)}=0.7V$ ,  $\beta=100$ ,  $V_A=\infty$ ,  $I_{CQ}=0.25mA$ , and  $V_{CEQ}=3V$ .

$V_T$

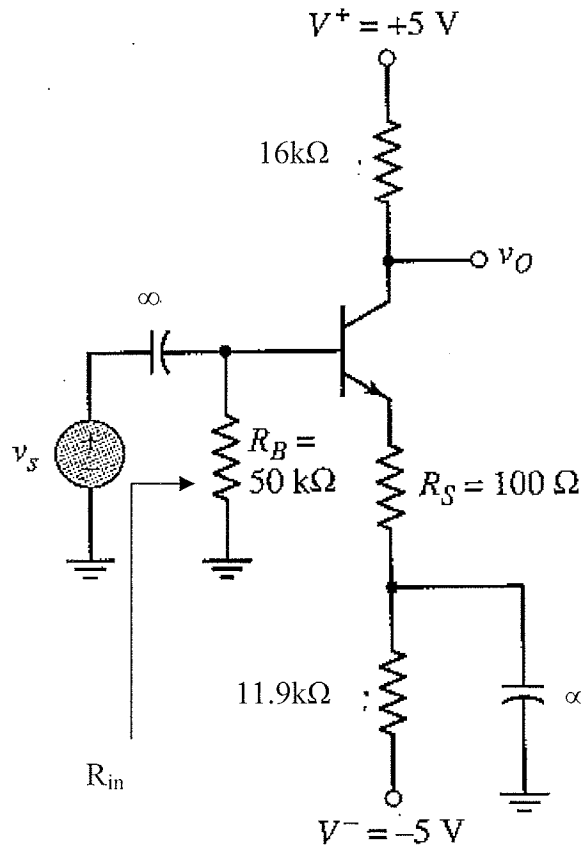

$$r_{\pi} = \frac{\beta}{g_m}$$

$$g_m = \frac{I_C}{V_T}$$

$$= \frac{0.25mA}{25mV}$$

$$g_m = 1 \times 10^{-2}$$

$$\frac{100}{0.01} = 10^4$$

- (1) 50kΩ
- (2) 10kΩ
- (3) 8.33kΩ
- (4) 14.34kΩ
- (5) 20.1kΩ
- (6) None of the above

Common emitter amplifier

$$R_{in} = R_B \parallel R_{iB}$$


$$= R_B \parallel r_{\pi} (1 + g_m R_E)$$

$$= 50k \parallel 1 \times 10^4 (1 + \frac{10^{-2}}{10^{-4}})$$

$$= 50k \parallel 120k$$

$$= 14.28k$$

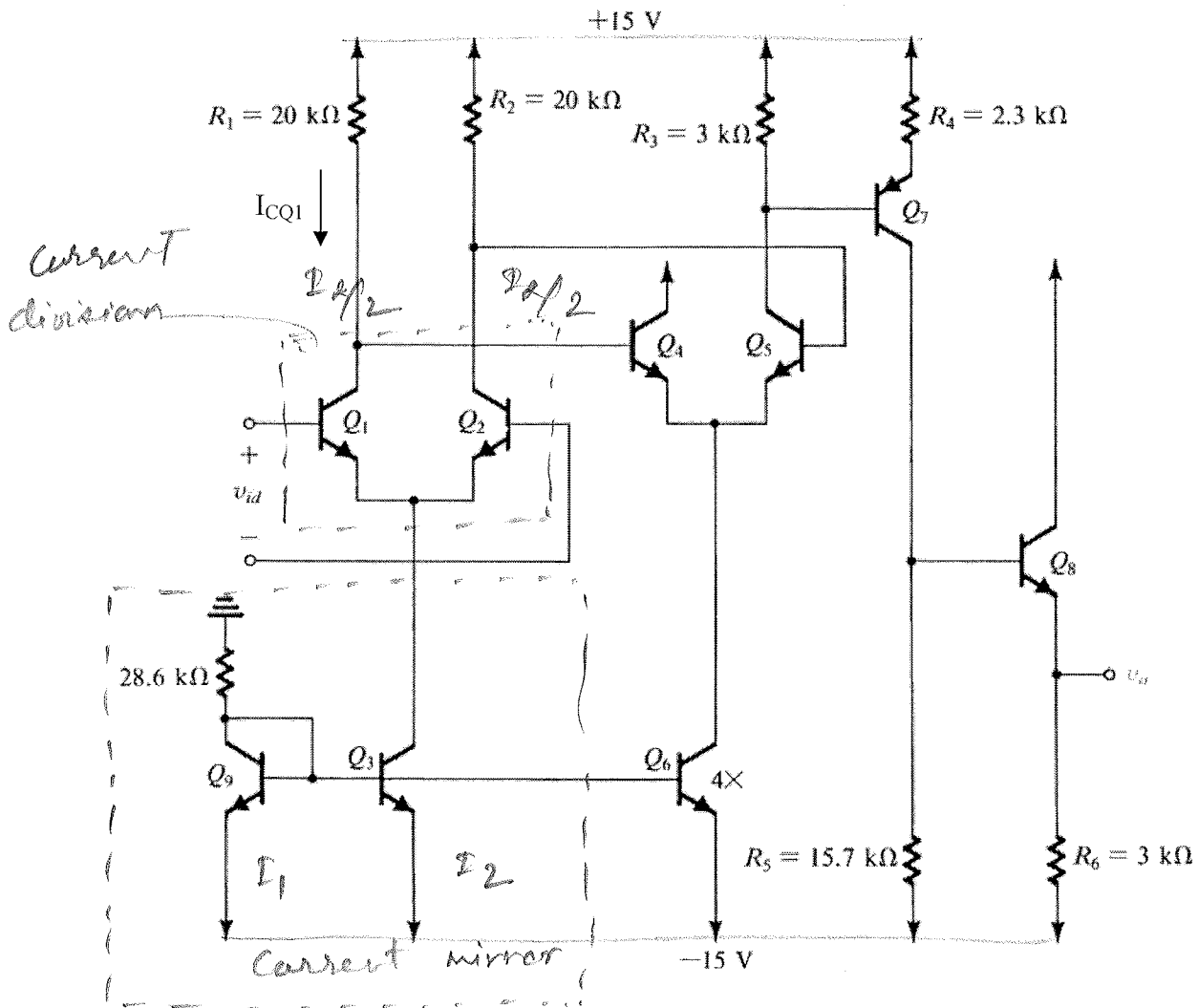10) Figure below is internal structure of an OpAmp, what is the current  $I_{CQ1}$ ? Assume  $Q_1$  and  $Q_2$  are identical,  $\beta=100$ , and  $V_{BE(ON)}=0.7V$



- (1) 0.5mA
- (2) 0.25mA
- (3) 0mA
- (4) 0.27mA
- (5) 1mA
- (6) None of the above

Current divides equally if  $V_{id} = 0$

$$0 - I_1 \times 28.6k - 0.7 = -15$$

$$\frac{15 - 0.7}{28.6k} = I_1 = \underline{\underline{0.5m}}$$

$$I_{CQ1} = I_1 / 2 = \underline{\underline{0.25m}} \quad \underline{\underline{As}} \quad \underline{\underline{(2)}}$$

