

**ECE-255**  
**FINAL EXAM**  
**May/3/2010**

Name: \_\_\_\_\_  
(Please print clearly)


Student ID: \_\_\_\_\_

**INSTRUCTIONS**

- This is a closed book, closed notes exam.
- Carefully mark your multiple choice answers on the scantron form. Work on multiple choice problems and marked answers in the test booklet will not be graded. Nothing is to be on the seat beside you.
- When the exam ends, all writing is to stop. This is not negotiable. No writing while turning in the exam/scantron or risk an F in the exam.
- All students are expected to abide by the customary ethical standards of the university, i.e., your answers must reflect only your own knowledge and reasoning ability. As a reminder, at the very minimum, cheating will result in a zero on the exam and possibly an F in the course.
- Communicating with any of your classmates, in any language, by any means, for any reason, at any time between the official start of the exam and the official end of the exam is grounds for immediate ejection from the exam site and loss of all credit for this exercise.

**NOTE: Choose the answer that is closest to what you have calculated; many answers are rounded to the first non-decimal point**

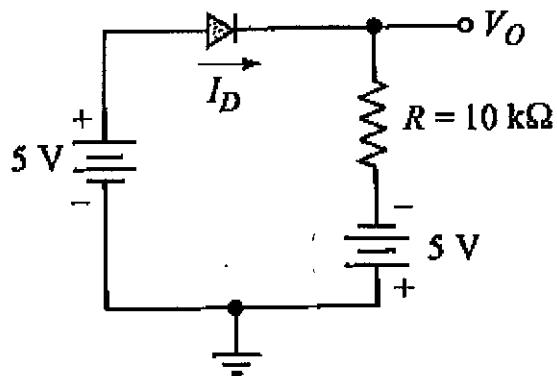1. What is  $V_o$  in the circuit shown below, for the diode assume  $V_{on}=0.7V$  and  $R_D=500\Omega$



(1) 3.86 V

(2) -5V

(3) 0V

(4) 4.3V

(5) Open circuit

(6) None of these


$$I_D = \frac{10 - 0.7}{10.5} = 0.886 \text{ mA}$$

$$V_o = 0.886(I_o) - 5 = 3.86 \text{ V}$$

2. In a power supply using full bridge rectifier, one can reduce the ripple voltage by

- (1) Decreasing the input frequency
- (2) Increasing the filter capacitor value and decreasing the input frequency
- (3) Increasing the filter capacitor value and increasing the input frequency
- (4) Decreasing the filter capacitor value
- (5) Using Schottky diodes
- (6) None of the above

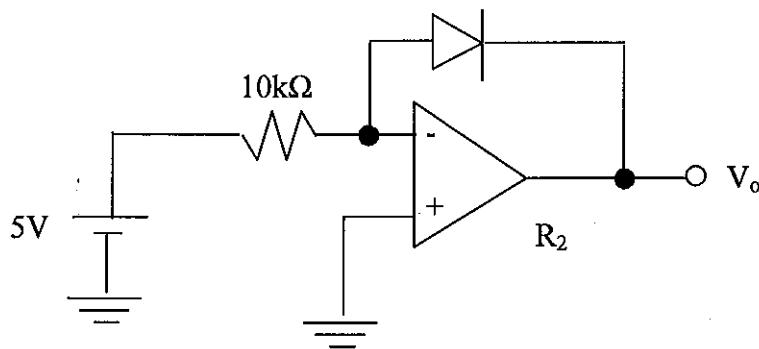3. What is  $V_o$ ? for the diode  $I_s=10^{-14}A$  (Assume  $V_T=25mV$ )









- (1) 0.7V
- (2) -0.61V**
- (3) 0.61V
- (4) 0.7V
- (5) 0V
- (6) None of the above

$$I_{in} = \frac{5}{10} = 0.5 \text{ mA}$$

$$V_o = -0.025 \ln \frac{0.5 \times 10^{-3}}{10^{-14}}$$


$$V_o = -0.61 \text{ V}$$

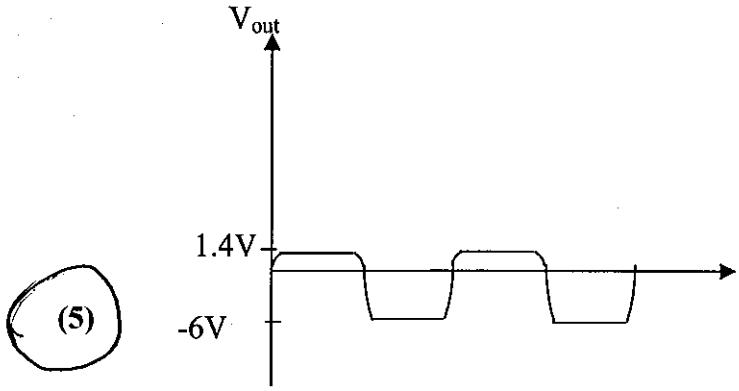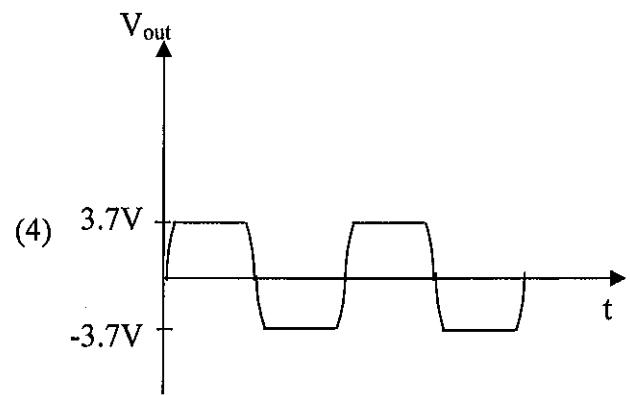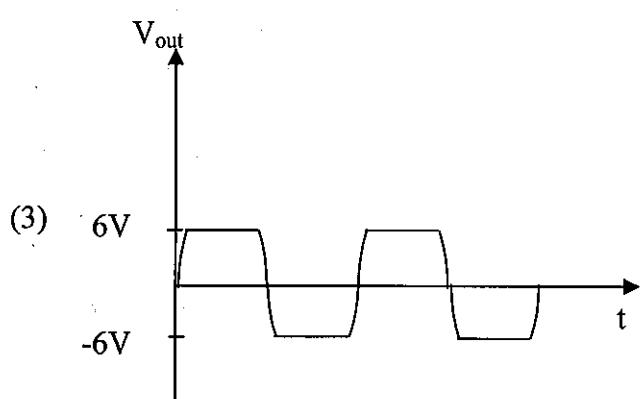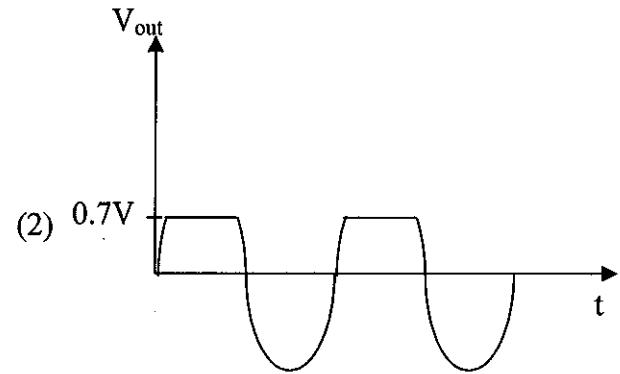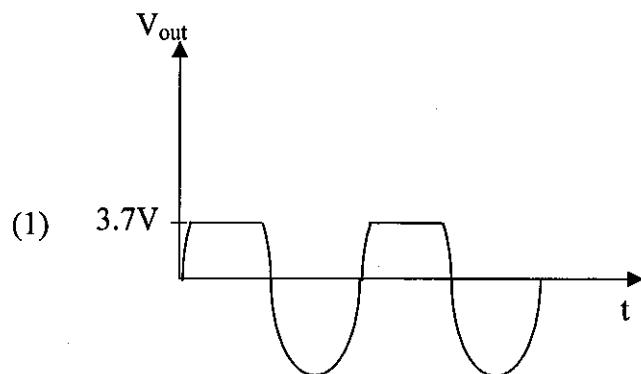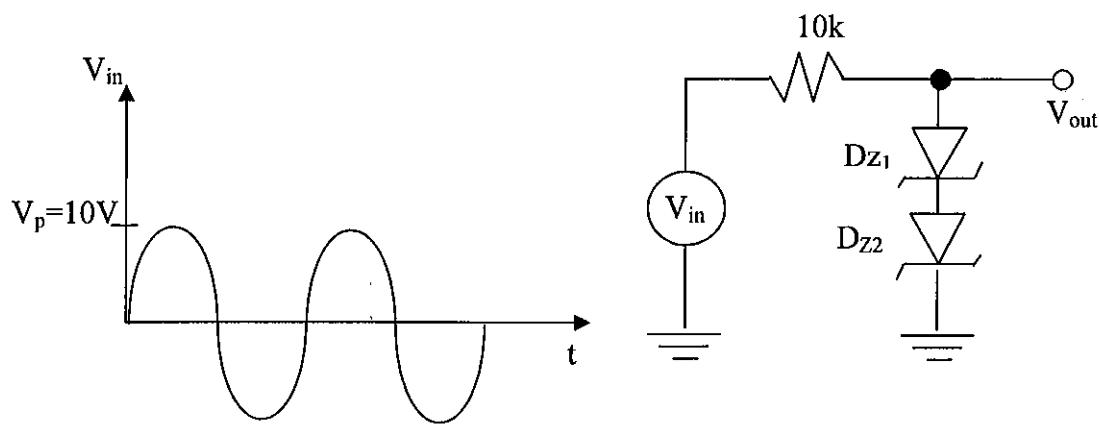4. For the circuit shown below, if a sinusoidal wave is applied to the input, which one of the curves is the output voltage? ( $V_{on}=0.7V$ ,  $V_Z=3V$ )




(6) None of these

5. The circuit shown below is a

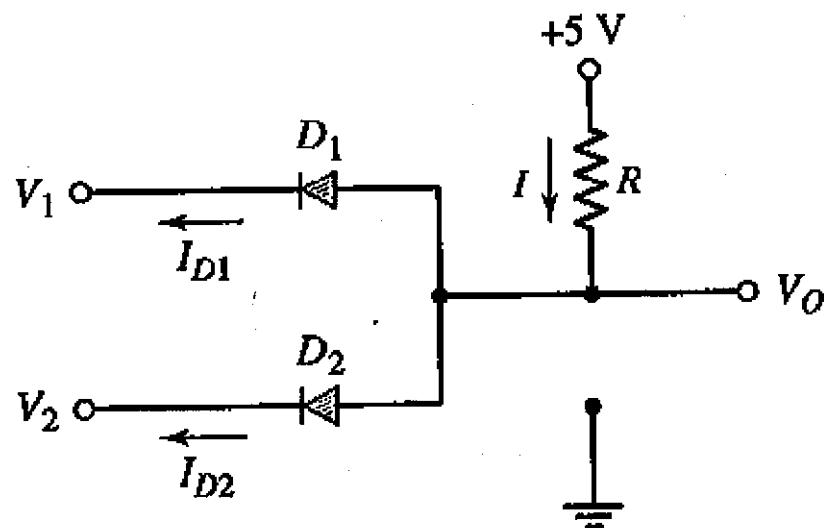

- (1) Two input AND gate  
 (2) Two input OR gate  
 (3) Two input NAND gate  
 (4) Two input NOR gate  
 (5) Two input XOR gate  
 (6) None of the above

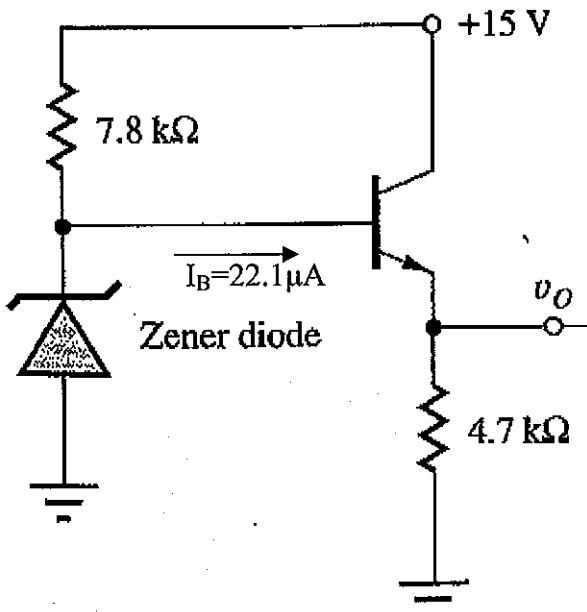6. For the circuit shown below what is the value of  $\beta_F=50$ ? Assume for transistor  $V_{BE(on)}=0.7V$ .  
 For Zener diode  $V_Z=6V$ ,  $R_Z=0$ ,  $I_S=10^{-16}A$ ,




- (1) 100
- (2) 80
- (3) 75
- (4) 125
- (5) 50**
- (6) None of the above

$$I_E = \frac{6 - 0.7}{4.7k} = \cancel{1.128} \text{ mA}$$

$$\beta + 1 = \frac{I_E}{I_B} = \cancel{1.128} / 0.0221$$

$$\beta = 50$$

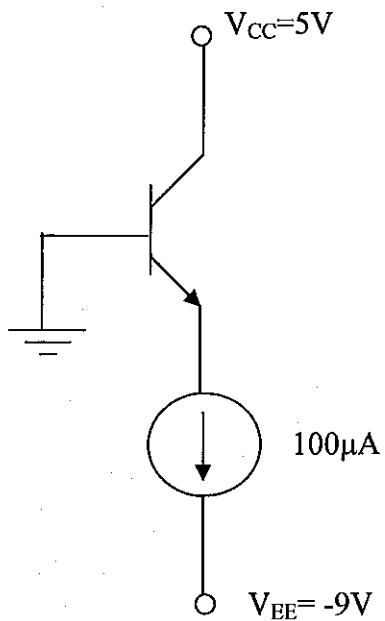7. For the bipolar circuit shown below,  $V_{CE}=?$   
 $\beta=100$ ,  $I_s=10^{-14}$ A, and  $V_T=25$ mV



- (1) 14V      (2) 5.57V      (3) 0.7V      (4) 5V  
 (5) 4.42      (6) None of the above


$$V_{BE} = 0.025 \text{ V} \quad \frac{100 \times 10^{-6}}{10^{-14}} = 0.576$$

$$V_E = -0.576$$

$$V_{CE} \approx 5.57$$

8. The circuit shown below can be used to measure the ionizing radiation ( $X$  rays and  $\gamma$  rays). The FET is called a RADFET and its threshold voltage is a function of the amount of radiation. What is the MOSFET threshold voltage if  $V_o$  is measured to be 1.5V. (10 Points)

Assume  $K_N = 0.1 \text{ mA/V}^2$

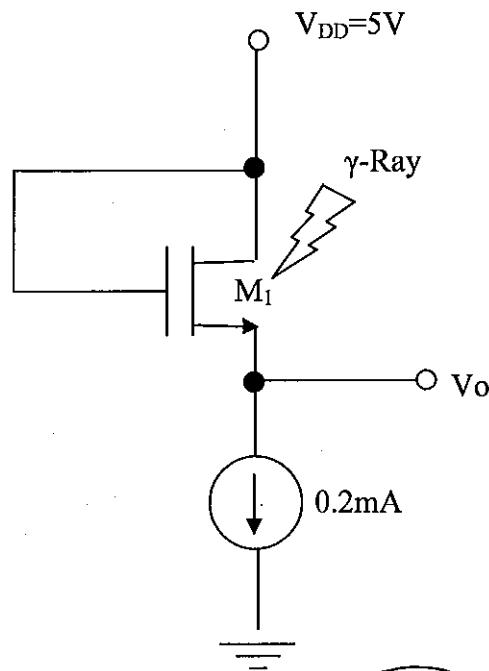


- (1) 1V      (2) 2V      (3) -5V      (4) 3V      (5) 1.5V  
 (6) None of the above

$$V_{GS} = 5 - 1.5 = 3.5$$

$$I_D = \frac{K_N}{2} (V_{GS} - V_{TN})^2$$

$$0.2 = \frac{0.1}{2} (3.5 - V_{TN})^2 \Rightarrow V_{TN} = 1.5 \text{ V}$$

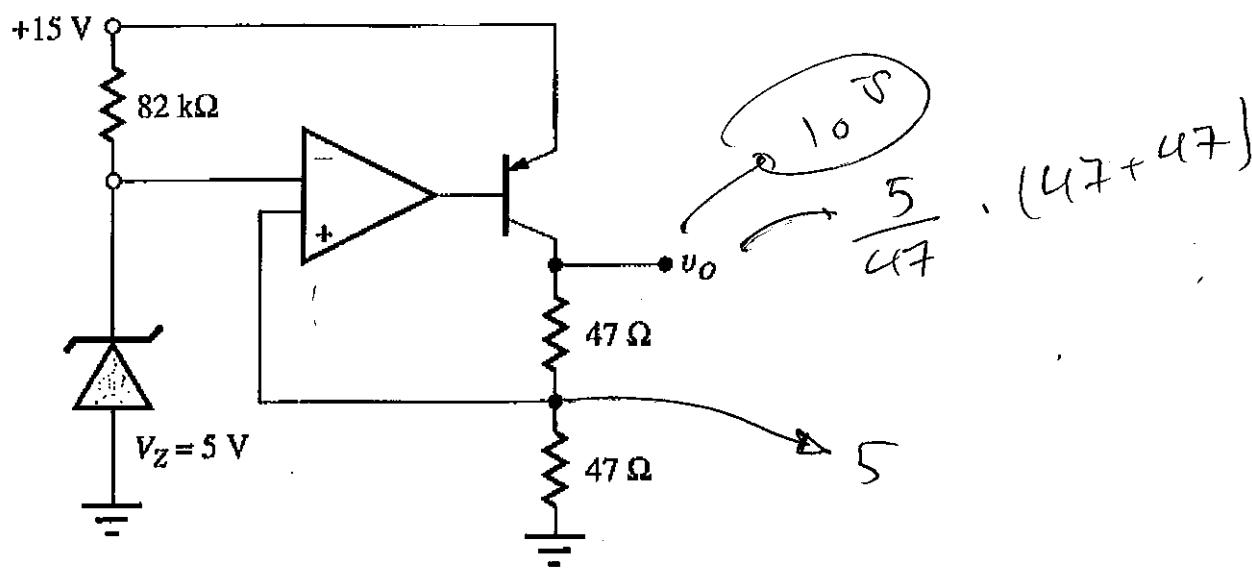
9. For the circuit shown below V<sub>CE</sub>? Assume OpAmp is ideal and  $\beta=40$



- (1) 5V      (2) 10V      (3) -5V      (4) -10V      (5) -0.7V  
 (6) None of the above

$$V_o = i_o \cdot 10 \text{ V} \rightarrow V_{CE} = i_o \cdot 15 = -5 \text{ V}$$

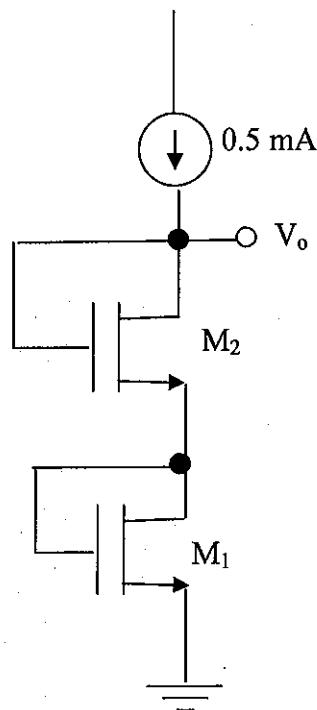10. Find the output voltage ( $V_o$ ) for the circuit shown below,  
 $V_{TN}=0.75V$ ,  $K_N=100\mu A/V^2$ ,  $(W/L)_1=(W/L)_2=10/1$



(1) ~~3.5V~~  
 (4) 7.8V

- (2) 1.75V      (3) 0V since both MOSFETS have their gate and drain shorted  
 (5) it is open circuit      (6) None of the above


$$V_o = V_{GS1} + V_{GS2} = 2V_{GS1}$$

$$I_D = \frac{K_N}{2} (V_{GS} - V_T)^2$$

$$0.5 = \frac{0.1}{2} \times 10 (V_{GS} - 0.75)^2$$

$$V_{GS} = 1.75 \rightarrow V_o = \cancel{3.5V} \quad 3.5 \text{ V}$$

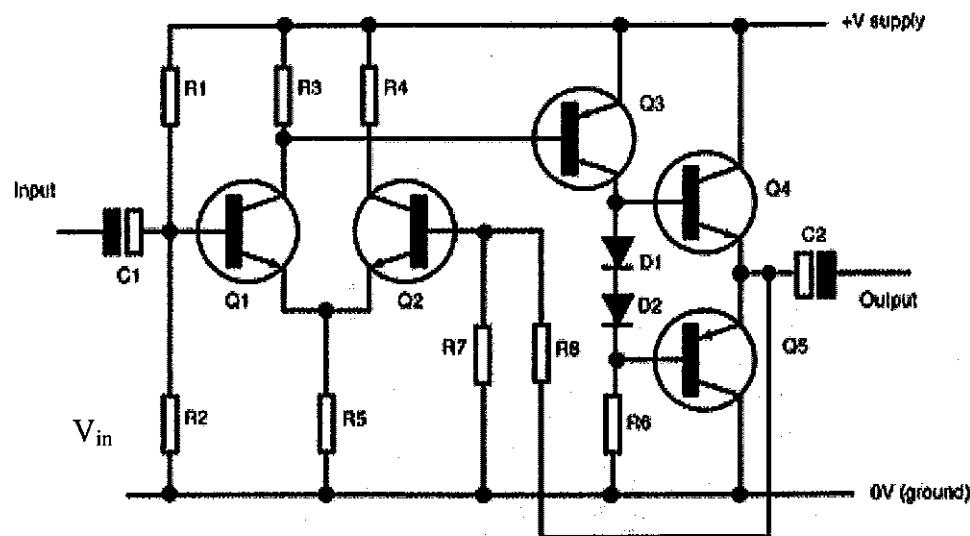
11. What is the configuration of the multi-stage amplifier shown below?



- (1) CE-CE-CC  
(5) CB-CE-CC

- (2) CE-CC-CE      (3) CE-CE-CE      (4) CE-CC-CC  
(6) None of the above

12. Figure below is internal structure of an OpAmp, what is the common mode gain of the first stage ( $|A_{dm}|$ )?  
 Assume identical transistors for differential pairs,  $\beta=100$ ,  $V_A=100V$ , and  $V_{BE(ON)}=0.7V$

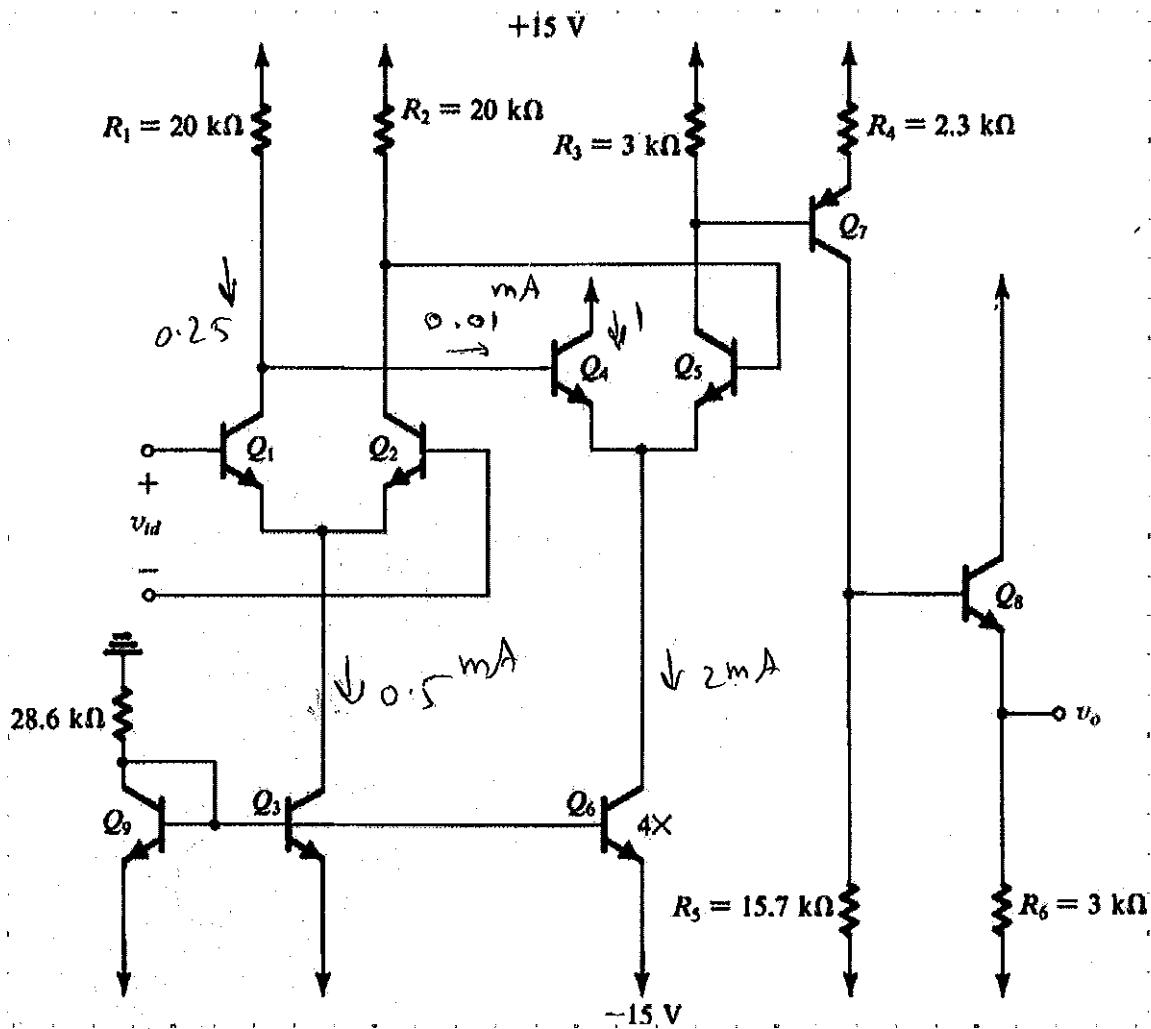

- (1) 200      (2) 125  
 (6) None of the above

- (3) 400      (4) 22      (5) 12

$$A_d = g_m R_L$$

$$\frac{0.25 \times 10^{-3}}{0.025} \times 2.2 \times 10^3$$

22


$$R_L = 20k \parallel R_{o1} \parallel R_{\pi 4}$$

$$R_{o1} = \frac{V_A}{0.25} = \frac{100}{0.25} = 400 \text{ k}\Omega$$


$$R_{\pi 4} = \frac{V_T}{I_{\pi 4}} = \frac{0.025}{0.01 \times 10^{-3}} = 2500 \Omega$$

$$R_L = 20k \parallel 400k \parallel 2.5k = 2.2k$$

13. What is the common mode gain ( $|A_{cm}|$ ) for the circuit shown below?

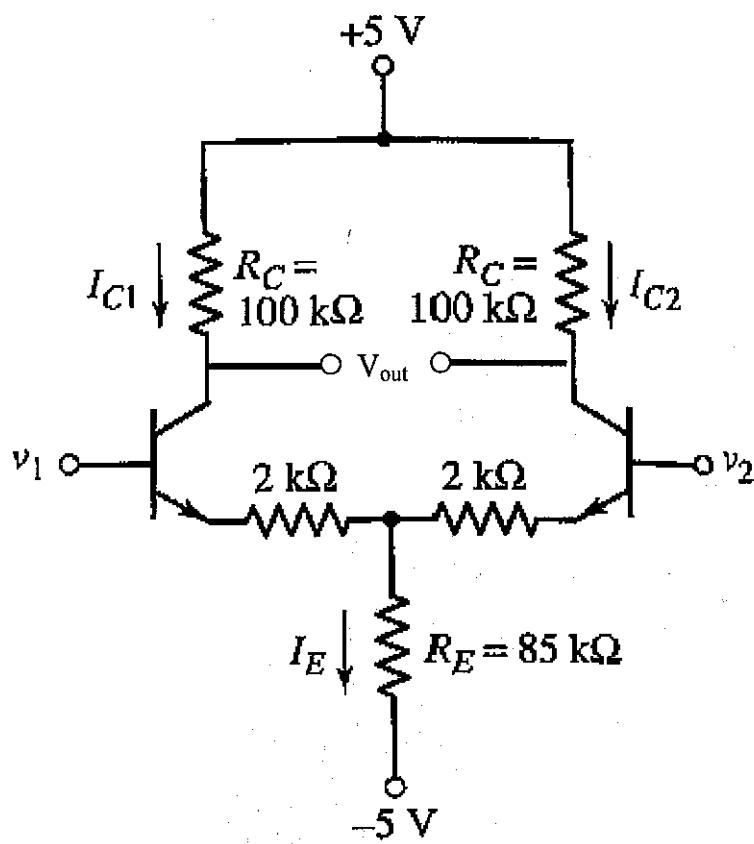

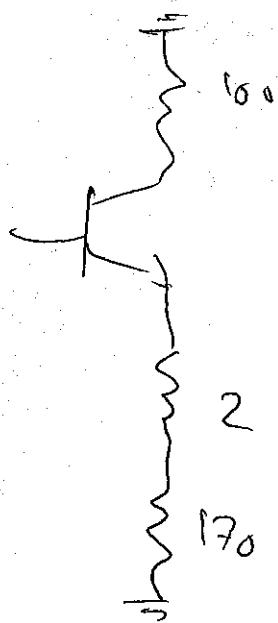
- (1) 50      (2) 0      (3) 1      (4) 0.25      (5) 0.58  
 (6) None of the above



$$A_{cm} = \frac{100}{172} = 0.58$$

Half circuit

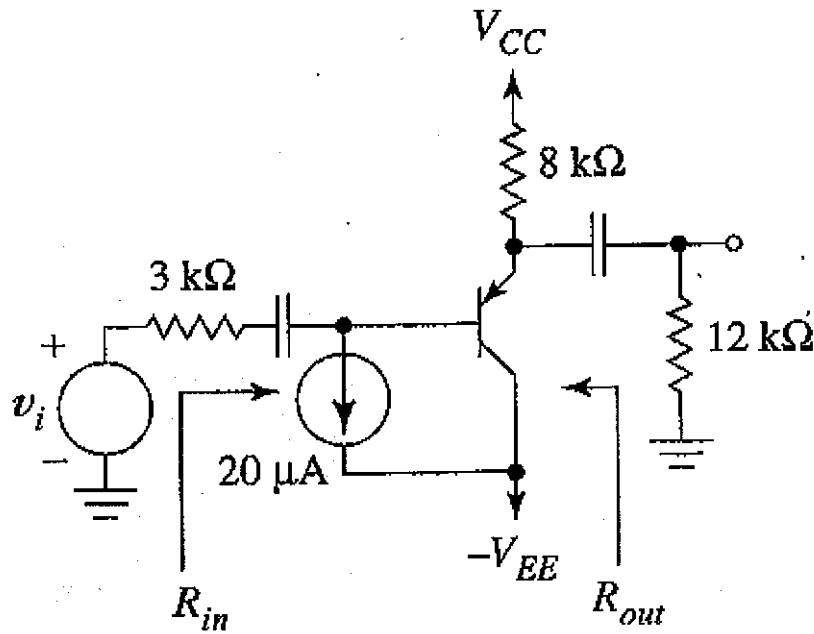14. For the emitter-follower shown below, what is  $R_{in}$ ? Assume  $\beta=100$ ,  $V_{BE(on)}=0.7$ ,  $V_A=\infty$ ,  $V_T=25\text{mV}$



(1)  $1.25\text{k}\Omega$   
 (5)  $500\Omega$

(2)  $800\text{k}\Omega$   
 (6) None of the above

(3)  $48\Omega$

(4)  $480\text{k}\Omega$

~~$$R_{in} = \frac{V_T}{I_B} = \frac{0.025}{20 \times 10^{-6}} = 1250\Omega$$~~

$R_{in} = (12118)(100) + r_n$

$R_{in} = 1211800 + 960 \approx 1212760\Omega$

$$R_{in} = (12118)(100) + r_n$$

$$= 1211800 + 1.25 \times 10^6 \approx 2.486 \times 10^6 \Omega$$


15. What is the output impedance of the following multi-stage amplifier? Assume the following parameters and small signal parameters for the transistors,

**TABLE 14.17**  
Transistor Parameters for Figs. 14.38–14.43

$M_1$	$K_n = 10 \text{ mA/V}^2, V_{TN} = -2 \text{ V}, \lambda = 0.02 \text{ V}^{-1}$
$Q_2$	$\beta_F = 150, V_A = 80 \text{ V}, V_{BE} = 0.7 \text{ V}$
$Q_3$	$\beta_F = 80, V_A = 60 \text{ V}, V_{BE} = 0.7 \text{ V}$

**TABLE 14.18**  
Q-Points and Small-Signal Parameters for the Transistors in Fig. 14.39


	Q-POINT VALUES	SMALL-SIGNAL PARAMETERS
$M_1$	(5.00 mA, 10.9 V)	$g_{m1} = 10.0 \text{ mS}, r_o = 12.2 \text{ k}\Omega$
$Q_2$	(1.57 mA, 5.09 V)	$g_{m2} = 62.8 \text{ mS}, r_{\pi 2} = 2.39 \text{ k}\Omega, r_{o2} = 54.2 \text{ k}\Omega$
$Q_3$	(1.99 mA, 8.36 V)	$g_{m3} = 79.6 \text{ mS}, r_{\pi 3} = 1.00 \text{ k}\Omega, r_{o3} = 34.4 \text{ k}\Omega$

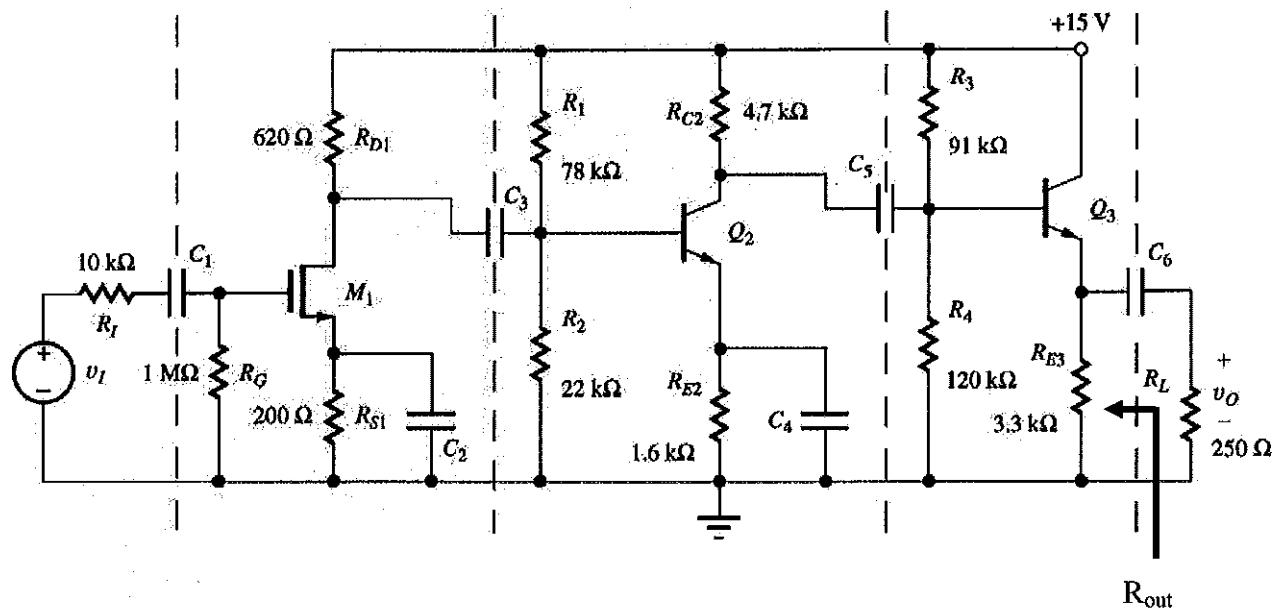

- (1)  $\sim 60 \Omega$       (2)  $\sim 3.3 \text{ k}\Omega$       (3)  $\sim 33 \text{ k}\Omega$       (4)  $\sim 120 \Omega$       (5)  $1250 \Omega$   
 (6) None of the above

$$R_{out} = \frac{(4.7 \parallel 54.2 \parallel 120 \parallel 91) + 1 \text{ k}\Omega}{81} \parallel 3.3 \text{ k}\Omega$$

16. What is the Mid-band gain ( $|A_{mid}|$ ) of the following amplifier?  $V_+ = 5V$ ,  $Q_0$ ,  $Q_1$ , and  $Q_2$  are identical and have the following parameters,  $\beta = 100$ ,  $V_{BE(on)} = 0.7V$ ,  $V_A = 100$ ,  $V_T = 0.025$

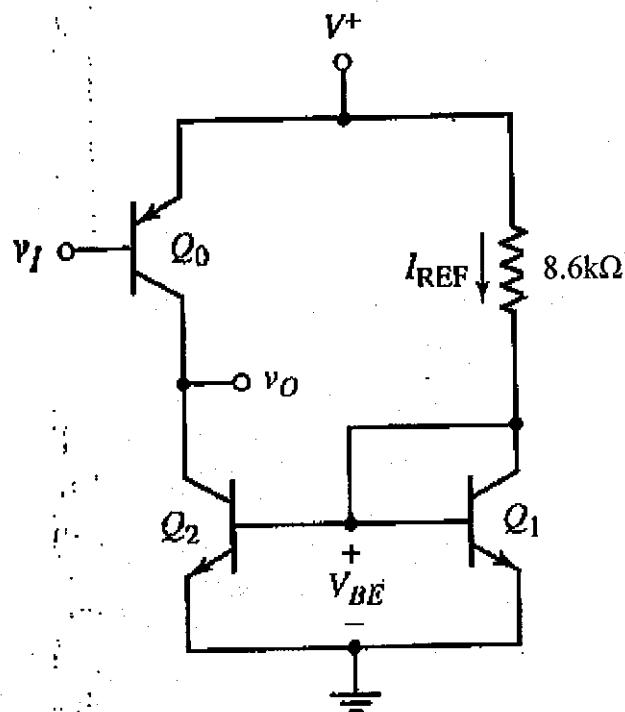

- (1) 1000      (2) 2000      (3) 4000      (4) 500      (5) 250  
 (6) None of the above

$$A = g_m R_L = \frac{0.5 \times 10^{-3}}{0.025} \times 100 \times 10^3 = 2000$$

$$I_{ref} = \frac{5 - 0.7}{8.6} = 0.5 \text{ mA}$$

$$R_L = R_0 / (1/\beta) = 100 \text{ k}\Omega$$

$$r_o = \frac{V_p}{I_C} = \frac{100}{0.5} = 200 \text{ k}\Omega$$

17. For an amplifier, the high frequency gain transfer function is given by

$$A_H(s) = \frac{2.5 \times 10^{10} (s + 2 \times 10^5)}{(s + 10^5)(s + 10^8)}$$


Mid-band gain ( $A_{\text{mid}}$ ) and higher cutoff frequency ( $\omega_H$ ) are? Assume dominant pole approximation when trying to find  $\omega_H$

- (1)  $A_{\text{mid}}=500, \omega_H=10^8 \text{ rad/s}$   
 (2)  $A_{\text{mid}}=250, \omega_H=10^5 \text{ rad/s}$   
 (3)  $A_{\text{mid}}=2.5 \times 10^{10}, \omega_H=10^5 \text{ rad/s}$   
 (4)  $A_{\text{mid}}=500, \omega_H=10^5 \text{ rad/s}$   
 (5)  $A_{\text{mid}}=2.5 \times 10^{10}, \omega_H=10^8 \text{ rad/s}$   
 (6) None of the above


$$A_H(s) = \frac{2.5 \times 10^{10} s}{(s + 10^5)(s + 10^8)} = \frac{2 \times 10^5 \left( 1 + \frac{s}{2 \times 10^5} \right)}{10^5 \times 10^8 \left( 1 + \frac{s}{10^5} \right) \left( 1 + \frac{s}{10^8} \right)}$$

$$= \frac{500}{1 + \frac{s}{10^5}}$$

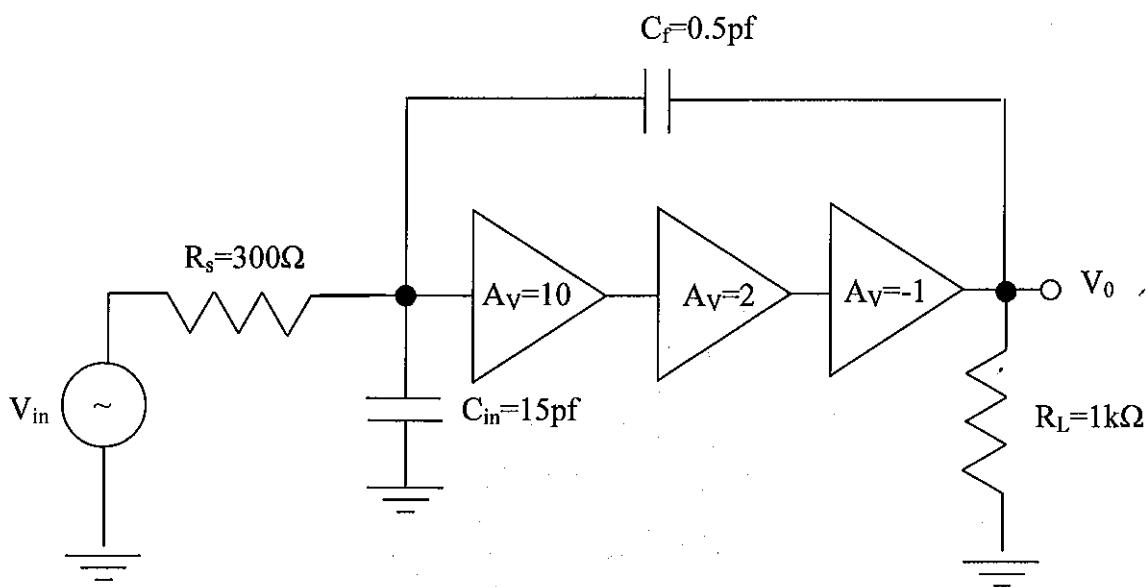18. For the amplifier circuit shown below, find  $f_H$ ?




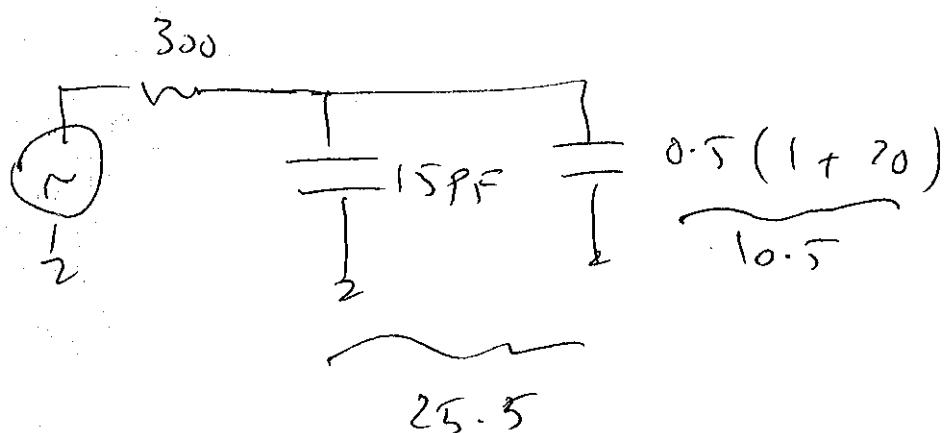- (1) ~106MHz      (2) ~15MHz      (3) ~35MHz      (4) ~50MHz  
 (5) ~24MHz      (6) None of the above



$$f_H = \frac{1}{2\pi \times 300 \times 25.5 \times 10^{-12}} \approx 21 \text{ MHz}$$

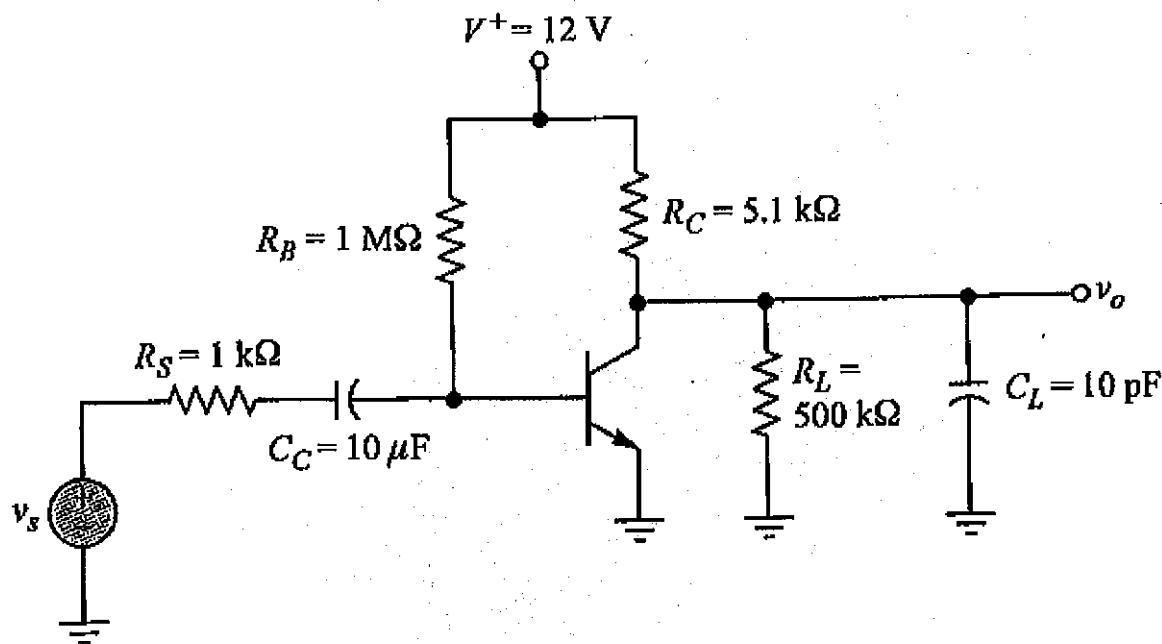19. What is the lower cutoff frequency ( $f_L$ ) of the common emitter amplifier shown below? Assume  $\beta=100$ ,  $V_{BE(on)}=0.7$ ,  $V_A=\infty$



- (1) ~0.016Hz  
 (2) ~5Hz  
 (3) ~0.3Hz  
 (4) ~50Hz  
 (5) ~1Hz  
 (6) None of the above

$$\text{Handwritten circuit diagram showing a source } v_s \text{ connected to the base of a transistor. The base is connected to ground through a resistor } R_B = 1 \text{ M}\Omega \text{ and to the collector through a resistor } R_C = 5.1 \text{ k}\Omega. \text{ The collector is connected to ground through a load resistor } R_L = 500 \text{ k}\Omega \text{ and a capacitor } C_L = 10 \text{ pF. A bypass capacitor } C_C = 10 \mu\text{F} \text{ is connected between the base and ground.}$$


$$r_T = \frac{V_T}{I_B} = \frac{0.025}{11.3 \times 10^{-6}} = 2212 \Omega$$

$$I_B = \frac{12 - 0.7}{1 \text{ M}\Omega} = \frac{11.3}{1 \text{ M}\Omega} = 11.3 \mu\text{A}$$

$$R_{\text{total}} = 2212 + 1000 = 3212$$


$$f_L = \frac{1}{2\pi \times 10 \times 10^6 \times 3212} = 5 \text{ Hz}$$

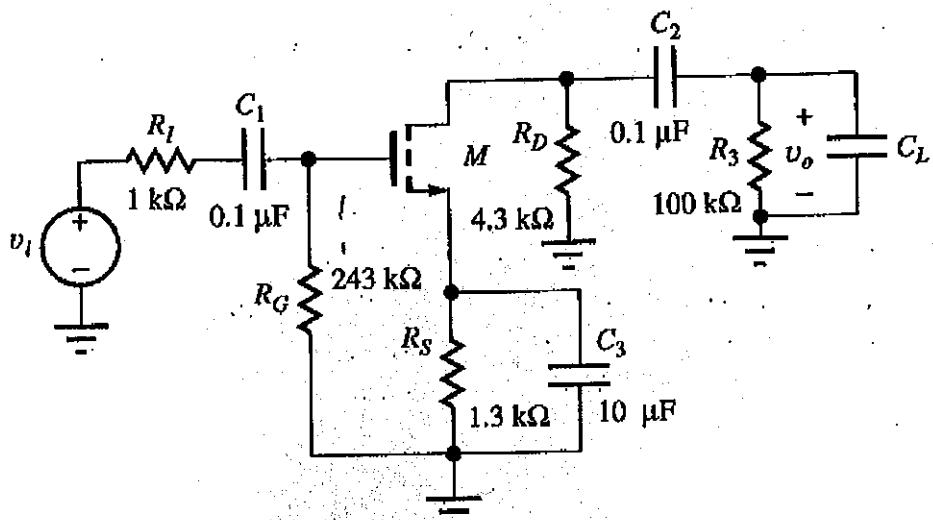20. The short circuit time constant associated with  $C_{gs}$  in the common source amplifier shown below is? (Assume  $C_{gs}=10\text{pF}$ )



- (1) ~2.5s      (2) ~5ns      (3) ~10ns      (4) ~10μs  
 (5) ~1ns      (6) None of the above

$$C_{gs} = 10 \text{ pF}$$

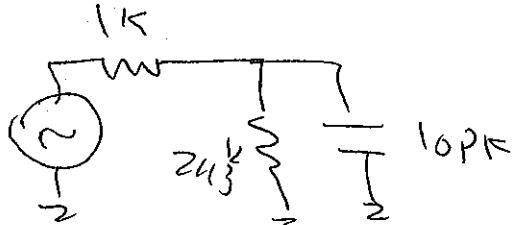

$$\tau = (1 \text{ K} \parallel 243 \text{ k}) \cdot 10 \text{ pF} = 1 \text{ K} \cdot 10 \text{ pF} = 10 \text{ ns}$$