

1. A silicon sample at room temperature has an intrinsic carrier concentration of  $n_i = 5 \times 10^9 \text{ cm}^{-3}$ . It is doped with  $N_D = 6.1 \times 10^{16}$  arsenic atoms/cm<sup>3</sup> and  $N_A = 6 \times 10^{12}$  boron atoms/cm<sup>3</sup>. The electron mobility is measured as  $\mu_n = 1600 \text{ cm}^2/\text{V}\cdot\text{s}$  and the hole mobility is  $\mu_p = 480 \text{ cm}^2/\text{V}\cdot\text{s}$ .

Is this material p or n-type?  b


- (a) p-type (b) n-type

What is the hole concentration?  a

- (a)  $p = 4.1 \times 10^2 / \text{cm}^3$  (b)  $p = 6 \times 10^{12} / \text{cm}^3$  (c)  $p = 6.1 \times 10^{16} / \text{cm}^3$   
 (d)  $p = 2.5 \times 10^{19} / \text{cm}^3$

If an external electrical field of  $E = 90 \text{ V/cm}$  is applied across this silicon sample, what is the electron current density in this material?  b

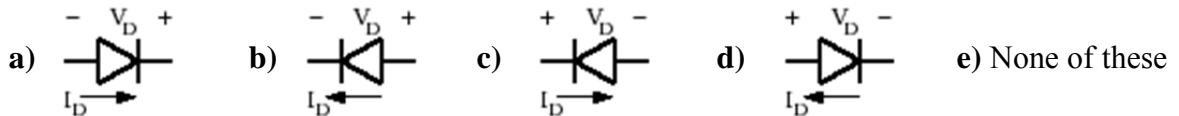- (a)  $j_n = 2.8 \times 10^{-12} \text{ A/cm}^2$  (b)  $j_n = 1404 \text{ A/cm}^2$  (c)  $j_n = 15.6 \text{ A/cm}^2$   
 (d)  $j_n = 3.2 \times 10^{-14} \text{ A/cm}^2$




2. Which figure above shows the correct sign convention for both positive diode voltage and positive diode current?  b

3. A diode has  $I_S = 10^{-10} \text{ A}$  and the nonideality factor,  $n = 2$ . What is the diode voltage if the diode current is 40A?  $V_T = 0.025 \text{ V}$  for room temperature.  c


- (a)  $V_D = 3.2 \text{ V}$  (b)  $V_D = -5.1 \text{ V}$  (c)  $V_D = 1.34 \text{ V}$  (d)  $V_D = 0 \text{ V}$

4. Find the current in each diode in the circuit shown below using the constant voltage drop model with  $V_{on} = 0.70 \text{ V}$ . d

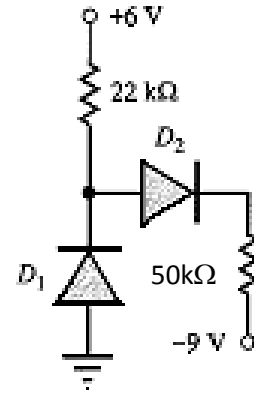- (a)  $I_{D1} = 0 \text{ A}$ ,  $I_{D2} = 0 \text{ A}$       (b)  $I_{D1} = 0.199 \text{ mA}$ ,  $I_{D2} = 0 \text{ A}$   
 (c)  $I_{D1} = 0 \text{ A}$ ,  $I_{D2} = 0.3 \text{ mA}$       (d)  $I_{D1} = 0 \text{ A}$ ,  $I_{D2} = 0.199 \text{ mA}$




5. In the circuit below, the Zener diode has a breakdown voltage  $V_{Z0} = |V_{BR}| = 8.0 \text{ V}$  and a measurement has shown that  $V_Z = 8.6 \text{ V}$  when  $I_Z = 30 \text{ mA}$ . What is the value of  $V_{out}$  when  $R_L$  becomes infinitely large? c

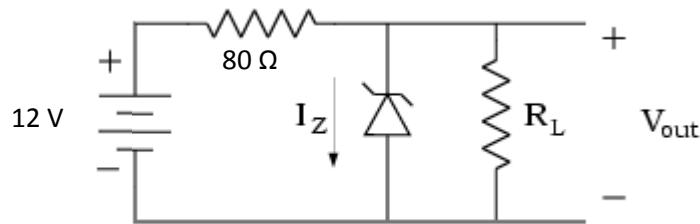

- (a)  $V_{out} = 0 \text{ V}$       (b)  $V_{out} = 8.2 \text{ V}$       (c)  $V_{out} = 8.8 \text{ V}$       (d)  $V_{out} = 8.4 \text{ V}$







6. The Zener diode in the circuit has an equivalent resistance  $R_Z = 10 \Omega$ . From the diode data sheet we find that if the voltage across the Zener diode is  $6.4 \text{ V}$  at  $I_Z = 20 \text{ mA}$ . Determine the output voltage  $V_{out}$  c

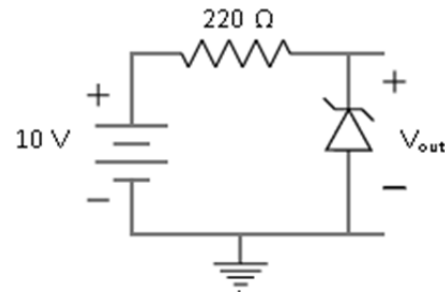- (a)  $V_{out} = 6.4 \text{ V}$       (b)  $V_{out} = 6.2 \text{ V}$   
 (c)  $V_{out} = 6.365 \text{ V}$       (d)  $V_{out} = 10 \text{ V}$



7. Which one of the curves shown below represents the transfer characteristics ( $v_{in}$ - $v_{out}$ ) for the Clipper Circuit? (Assume constant voltage drop model with  $V_{on} = 0.7V$ )








Answer:       **b**      

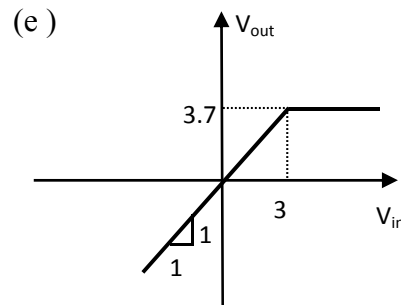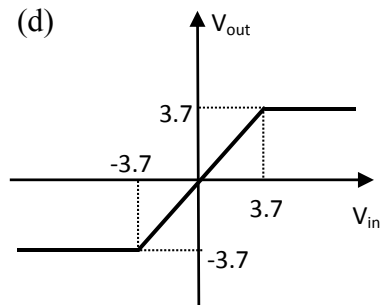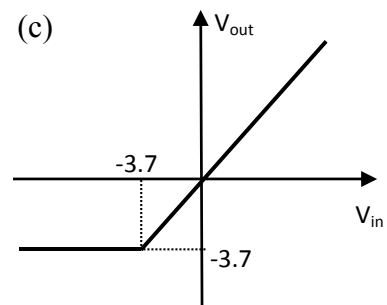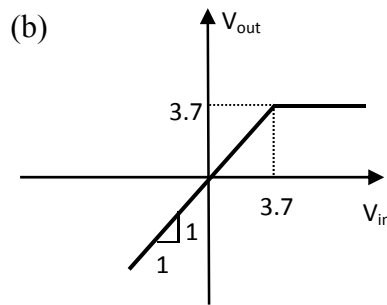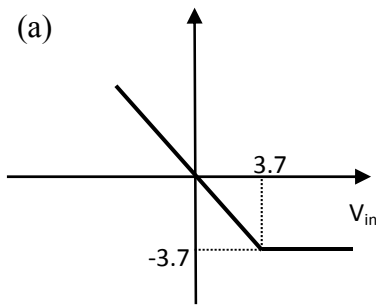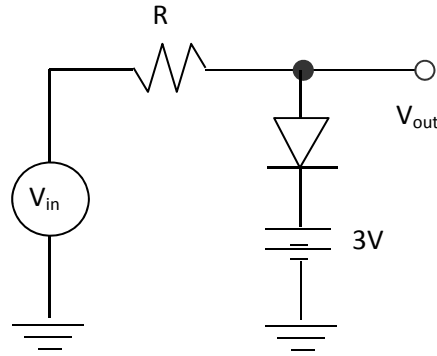

(f) None of these



8. For the circuit shown below, if a sinusoidal wave is applied to the input, which one of the curves is the output voltage? (Assume  $V_{on}=0.7V$ )

Answer:       e      

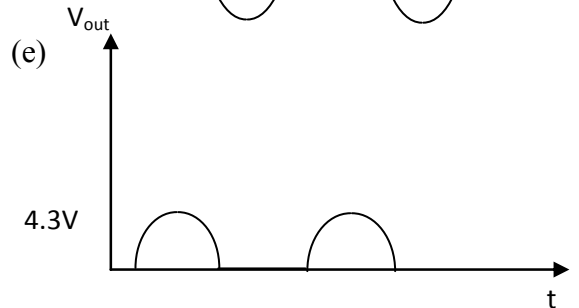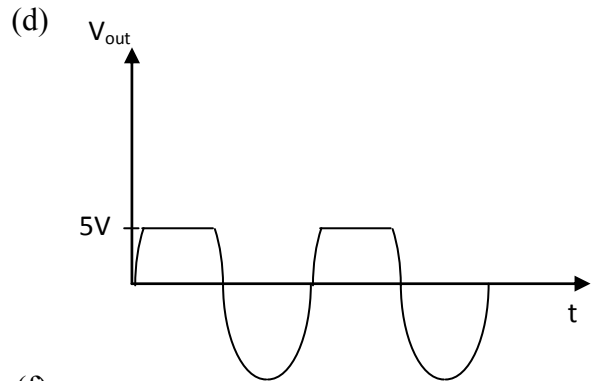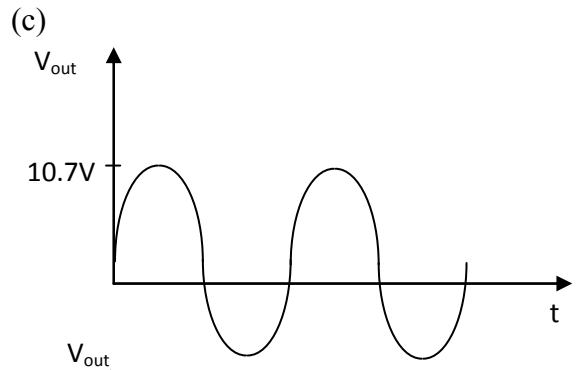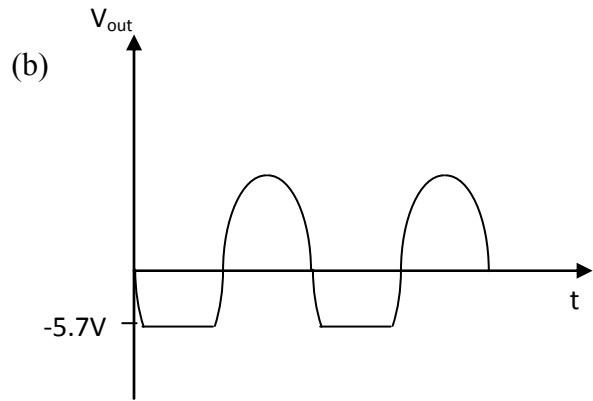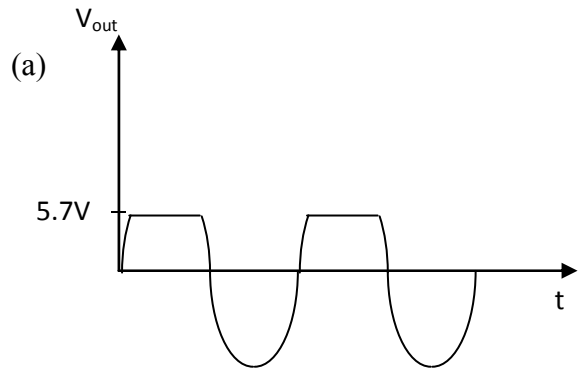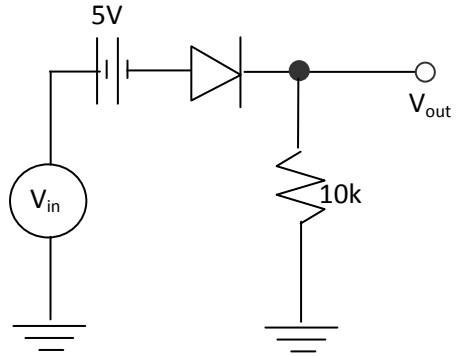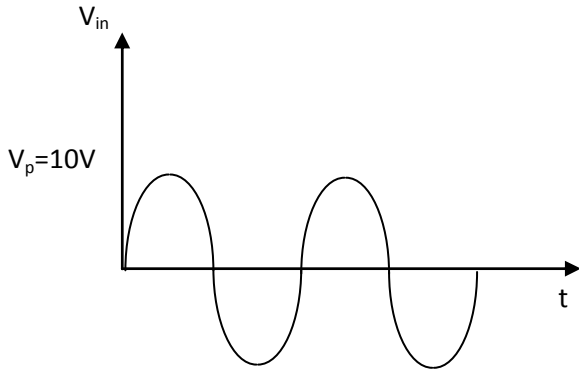

(f) None of these

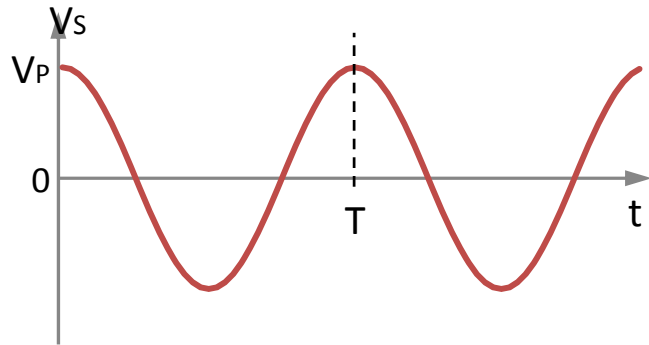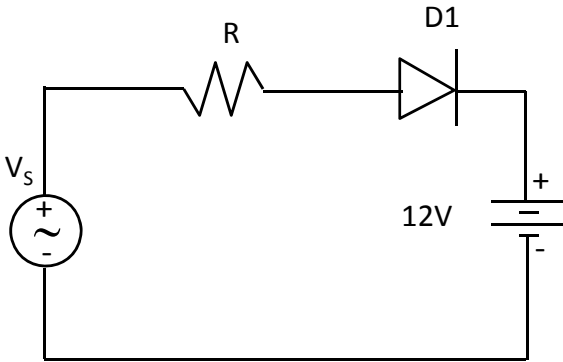9. You are asked to design an automotive battery charger using a 60 Hertz sinusoidal voltage source described by,  $V_s = V_p \cos(\omega t) = V_p \cos(2\pi 60t)$ . In order to prevent the battery from overheating, the charging cycle must be kept to 1/3 of a cycle (i.e. charging only occurs for 1/3 of the 60 Hertz cycle). Using the ideal diode model, determine the proper value of  $V_p$  to achieve the design goal.   **b**  



(a)  $V_p = 12\sqrt{2}V$

(b)  $V_p = 24V$

(c)  $V_p = 36V$

(d)  $V_p = 28V$