

HOMEWORK #10

7.24

$$g_{m1} = 1 \text{ mA/V}$$

$$R_o = 400 \text{ k}\Omega$$

$$V_{tn} = 0.5 \text{ V}$$

$$V_A' = 5 \text{ V}(\mu\text{m})^{-1}$$

$$k_n' = 400 \mu\text{A/V}^2$$

$L, W/L, V_{d2}, I?$

$$V_{ov} = 0.2 \text{ V}$$


$$g_{m1} = I / (V_{ov}/2) \Rightarrow I = g_m \cdot \frac{V_{ov}}{2} = 1 \text{ mA/V} \cdot \frac{0.2 \text{ V}}{2} = 0.1 \text{ mA} //$$

$$R_o = (g_{m2} r_{o2}) r_{o1} = \frac{1}{V_A'^2} \cdot \frac{V_{ov}}{2} \cdot I_D$$

$$\Rightarrow 400 \text{ k} = \frac{1}{V_A'^2} \cdot \frac{V_{ov}}{2} \cdot I_D$$

$$\Rightarrow |V_A| = 2 \text{ V} \rightarrow V_A \text{ (NMOS)}$$
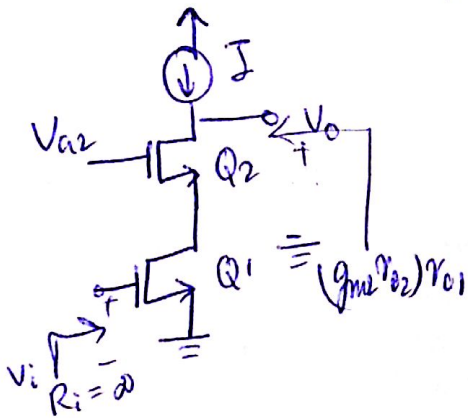
$$L = \frac{2}{5(\mu\text{m})^{-1}} = 0.4 \mu\text{m} \quad (\sim 2 \times 0.18 \mu\text{m})$$



$$V_{ov} = V_{ds} - V_t$$

$$\Rightarrow V_{ds} = V_{ov} + V_t = 0.2 + 0.5 = 0.7 \text{ V}$$

Q1 → Saturation (minimum voltage across Q1 & Q2 i.e. edge of saturation operation)

$$\Rightarrow V_{d1} = 0.2 \text{ V} = V_{s2}$$

$$\Rightarrow V_{d2} = 0.7 + V_{s2} = 0.7 + 0.2 = 0.9 \text{ V} //$$


$$I = \frac{1}{2} k_n' \frac{W}{L} V_{ov}^2 \left(1 + \frac{V_{ds}}{V_A}\right)$$

$$0.1 \text{ mA} = \frac{1}{2} \cdot 400 \frac{\mu\text{A}}{\text{V}^2} \cdot \left(\frac{W}{L}\right) (0.04) \left(1 + \frac{0.2}{2}\right)$$

$$\frac{1}{2} = \left(\frac{W}{L}\right) (0.04) (1.1) \Rightarrow \frac{W}{L} = \frac{100}{2.2 \times 4} \approx 12 //$$

$$V_o = V_{d2} = V_{ds2} + V_{s2} = 0.2 + 0.2 = 0.4 \text{ V} //$$

7.50

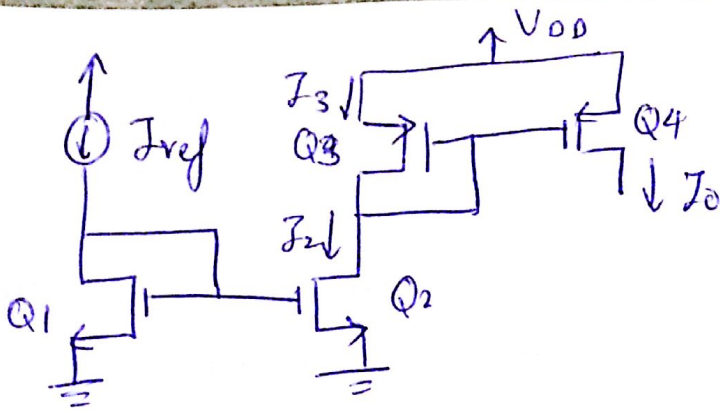

$$I_2 = \frac{(W/L)_2}{(W/L)_1} I_{ref} = I_3$$

$$I_4 = \frac{(W/L)_4}{(W/L)_3} I_3 \Rightarrow I_0 = \frac{(W/L)_4}{(W/L)_3} \frac{(W/L)_2}{(W/L)_1} I_{ref}$$


7.51

$\mu_n C_{ox} = 200 \mu A V^{-2}$, $\mu_p C_{ox} = 80 \mu A V^{-2}$, $|V_{th}| = 0.6 V$

$V_{An} = 10 V/\mu m$, $|V_{Ap}| = 12 V/\mu m$

$L = 0.8 \mu m$

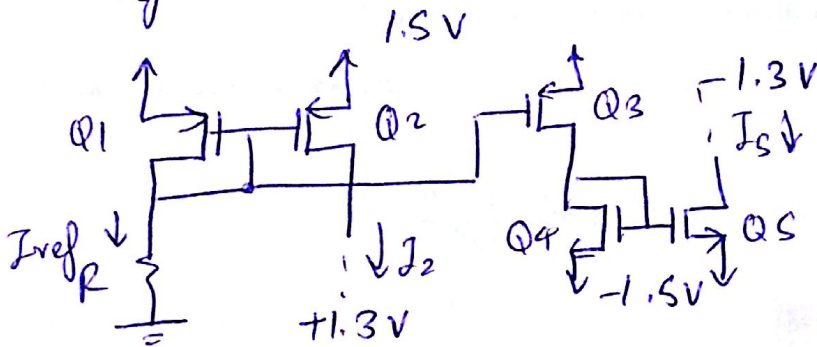$I_{ref} = 20 \mu A$, $I_2 = 100 \mu A$, $I_3 = I_4 = 20 \mu A$, $I_5 = 50 \mu A$



$$I_2 = \frac{(W/L)_2}{(W/L)_1} I_{ref} \Rightarrow \frac{W_2}{W_1} = \frac{I_2}{I_{ref}} = \frac{100 \mu}{20 \mu} = 5 \dots \textcircled{1}$$

$$I_3 = I_4 = \frac{(W/L)_3}{(W/L)_1} I_{ref} \Rightarrow \frac{W_3}{W_1} = \frac{I_3}{I_{ref}} = \frac{20 \mu}{20 \mu} = 1 \dots \textcircled{2}$$

$$I_5 = \frac{W_5}{W_4} I_4 \Rightarrow \frac{W_5}{W_4} = \frac{I_5}{I_4} = \frac{50 \mu}{20 \mu} = 2.5 \dots \textcircled{3}$$

Q2 → Edge of Saturation $V_{SD} = |V_{ov}| = 0.2 V$

$$\Rightarrow V_{SG2} - |V_{tp}| = 0.2 \Rightarrow V_{SG2} = 0.8 V$$

$$\Rightarrow V_{G2} = 1.5 - 0.8 = 0.7 V = V_{O1}$$

$$R = \frac{V_{O1}}{I_{ref}} = \frac{0.7}{20 \mu} = \frac{0.35}{10 \mu} = \frac{0.35}{10^{-5}} = 0.35 \times 10^5 \Omega = 35 k\Omega //$$

$$I_2 = 100 \mu A = \frac{1}{2} \mu_p C_{ox} \frac{W_2}{L} V_{ov}^2$$

Q2, Q5
edge of saturation

$$\Rightarrow 100 \mu = \frac{1}{2} \frac{80 \mu}{0.2 \mu} W_2 (0.1)^2$$

$$\Rightarrow 2.5 = W_2 \frac{0.1}{2} \Rightarrow W_2 = 50 \mu m$$

$$W_2/W_1 = 5 \Rightarrow W_1 = 10 \mu m = W_3$$

$$\Rightarrow V_{GS} = 0.2 V \Rightarrow V_{DS} = V_{GS} = V_{DQ1} = 0.2 + 1.5 = 1.7 V$$

$$0.2 = V_{GS} - 0.6 \Rightarrow V_{GS} = 0.8 \Rightarrow V_{GS} = V_{GSP} = V_{DQ4} = -0.7 V$$

$$I_5 = 50 \mu A = \frac{1}{2} \mu_n C_{ox} \frac{W_5}{L} V_{ov}^2$$

$$\Rightarrow 50 \mu = \frac{1}{2} \frac{200 \mu}{0.2 \mu} W_5 (0.1)^2 \Rightarrow W_5 = 10 \mu m, W_4 = \frac{W_5}{2.5} = 4 \mu m$$

$$r_{o2} = \frac{V_{AQP}}{I_2} = \frac{12 \times 0.8}{100 \mu} = 9.6 \times 10^4 = 96 K\Omega //$$

$$r_{o3} = \frac{V_{AN}}{I_5} = \frac{10 \times 0.8}{50 \mu} = \frac{80}{50 \mu} = \frac{16}{100 \mu} = 160 K\Omega //$$

7.59 Textbook for the figure

$$V_{E1} = V_{E3} = V_{E4} = 10V$$

$$V_{B1} = 9.3V = V_{B3} = V_{B4}$$

$$V_{C1} = V_{B1} = 9.3V$$

