

HOMEWORK #12

9.1

$$g_m = 1 \text{ mA/V}^{-1}$$

$$r_o = \infty$$

(Using $\pi^2 \approx 10$)


$$f_{p2} \approx f_c = 20 \text{ Hz} = \frac{g_m}{2\pi C_s}$$

↳ dominant pole

$$\Rightarrow C_s = \frac{g_m}{2\pi f_c} = \frac{1 \times 10^{-3}}{2\pi \times 20}$$

$$\approx \frac{\pi^2 \times 10^{-5}}{2\pi \times 20} \approx \frac{\pi}{4} \times 10^{-5}$$
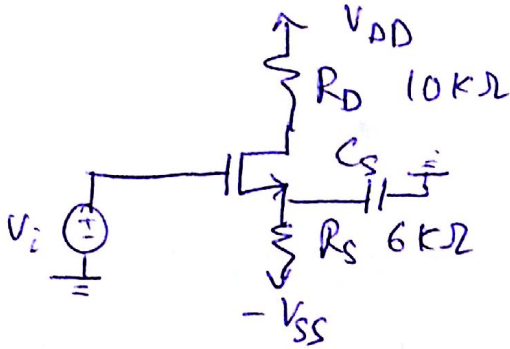
$$= 0.77 \times 10^{-5} \text{ s} = \boxed{7.7 \mu\text{F}}$$




$$A_{mid} = \frac{g_m R_D}{1 + g_m R_S}$$

$$= \frac{1 \times 10}{1 + 1 \times 6} = \frac{10}{7} = \boxed{1.43 \text{ V/V}}$$

9.3

$$g_m = 5 \text{ mA/V}^{-1}$$

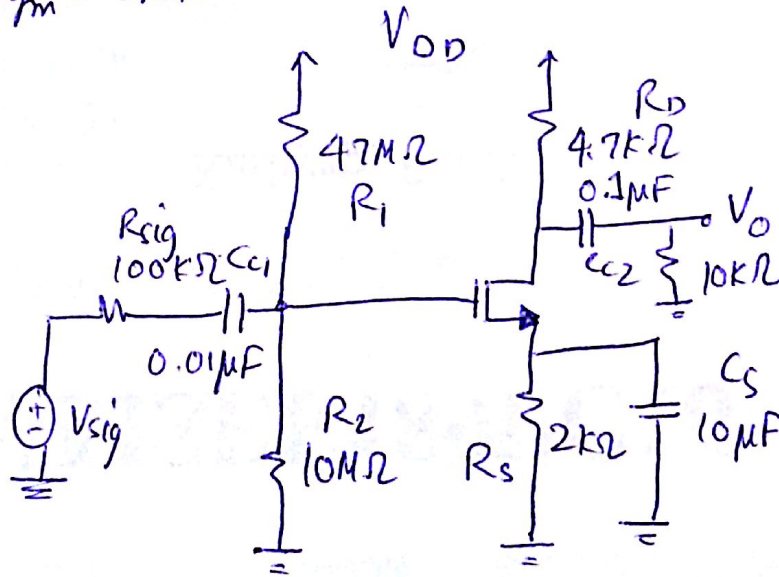

$$A_{mid} = - \frac{R_{in}}{R_{in} + R_{sig}} \cdot \frac{g_m (R_D || R_o || R_L)}{1 + g_m R_S}$$

$R_{in} || R_1 || R_2 \approx 8 \text{ M}\Omega$

$$= - \frac{8 \text{ M}}{8 \text{ M} + 100 \text{ k}} \cdot \frac{5 \text{ m} (4.7 \text{ k} || 10 \text{ k} || \overset{\text{high}}{\infty})}{1 + 5 \times 2}$$

≈ 1

$$\approx \frac{5 \text{ m} (3 \text{ k})}{15} \approx 100 \text{ V/V}$$

$$f_{p2} \left(\frac{\approx f_L}{\text{not low}} \right) = \frac{g_m}{2\pi C_S} = \frac{5\text{m}}{2\pi \times 10\mu} = \frac{5 \times 10^{-3}}{2\pi \times 10^{-5}} = \frac{500}{2} \approx \underline{\underline{75\text{Hz}}}$$

$$f_{p1} = \frac{1}{2\pi C_1 (R_a + R_{sig})} = \frac{1}{2\pi \times 10^{-8} \times (8\text{M} + 100\text{k})}$$


$$\hookrightarrow R_{in} = R_1 || R_2 = \frac{10^8}{2\pi \times 8\pi} = \frac{10^8}{16\pi} \approx \underline{\underline{2\text{Hz}}}$$

$$f_{p3} = \frac{1}{2\pi C_2 (R_D + R_L)} = \frac{1}{2\pi \times 10^{-7} \times (4.7\text{k} + 10\text{k})} = \frac{10^7}{2\pi \times 15\pi}$$

$$= \frac{10^7}{2\pi \times 15\pi} \approx \underline{\underline{100\text{Hz}}}$$

$$f_L \approx \sum f_{pi}$$

$$\approx 180\text{Hz}$$

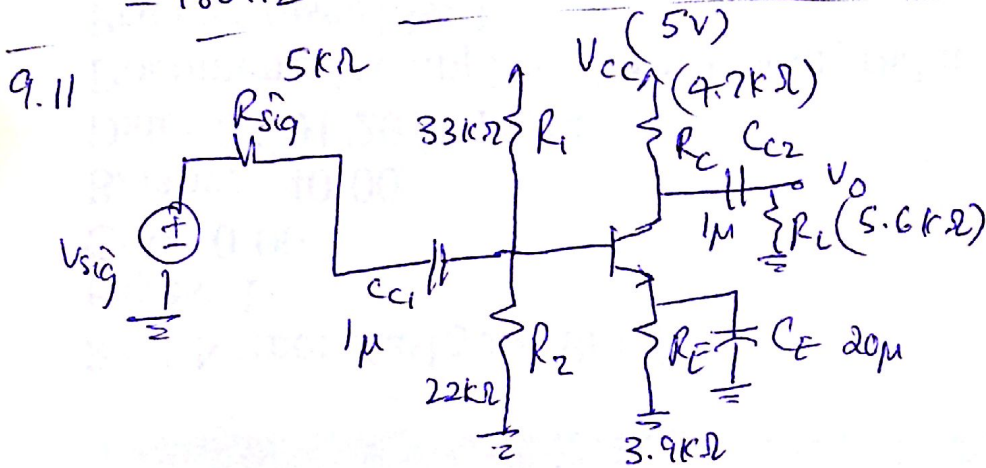

$$I_E \approx 0.3\text{mA}$$

$$\beta = 120$$

$$r_n = \frac{\beta}{g_m} \rightarrow \frac{0.3}{25} = 12\text{m}\Omega$$

$$= \frac{\beta V_T}{I_E}$$

$$= \frac{120 \times 25\text{mV}}{0.3\text{mA}}$$

$$\approx 40\text{k}\Omega$$

$$R_{in} = (R_1 || R_2) || R_n = R_B || r_n$$

$$= 33\text{k} || 22\text{k} || 40\text{k} = 10\text{k}\Omega$$

$$r_o = \frac{V_A}{I_E} \rightarrow \infty$$

$$A_m = \frac{-R_{in}}{R_{in} + R_{sig}} g_m (R_C || R_E || r_o)$$

$$= \frac{10\text{k}}{(10+5)\text{k}} \times 12\text{m} \times (4.7 || 5.6\text{k}) = \frac{2}{3} \times 12 \times 2.5 = \underline{\underline{-20\text{V/V}}}$$

$$f_{p1} = \frac{1}{2\pi C_{c1} (R_{in} + R_{sig})} = \frac{10^6}{2\pi \times (10\text{k} + 5\text{k})} = \frac{10^6}{3\pi} \approx 10\text{Hz}$$


$$f_{p2} = \frac{\beta}{2\pi C_{c2} [r_n + R_B || R_{sig}]}$$

$$= \frac{3 \times 10^8}{2\pi \times 20 \times [40\text{k} + 33\text{k} || 22\text{k} || 5\text{k}]} \approx 22\text{Hz}$$

9.11 (Cont'd) $f_{p3} = \frac{1}{2\pi C_2(R_E + R_C)} = \frac{10^6}{2\pi \times (4.7k + 5.6k)} = \frac{10^8 \times 2}{2\pi \times 10^4} = \frac{10^4}{\pi} \approx 15 \text{ Hz}$


$f_L \approx \sum f_{pi} = 47 \text{ Hz} //$

9.41

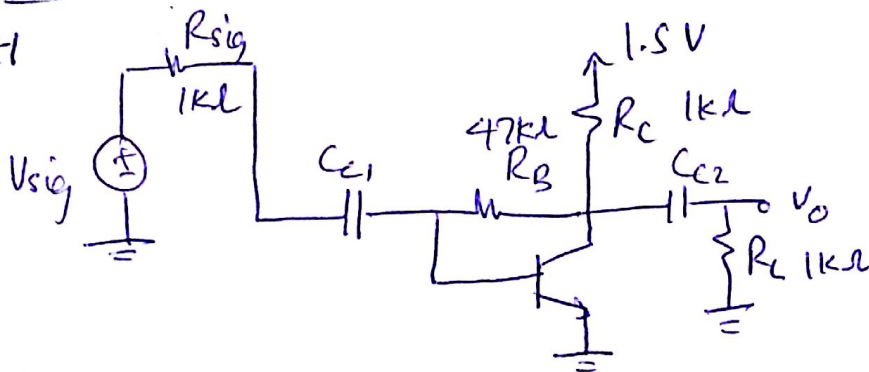

$\beta = 100$
 $C_{\mu} = 0.5 \text{ pF}$
 $f_T = 600 \text{ MHz}$
 Assume $V_{BE(on)} = 0.7 \text{ V}$

(a)

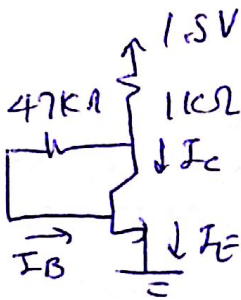

$1.5 \text{ V} = I_E (1k\Omega) + 47k\Omega (I_B)$
 -0.7 V

$0.8 \text{ V} = I_B (101) + 47k\Omega I_B$

$\Rightarrow I_B = \frac{0.8 \text{ mA}}{148} = 5.4 \mu\text{A}$


$I_E = 0.55 \text{ mA} // \approx I_C$

(b) $g_m = \frac{I_C}{V_T} = \frac{0.55 \text{ mA}}{25 \text{ mV}} = 21.8 \text{ mS}$

$r_n = \frac{\beta}{g_m} = \frac{100}{21.8} = 4.6 \text{ k}\Omega$

(c) $A_{mid} = \frac{R_{in}}{R_{in} + R_{sig}} g_m (R_C || R_L) = \frac{4.6 \text{ k}\Omega}{5.6 \text{ k}\Omega} \times 21.8 \text{ mS} \times \frac{1 \text{ k}\Omega}{2} = 8.95 \text{ V/V}$
 (Note: R_{in} is neglected R_B)

(d)

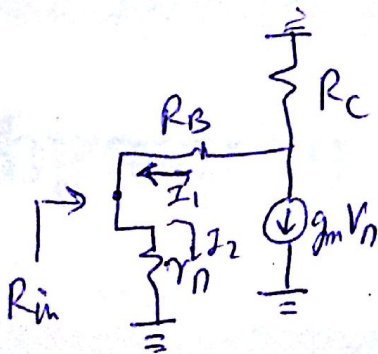


$R_{in} = \frac{V_n}{-I_1 + I_2}$
 was neglected
 $\Rightarrow i_e R_C + i_b R_B + \frac{(i_b + I)}{\beta} r_n = 0$
 $\Rightarrow V_n = i_e R_C + i_b R_B + i_b r_n$
 $R_{in} = \frac{V_n}{I} = (\beta + 1) R_C + R_B + r_n$
 $\approx 150 \text{ k}\Omega$

(e) $A_{mid} \rightarrow g_m(R_E || R_L) \approx 11 V/V$
 r_n neglected ≈ 95

(f) $C_{in} = C_{\mu}(1 + g_m R_L) + C_n = 5pF + 0.8pF(1 + 21.8m \cdot \frac{1k}{2}) \approx 15pF //$

$f_T = \frac{g_m}{2\pi(C_n + C_{\mu})} \Rightarrow C_n = \frac{g_m}{2\pi f_T} - C_{\mu} = \frac{21.8m}{2\pi \times 600M} - 0.8pF \approx 5pF //$

(g) $f_H \approx \frac{1}{2\pi C_{in} R_{sig}}$
 $r_n || R_B || R_{sig} = 1k\Omega$ $\Rightarrow f_H = \frac{10^9}{2\pi \times 15p \times 1k} = \frac{1000 \times 10^6}{2\pi \times 15} = 10MHz$
($f_T = 60f_H$... make sure)

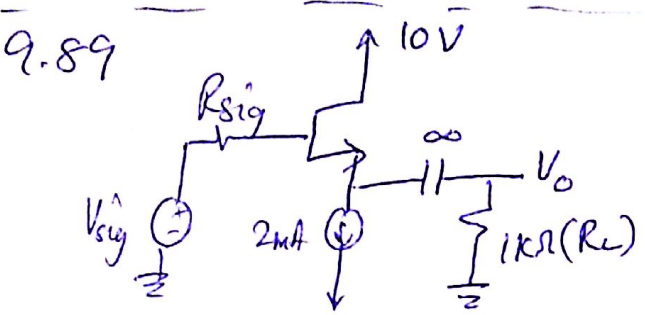

$\beta = 100$ $f_T = 400MHz$ $C_{\mu} = 2pF$
 $g_m = \frac{I_C}{V_T} = \frac{2m}{25m} = 80mS$
 $r_n = \frac{\beta}{g_m} = 1.25k\Omega$
 $A = \frac{R_{in}}{R_{in} + R_{sig}} \cdot g_m R_L$

(a) $R_{sig} = 1k\Omega$

$A = \frac{1.25k \cdot 80mS \cdot 1k\Omega}{1.25k + 1k} = 44.44 V/V$
 $f_H = \frac{1}{2\pi R_{sig}' C_{in}} = \frac{1}{2\pi \times 0.5k \times 192p} = 1.65MHz$
 $R_{sig}' = r_n || R_{sig} = 1.25k || 1k$
 $C_{in} = C_n + C_{\mu}(1 + g_m R_L)$
 $C_n = \frac{g_m}{2\pi f_T} - C_{\mu} = \frac{80mS}{2\pi \cdot 400M} - 2p = (31.8 - 2)pF \approx 30pF$
 $\Rightarrow C_{in} = 30p + 2p(1 + 80) = 192pF //$

(b) $R_{sig} = 10k\Omega$

$A = \frac{1.25}{1.25 + 10} \times 80 = 8.8 V/V$
 $f_H = \frac{1}{2\pi R_{sig}' C_{in}} = \frac{1}{2\pi \times 1k \times 192p} = 0.8MHz$
 $10k || 1.25k$

(c) $R_{sig} = 100k\Omega$

$A = \frac{1.25}{101.25} \times 80 = 0.98 V/V$
 $f_H = \frac{1}{2\pi \times R_{sig}' C_{in}} \approx 0.8MHz$
 $100k || 1.25k$