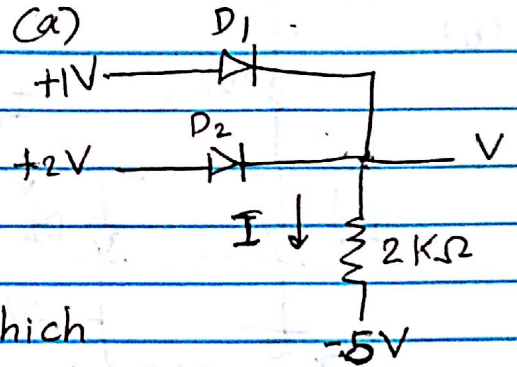


ECE 255 HW3

4.3

D_2 is Forward biased.
 so $V = 2V$ and that
 makes D_1 Reverse biased.




If D_1 is FB, then $V = 1V$, which
 makes D_2 FB as well making $V = 2V$
 which creates ambiguity. so this assumption does
 not work.

$$\underline{V = 2V} \quad I = \frac{2 - (-5)}{2K} = \frac{7}{2K} = \underline{3.5 \text{ mA}}$$

$$\underline{V = 1V} \quad I = \frac{5 - 1}{2K}$$


$$= \frac{4}{2K} = \underline{2 \text{ mA}}$$

(b)

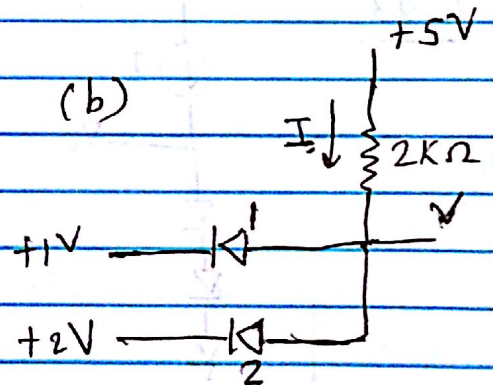

4.9

(a)

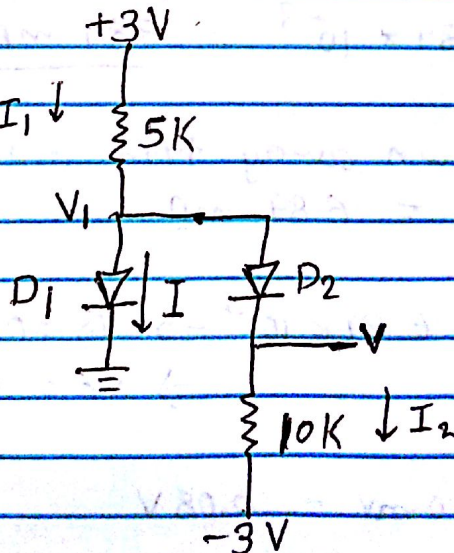

If D_1 is FB, $V_1 = 0V$.


if D_2 is FB, $V = V_1 = 0V$

$$I_2 = \frac{(3)}{10K} = \underline{0.3 \text{ mA}}$$

$$I_1 = \frac{3}{5K} = 0.6 \text{ mA}$$

hence $\underline{I = 0.3 \text{ mA}}$ (KCL)

(b)

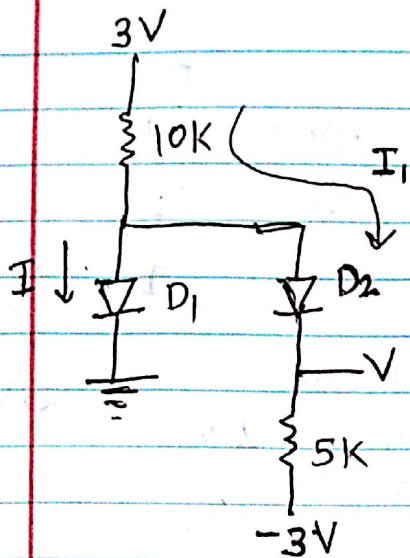

D_1 and D_2 can't be FB as before
~~since~~,

D_1 will be RB, D_2 will be FB


$$\underline{I = 0} \quad I_1 = \frac{3 - (-3)}{(10+5)K}$$

$$= \frac{6}{15K} = 0.4 \text{ mA}$$

$$\frac{V - (-3)}{5K} = 0.4$$

$$V + 3 = 2 \Rightarrow \underline{V = -1V}$$

4.23

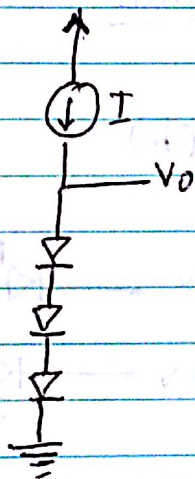

3 identical diodes. so $V_D = \frac{V_O}{3} = \frac{2.4}{3}$
 $= 0.8V$

$$I_D = I_S (e^{V_D/V_T} - 1) = I$$

$$I = 10^{-16} (e^{0.8/0.025}) \text{ can be neglected}$$


$$= 7.89 \times 10^{-3} = \underline{7.89 \text{ mA}}$$

1 mA is drawn away from output terminal,
 $I = 7.89 - 1 = 6.89 \text{ mA}$

$$I = I_S (e^{V_D/0.025}) = 6.89 \times 10^{-3} \Rightarrow V_D = 0.796 \text{ V}$$

$$\Rightarrow V_O = 3V_D = \underline{2.39 \text{ V}}$$

4.26

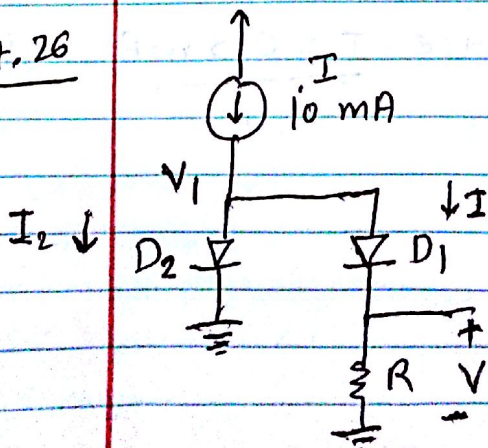

$$V = 80 \text{ mV} = 0.08 \text{ V}$$

$$\text{For } D_2, I_2 = I_S e^{V_1/V_T}$$

For, D_1

$$I_1 = I_S e^{(V_1 - 0.08)/V_T}$$

$$\downarrow I_1 = 0.01 - I_2$$

$I_2 \downarrow$

Identical diodes, so same I_s for D_1 & D_2

$$\frac{I_1}{I_2} = e^{(-0.08/V_T)} \quad \text{and } I_1 + I_2 = 0.01$$

$$= 0.04$$

$$I_1 = \underline{0.4 \text{ mA}}$$

$$I_2 (0.04) + I_2 = 0.01$$

$$I_2 (1.04) = 0.01$$


$$\Rightarrow I_2 = 0.0096 \text{ A}$$

$$= \underline{9.6 \text{ mA}}$$

$$V = I_1 R \Rightarrow R = \frac{0.08}{0.4} = 0.2 \text{ k}\Omega$$

$$\approx 200 \Omega$$

4.59

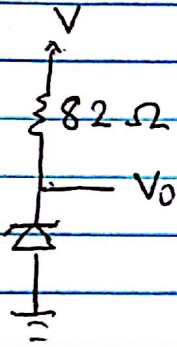

$$\Delta V = 1 \text{ V}, \quad V_0 = V_{z0} + I_z R_z \quad R_z = 5 \Omega$$

$$\Delta V_0 = \frac{R_z}{R_z + 82} (\Delta V)$$

$$= 1 \left(\frac{5}{5 + 82} \right) = \underline{0.057 \text{ V}}$$

change in regulated output voltage