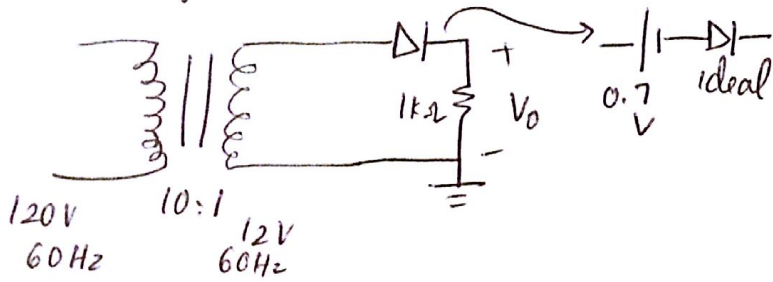


HOMEWORK #4

4.68 half-wave rectifier circuit



$V_p = 12\sqrt{2} \text{ V}$ as $V_{rms} = 12 \text{ V}$
 ↳ of input

V_p of rectified voltage = $12\sqrt{2} - 0.7$
 $= 16.97 - 0.7$
 $= 16.27 \text{ V}$

The diode is on for $V_{ip} > V_D$
 i.e. $V_p \sin \omega t > V_D$

from the graph
 $t_1 = \left(\frac{\sin^{-1} \frac{V_D}{V_p}}{\omega} \right) = \frac{2.36}{\omega}$


Diode conducts for $\pi/2 - 2t_1$

$C = \frac{1}{2f} \left(1 - \frac{2 \sin^{-1}(V_D/V_p)}{\pi} \right)$

% it's ON = $\frac{C}{T} = Cf = \frac{1}{2} \left(1 - \frac{2 \sin^{-1}(V_D/V_p)}{\pi} \right)$
 $= 48.69\%$


Average o/p voltage = $\frac{1}{\pi} V_p - \frac{V_D}{2} = \frac{16.97}{2} - \frac{0.7}{2} \approx 8.05 \text{ V}$

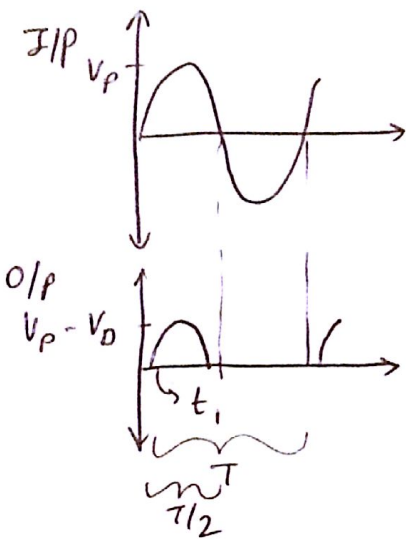Average current through the load = $\frac{8.05}{1k\Omega} = 8.05 \text{ mA}$



4.74 +ve half cycle diodes D1 and D2 conduct
 -ve D3 and D4


Consider diode D1, D2 in +ve half cycle

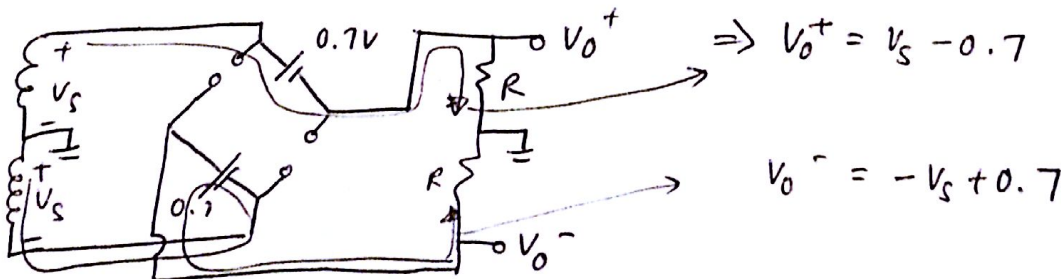

$\Rightarrow V_o^+ = V_s - 0.7$

$V_o^- = -V_s + 0.7$

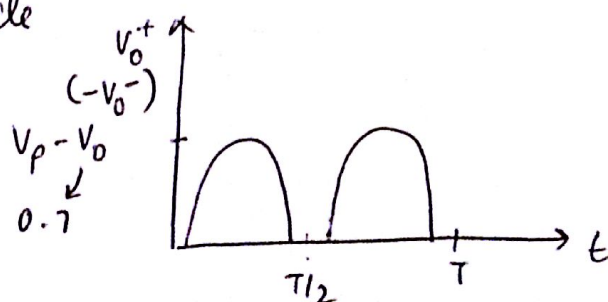Similarly for -ve half cycle
 \Rightarrow Waveforms are like




Average output $v_o^+ = \langle v_s \rangle - 0.7$
 $= \frac{2}{\pi} v_p - 0.7$ over $T/2$ period $\Rightarrow \sim$ full wave rectifier

$\Rightarrow v_{s \text{ or } v_p} = \frac{\pi}{2} (\bar{v}_o^+ + 0.7)$ Given $\bar{v}_o^+ = \bar{v}_o^- = 15V$
 $= \pi/2 (15.7) = 24.7V$

Consider the +ve half cycle, D2 and D4 in RB


Forward voltage $= v_s + v_o = 2v_s - v_o = 2v_s - 0.7 = 48.7V //$

4.88 $-20V \leq v_i \leq 20V$

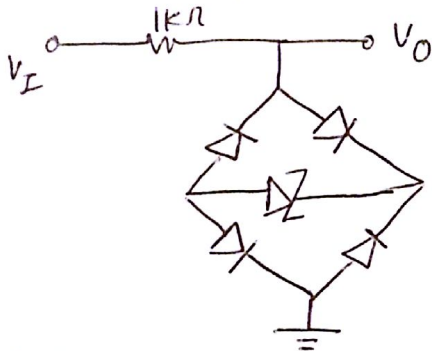


$v_o = 0.7V$
 $v_z = 8.2V$

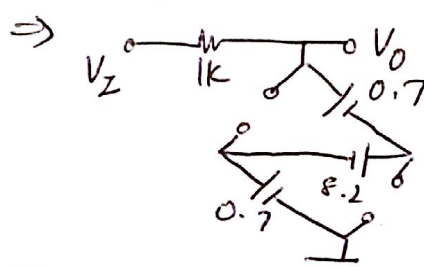For $v_i > 0$ & $v_i < (0.7 + 8.2 + 0.7)V$




$\hookrightarrow 9.6$
 $\Rightarrow v_i = v_o$
 & $v_i > 9.6V$
 $v_o = 9.6V$

(not to scale)


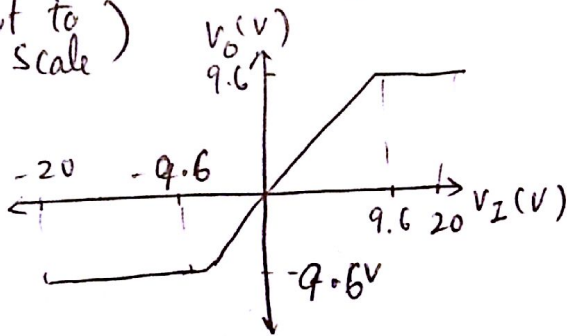


For $v_i < 0$ & $v_i > -9.6V$


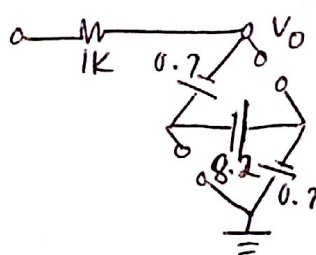


$\Rightarrow v_o = v_i$
 $v_i < -9.6V$
 $\Rightarrow v_o = -9.6V$

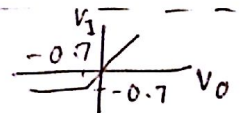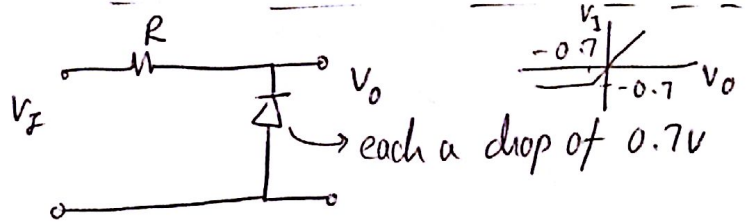4.90 (a) $-0.7V$ and above \rightarrow
 $R = 10k\Omega$



(b) $-2.1V$ and above \rightarrow

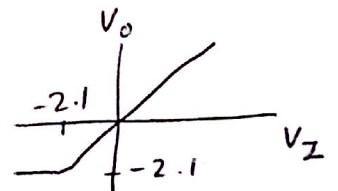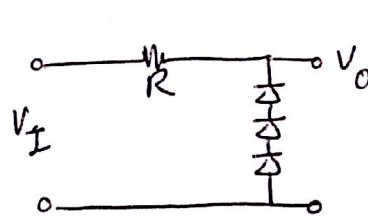

(c) $\pm 1.4V$ \rightarrow

