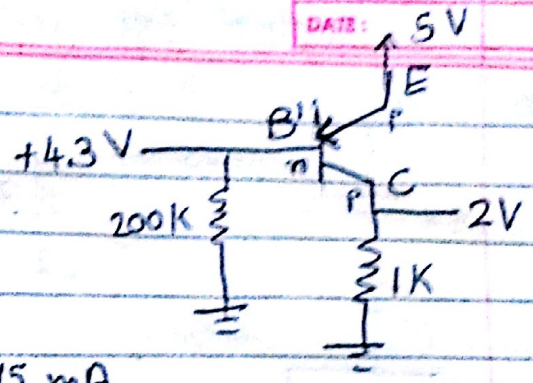


6.29

(a) $V_{EB} = 0.7V$ (FB) } FA
 $V_{BC} = 2.3V$ (RB)




$$I_C = \frac{2}{1k} = 2mA, \quad I_B = \frac{4.3}{200k} = 0.0215mA$$

$$\beta = \frac{I_C}{I_B} = \frac{2}{0.0215} = 93$$

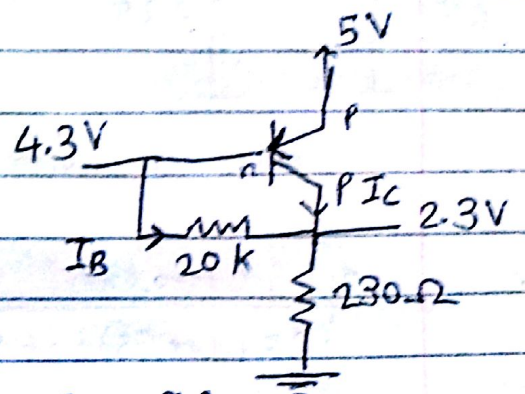(b) based upon the biasing: FA

$$I_E = I_B + I_C = \frac{2.3}{230} = 10mA$$



$$I_B = \frac{4.3 - 2.3}{20k} = \frac{2}{20k} = 0.1mA, \quad I_C = 9.9mA$$


$$\beta = \frac{I_C}{I_B} = \frac{9.9}{0.1} = 99$$

(c) $I_E = \frac{10 - 7}{1k} = 3mA$

~~assuming FA~~, $\frac{6.3 - V_C}{100k} = I_B$

$$\frac{V_C}{1k} = I_B + I_C = I_E = 3mA \Rightarrow V_C = 3V$$

$$I_B = \frac{3.3}{100k} = 0.033mA$$

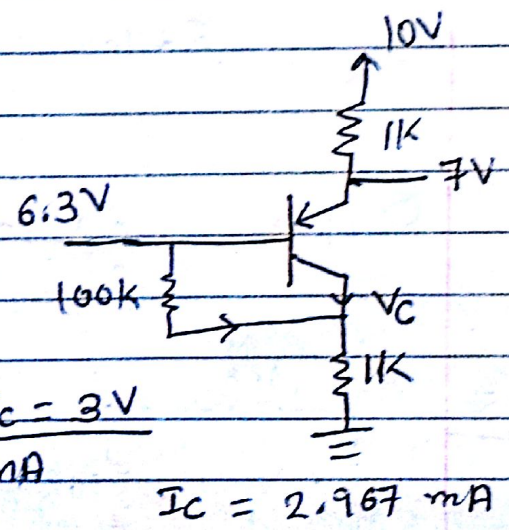

$$I_C = 2.967mA$$

$$\beta = \frac{I_C}{I_B} = \frac{2.967}{0.033} = 89.9$$

6.3

$$I_C = I_S e^{V_{BE}/V_T}, \quad 100\mu A = I_S e^{28}$$

$$\Rightarrow I_S = 6.9 \times 10^{-17} A \quad (\text{sat}^n \text{ current})$$

with E Junction 32 times larger, $I_S = 32 \times 6.9 \times 10^{-17}$

Since $I_S \propto A_E$

$$I_C = I_S e^{V_{BE}/V_T} = 220.8 \times 10^{-17} e^{28} = 3200\mu A$$

$$1mA = 220.8 \times 10^{-17} e^{V_{BE}/V_T} \Rightarrow 4.5 \times 10^{11} = e^{V_{BE}/V_T}$$

$$\Rightarrow V_{BE} = 0.67V$$

6.17 $\beta = 100$, $I_S = 10^{-15} \text{ A}$

Assuming FA, $V_E = -0.7 \text{ V}$
 $I_E = 3 \text{ mA}$


$$I_C = \alpha I_E = \frac{\beta}{\beta + 1} I_E$$
$$= \frac{100}{101} (3) = \underline{2.97 \text{ mA}}$$

$$V_C = 10 - 2\text{k}(2.97 \text{ mA}) = \underline{4.06 \text{ V}}$$

$$V_{CE} = 4.76 \text{ V} > 0.2 \text{ V}$$

$$I_B = I_E - I_C = 3 - 2.97 = \underline{0.03 \text{ mA}}$$

confirm: FA

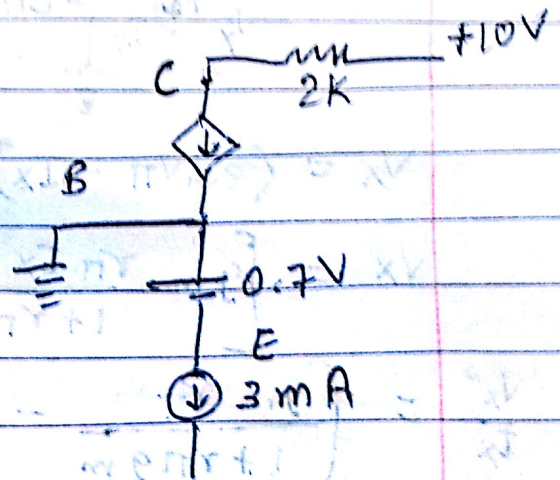

6.28

(a) $V_{EB} = 0.7$ (FB)

assume FA $I_1 = \frac{10.7 - 0.7}{10k}$

$= 1 \text{ mA}$

$\beta \rightarrow \text{large } I_C \approx I_E = 1 \text{ mA}$

$\frac{V_2 - (-10.7)}{10k} = 1 \text{ mA}$

$V_2 + 10.7 = 10 \Rightarrow V_2 = \underline{-0.7 \text{ V}}$

$V_{CE} = V_2 - 0.7 = -0.7 - 0.7 = -1.4 < -0.2 \text{ V}$

confirmed: FA

(b) $V_{CB} = -4 - (-2.7) = -4 + 2.7 = -1.3$ (RB)

assume FA

$I_C = \frac{-4 - (-10)}{2.4k} = \frac{6}{2.4k} = 2.5 \text{ mA}$

$I_E \approx I_C = 2.5 \text{ mA}$

$\frac{12 - V_3}{5.6k} = 2.5$

$\Rightarrow \underline{V_3 = -2 \text{ V}}$

$V_{EB} = -2 - (-2.7) = 0.7 \text{ V}$ (FB)

$V_{CE} = -4 - (-2) = -2 \text{ V} < -0.2 \text{ V}$

confirmed: FA

(c) β large, assume $I_B \approx 0 \Rightarrow \underline{V_4 = 1 \text{ V}}$

assume FA

$I_C = \frac{0 - (-10)}{10k} = 1 \text{ mA}$

$I_S \approx I_E \approx I_C = \underline{1 \text{ mA}}$

$V_{CB} = -1 \text{ V}$ (RB)

$$\text{cd) } I_B \approx 0, \quad V_7 = 0.7V, \quad V_7 \approx V_B$$

$$V_{BE} = 0.7V \quad (\text{given}) \quad (\text{FB})$$

$$\frac{10 - V_7}{15K} = I_E \quad \text{and} \quad \frac{V_E - (-10)}{5K} = I_E = I_6$$

$$\frac{10 - V_7}{15} = \frac{V_E + 10}{5} \Rightarrow 10 - V_7 = 3V_E + 30$$

$$V_{BE} = 0.7 \Rightarrow V_7 - V_E = 0.7$$

$$10 - [V_E + 0.7] = 3V_E + 30$$

$$\Rightarrow 9.3 = 4V_E + 30 \Rightarrow \underline{V_E = -5.175V}$$

$$\underline{V_7 = V_B = -4.475V}$$

$$I_6 = \frac{10 - 5.175}{5K}$$

$$= \underline{0.965 \text{ mA}}$$

6.35 (a) $V_B = 0V$, $V_{BE} = 0.8V$ \Rightarrow $V_E = -0.8V$

$$I_E = \frac{-0.8 - (-1.5)}{2.2k} = \underline{0.318 \text{ mA}}$$

$$\alpha = \frac{\beta}{\beta + 1} \quad I_C = \alpha I_E \approx \frac{50}{51} (0.318) = \underline{0.312 \text{ mA}}$$

$$= \frac{50}{51} \quad \frac{1.5 - V_C}{2.2k} = I_C \Rightarrow V_C = 1.5 - 0.69 = \underline{0.81 V}$$

$$I_B = \frac{I_C}{\beta} = \frac{0.312}{50} = 6.24 \times 10^{-3} \text{ mA}$$

(b) $V_B = 0V$, $V_{EB} = 0.8V$, $V_E = 0.8V$

$$\frac{1.5 - 0.8}{1k} = \underline{0.7 \text{ mA}} = I_E \quad I_C = \alpha I_E = \frac{0.69}{\text{mA}}$$

$$\frac{V_C + 1.5}{1} = 0.69 \Rightarrow \underline{V_C = -0.81 V} \quad I_B = \frac{I_C}{\beta} = \frac{13.8 \times 10^{-3}}{\text{mA}}$$

$$\underline{cc)} \quad \underline{V_B = 1V} \quad V_{EB} = 0.8 \Rightarrow \underline{V_E = 1.8V}$$

$$I_E = \frac{3 - 1.8}{1.1K} = \underline{1.2 mA} \quad I_C = \alpha I_E = \underline{1.18 mA}$$

$$V_C = I_C (0.56) = \underline{0.66 V}$$

$$I_B = \frac{I_C}{\beta} = \underline{23.6 \times 10^{-3} mA}$$

$$\underline{cd)} \quad \underline{V_B = 1.5V} \quad V_{BE} = 0.8 \Rightarrow \underline{V_E = 0.8V}$$

$$I_E = \frac{V_E}{0.47} = \underline{1.7 mA} \quad I_C = \alpha I_E = \underline{1.67 mA}$$

$$\frac{3 - V_C}{1} = 1.67 \Rightarrow \underline{V_C = 1.33V}$$

$$I_B = \frac{I_C}{\beta} = \underline{33.4 \times 10^{-3} mA}$$