

HW 7 sol<sup>n</sup> ECE 255

5.5  $V_{DS}$  is kept small,  $r_{DS} = \frac{1}{\mu_n C_{ox} (W/L) (V_{GS} - V_t)}$   
 $k_n' = \mu_n C_{ox} = 400 \text{ mA/V}^2$   
 max allowed voltage  $1.8 \text{ V} = V_{GS}$ ,  $r_{DS} \rightarrow \text{min.}$   
 $50 \text{ } 200 = \frac{1}{400 \times 10^6 \times W \times (1.8 - 0.4)} \Rightarrow W = 1.6 \times 10^{-6} \text{ m}$   
 $= 1.6 \text{ } \mu\text{m}$

$1 \text{ k}\Omega = \frac{1}{400 \times 10^6 \times \frac{1.6}{0.18} \times (V_{GS} - 0.4)} \Rightarrow V_{GS} - 0.4 = 0.28$   
 $\Rightarrow V_{GS} = 0.12 \text{ V}$   
 range of  $V_{GS}$   $(0.12, 1.8) \text{ V}$ ,  $W = 1.6 \text{ } \mu\text{m}$

5.9  $V_{GS} > V_t$  (on),  $V_{OV} = V_{GS} - V_t = 2.5 - 1 = 1.5 \text{ V}$   
 when  $V_{OV} = V_{DS} \Rightarrow \text{sat}^n$  (entered into)  
 $I_D = \frac{1}{2} k_n V_{OV}^2 = \frac{1}{2} (1) (1.5)^2 = 1.125 \text{ mA}$

5.14  $t_{ox} = 9 \text{ nm}$ ,  $\mu_n = 500 \text{ cm}^2/\text{V}\cdot\text{s}$ ,  $V_t = 0.7 \text{ V}$ ,  $W/L = 10$   
 (a)  $V_{GS} = 5 \text{ V}$ ,  $V_{DS} = 1 \text{ V}$   $C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = \frac{3.45 \times 10^{-11}}{9 \times 10^{-9}} = 3.8 \text{ mF/m}^2$   
 $V_{GS} > V_t$   $V_{OV} = 5 - 0.7 = 4.3 \text{ V}$   
 $V_{DS} < V_{OV} \Rightarrow \text{linear reg}^n$   
 $I_D = k_n \left[ V_{OV} - \frac{1}{2} V_{DS} \right] V_{DS}$   $\mu_n C_{ox} \frac{W}{L} = 500 \times 10^4 \times 3.8 \times 10^{-3} \times 10 = 1.9 \times 10^{-4} = 1.9 \text{ mA/V}^2$   
 $= 1.9 \left( 4.3 - \frac{1}{2} (1) \right) = 7.22 \text{ mA}$

(b)  $V_{GS} = 2 \text{ V}$ ,  $V_{DS} = 1.3 \text{ V}$ ,  $V_{GS} > V_t$ ,  $V_{OV} = 1.3 \text{ V} = V_{DS} \Rightarrow \text{sat}^n$   
 $I_D = \frac{1}{2} k_n V_{OV}^2 = \frac{1}{2} (1.9) (1.3)^2 = 1.6 \text{ mA}$

(c)  $V_{GS} = 5 \text{ V}$ ,  $V_{DS} = 0.2 \text{ V}$ ,  $V_{GS} > V_t$ ,  $V_{OV} = 4.3 \text{ V} > V_{DS} \Rightarrow \text{linear}$   
 $I_D = k_n \left[ V_{OV} - \frac{1}{2} V_{DS} \right] V_{DS}$   
 $= 1.9 (4.3 - 0.1) 0.2 \approx 1.6 \text{ mA}$

(d)  $V_{GS} = V_{DS} = 5 \text{ V}$ ,  $V_{OV} = 4.3 \text{ V} < V_{DS} \Rightarrow \text{sat}^n$   
 $I_D = \frac{1}{2} k_n V_{OV}^2 = \frac{1}{2} (1.9) (4.3)^2 = 17.56 \text{ mA}$




5.21  $I_D = K_n [V_{OV} - \frac{1}{2}V_{DS}] V_{DS}$   
 $\frac{I_{D1}}{I_{D2}} = \frac{(V_{OV1} - \frac{1}{2}V_{DS1}) V_{DS1}}{(V_{OV2} - \frac{1}{2}V_{DS2}) V_{DS2}} \Rightarrow \frac{6\mu}{16\mu} = \frac{V_{OV1} - 0.05}{V_{OV2} - 0.05}$   
 $\frac{6}{16} = \frac{V_{GS1} - V_t - 0.05}{V_{GS2} - V_t - 0.05} = \frac{1.95 - V_t}{3.95 - V_t}$   
 $1.48 - 0.375V_t = 1.95 - V_t \Rightarrow V_t(0.625) = 0.47$   
 $\Rightarrow \underline{V_t = 0.752 V}$

$K_n' = 50 \mu A/V^2$   
 $6\mu A = 50 \frac{W}{L} [1.198] 0.1 \Rightarrow \frac{W}{L} \approx 10$

$V_{GS} = 3V > V_t$ .  $V_{OV} = 2.248V > V_{DS} \Rightarrow$  linear reg<sup>n</sup>  
 $I_D = 500 [2.248 - 0.075] 0.15 \Rightarrow I_D = \underline{0.16 mA}$  (162.97  $\mu A$ )

$V_{GS} = 3V$ , drain: pinch off,  $\Rightarrow$  edge of sat<sup>n</sup>  $\Rightarrow V_{DS} = V_{OV}$   
 $V_{OV} = 2.248 = V_{DS}$   $I_D = \frac{1}{2} K_n (V_{OV})^2 = \frac{1}{2} 500 (2.248)^2$   
 $= \underline{1.26 mA}$

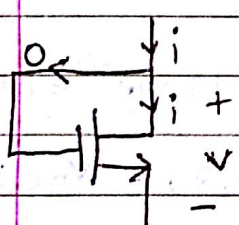5.24 (a)  $V_{GS} = V_{DS}$  since  $V_G = V_D$  now.  $V_{GS} - V_t = V_{OV} < V_{DS}$   
 $\Rightarrow$  always sat<sup>n</sup> reg<sup>n</sup>



$i = \frac{1}{2} K_n' \frac{W}{L} V_{OV}^2$   $V_{OV} = V_{GS} - V_t$   
 $= V_{DS} - V_t = V - V_t$

if PMOS,  $V_{GS} = V_{DS}$  (-ve) and  $V_{DS} < V_{OV}$   
 $V_{OV} = V_{SD} - |V_{tp}|$

so ultimately,  $i = \frac{1}{2} K_n' \frac{W}{L} (V - |V_{tp}|)^2$

(b)  $V = |V_t| + V_{OV}$  (sat<sup>n</sup>) differentiate the equation in part (a)  
 $\frac{\partial i}{\partial V} = \frac{1}{2} K_n' \frac{W}{L} 2(V - |V_t|) = K_n' \frac{W}{L} V_{OV}$   
 $\Rightarrow r = \frac{1}{\left[\frac{\partial i}{\partial V}\right]} = \frac{1}{K_n' \frac{W}{L} V_{OV}}$

5.26  $V_{DS} = V_{GS}$  (sat<sup>n</sup>)  $I_D = \frac{1}{2} K_n (V_{OV})^2$   
 quadratic dependence on  $V_{GS} = V_{DS}$

