

SPICE PROJECT 3

Figure below shows two BJT current mirrors, the one on the left using 2 transistors and the one on the right using 3 with the third one being used to reduce the effect of finite β on the current mirror performance. Simulate the circuits for various values of β from 20-200 and plot I_o vs. β .

