

Name:

PUID:

ECE 559  
Exam 2

Time : 1 Hr 10 Mins

Total Points : 100

There are 6 pages in this exam booklet.

It is a closed book closed notes exam. No calculators permitted.

State clearly any assumptions you make.

Question 1:


(a) Draw a schematic of a 3-input NAND gate implemented using domino logic with a PMOS keeper. Clearly label the input and output signals in your schematic.

(15 points)

Input :  $a, b, c$

$$f = \overline{abc}$$
 
$$\bar{f} = \overline{\overline{abc}} = \overline{\overline{a + b + c}}$$



Name:

PUID:

(b) Suppose the three inputs in the schematic in part (a) have signal probabilities  $5/8$ ,  $1/2$  and  $2/5$  respectively. Determine the probability of switching for the output node, neglecting spatial and temporal correlation between the signals.

(15 Points)

Output switching happens

when  $a=0$  or  $b=0$  or  $c=0$

$$\begin{aligned} \therefore P &= 1 - P(a=1)P(b=1)P(c=1) \\ &= 1 - \frac{5}{8} \times \frac{1}{2} \times \frac{2}{5} = \frac{7}{8} \end{aligned}$$

Name:


PUID:

(c) Suppose all the NMOS transistors in your schematic of part (a) have  $W/L = 2$ . The output inverter has the logic threshold voltage ( $V_M$ ) =  $V_{dd}/2$ . If  $k_N = 2 \text{ mA/V}^2$ ,  $V_{tn} = 1 \text{ V}$ ,  $V_{tp} = -1 \text{ V}$  and  $V_{dd} = 5 \text{ V}$ , determine  $W/L$  for the keeper that ensures correct functionality of the circuit.

(40 points)

(Hints: To ensure correct functionality, worst case should be considered.  
It may be easier to solve the problem by breaking the keeper feedback.)

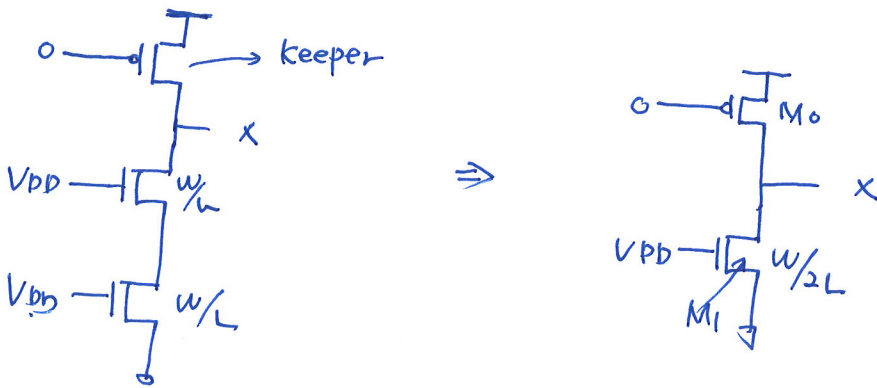1. The ~~worst~~ worst case: only one Nmos turns on
2. Feedback need to be broken.



~~x = n~~ For correct functionality,  $V_x \leq V_M = \frac{V_{DD}}{2}$

When  $V_x = \frac{V_{DD}}{2}$ ,

for  $M_0$ ,  $V_{gs} = -V_{DD}$ ,  $V_{ds} = -\frac{V_{DD}}{2} \Rightarrow$  linear  
( $\because V_{tp} = -1$ )

for  $M_1$ ,  $V_{gs} = V_{DD}$ ,  $V_{ds} = \frac{V_{DD}}{2} \Rightarrow$  linear

$$I_{M_0} = k_p \left(\frac{W}{L}\right)_p \left[ (5-1) \times 2.5 - 2.5^2 \right]$$

$$\leq I_{M_1} = k_n \left(\frac{W}{2L}\right)_n \times \left[ (5-1) \times 2.5 - 2.5^2 \right]$$



$$\therefore \left(\frac{W}{L}\right)_p \leq \frac{k_n}{k_p} = 2$$

Name:

PUID:

Question 2:  
For each of the circuits given below, determine if race condition exists in case of 0-0 overlap. Clearly explain your reasoning.


(a) (30 Points)

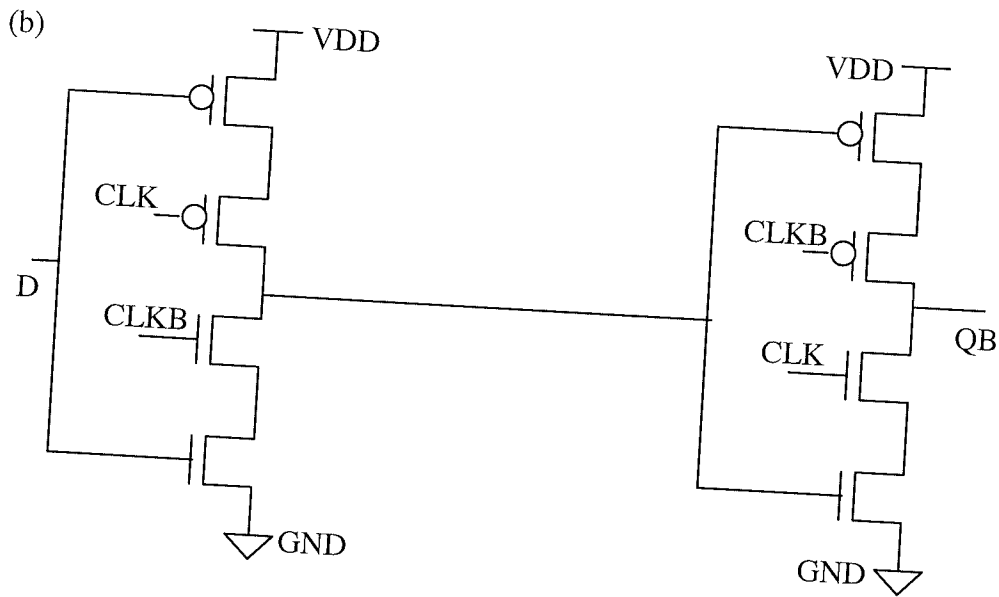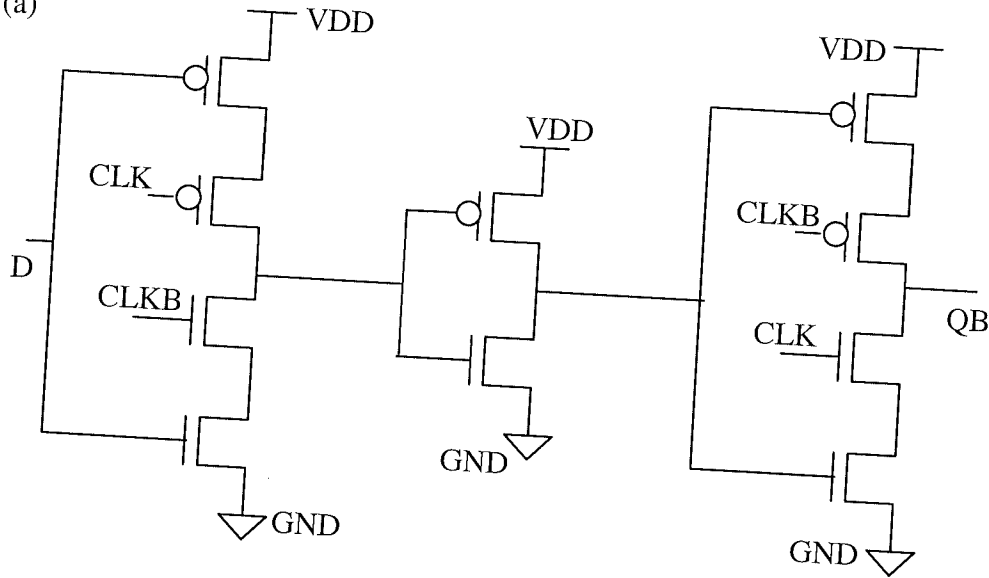

Name:


PUID:

(a)

 


race condition

(b)

 

No race condition

 

(This page has been intentionally left blank)