

# Homework 1


*ECE 559: MOS VLSI Design (Fall 2009)*

*ECE Department, Purdue University*

Assigned: 17-Sep-2009

Due: 24-Sep-2009

 **Problem 1 (Latchup):** The schematic and equivalent circuit of parasitic resistors and bipolar transistors in a CMOS is shown below. Here, the latchup is triggered at the point when the *npn*-transistor is turned on, i.e., the voltage drop across the resistor  $R_s$  is larger than the turn-on voltage of *npn*-transistor.



From this condition, derive the following inequality for the triggering of the latchup

$$\beta_{nnp} \beta_{pnp} > 1 + \frac{(\beta_{nnp} + 1)(I_{RS} + I_{RW} \beta_{pnp})}{(I_{dd} - I_{RS})}$$

Where  $\beta_{pnp}$  and  $\beta_{nnp}$  are the common-emitter current gains for the *pnp* and *nnp* transistors, respectively.

**Problem 2 (CMOS Limits):** Prove that the minimum  $V_{DD}$  for CMOS circuit operation is

$$V_{DD} |_{\min} = 2 \ln(2) \frac{KT}{q}.$$

**Problem 3 (Pseudo-NMOS):** Consider a pseudo-NMOS 2-input NAND gate as in the figure below. Use the following

$$V_{DD} = 1 \text{ V}$$

$$K_p' = \mu_p C_{ox} = 30 \text{e-}6 \text{ A/V}^2$$

$$K_n' = \mu_n C_{ox} = 60 \text{e-}6 \text{ A/V}^2$$

$$V_{tp} = -0.3 \text{ V}$$

$$V_{tn} = 0.3 \text{ V}.$$

Assume there is no sub threshold current, no body effect, and every transistor has ideal long-channel characteristics.

Determine the output voltage ( $V_{out}$ ) when the input voltage is i) 0 V ii) 0.2 V iii) 0.3 V iv) 0.4 V v) 0.7 V vi) 1 V.

