

# The Inverter

## References:

Adapted from: *Digital Integrated Circuits: A Design Perspective*, J. Rabaey, Prentice Hall © UCB

*Principles of CMOS VLSI Design: A Systems Perspective*,  
N. H. E. Weste, K. Eshraghian, Addison Wesley

# Regions of Operation

	Cutoff	Non-saturated	Saturated
p-device	$V_{gsp} > V_{tp}$ $V_{in} > V_{tp} + V_{DD}$	$V_{gsp} < V_{tp}$ $V_{in} < V_{tp} + V_{DD}$  $V_{dsp} > V_{gsp} - V_{tp}$ $V_{out} > V_{in} - V_{tp}$	$V_{gsp} = V_{tp}$ $V_{in} < V_{tp} + V_{DD}$  $V_{dsp} < V_{gsp} - V_{tp}$ $V_{out} < V_{in} - V_{tp}$
n-device	$V_{gsn} < V_{tn}$ $V_{in} < V_{tn}$	$V_{gsn} > V_{tn}$ $V_{in} > V_{tn}$  $V_{dsn} < V_{gs} - V_{tn}$ $V_{out} < V_{in} - V_{tn}$	$V_{gsn} > V_{tn}$ $V_{in} > V_{tn}$  $V_{dsn} > V_{gs} - V_{tn}$ $V_{out} > V_{in} - V_{tn}$


# Digital Gates

## Fundamental Parameters


- Area and Complexity
- Robustness and Reliability
- Performance
- Power Consumption
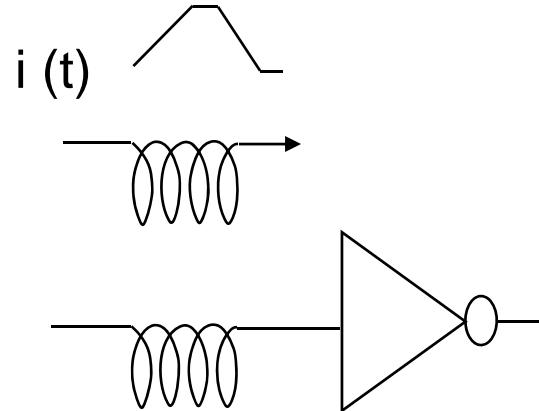
# Noise in digital Integrated Circuits


unwanted variations of voltages and currents at the logic nodes



(a) Inductive coupling

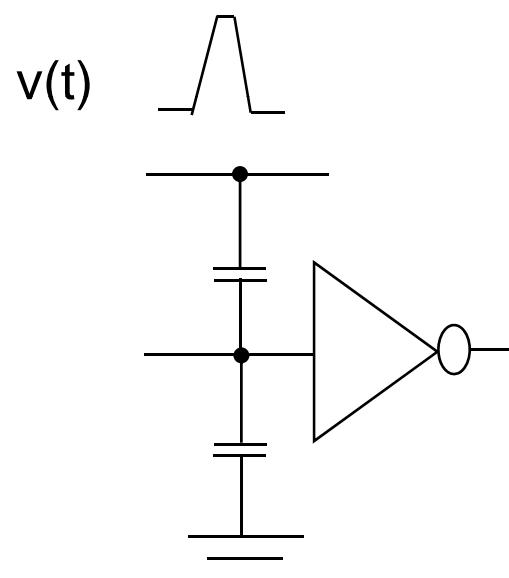


(b) Capacitive coupling

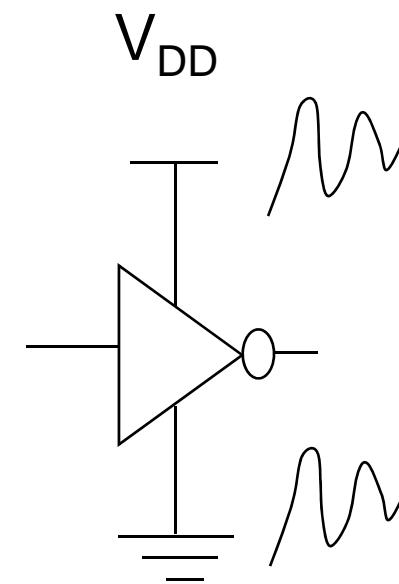


(c) Power and ground noise

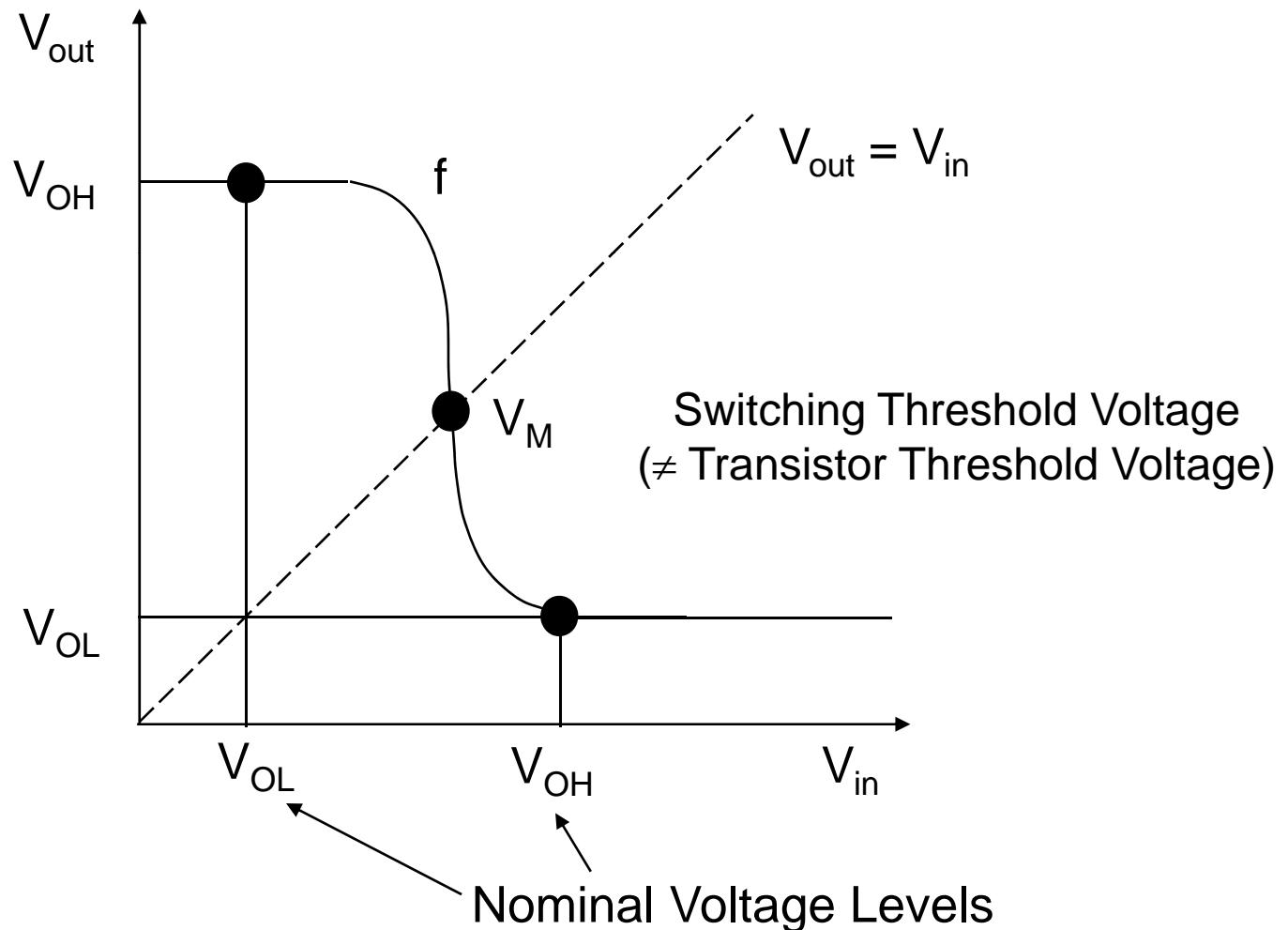
# DC Operation: Voltage Transfer Characteristic (VTC)



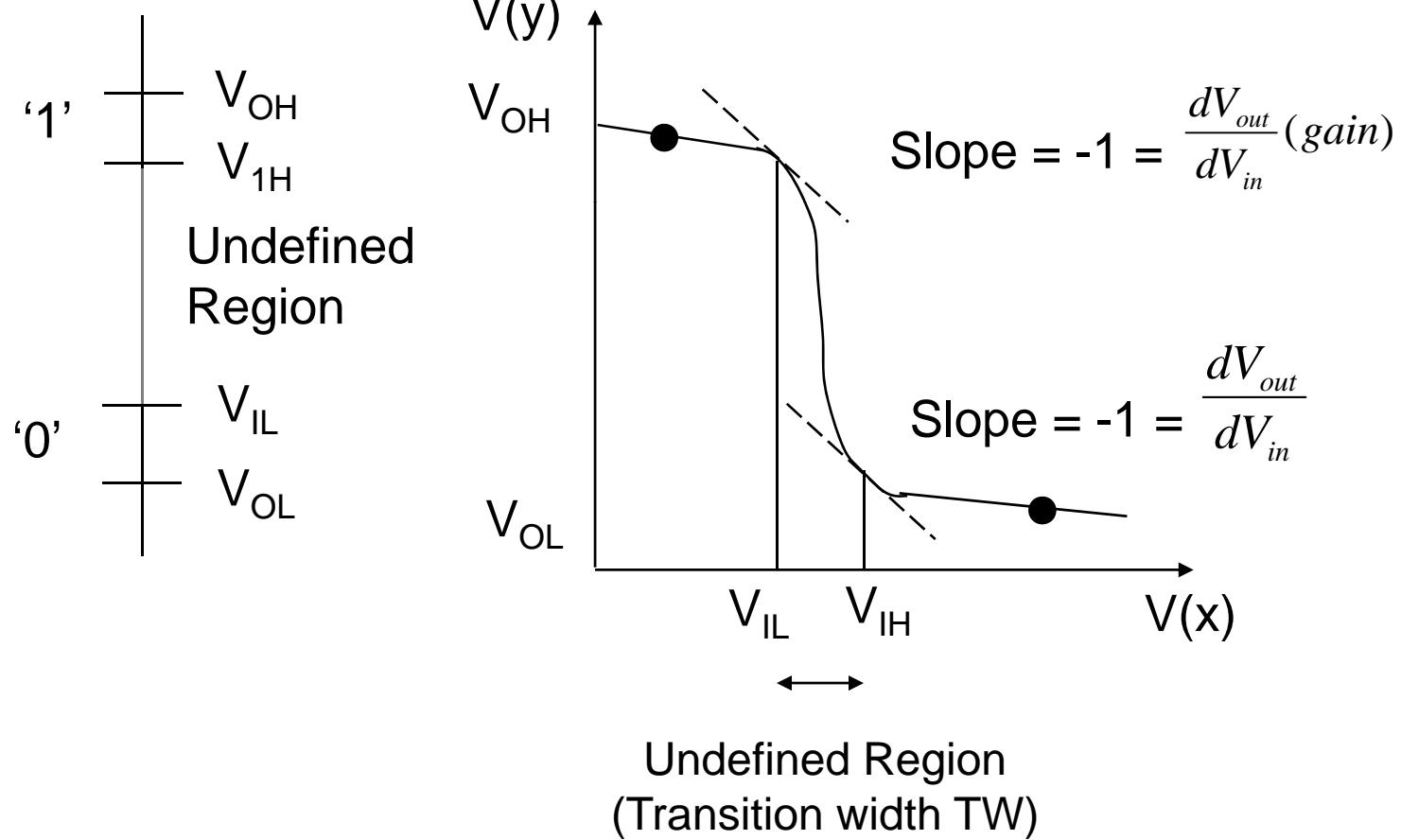
# Mapping between analog and digital signals




# Definition of Noise Margins

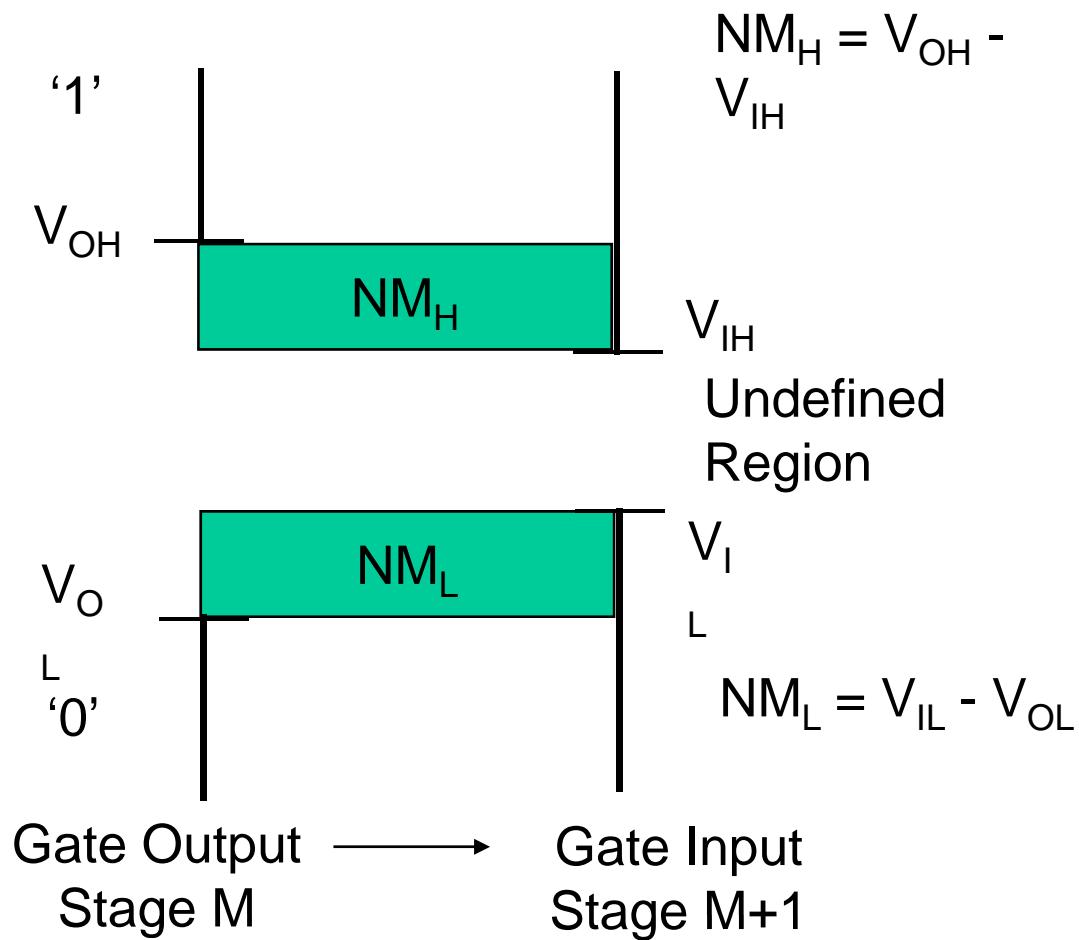


# The Regenerative Property

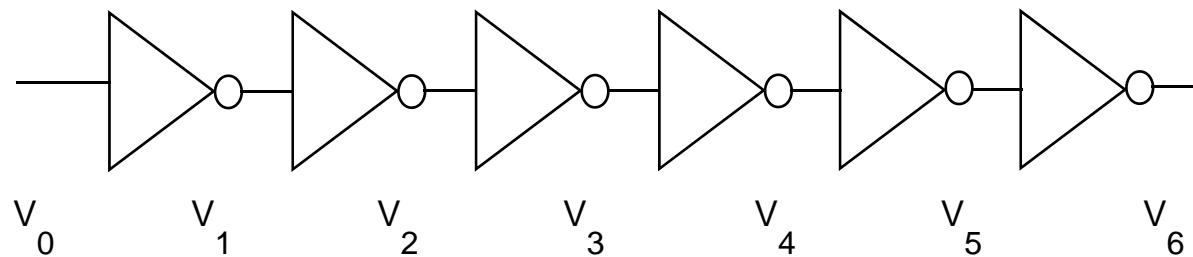


A chain of inverters

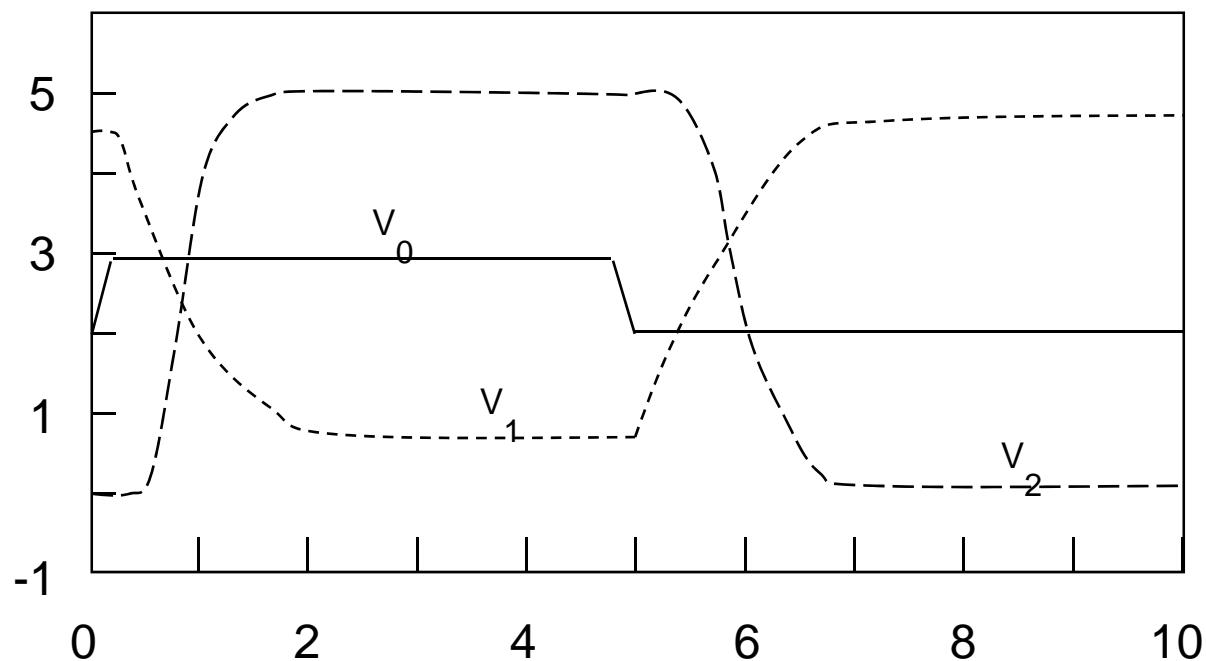

# Conditions for Regeneration

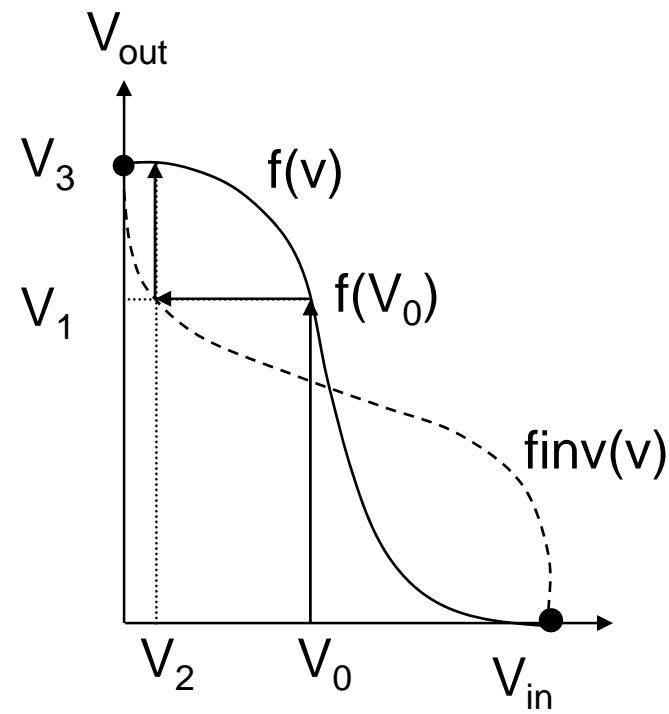


(a) Regenerative gate

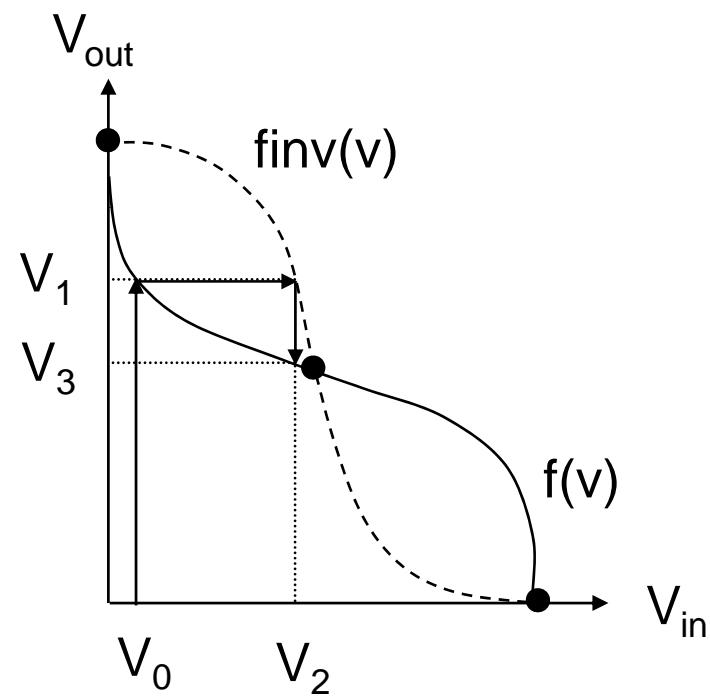


(b) Non-regenerative gate


# Fan-in and Fan-out

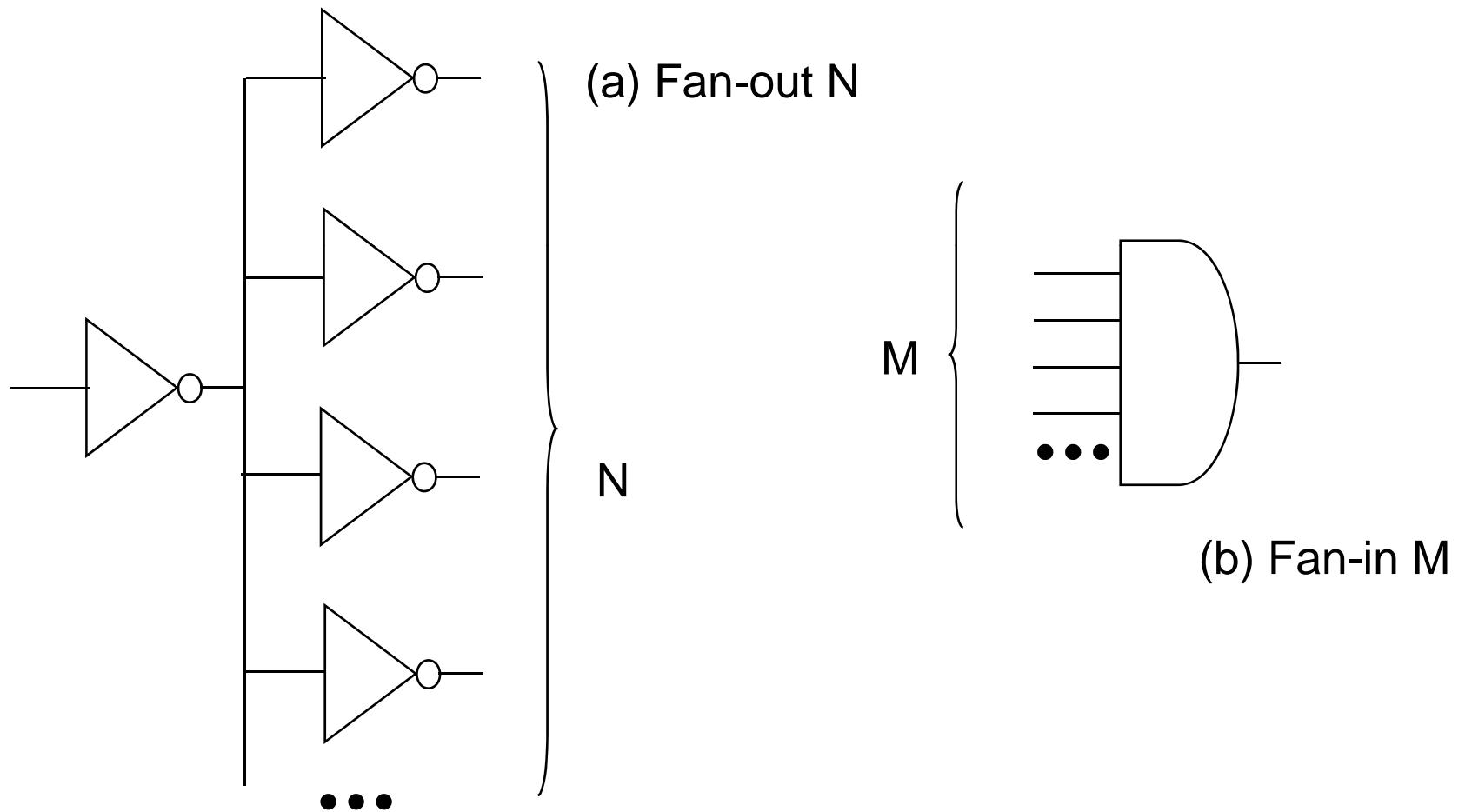


# The Ideal Gate

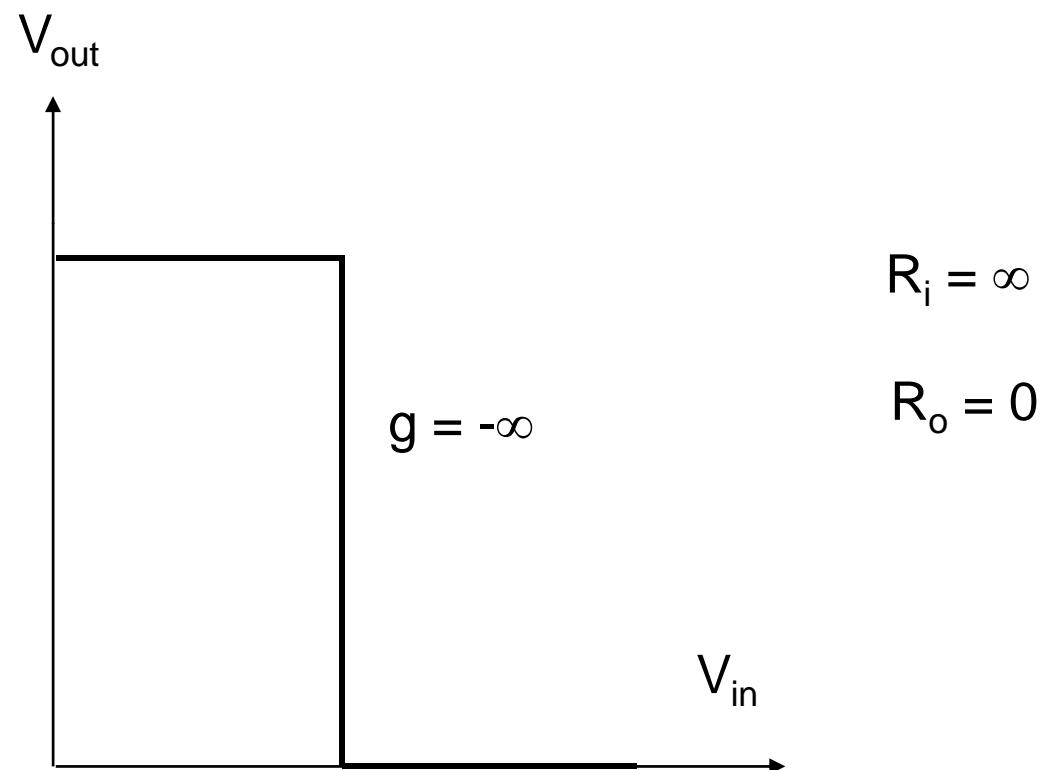



# VTC of Real Inverter

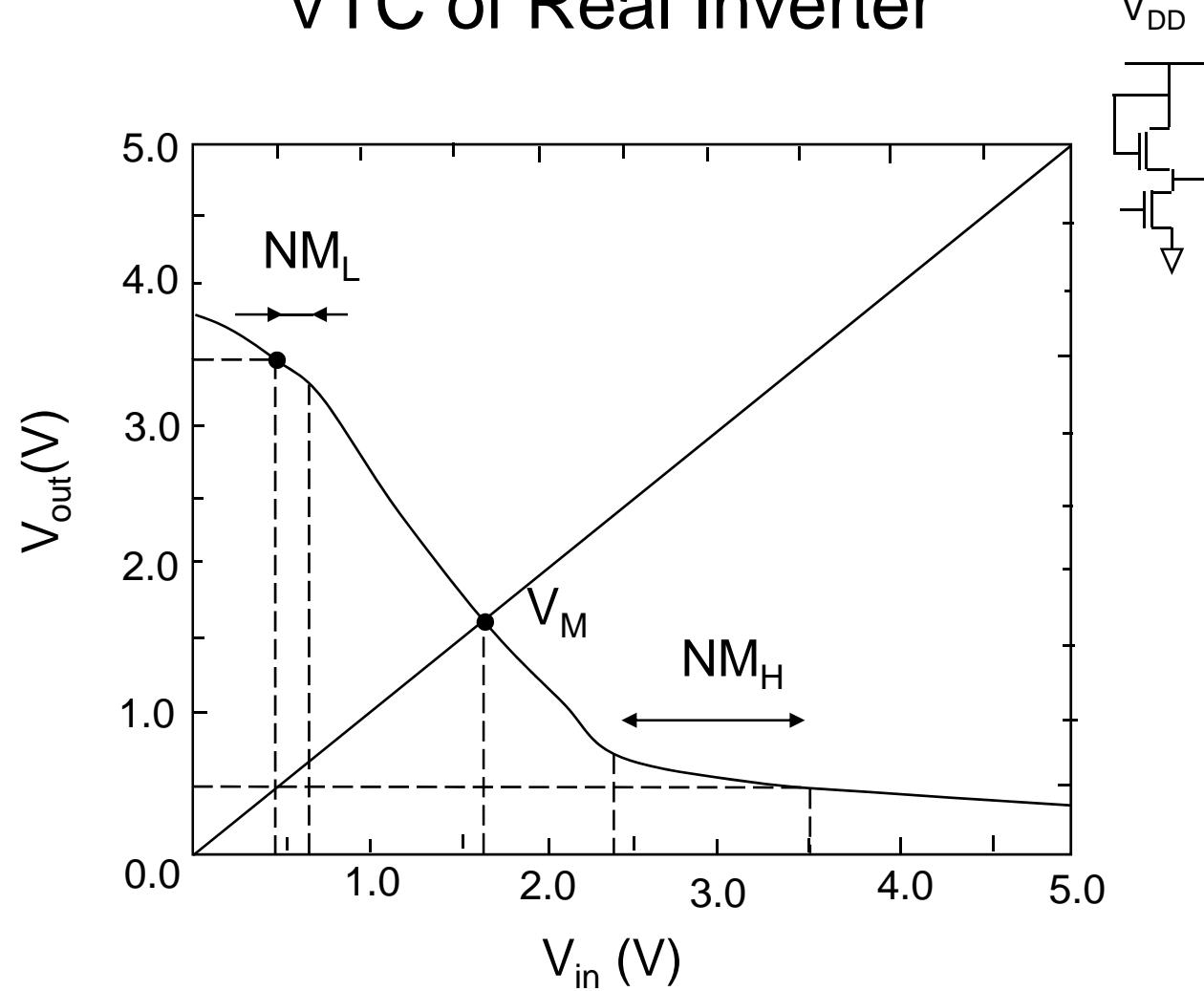

# Delay Definitions

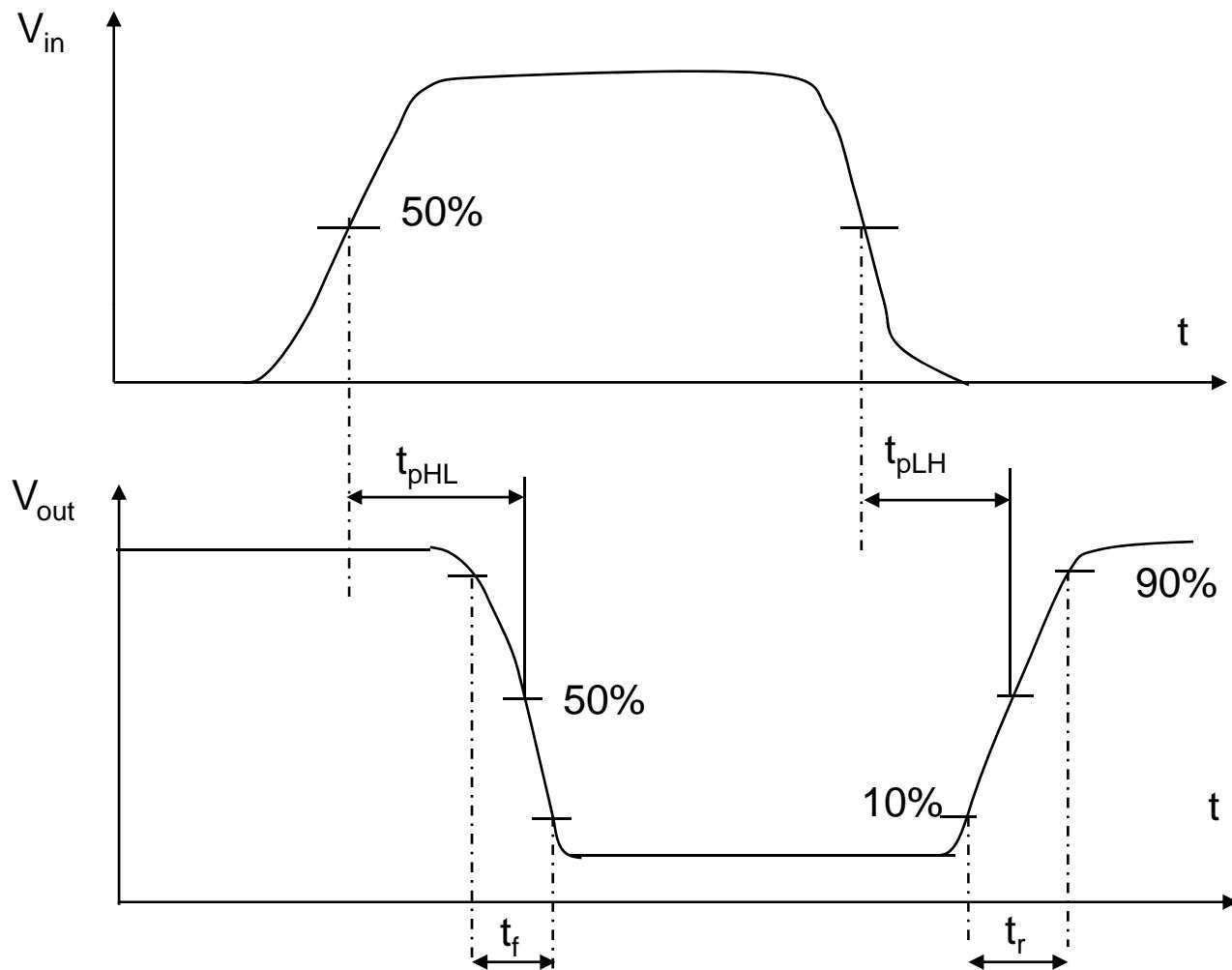

# Ring Oscillator

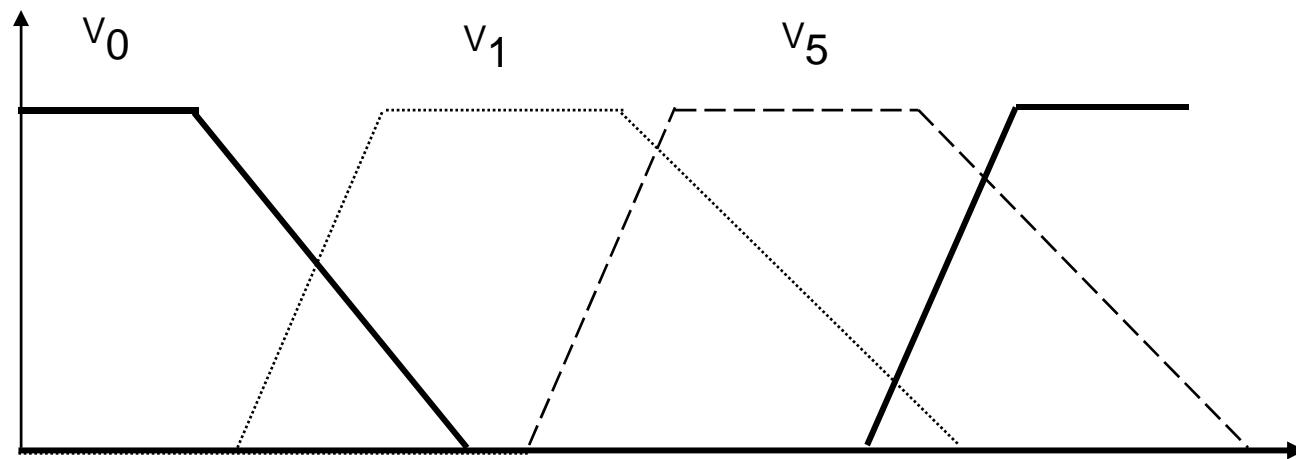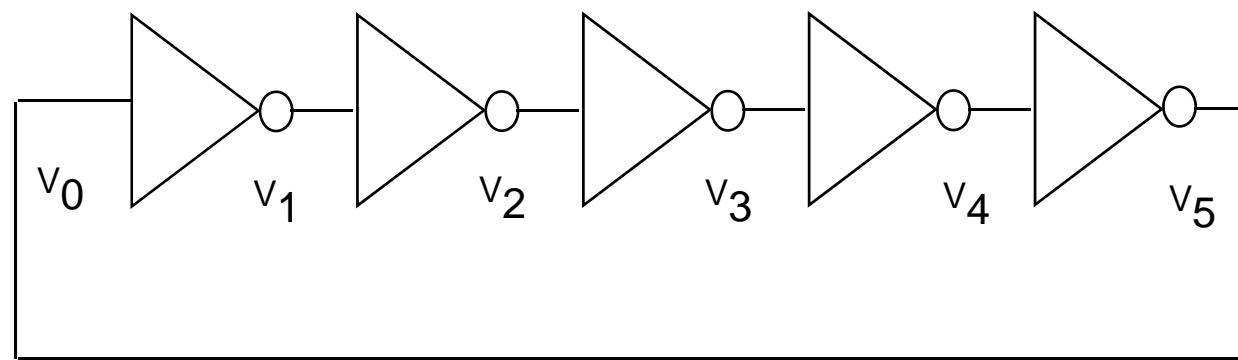

$$T = 2 \times t_p \times N$$

$$2Nt_p \gg t_f + t_r$$

# Power Dissipation

$P(t)$  = instantaneous power

$$P_{\text{peak}} = i_{\text{peak}} V_{\text{supply}} = \max(p(t))$$

$$P_{\text{av}} = \frac{1}{T} \int_0^T p(t) dt = \frac{V_{\text{supply}}}{T} \int_0^T i_{\text{supply}}(t) dt$$



## Power-Delay Product

$$\text{PDP} = t_p \times P_{\text{av}}$$


= Energy dissipated per operation

# Static Load MOS Inverters

# Static Load MOS Inverters

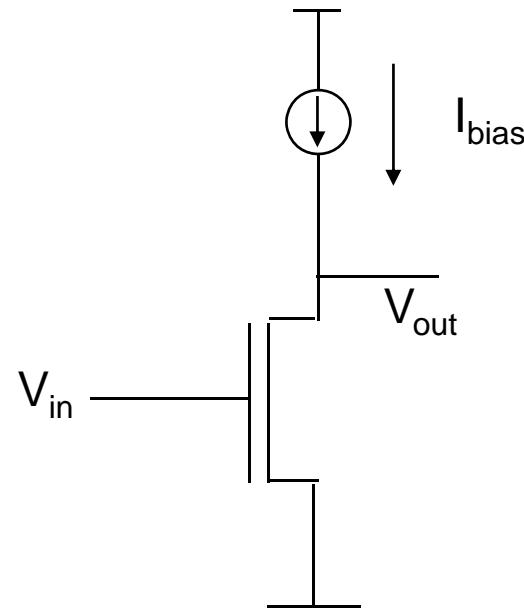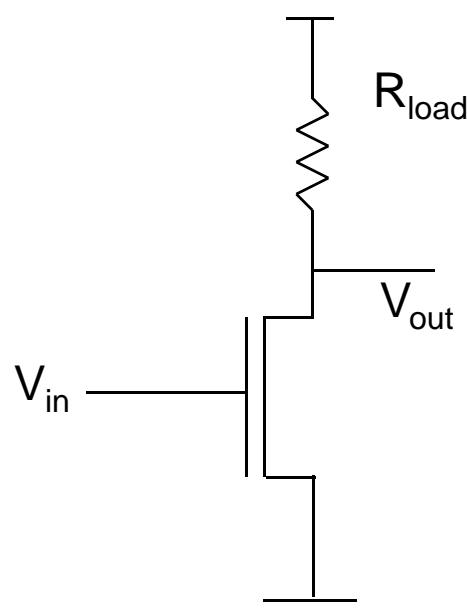


## Basic Inverter

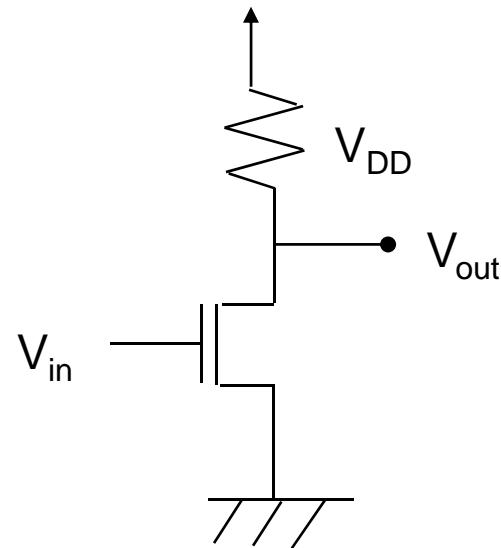


- $V_{in} < V_{th}$ ; NMOS off;  $V_{out}$  pulled to  $V_{DD}$
- $V_{in} > V_{th}$ ; NMOS on, current flows through R to ground
- If R is sufficiently large,  $V_{out}$  could be pulled down well below  $V_{th}$ ;

# Static Load MOS INverter

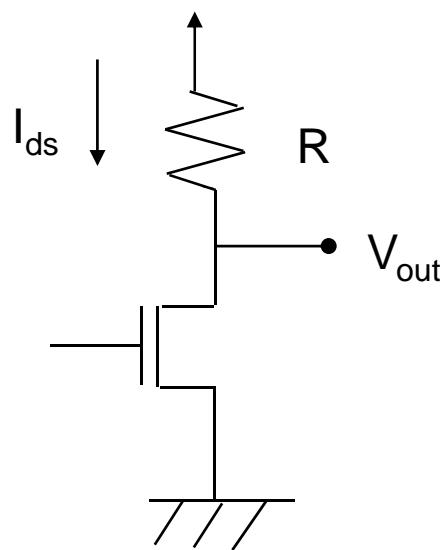


$$V_{out} = V_{ds}$$

$$I_{ds} \cdot R = V_{DD} - V_{ds}$$

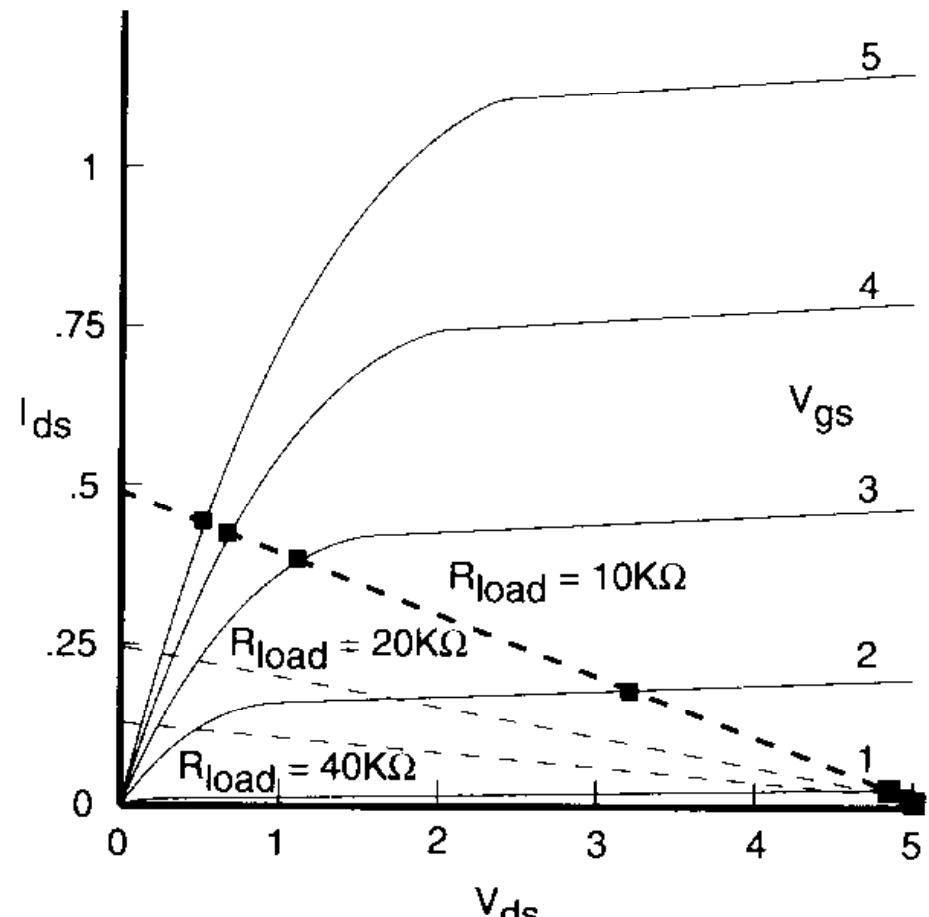


(b)

## VTC of Resistive Load

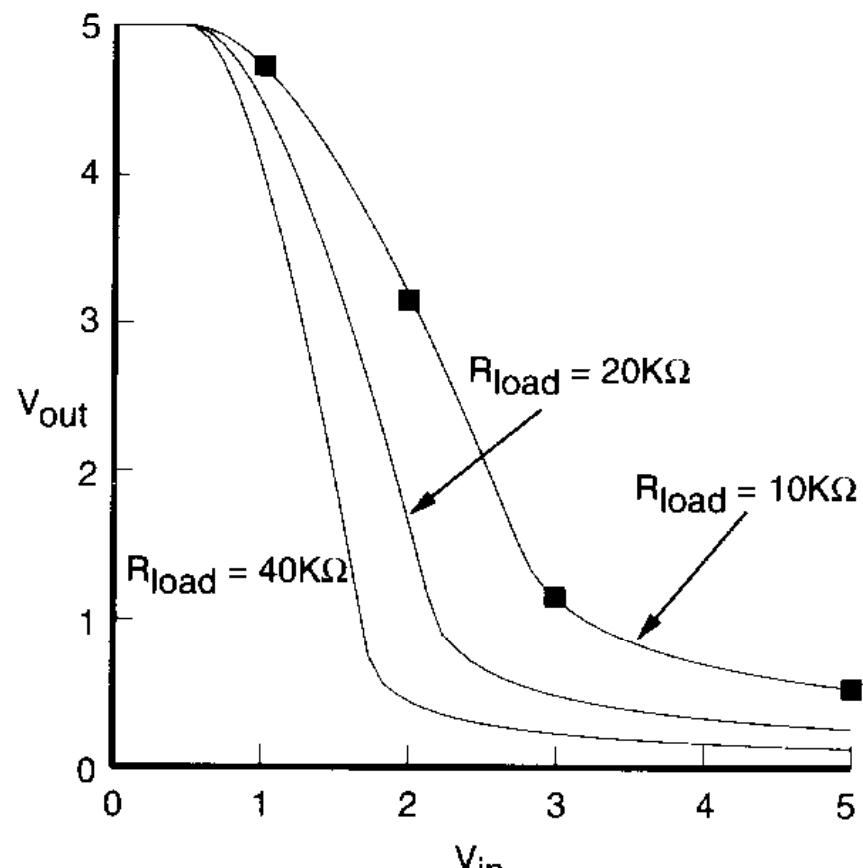

(c)

# Resistive Load Device

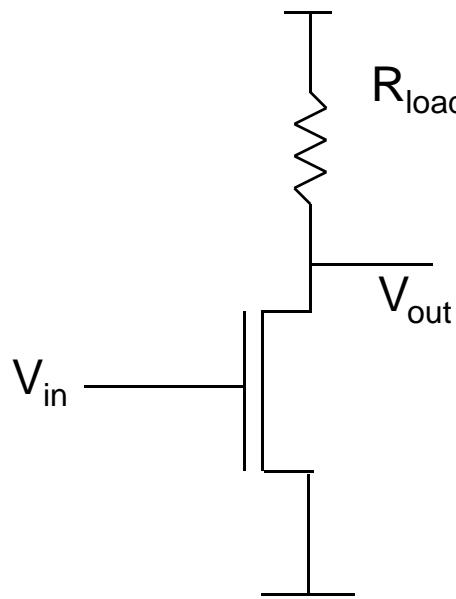

$$V_{oh} = 5.0V$$

$$V_{ol} = ???$$

$$I = (V_{dd} - V_{ol})/R$$

$$I = \beta \cdot ((V_{dd} - V_t)V_{ol} - 0.5V_{ol}^2)$$

$$R = \frac{(V_{dd} - V_{ol})}{\beta \cdot ((V_{dd} - V_t)V_{ol} - 0.5V_{ol}^2)}$$

## Sizing for $V_{OL}$

$$R = \frac{(V_{dd} - V_{ol})}{\beta \cdot ((V_{dd} - V_t)V_{ol} - 0.5V_{ol}^2)}$$

Assume:

$$\begin{aligned}V_{dd} &= 5.0V \\V_t &= 1.0V \\\beta &= 10^{-4}A/V\end{aligned}$$

Proper design:  $V_{ol} < V_t$


Let:  $V_{ol} = 0.5V$

$$R = 24k\Omega$$

## Resistor and Current-Source Loads


- Resistance/length of minimum-width lines of various connecting elements is far less than effective resistance of the switched on MOSFET
- In some memory processes, resistors are implemented by highly resistive undoped polysilicon
- Normally use transistors in CMOS to implement resistor and current-source loads
- If biased for use as a resistor, called an unsaturated load inverter
- If load transistor operates in saturation as a constant current source, called a saturated load inverter

# Pseudo NMOS Inverter

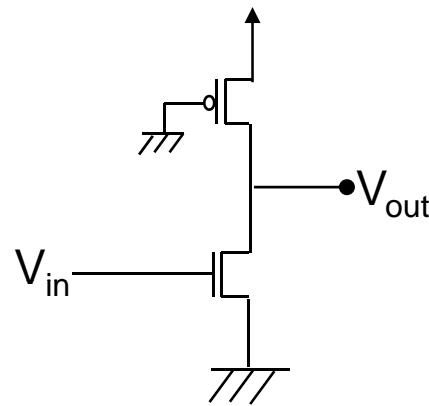


$$\begin{aligned}
 V_{DD} + V_{dsp} &= V_{out} \\
 \Rightarrow V_{dsp} &= V_{out} - V_{DD} \\
 \Rightarrow V_{dsp} &= V_{out} + V_{gsp}
 \end{aligned}$$

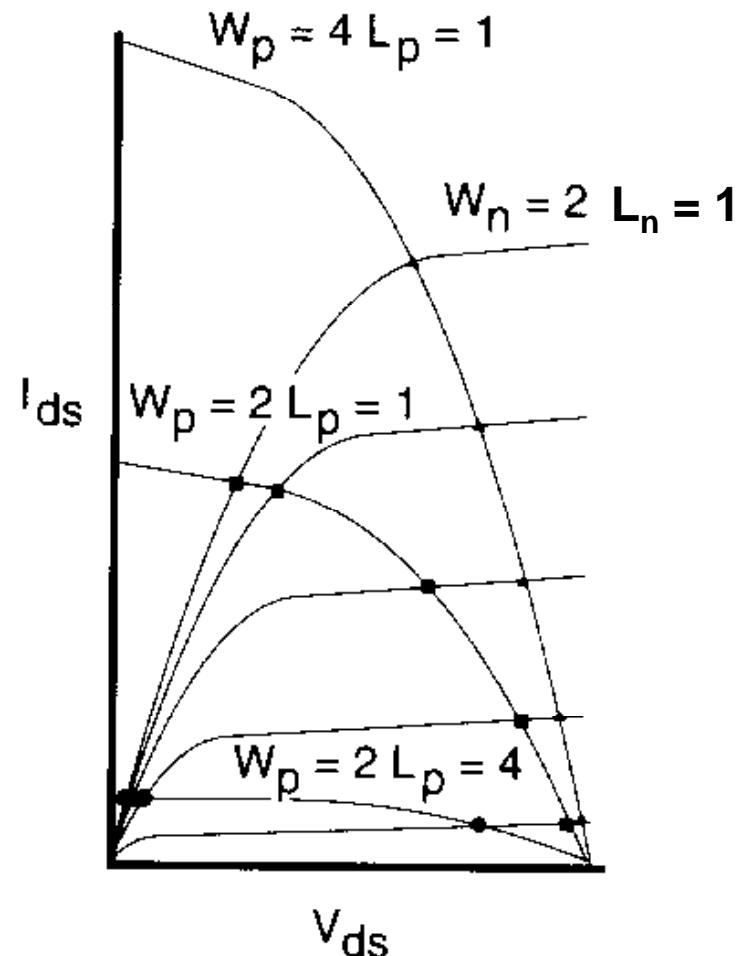
$\therefore V_{dsp} > V_{gsp} - V_{tp}$  or  $V_{out} > -V_{tp}$   
 $\Rightarrow$  Non-saturated region



# DC Transfer Characteristics

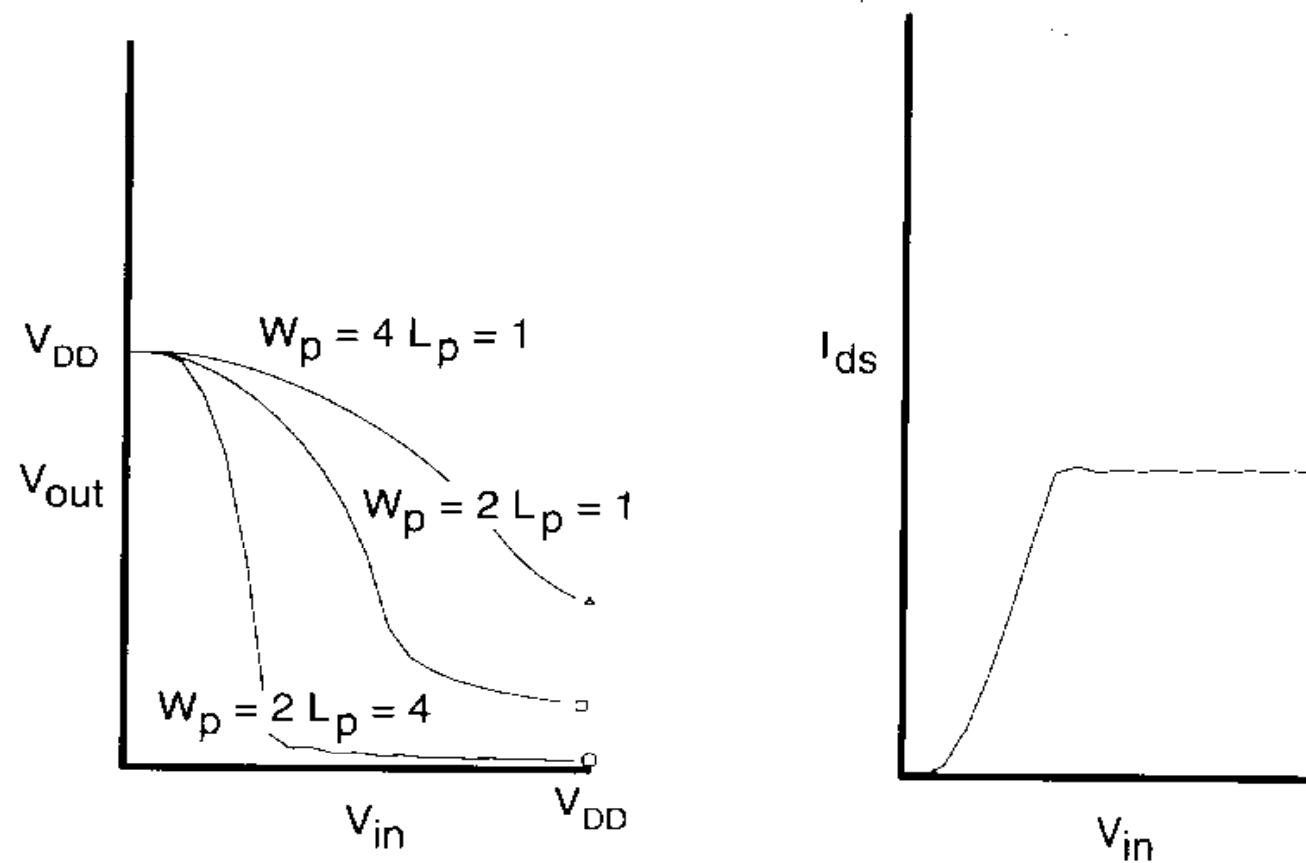


# Pseudo-NMOS Inverter

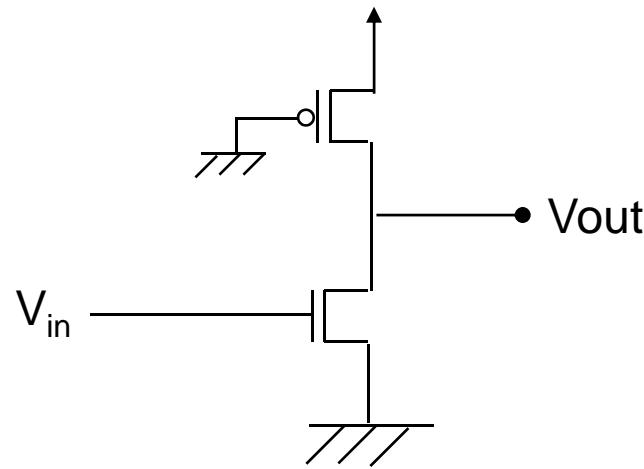

- DC current flows when the inverter is turned on unlike CMOS inverter
- CMOS is great for low power unlike this circuit (e.g. watch needs low power lap-tops etc)
- Need to be turned off during IDDQ ( $V_{DD}$  Supply Current Quiescent) testing

# PMOST Load with Constant $V_{GS}$

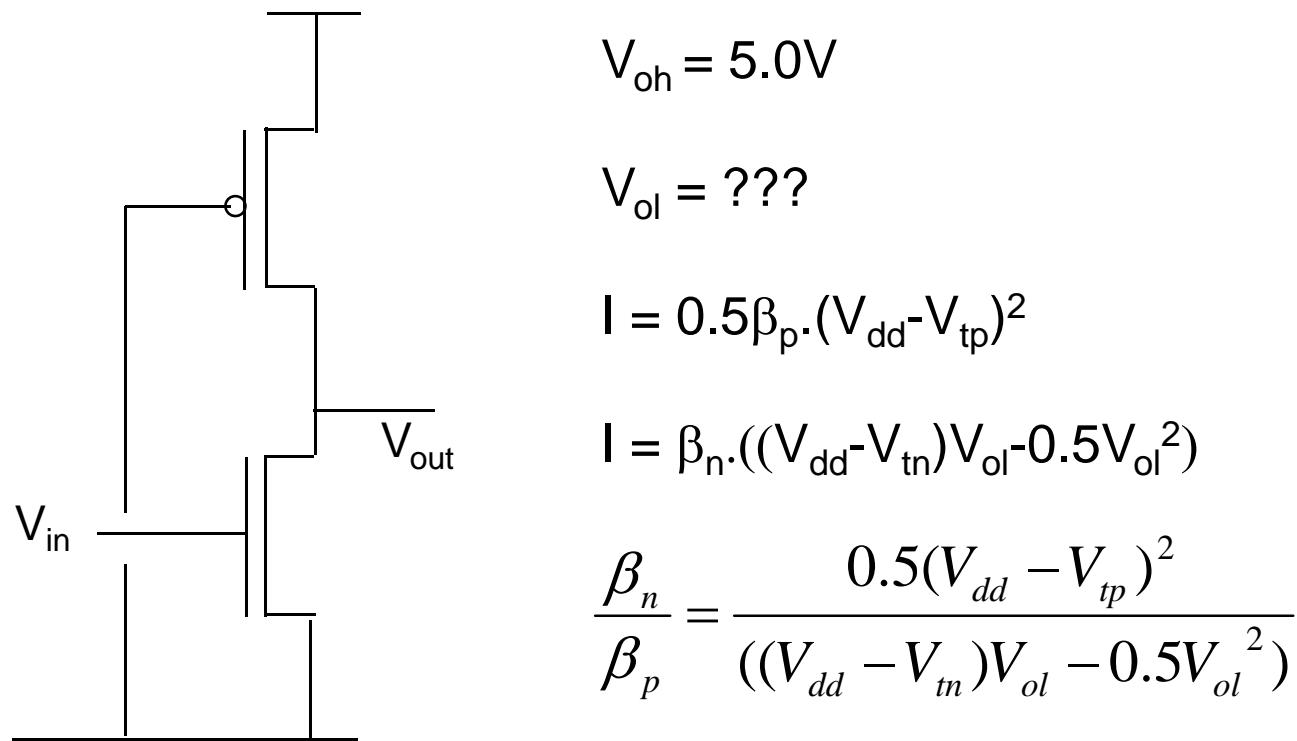

## Sizing for $V_{OL}$

$$\frac{\beta_n}{\beta_p} = \frac{0.5(V_{dd} - V_{tp})^2}{((V_{dd} - V_{tn})V_{ol} - 0.5V_{ol}^2)}$$

Assume:  $V_{dd} = 5.0V$   
 $V_{tn} = V_{tp} = 1.0V$

Proper design:  $V_{ol} < V_{th}$

Let:  $V_{ol} = 0.5V$

$$\frac{\beta_n}{\beta_p} = 4.26$$

# Sizing for Gate Threshold Voltage (Trip Point)

N-device: saturated ( $V_{out} > V_{in} - V_{tn}$ )

$$I_{dsn} = \frac{\beta_n}{2} (V_{in} - V_{tn})^2$$

P-device: non-saturated

$$V_{gsp} = -V_{DD}$$

$$I_{dsp} = \beta_p [(-V_{DD} - V_{tp})(V_{out} - V_{DD}) - \frac{(V_{out} - V_{DD})^2}{2}]$$

Equating the two currents we obtain,

$$\frac{\beta_n}{2} (V_{in} - V_{tn})^2 = -\beta_p [(-V_{DD} - V_{tp})(V_{out} - V_{DD}) - \frac{(V_{out} - V_{DD})^2}{2}]$$

# Sizing for Gate Threshold Voltage

Solving for  $V_{out}$

$$V_{out} = -V_{tp} + \sqrt{(V_{DD} + V_{tp})^2 - C}$$

Where  $C = k (V_{in} - V_{tn})^2$

$$k = \frac{\beta_n}{\beta_p}$$

Also,  $\frac{\beta_n}{\beta_p} = \frac{(V_{DD} + V_{tp})^2 - (V_{out} + V_{tp})^2}{(V_{in} - V_{tn})^2}$


To make gate threshold voltage =  $0.5V_{DD}$

$$\frac{\beta_n}{\beta_p} = 6.11$$


# Noise Margin

$\beta_n/\beta_p$	$V_{IL}$	$V_{IH}$	$V_{OL}$	$V_{OH}$	$NM_L$	$NM_H$
2	3.4	4.5	1.4	5	2.0	0.5
4	1.8	3.3	0.6	5	1.2	2.7
6	1.4	2.8	0.35	5	1.05	3.2
8	1.1	2.4	0.24	5	0.86	3.6
100	0.5	1.1	0.00	5	0.5	3.9

## VTC of Pseudo-NMOS Inverter

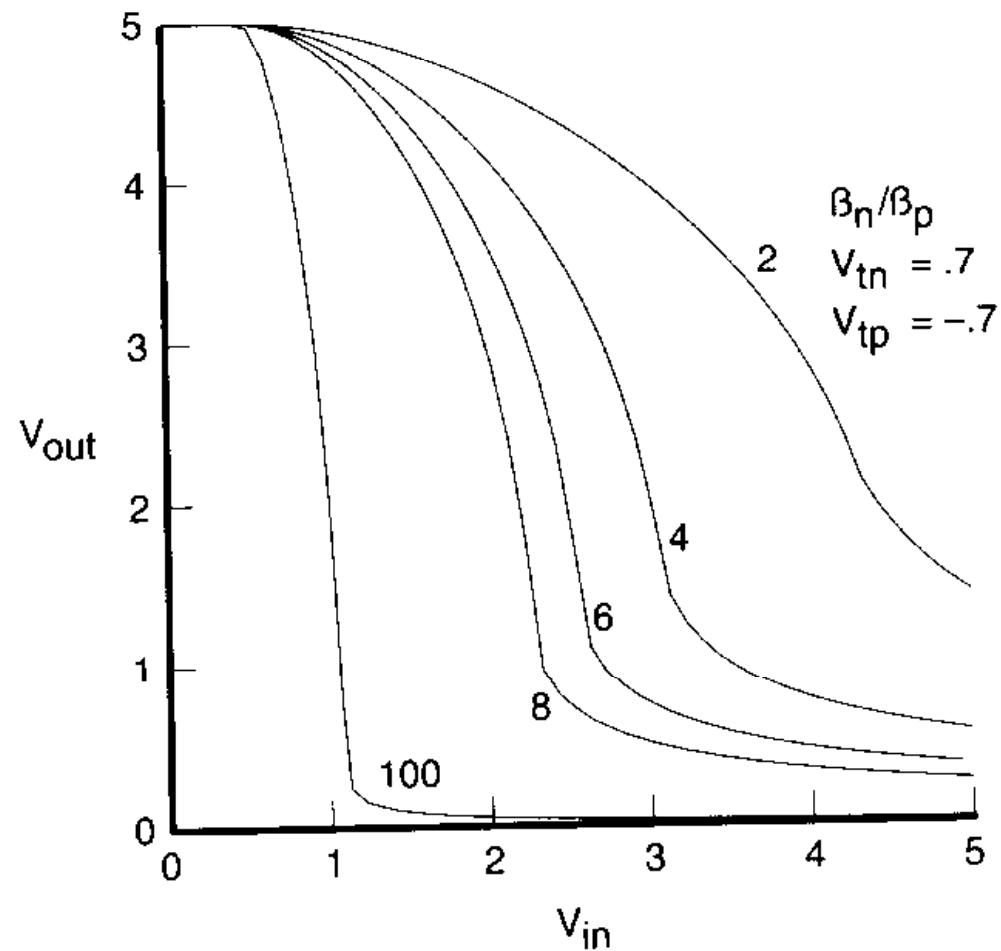


# Unsaturated Load Inverter

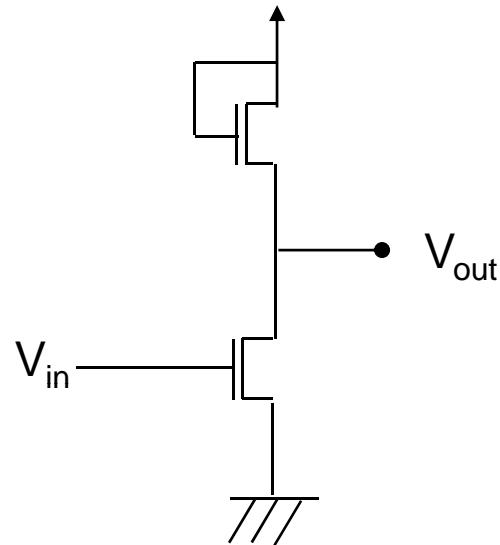


- High is n threshold down from  $V_{DD}$
- Used when depletion mode transistors were not available
- Low noise margin
- Might be used in I/O structures where p-transistors were not wanted


## VTC of Unsaturated Load Inverters

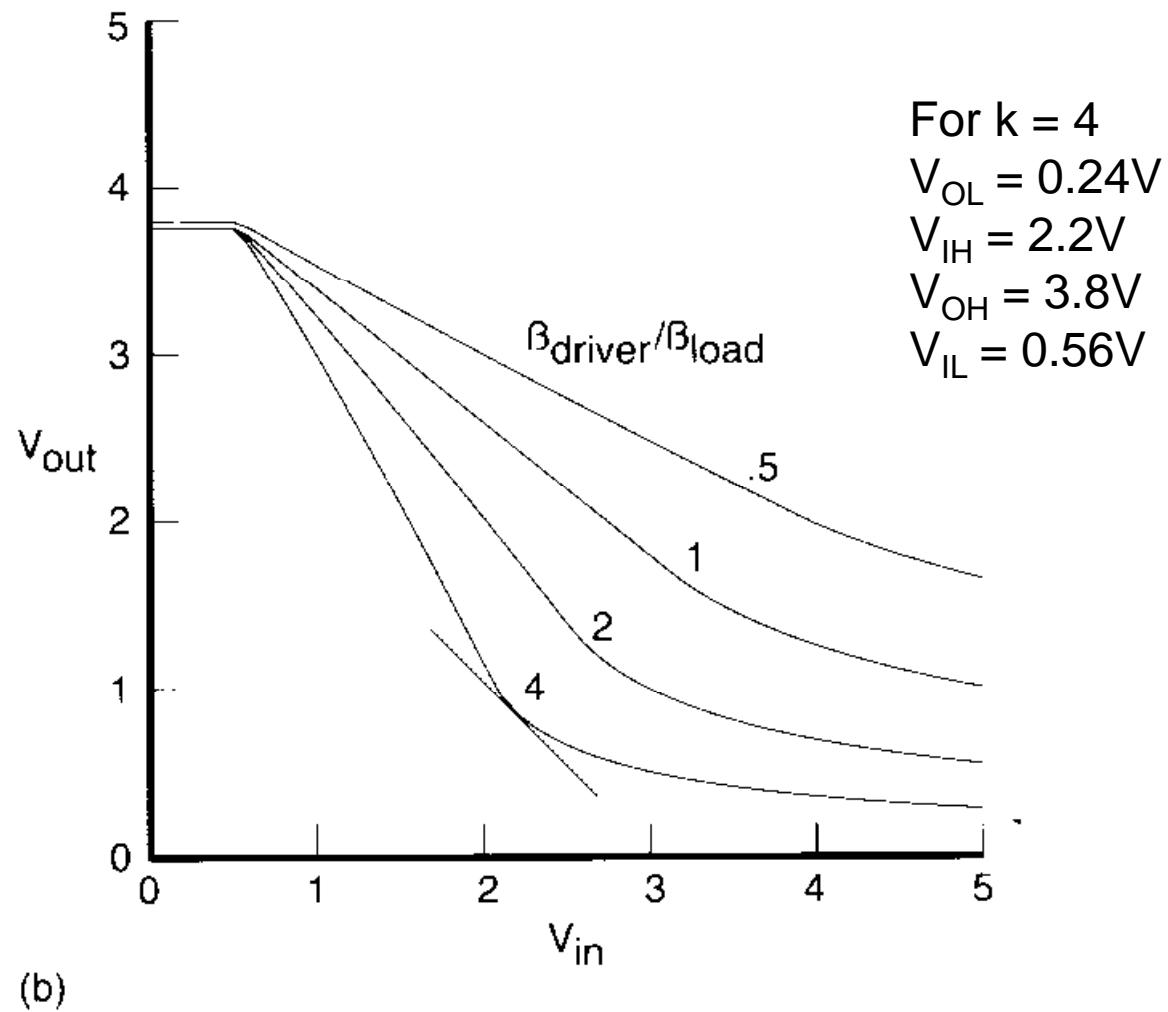

# Current Source Load

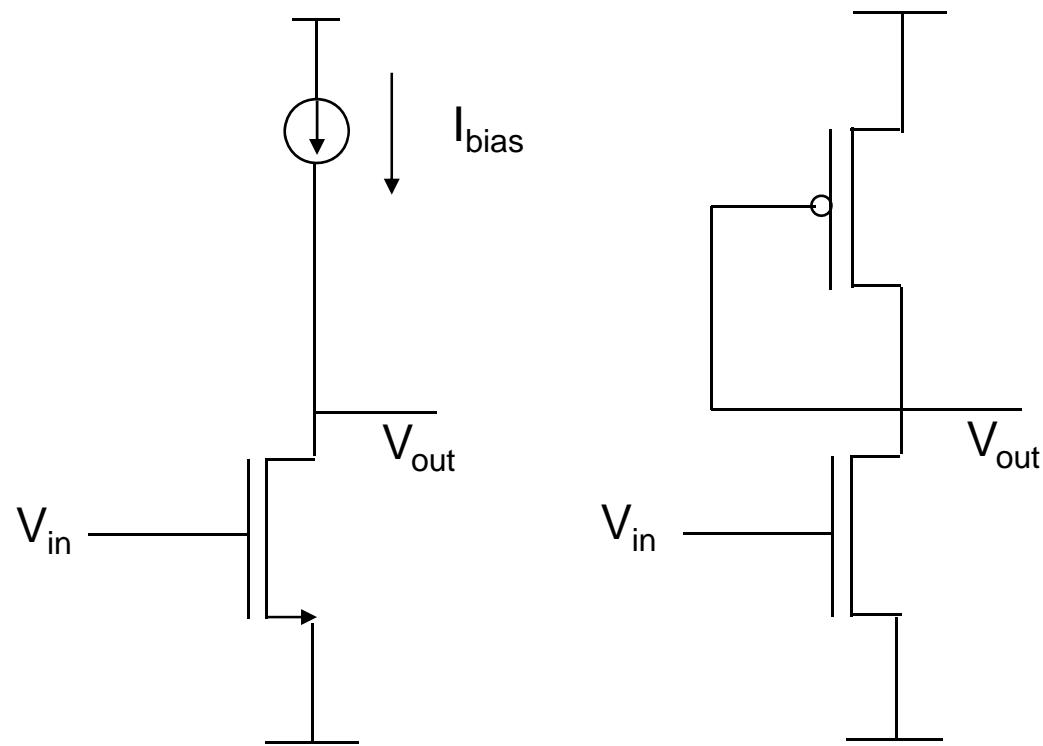

## Saturated Load Inverter

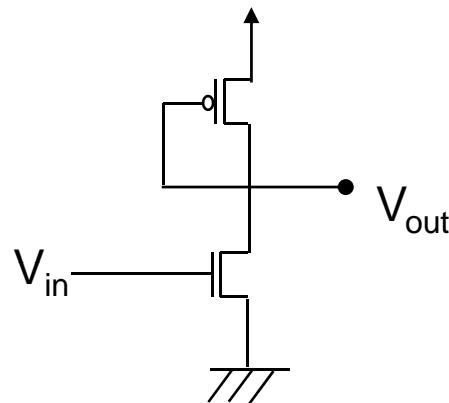

- $V_{out} > V_{in} - V_{tn} \Rightarrow$  driver transistor in saturation
  - When  $V_{in}$  is small
- Load transistor permanently in saturation
  - $V_{dsp} = V_{gsp}$
  - $\therefore V_{dsp} < V_{gsp} - V_{tp}$  or  $0 < -V_{tp} \Rightarrow$  Saturated region

## When $V_{in}$ is Small

$$I_{ds,driver} = \frac{\beta_{driver}}{2} (V_{in} - V_{tn})^2$$

Load in saturation:


$$I_{ds,load} = -\frac{\beta_{load}}{2} (V_{out} - V_{DD} - V_{tp})^2$$

Equating the currents:

$$V_{out} = V_{DD} + V_{tp} + \sqrt{k} (V_{in} - V_{tn})$$

where  $k = \frac{\beta_{driven}}{\beta_{load}}$


# VTC of Saturated Load Inverter

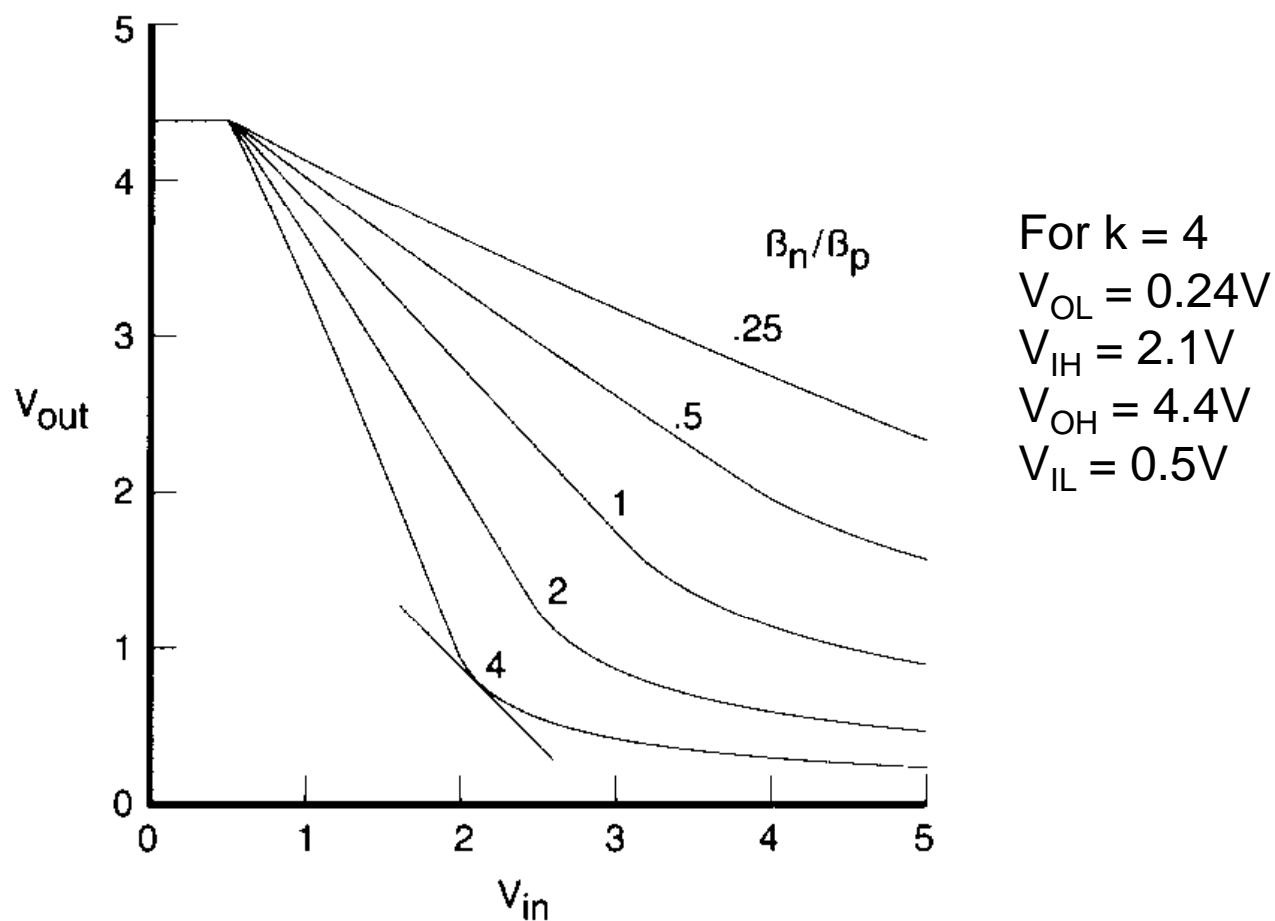
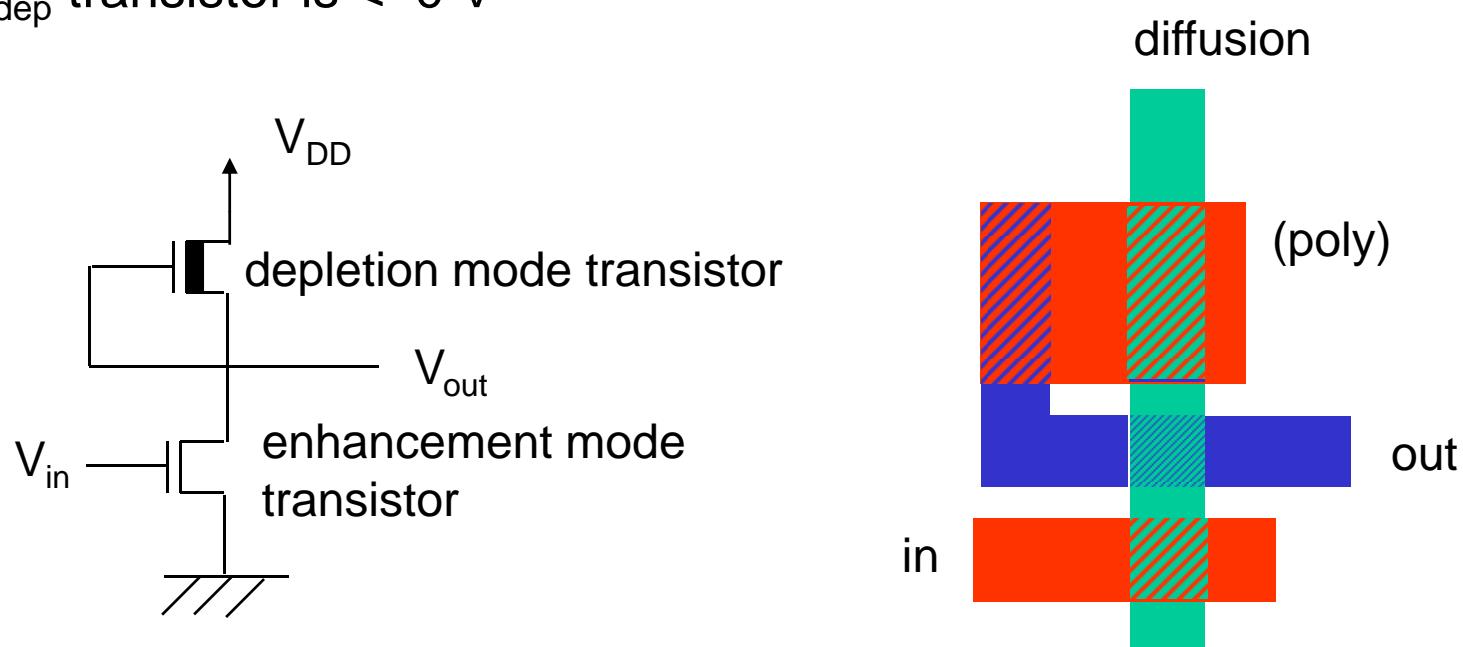
# NMOS Inverter

Use depletion mode transistor as pull-up





$V_{t\text{dep}}$  transistor is  $< 0 \text{ V}$



The depletion mode transistor is always ON:  
gate and source connected  $\Rightarrow V_{gs} = 0$

$V_{in} = 0 \Rightarrow$  transistor pull down is off  $\Rightarrow V_{out}$  is high
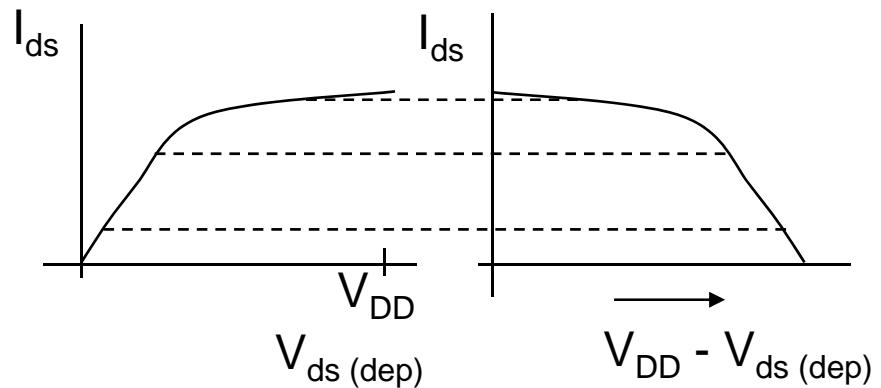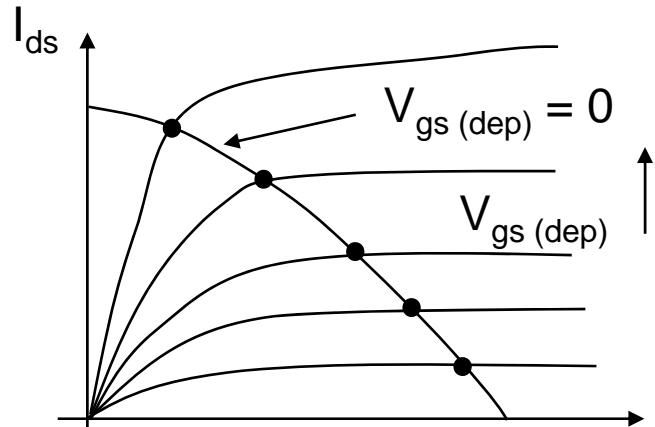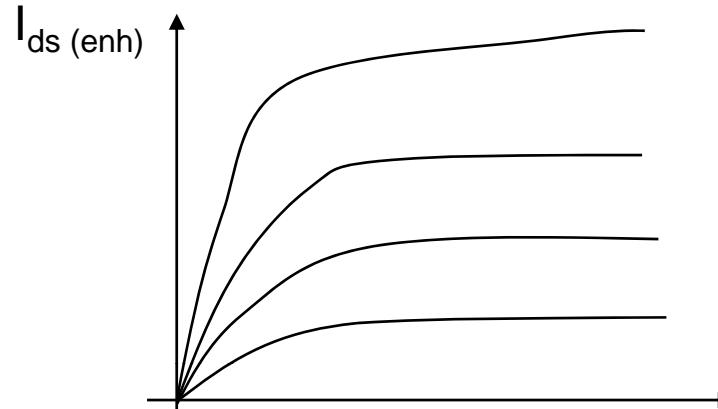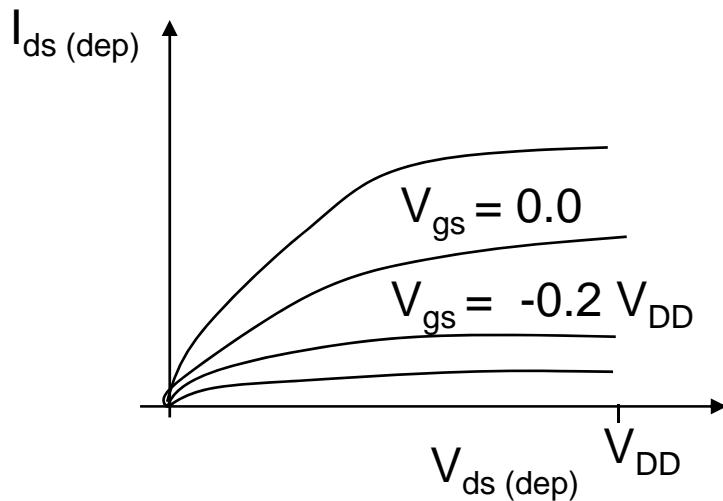
# $V_{out}$ vs $V_{in}$ using Graphical Method



$V_{DD} - V_{ds(dep)} = V_{ds(enh)} = V_{out}$   
 In a steady state,  
 $I_{ds}$  of both transistors are equal

$$\begin{aligned}
 V_{ds(enh)} &= V_{DD} - V_{ds(dep)} \\
 V_{ds(enh)} &= V_{out} \\
 \text{Therefore } V_{out} &= V_{DD} - V_{ds(dep)}
 \end{aligned}$$

# Gate Threshold Voltage

Gate threshold voltage =  $V_{inv}$   
= Input voltage at which  $V_{in} = V_{out}$


Assume that both driver and load are in saturation with input  $V_{inv}$

$$I_{DS(sat)} = \frac{\beta_{driver}}{2} (V_{gs} - V_t)^2$$


$$\therefore \frac{\beta_{driver}}{2} (V_{inv} - V_t)^2 = \frac{\beta_{load}}{2} (-V_{dep})^2$$

Hence,  $V_{inv} = V_t - V_{dep} \sqrt{\frac{\beta_{load}}{\beta_{driver}}}$

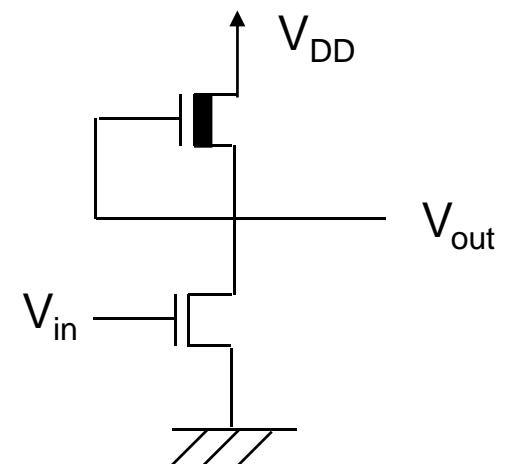If  $\beta_{driver}$  is increased relative to  $\beta_{load}$  then,  
 $V_{inv}$  decreases




## VTC of NMOS inverter

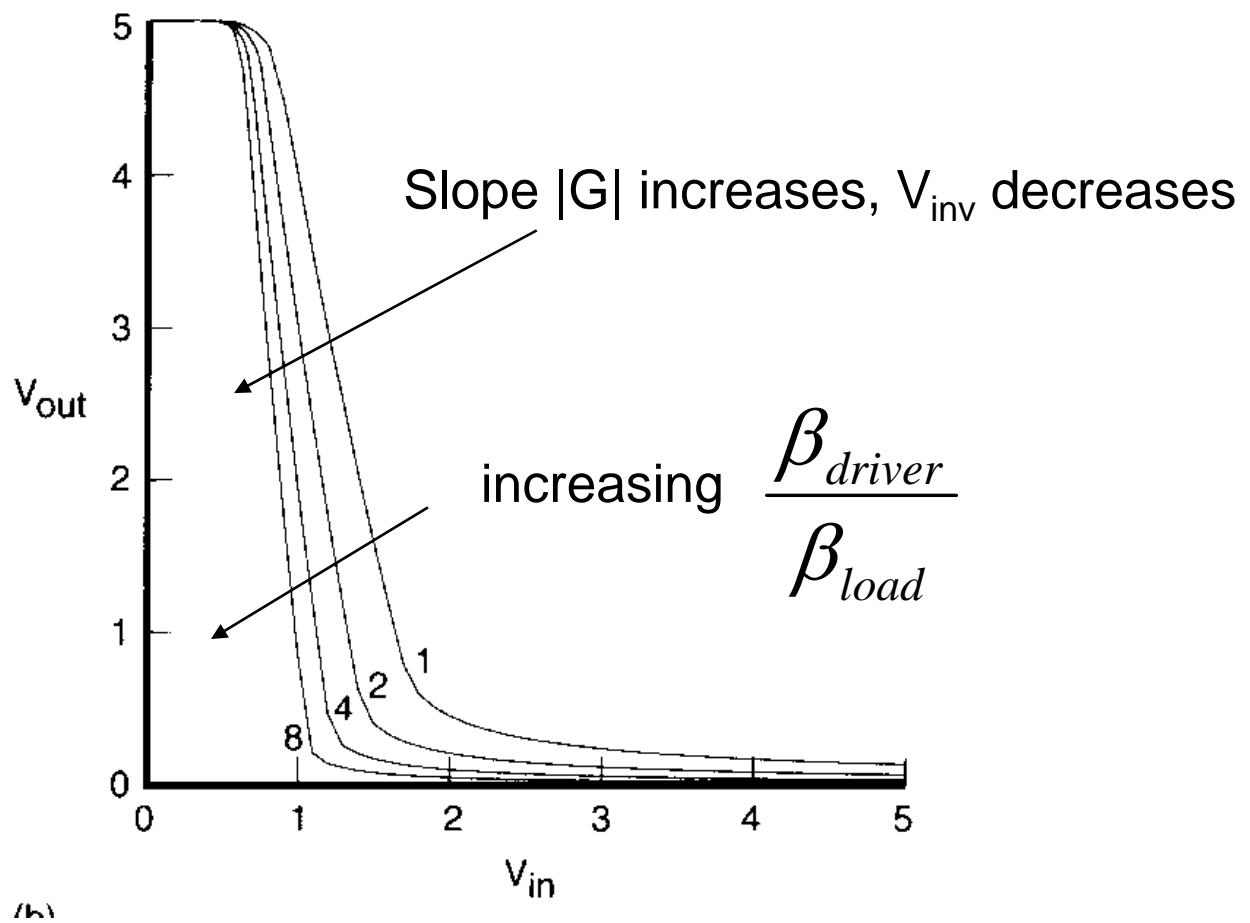


# CMOS INVERTER


# CMOS Inverters

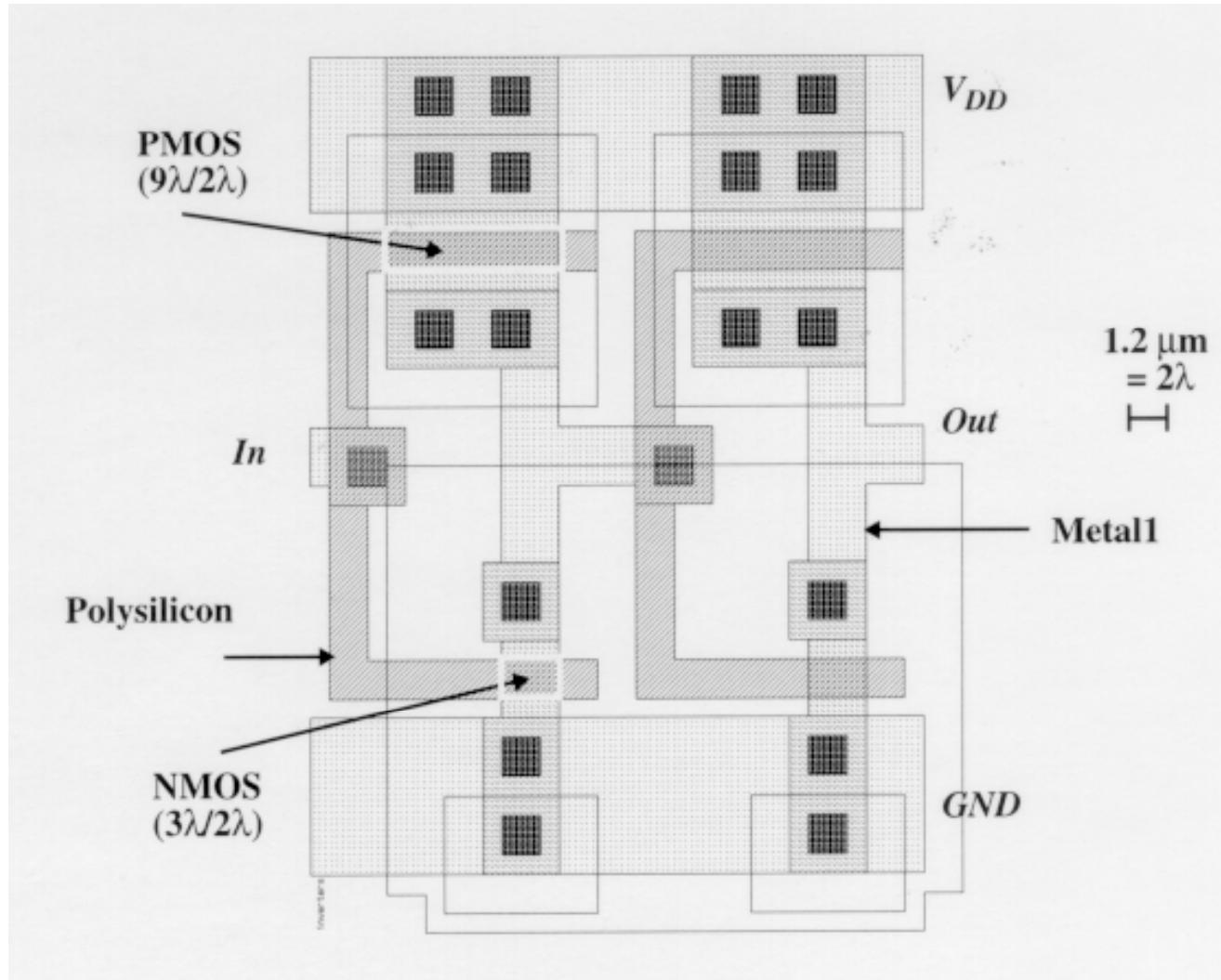


# The CMOS Inverter: A First Glance

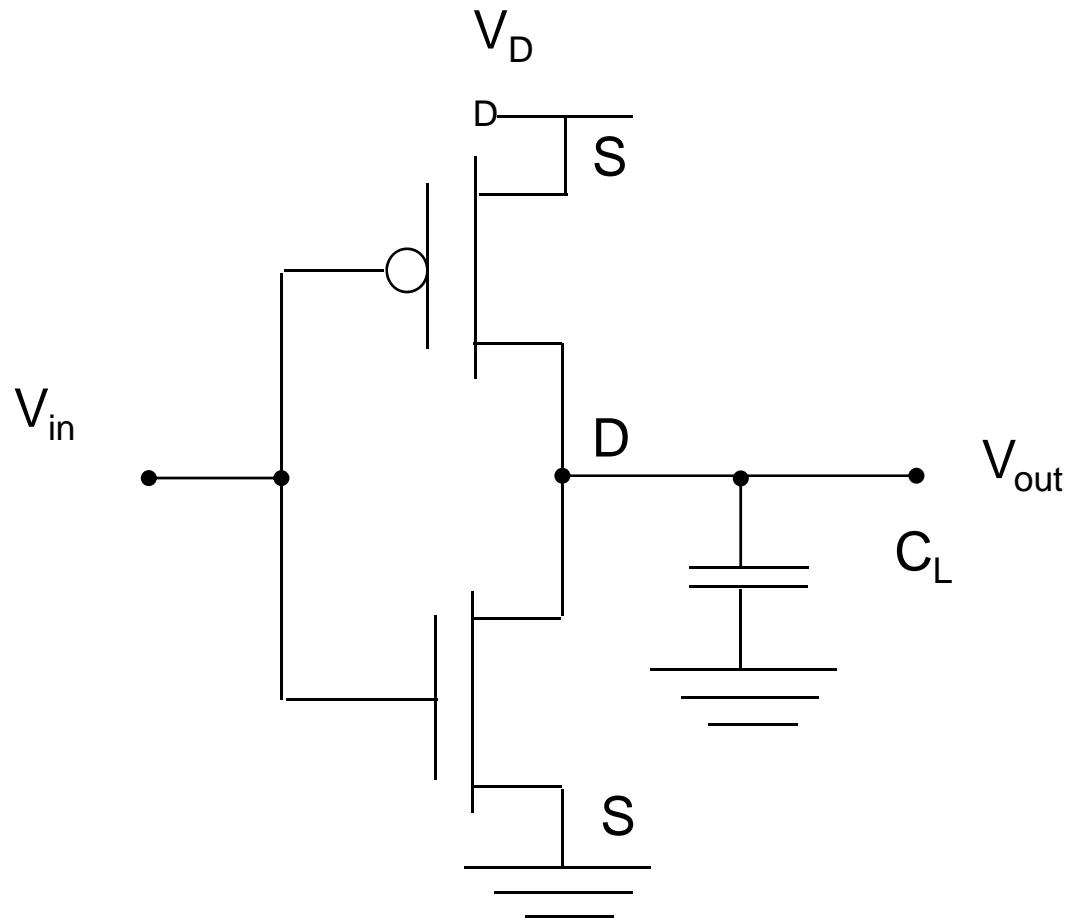


# Switch Model of MOS Transistor

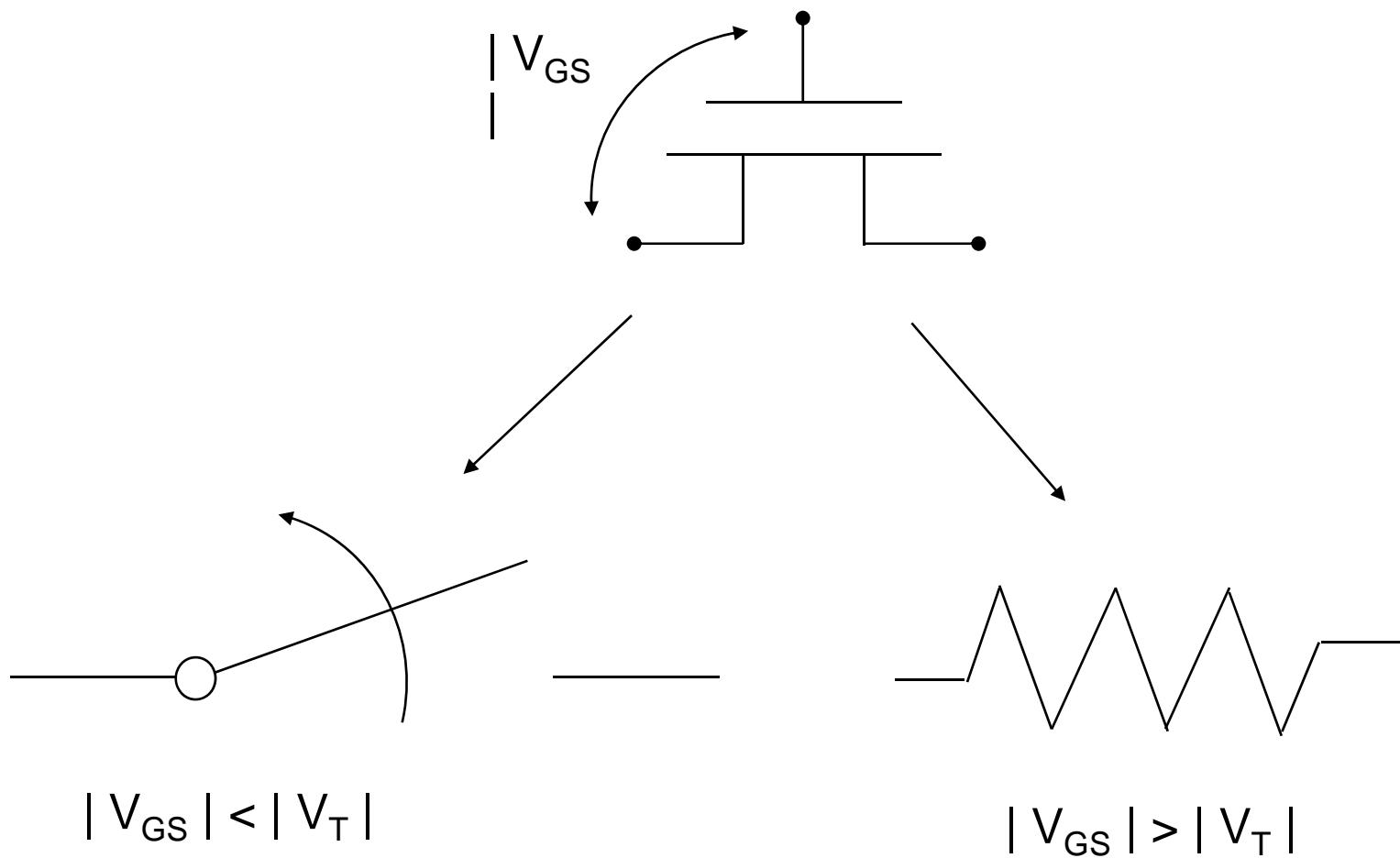

# CMOS Inverter: Steady State Response

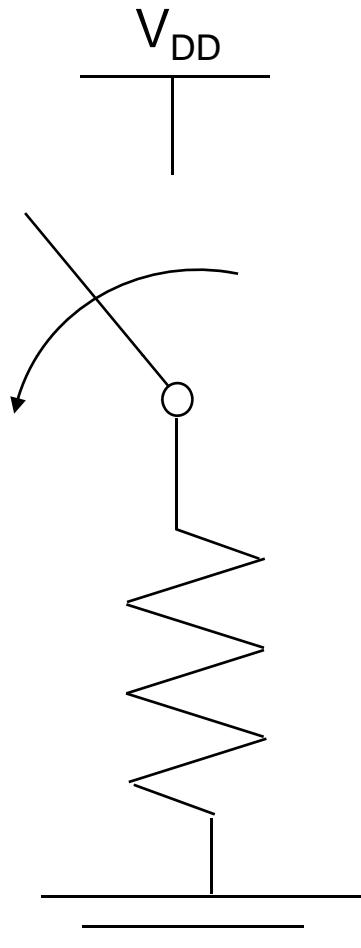

$$V_{in} = V_{DD}$$

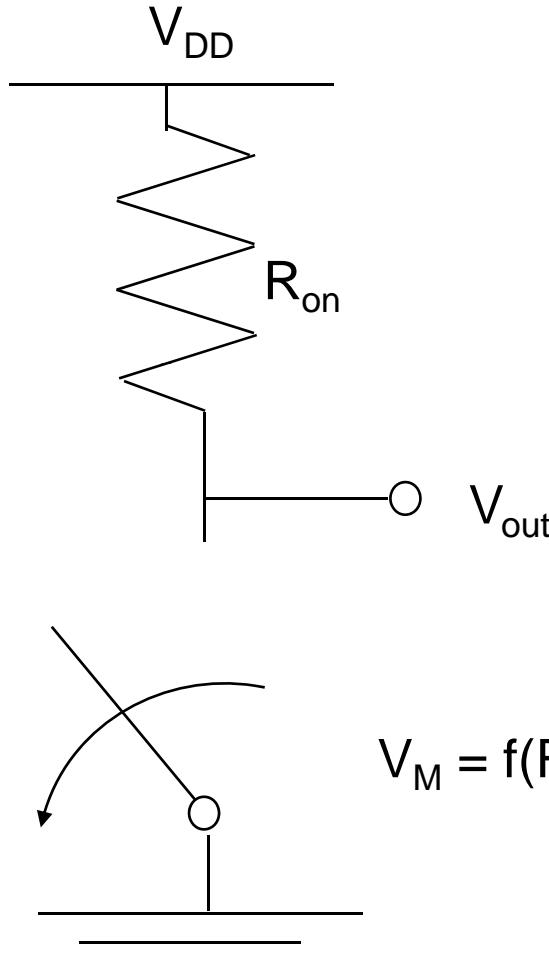

$$V_{in} = 0$$

$$\begin{aligned}V_{OH} &= V_{DD} \\V_{OL} &= 0\end{aligned}$$


$$V_M = f(R_{onN}, R_{onP})$$

# PMOS Load Lines


$$V_{in} = V_{DD} - V_{GSp}$$

$$I_{dn} = -I_{DP}$$


$$V_{out} = V_{DD} - V_{DSP}$$

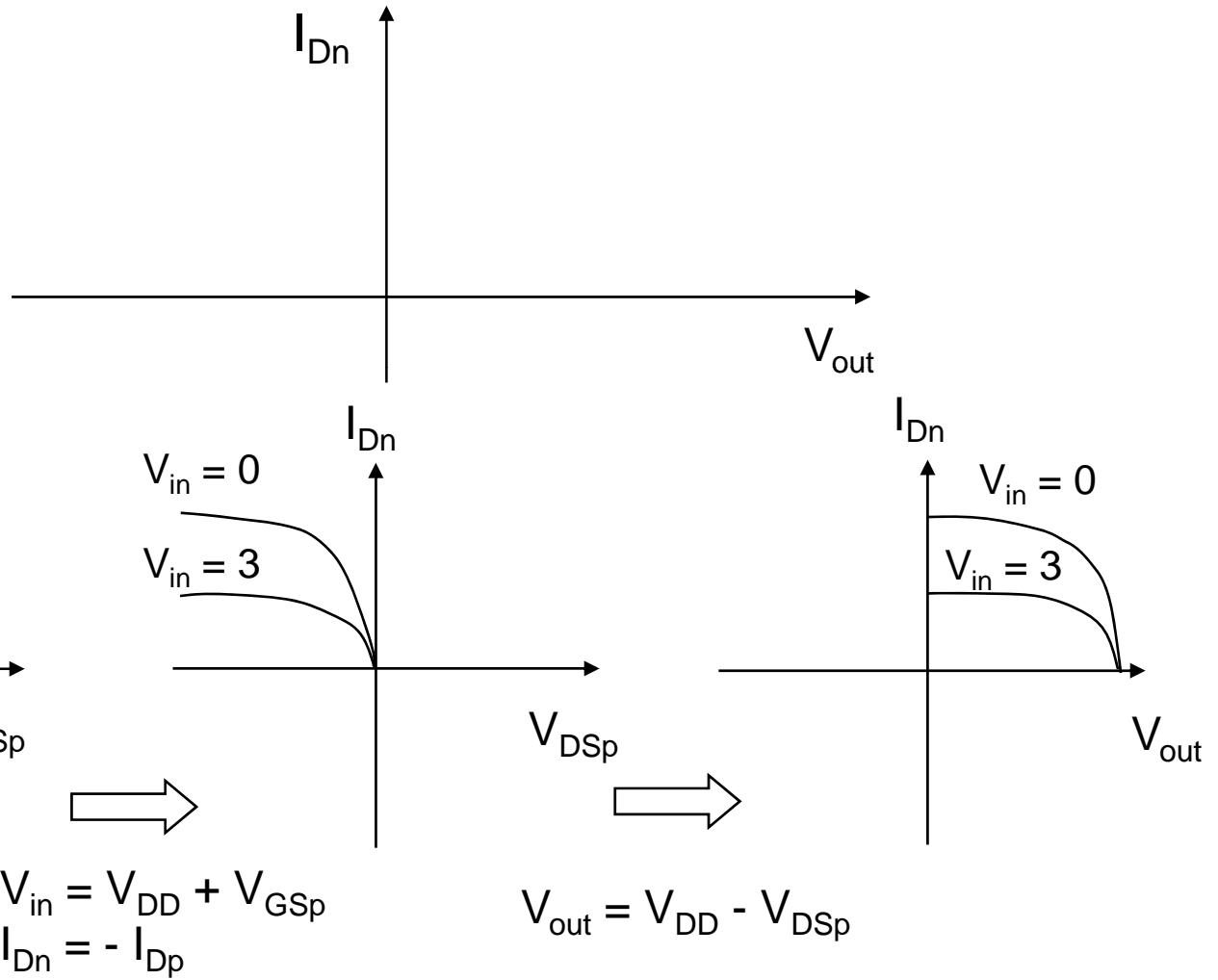


# Construction Of Inverter Curves

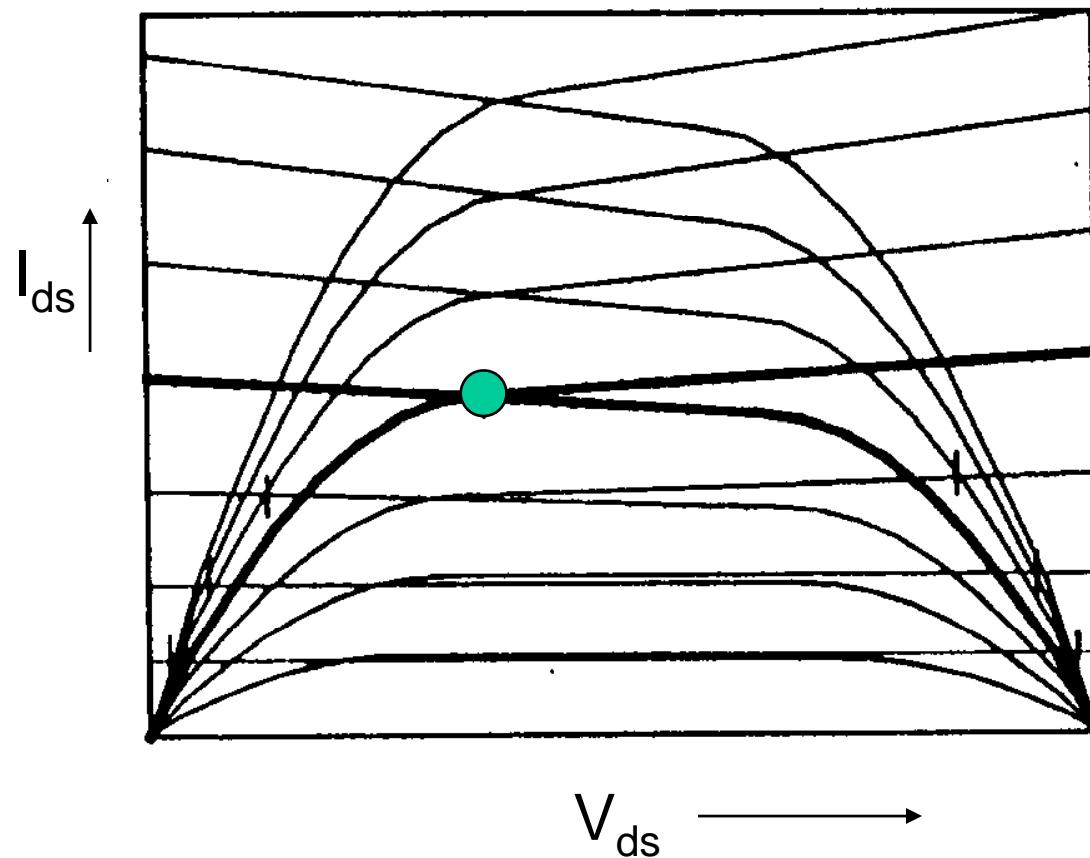


# Construction Of Inverter Curves

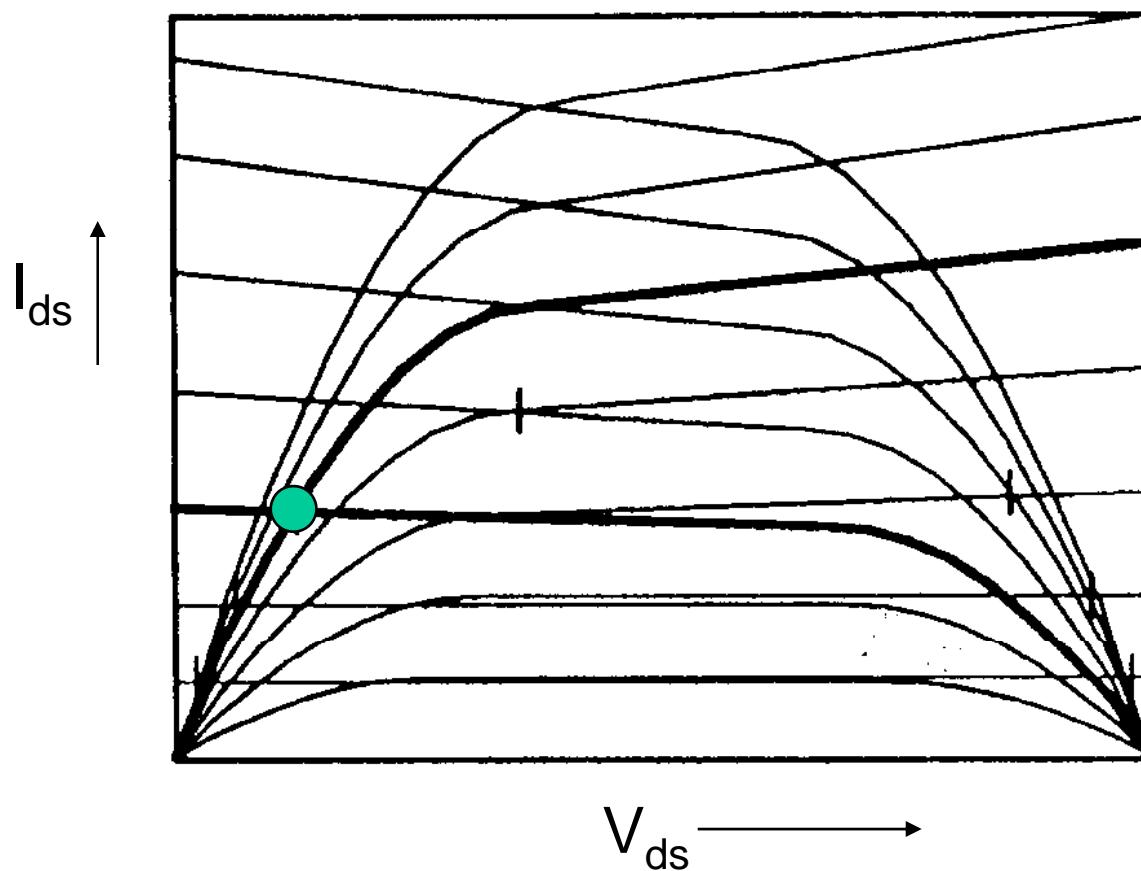


# Construction Of Inverter Curves

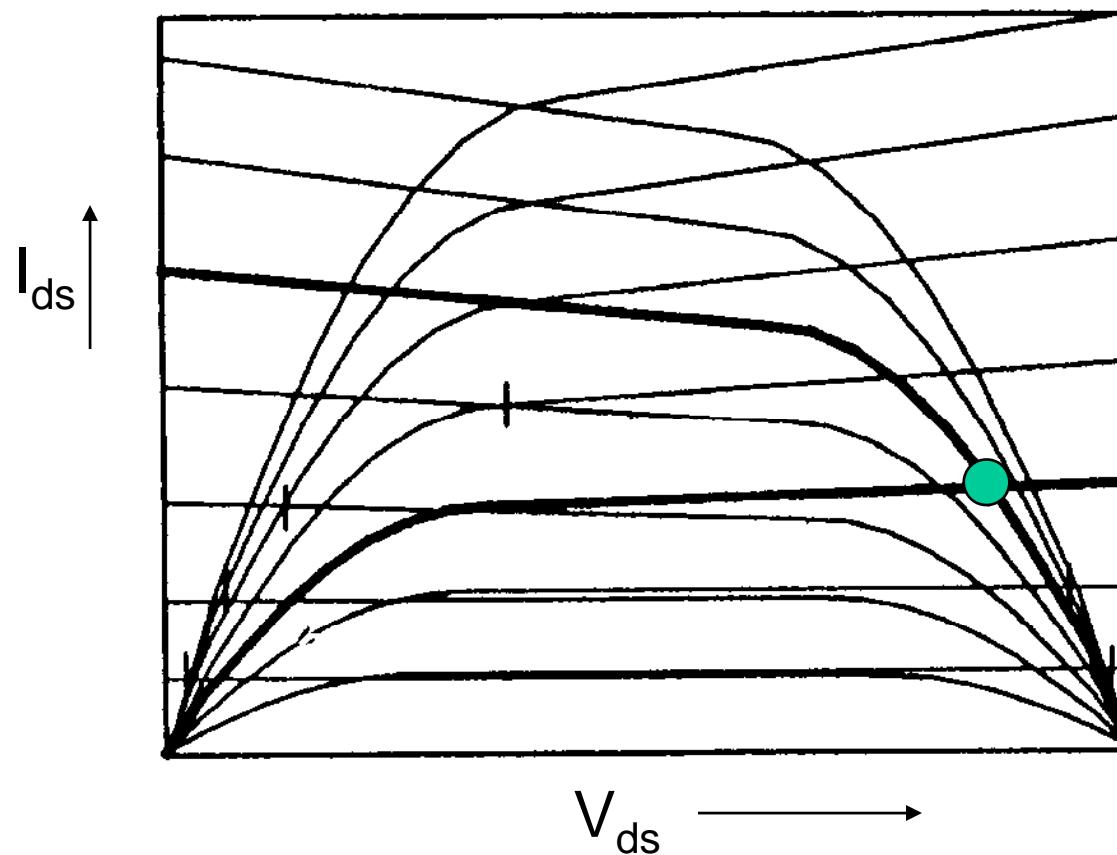


# CMOS Inverter Load Characteristics

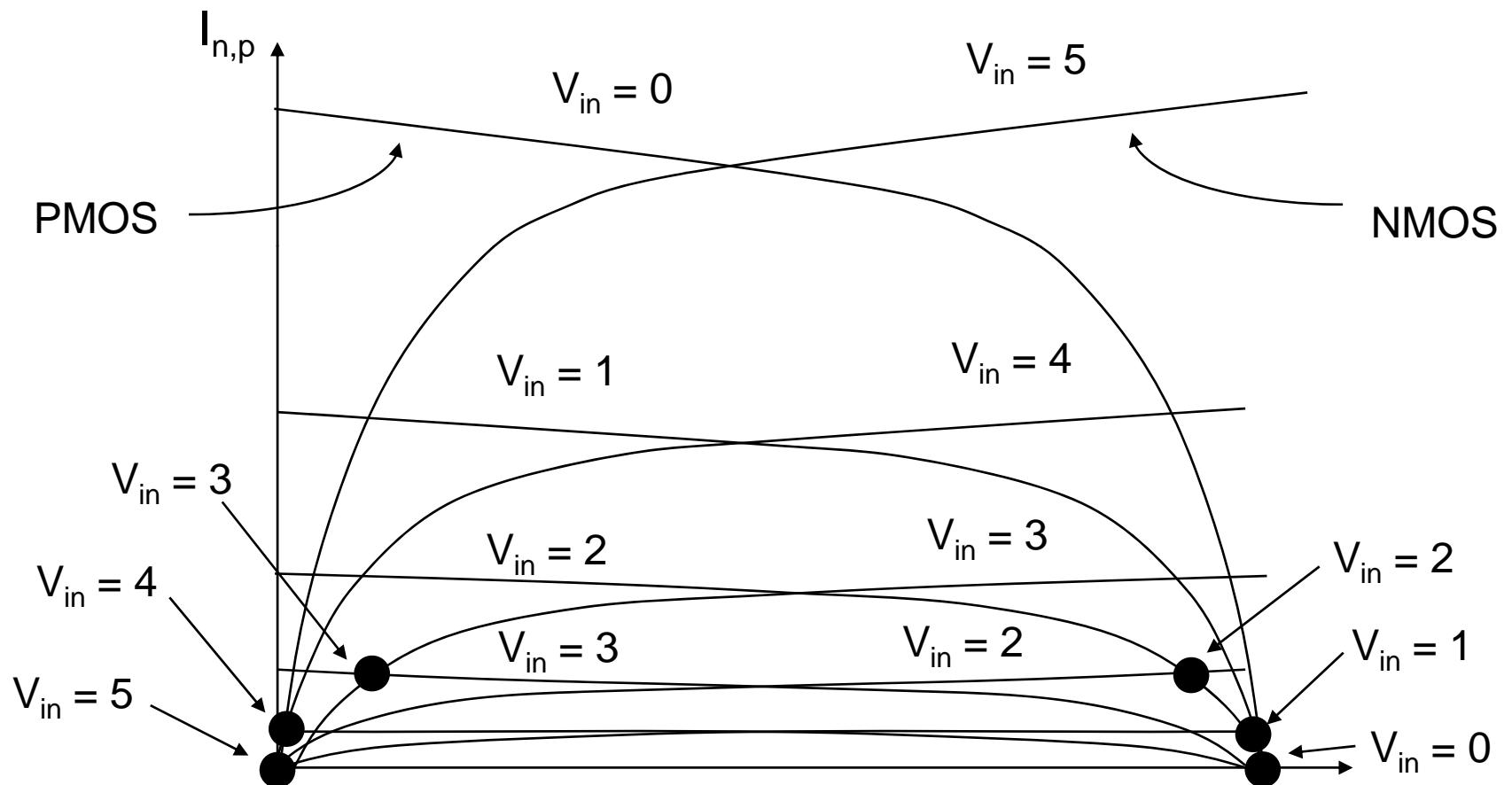

# CMOS Inverter VTC

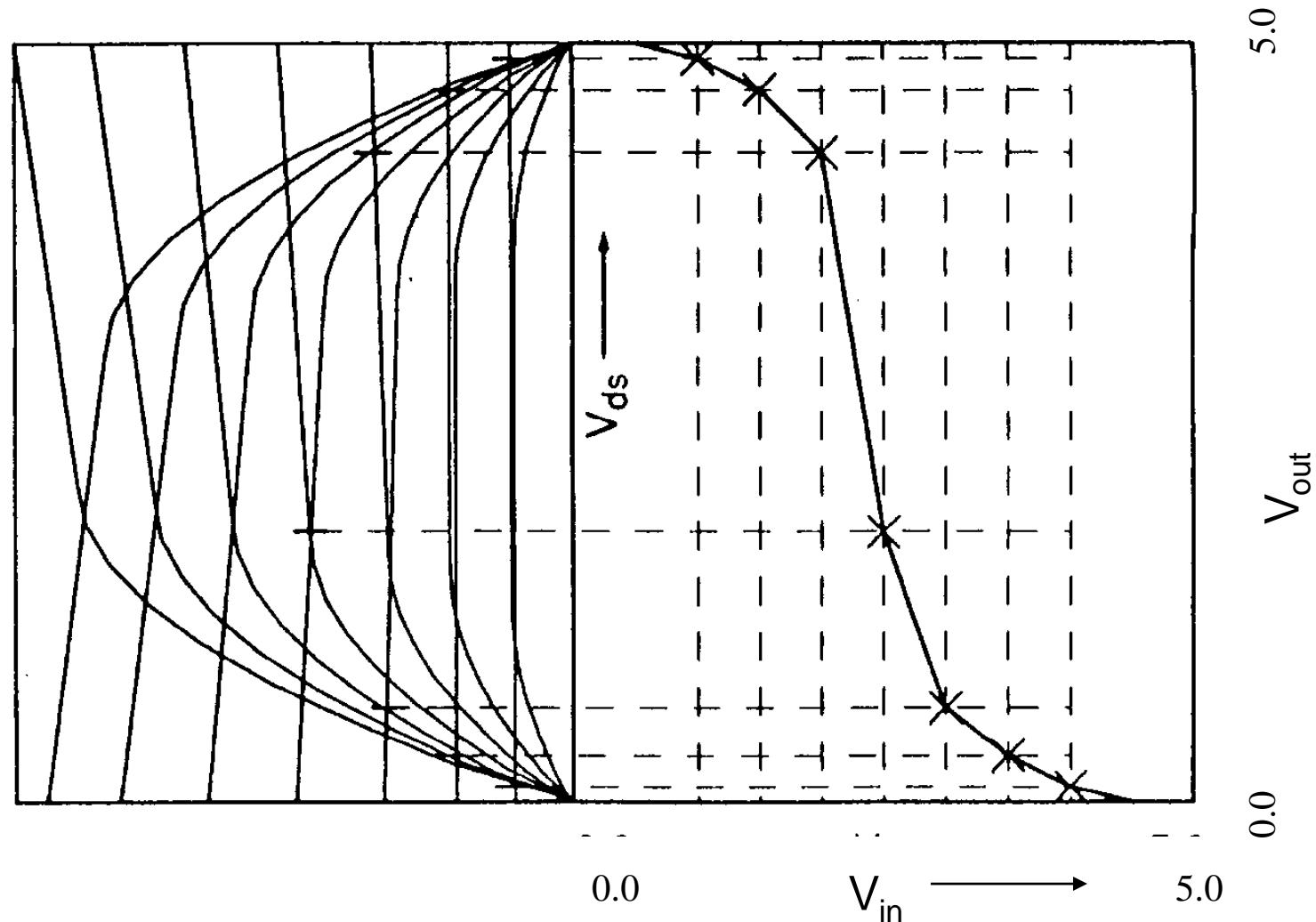


# Inverter Supply Current

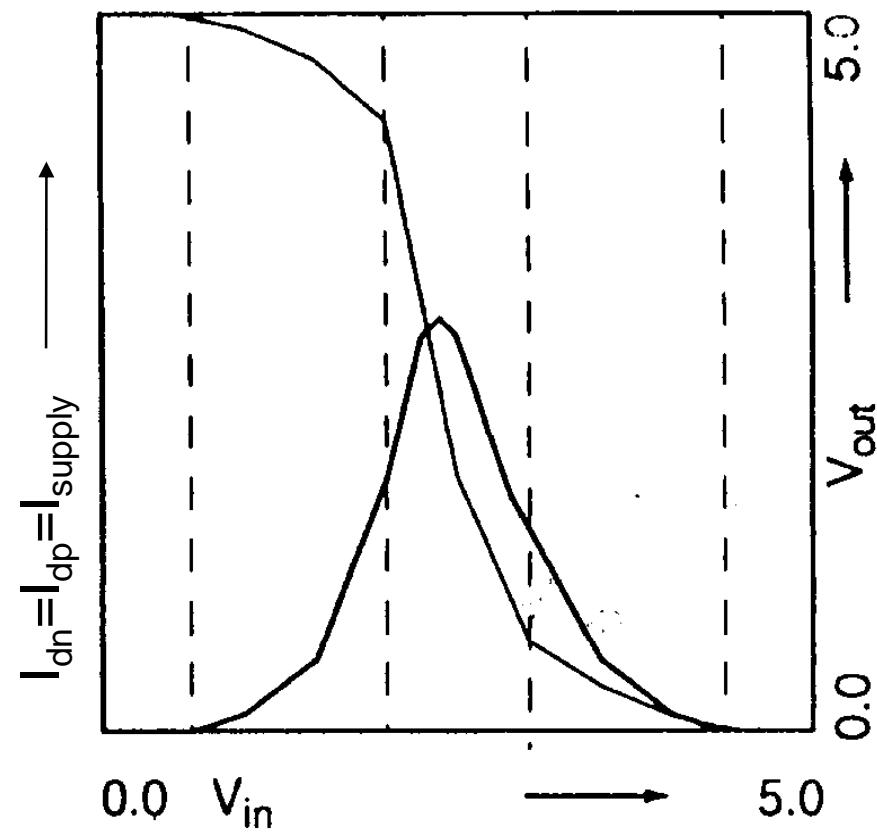
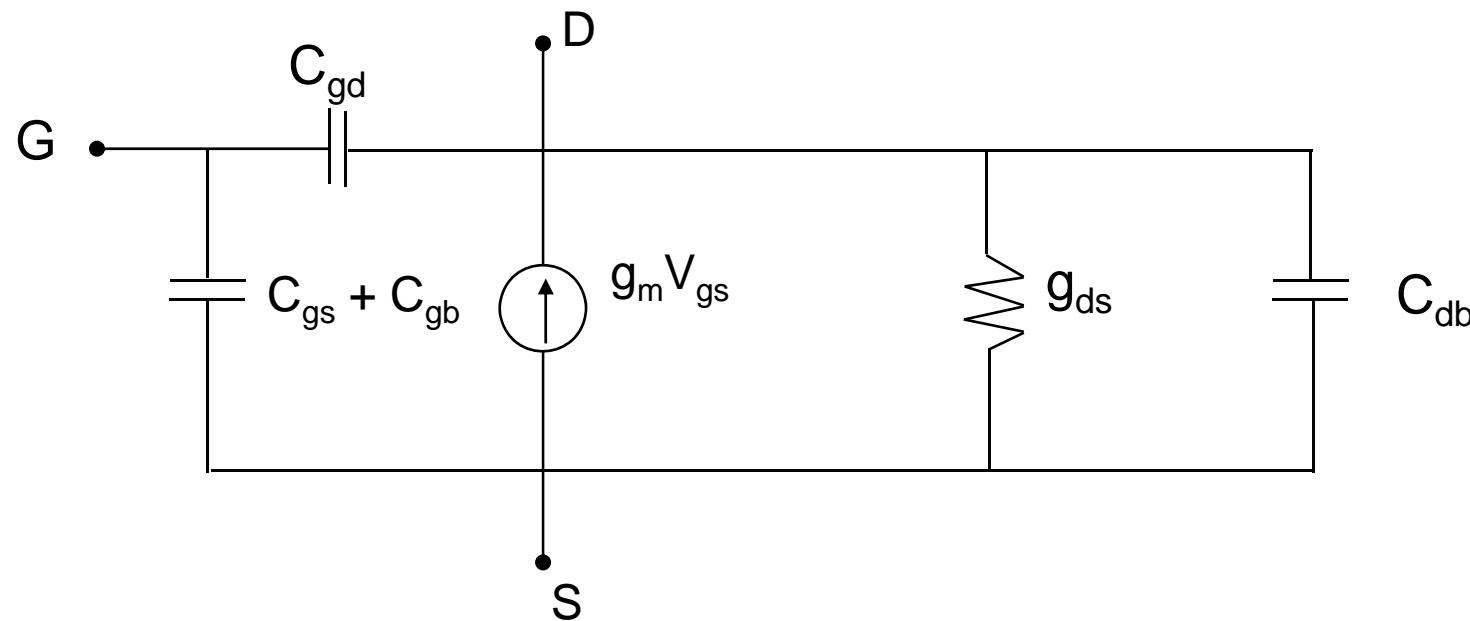
# Small Signal Model for an MOS Transistor

- $V_{sb} = 0$
- voltage-controlled current source ( $g_m$ )
- output conductance ( $g_{ds}$ )
- interelectrode capacitance



# Output Conductance

- By differentiating  $I_{ds}$  w.r.t.  $V_{ds}$
- In linear region

$$I_{ds} = \beta[(V_{gs} - V_t)V_{ds} - \frac{V_{ds}^2}{2}]$$

$$g_{ds} = \beta[(V_{gs} - V_t) - V_{ds}] \quad R_{linear} = \frac{1}{\beta(V_{gs} - V_t - V_{ds})}$$

- In saturation, device behaves like a current source: the current being almost independent of  $V_{ds}$

$$I_{ds} = [\frac{\beta}{2}(V_{gs} - V_t)^2]$$

$$\frac{dI_{ds}}{dV_{ds}} = \frac{d[\frac{\beta}{2}(V_{gs} - V_t)^2]}{dV_{ds}} = 0$$

- In reality, secondary effects result in a slope

$$g_{ds} = I_{ds}\lambda$$

# Transconductance


- Expresses relationship between output current and input voltage

$$g_m = \frac{dI_{ds}}{dV_{gs}} \mid V_{ds} = \text{constant}$$

$$g_m(\text{linear}) = \beta V_{ds}$$


$$g_m(\text{sat.}) = \beta(V_{gs} - V_t)$$

# MOS Transistor Small Signal Model

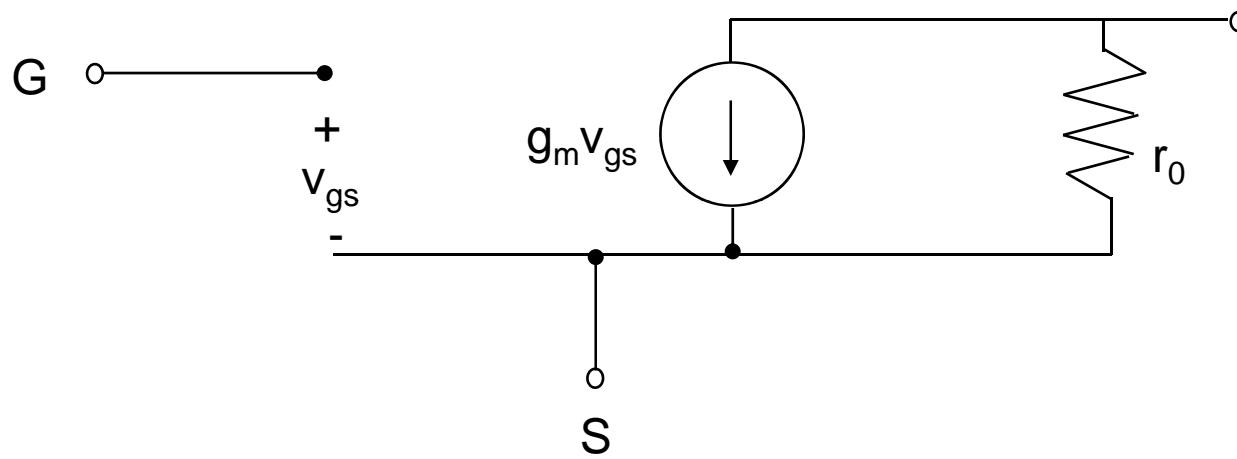

	$g_m$	$r_o$
Linear	$kV_{DS}$	$[k(V_{GS}-V_T-V_{DS})]^{-1}$
Saturation	$k(V_{GS}-V_T)$	$1/\lambda I_D$

# CMOS Inverter

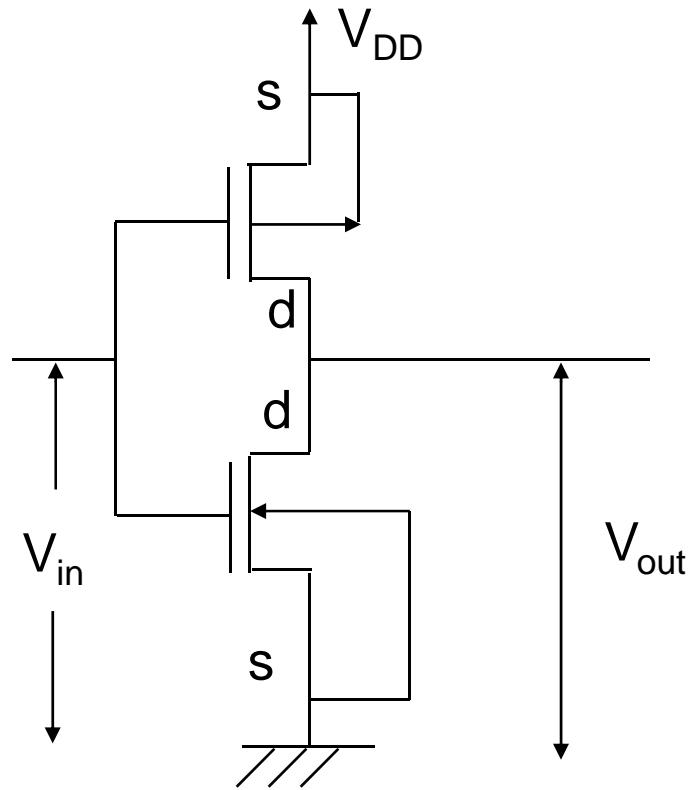


$$\begin{aligned}V_{out} &= V_{DD} - V_{sdp} \\&= V_{DD} + V_{dsp} \\V_{in} &= V_{DD} - V_{sgp} \\&= V_{DD} + V_{gsp}\end{aligned}$$

$$V_{in} = V_{gsn}, V_{out} = V_{dsn}$$

# Regions of Operation


	Cutoff	Non-saturated	Saturated
p-device	$V_{gsp} > V_{tp}$ $V_{in} > V_{tp} + V_{DD}$	$V_{gsp} < V_{tp}$ $V_{in} < V_{tp} + V_{DD}$  $V_{dsp} > V_{gsp} - V_{tp}$ $V_{out} > V_{in} - V_{tp}$	$V_{gsp} = V_{tp}$ $V_{in} < V_{tp} + V_{DD}$  $V_{dsp} < V_{gsp} - V_{tp}$ $V_{out} < V_{in} - V_{tp}$
n-device	$V_{gsn} < V_{tn}$ $V_{in} < V_{tn}$	$V_{gsn} > V_{tn}$ $V_{in} > V_{tn}$  $V_{dsn} < V_{gs} - V_{tn}$ $V_{out} < V_{in} - V_{tn}$	$V_{gsn} > V_{tn}$ $V_{in} > V_{tn}$  $V_{dsn} > V_{gs} - V_{tn}$ $V_{out} > V_{in} - V_{tn}$

# Inverter Operating Regions

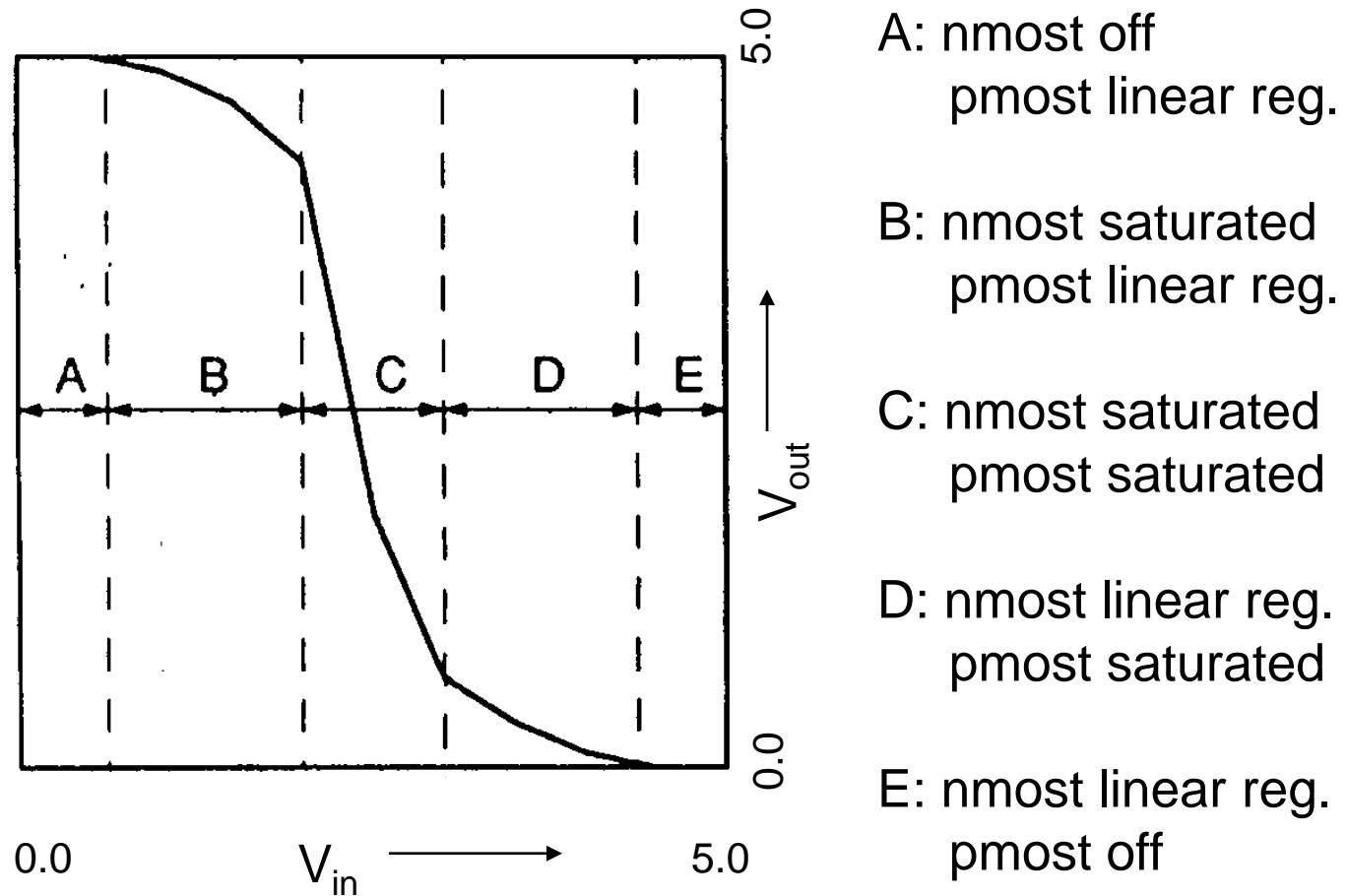

# Inverter Operating Regions

A: nmost off  
pmost linear region

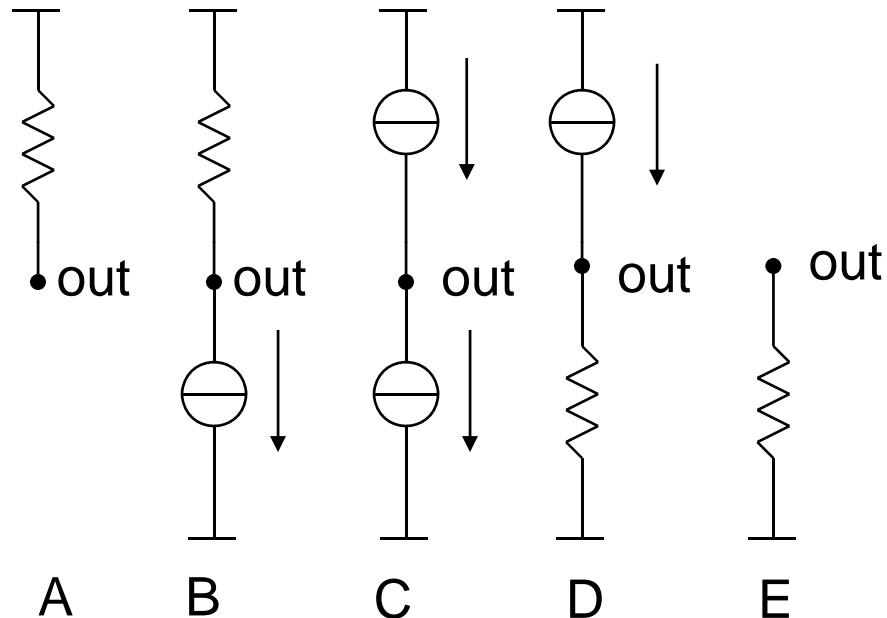

B: nmost saturated  
pmost linear region

C: nmost saturated  
pmost saturated

D: nmost linear region  
pmost saturated

E: nmost linear region  
pmost off

Assume infinite  $r_o$   
when a device is in saturation

## Region A


$(0 \leq V_{in} \leq V_{tn})$

$I_{dsn} = 0 \Rightarrow n\text{-device is cut-off}$   
 $p\text{-device in linear region}$

$$I_{dsn} = -I_{dsp} = 0, \text{ as } I_{dsn} = 0$$

$$V_{dsp} = V_{out} - V_{DD}$$

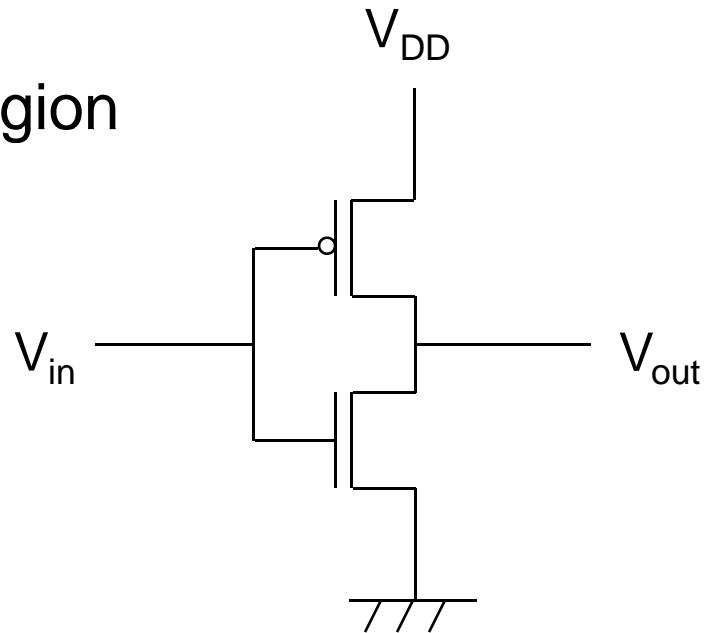
$$\text{With } V_{dsp} = 0, V_{out} = V_{DD}$$


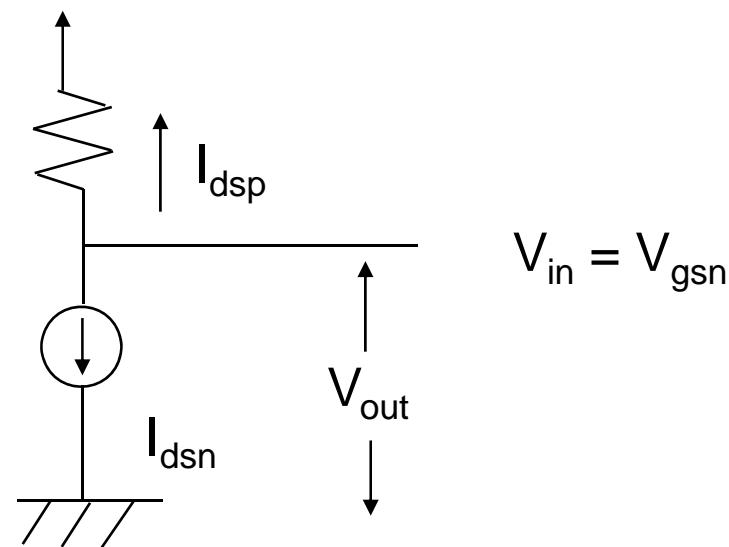
## Region B

$$(V_{tn} \leq V_{in} \leq \frac{V_{DD}}{2})$$

p-device in non-saturated region ( $V_{ds} \neq 0$ )  
n-device is in saturation



## Region B

$$I_{dsn} = \beta_n \frac{[V_{in} - V_{tn}]^2}{2}; \beta = \frac{\mu_n \epsilon}{t_{ox}} \left( \frac{W_n}{L_n} \right)$$

$$V_{gsp} = (V_{in} - V_{DD}) \quad \& \quad V_{dsp} = (V_{out} - V_{DD})$$

$$\therefore I_{dsp} = -\beta_p [(V_{in} - V_{DD} - V_{tp})(V_{out} - V_{DD}) - \frac{(V_{out} - V_{DD})^2}{2}]$$

$$\beta_p = \frac{\mu_p t}{t_{ox}} \left( \frac{W_p}{L_p} \right)$$

Equating  $I_{dsp} = -I_{dsn}$

$$V_{out} = (V_{in} - V_{tp}) + \sqrt{(V_{in} - V_{tp})^2 - 2(V_{in} - \frac{V_{DD}}{2} - V_{tp})V_{DD} - \frac{\beta_n}{\beta_p} (V_{in} - V_{tc})^2}$$

# Region D

$$\left( \frac{V_{DD}}{2} < V_{in} \leq V_{DD} - V_{tp} \right)$$

p : saturation


n : non-saturated

$$I_{dsp} = -\frac{1}{2} \beta_p (V_{in} - V_{DD} - V_{tp})^2$$

$$I_{dsn} = \beta_n [(V_{in} - V_{tn})V_{out} - \frac{V_{out}^2}{2}]$$

$$I_{dsp} = -I_{dsn}$$

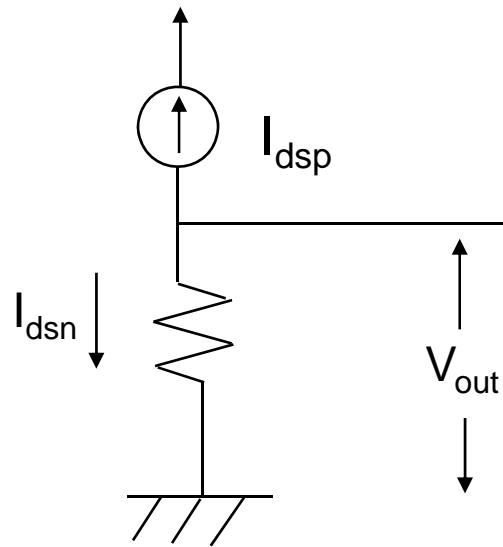
$$\therefore V_{out} = (V_{in} - V_{tn}) - \sqrt{(V_{in} - V_{tn})^2 - \frac{\beta_p}{\beta_n} (V_{in} - V_{DD} - V_{tp})^2}$$



# Determining $V_{IH}$ and $V_{IL}$

At  $V_{IH}$  ( $V_{IL}$ ):  $\frac{\partial V_{out}}{\partial V_{in}} = -1$

*small-signal model of inverter*

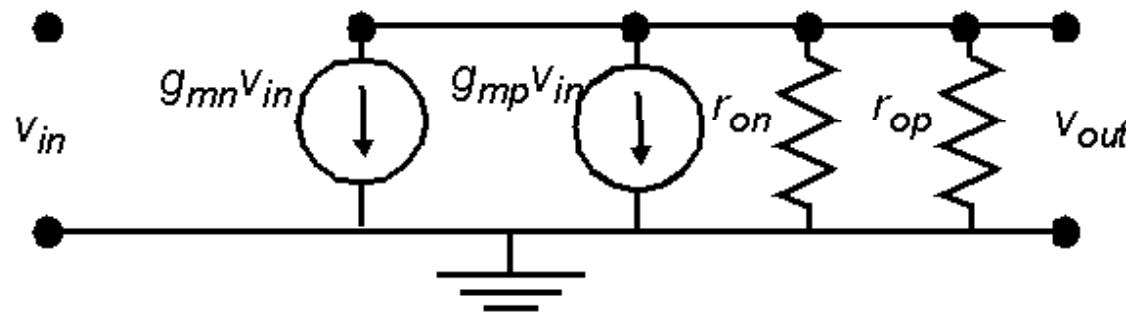

$$g = \frac{v_{out}}{v_{in}} = -(g_{mn} + g_{mp}) \times (r_{on} \parallel r_{op}) = -1$$

Region E  
 $(V_{in} \geq V_{DD} - V_{tp})$

p: cut-off  $I_{dsp} = 0$   
n: linear mode

$V_{gsp} = V_{in} - V_{DD} \rightarrow$  more positive than  $V_{tp}$

$V_{out} = 0$

## Region C (Both devices in Saturation)

$$I_{dsp} = -\frac{\beta_p}{2} (V_{in} - V_{DD} - V_{tp})^2$$

$$I_{dsn} = \frac{\beta_n}{2} (V_{in} - V_{tn})^2$$

Equating  $I_{dsp} = -I_{dsn}$

$$V_{in} = \frac{V_{DD} + V_{tp} + V_{tn} \sqrt{\frac{\beta_n}{\beta_p}}}{1 + \sqrt{\frac{\beta_n}{\beta_p}}}$$

# Gate Threshold Voltage

If  $\beta_n = \beta_p$  &  $V_{tn} = -V_{tp}$

$$V_{in} = \frac{V_{DD}}{2}$$

Region C exists for one value of  $V_{in}$

Possible values of  $V_{out}$  in region C

n-channel	$V_{in} - V_{out} < V_{tn}$	}
	$V_{out} > V_{in} - V_{tn}$	
p-channel	$V_{in} - V_{out} > V_{tp}$	}
	$V_{out} < V_{in} - V_{tp}$	

saturation conditions

$$V_{in} - V_{tn} < V_{out} < V_{in} - V_{tp}$$

In reality, region C has a finite slope

- because in reality  $I_{ds}$  increases slightly with  $V_{ds}$  in saturation

# Typical Parameter Values (1 μm process)

$$\mu_n = 500 \text{ cm}^2 / \text{V-sec}$$

$$\varepsilon = 3.9 \times 8.85 \times 10^{-14} \text{ F/cm}$$

$$t_{ox} = 200 \text{ Å}$$


$$\begin{aligned}\beta_n &= \frac{\mu\varepsilon}{t_{ox}} \left( \frac{W}{L} \right) \\ &= \frac{500 \times 3.9 \times 8.85 \times 10^{-14}}{.2 \times 10^{-5}} \frac{W}{L} \\ &= 88.5 \frac{W}{L} \mu\text{A}/\text{V}^2\end{aligned}$$

$$\mu_p \approx 180 \text{ cm}^2 / \text{V-sec}$$

$$\therefore \beta_p = 31.9 \frac{W}{L} \mu\text{A}/\text{V}^2$$

$$\frac{\beta_n}{\beta_p} = 2.8 \quad (\text{The ratio varies from 2-3})$$

## $\beta_n/\beta_p$ Ratio

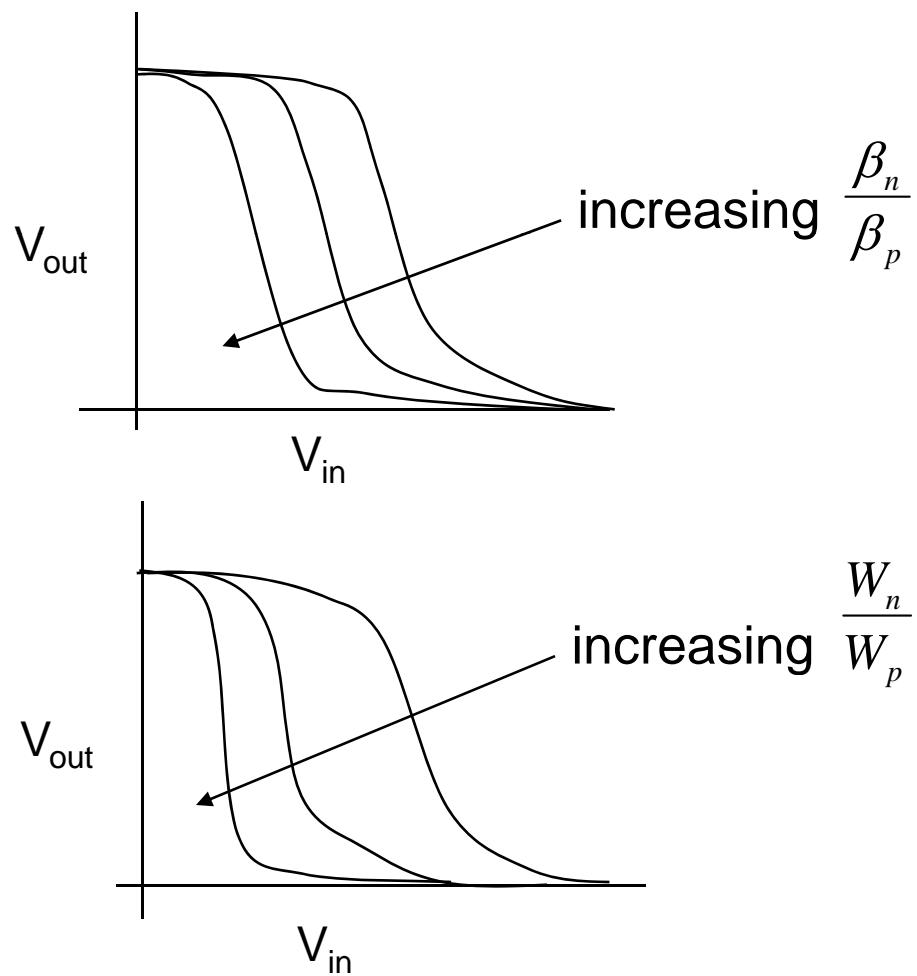

## Effect of $\beta_n/\beta_p$ Ratio

$V_m$  dependent on  $\frac{\beta_n}{\beta_p}$


with change in  $\beta_p$  transition still remains sharp and hence switching performance does not deteriorate

It is desirable to have

$$\frac{\beta_n}{\beta_p} = 1$$

⇒ allows capacitance load to change and discharge in equal times by providing equal current source & sink capability

# Gate Switching Threshold

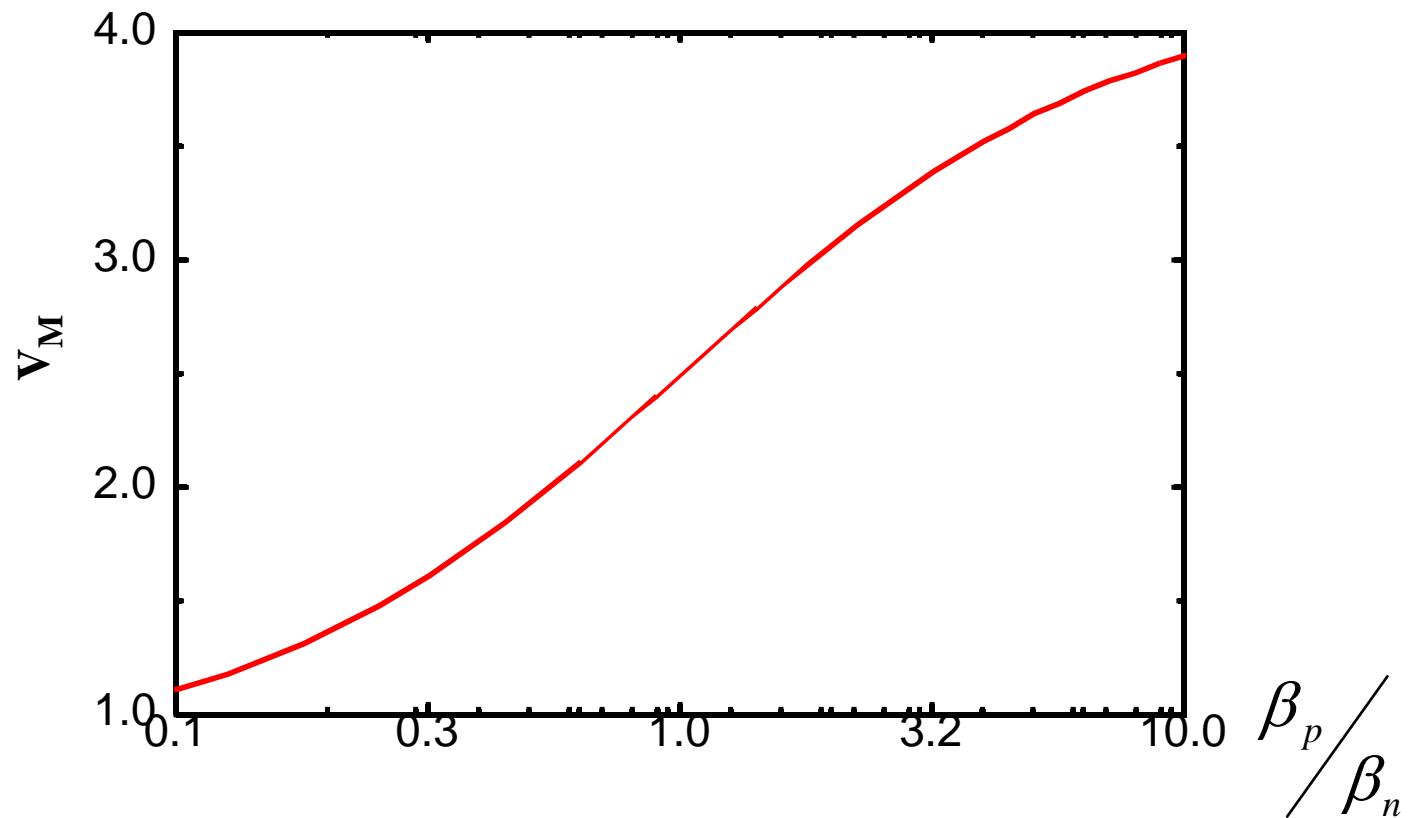

$$V_M = \frac{r(V_{DD} + V_{tp}) + V_{tn}}{r + 1} \quad \text{with} \quad r = \sqrt{\frac{\beta_p}{\beta_n}}$$


## Effect of Temperature

- Temperature similarly affects mobility of holes and electrons
- Temperature increases  $\Rightarrow \mu$  decreases  $\Rightarrow \beta$  decreases
$$\beta \propto T^{-1.5}$$
- Ratio  $\beta_n/\beta_p$  is independent of temperature to a good approximation
- Temperature, however, reduces threshold voltages
- Extent of region A reduces and extent of region E increases
- VTC shifts to the left as the temperature increases


## Switching Characteristics

- Switching speed - limited by time taken to charge and discharge,  $C_L$
- Rise time,  $t_r$  : waveform to rise from 10% to 90% of its steady state value
- Fall time,  $t_f$  : 90% to 10% of steady state value
- Delay time,  $t_d$  : time difference between input transition (50%) and 50% output level


# CMOS Inverter: Transient Response

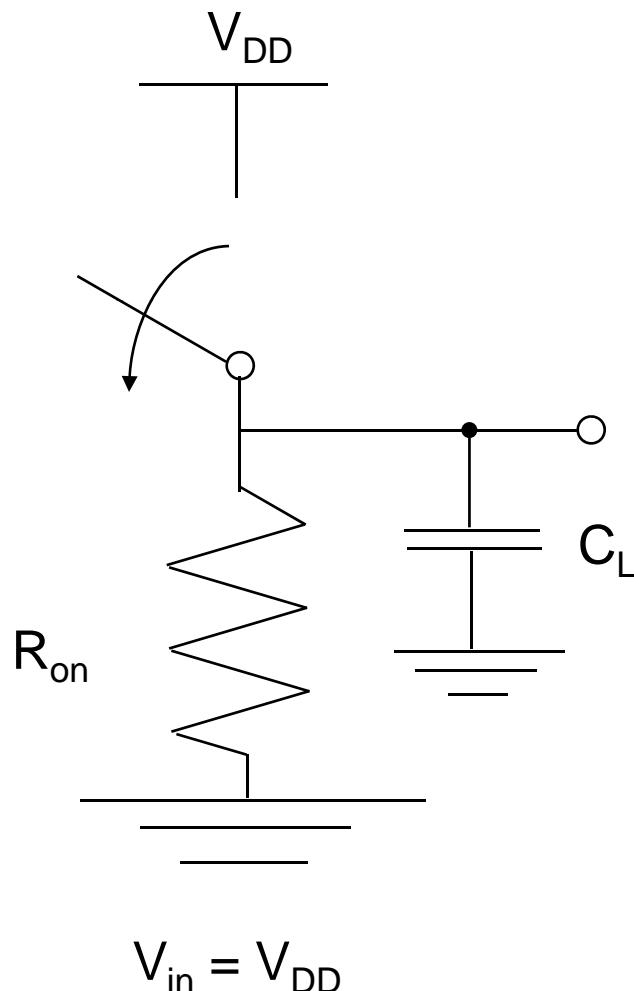
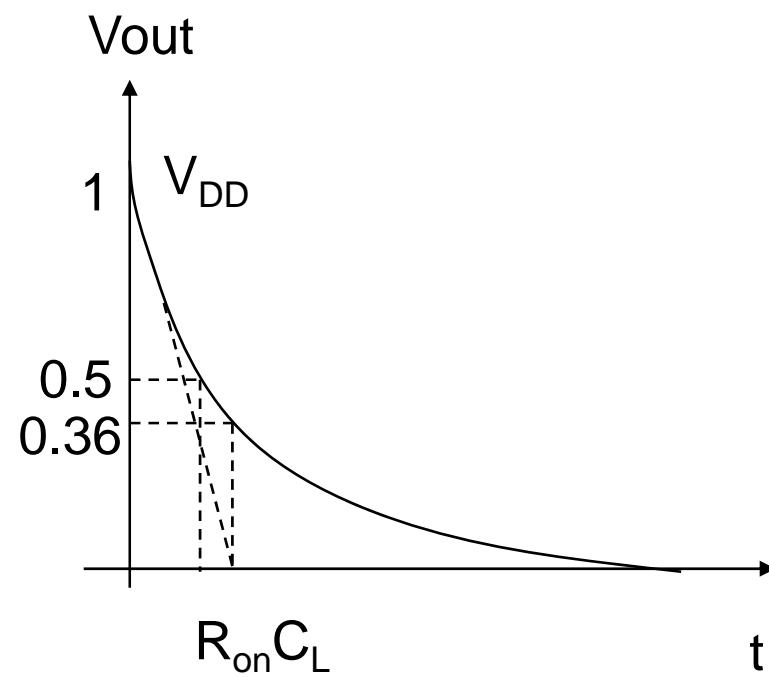
$$t_{pHL} = f(R_{on}C_L) \\ = 0.69 R_{on}C_L$$



# CMOS Inverter Propagation Delay

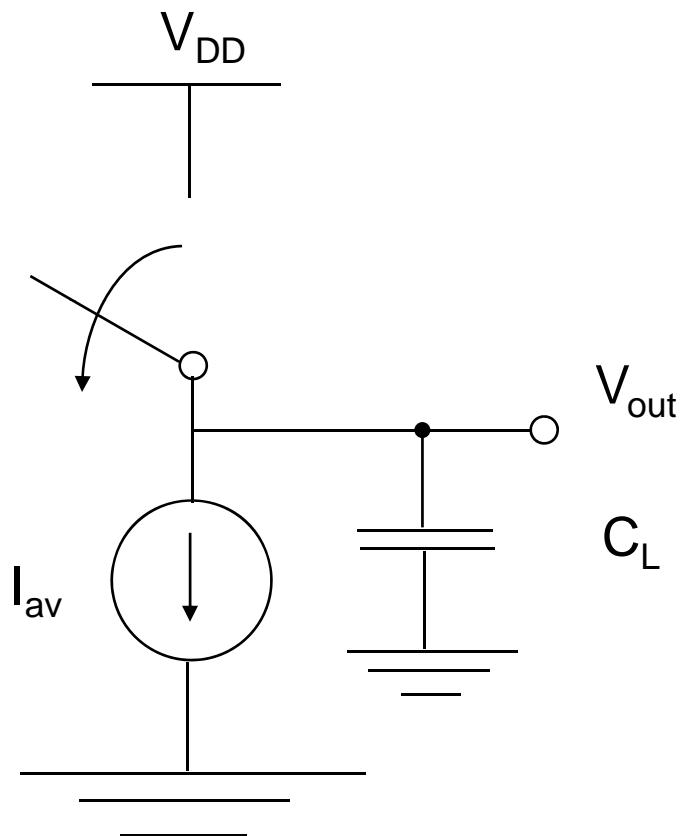

$$V_{in} = V_{DD}$$

$$t_{pHL} = \frac{C_L V_{swing} / 2}{I_{av}}$$

$$I_{av} = \frac{I(V_{out} = V_{DD}) + I(V_{out} = V_{DD}/2)}{2}$$

$$= \frac{\beta_n}{2} \left( \frac{7V_{DD}^2}{8} + \frac{V_{tn}^2}{2} - \frac{3V_{DD}V_{tn}}{2} \right)$$

# Inverter Propagation Delay

- Assume n-device still in saturation at  $V_{out} = V_{DD}/2$

$$I_{av} = \frac{\beta_n}{2} (V_{DD} - V_{tn})^2$$



$$t_{pHL} = \frac{C_L V_{DD}}{\beta_n (V_{DD} - V_{tn})^2}$$

$$\approx \frac{C_L}{\beta_n V_{DD}}$$

$$t_{pLH} \approx \frac{C_L}{\beta_p V_{DD}}$$

$$t_p \approx \frac{C_L}{2V_{DD}} \left( \frac{1}{\beta_p} + \frac{1}{\beta_n} \right)$$


# Analysis of Fall Time

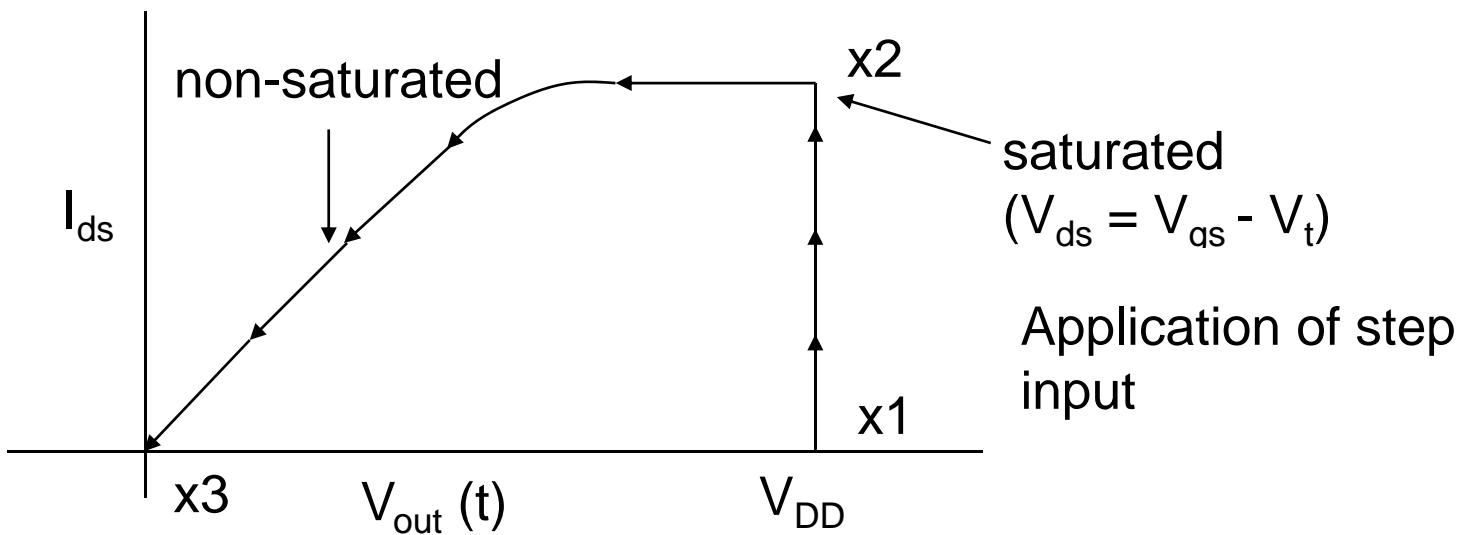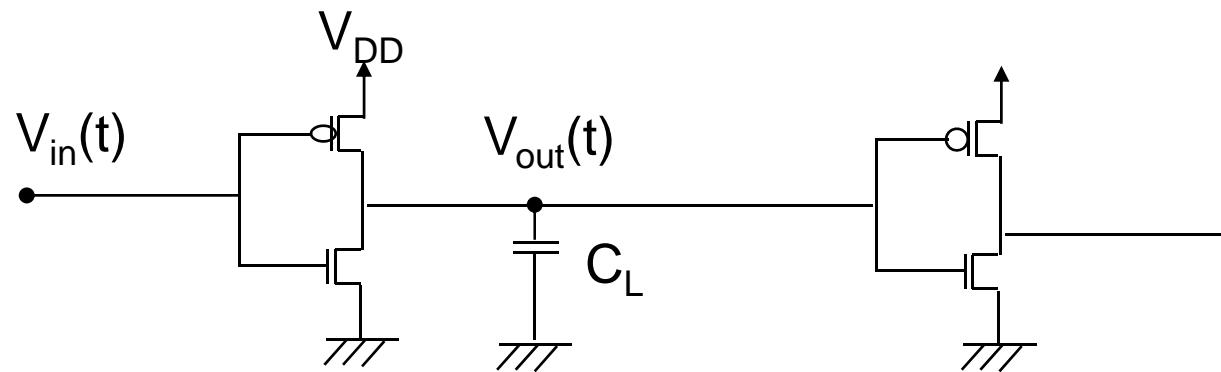
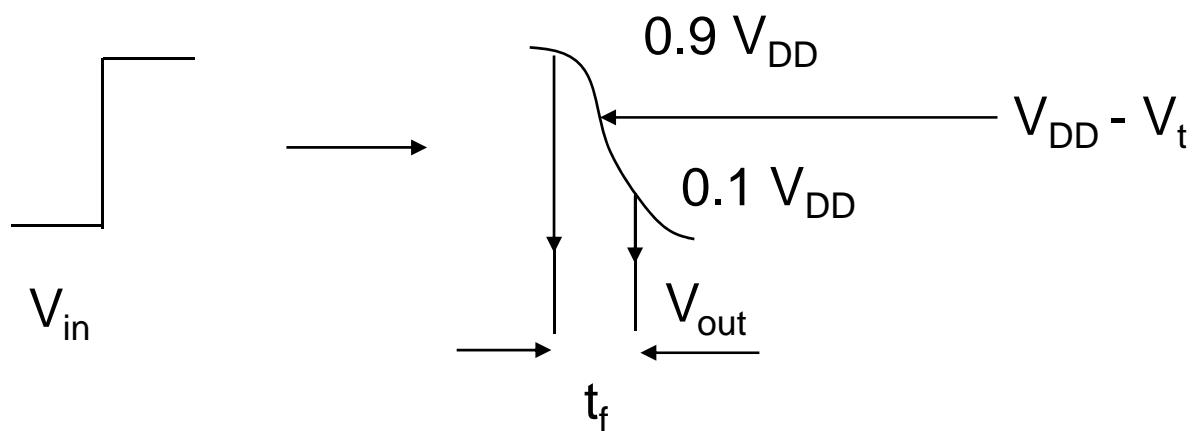
# Components of Fall Time

$t_f = t_{f1} + t_{f2} \longrightarrow V_{out}$  drops from  $V_{dd} - V_t$  to  $0.1 V_{DD}$


$V_{out}$  drops from  $0.9V_{dd}$  to  $V_{dd} - V_t$


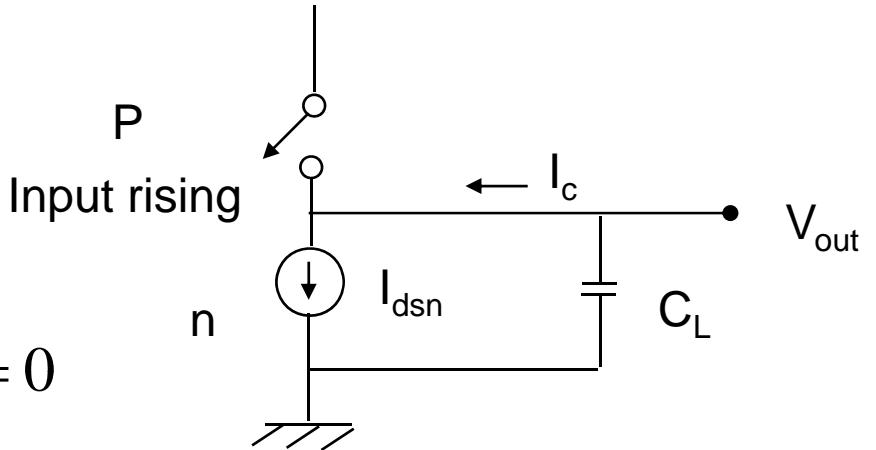
# Fall Time for Saturated Region

Saturated,  $V_{out} \geq V_{DD} - V_{tn}$

$$C_L \frac{dV_{out}}{dt} + \frac{\beta_n}{2} (V_{DD} - V_{tn})^2 = 0$$




Integrating from  $t = t_1$  (corresponding to  $V_{out} = 0.9 V_{DD}$ ) to  $t = t_2$  (corresponding to  $V_{out} = (V_{DD} - V_{tn})$ )

$$t_{f1} = 2 \frac{C_L}{\beta_n (V_{DD} - V_{tn})^2} \int_{V_{DD} - V_{tn}}^{0.9V_{DD}} dV_{out}$$

$$= \frac{2C_L (V_{tn} - 0.1V_{DD})}{\beta_n (V_{DD} - V_{tn})^2}$$

# Fall Time for Non-Saturated Region

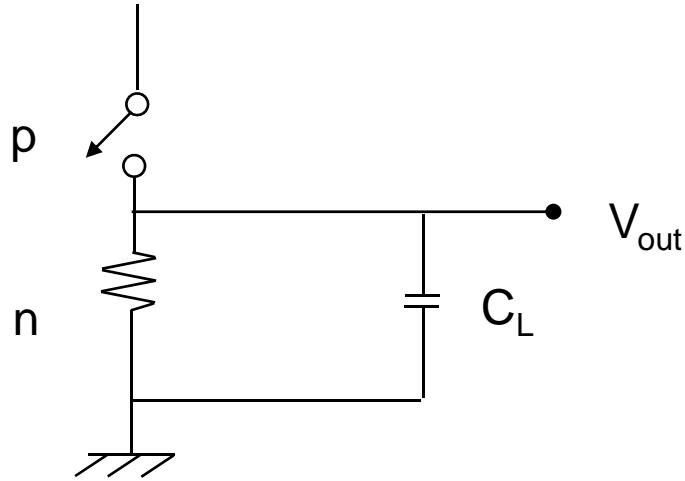

Non-saturated :  $0 \leq V_{out} \leq V_{DD} - V_{tn}$

$$C_L \frac{dV_{out}}{dt} + \beta_n [(V_{DD} - V_{tn}) \cdot V_{out} - \frac{V_{out}^2}{2}] = 0$$

$$t_{f2} = \frac{C_L}{\beta_n (V_{DD} - V_{tn})} \int_{V_{DD} - V_{tn}}^{0.1V_{DD}} \frac{dV_{out}}{\frac{V_{out}^2}{2(V_{DD} - V_{tn})} - V_{out}}$$

# Fall Time for Non-Saturated Region

$$\begin{aligned} t_{f2} &= \frac{C_L}{\beta_n(V_{DD} - V_{tn})} \int_{V_{DD}-V_{tn}}^{0.1V_{DD}} \frac{dV_{out}}{\frac{V_{out}^2}{2(V_{DD} - V_{tn})} - V_{out}} \\ &= \frac{C_L}{\beta_n(V_{DD} - V_{tn})} \ln\left(\frac{19V_{DD} - 20V_{tn}}{V_{DD}}\right) \\ &= \frac{C_L}{\beta_n V_{DD} (1-n)} \ln(19 - 20n) \end{aligned}$$

$$\text{where } n = \frac{V_{tn}}{V_{DD}}$$

# Fall Time Computation

$$t_f = t_{f1} + t_{f2}$$

$$= 2 \frac{C_L}{\beta_n V_{DD}(1-n)} \left[ \frac{(n-0.1)}{(1-n)} + \frac{1}{2} \ln(19 - 20n) \right]$$

$$t_f \approx k \frac{C_L}{\beta_n V_{DD}}$$

$k = 3 \sim 4$  for  $V_{DD} = 3 \sim 5V$  and  $V_{tn} = 0.5 \sim 1V$

# Rise Time

$$t_r = 2 \frac{C_L}{\beta_p V_{DD} (1-p)} \left[ \frac{(p-0.1)}{(1-p)} + \frac{1}{2} \ln(19 - 20p) \right]$$

with  $p = \frac{|V_{tp}|}{V_{DD}}$

$$t_r \approx k \frac{C_L}{\beta_p V_{DD}}$$

For equally sized n- and p transistors

$$\beta_n \approx 2\beta_p$$

$$t_f \approx \frac{t_r}{2}$$

## Sizing for Identical Rise/Fall Time

For same  $t_f$  and  $t_r$

$$\frac{\beta_n}{\beta_p} = 1$$

Increase the width of p-device to

$$W_p \approx 2 - 3W_n$$

## Delay Time: First Order Approximation

- Gate delay is dominated by the output rise and fall time

$$t_{dr} = \frac{t_r}{2}$$

$$t_{df} = \frac{t_f}{2}$$

# General Delay Time Computation

- Similar to the computation of rise/fall times
  - Saturation region from  $t = t_1$  (corresponding to  $V_{out} = V_{DD}$ ) to  $t = t_2$  (corresponding to  $V_{out} = (V_{DD} - V_{tn})$ )
  - Linear region from  $t = t_2$  (corresponding to  $V_{out} = (V_{DD} - V_{tn})$ ) to  $t = t_3$

$$\begin{aligned}t_2 - t_1 &= 2 \frac{C_L}{\beta_n (V_{DD} - V_{tn})^2} \int_{V_{DD} - V_{tn}}^{V_{DD}} dV_{out} \\&= \frac{2C_L(V_{tn})}{\beta_n (V_{DD} - V_{tn})^2}\end{aligned}$$

# Delay Time Computation

$$t_3 - t_2 = \frac{C_L}{\beta_n(V_{DD} - V_{tn})} \int_{V_{DD}-V_{tn}}^{V_{out}} \frac{dV'_{out}}{\frac{V'^2_{out}}{2(V_{DD} - V_{tn})} - V'_{out}}$$

$$= \frac{C_L}{\beta_n(V_{DD} - V_{tn})} \ln\left(\frac{2V_{DD} - 2V_{tn} - V_{out}}{V_{out}}\right)$$

$$= \frac{C_L}{\beta_n V_{DD}(1-n)} \ln\left(\frac{2(1-n) - V_o}{V_o}\right)$$

where  $n = \frac{V_{tn}}{V_{DD}}$ ,  $V_o = \frac{V_{out}}{V_{DD}}$

# Delay Time

$$t_{Dn} = t_3 - t_1 = A_n \frac{C_L}{\beta_n V_{DD}}$$


Delay  $\propto C_L$  (optimize  $C_L$  to decrease delay)

$\propto \frac{1}{V_{DD}}$  (decrease  $V_{DD}$  increases delay)

$\propto \frac{1}{\beta}$  (if  $W \uparrow$  or  $L \downarrow$ , delay decreases)

Three major parameters for optimizing speed of CMOS


# Components of $C_L$

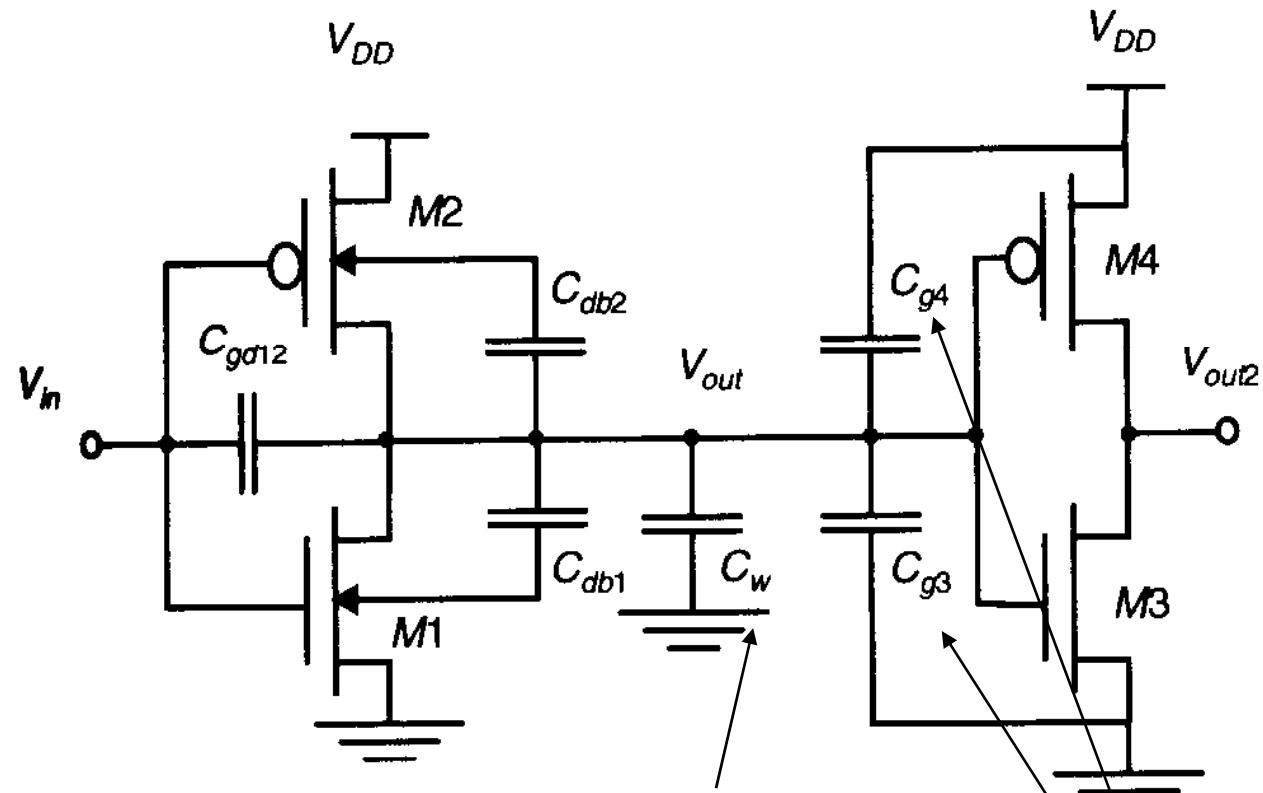

$C_w$  = wiring capacitance

$C_g$  = gate capacitance =  $C_{ox}WL$

# Miller Effect

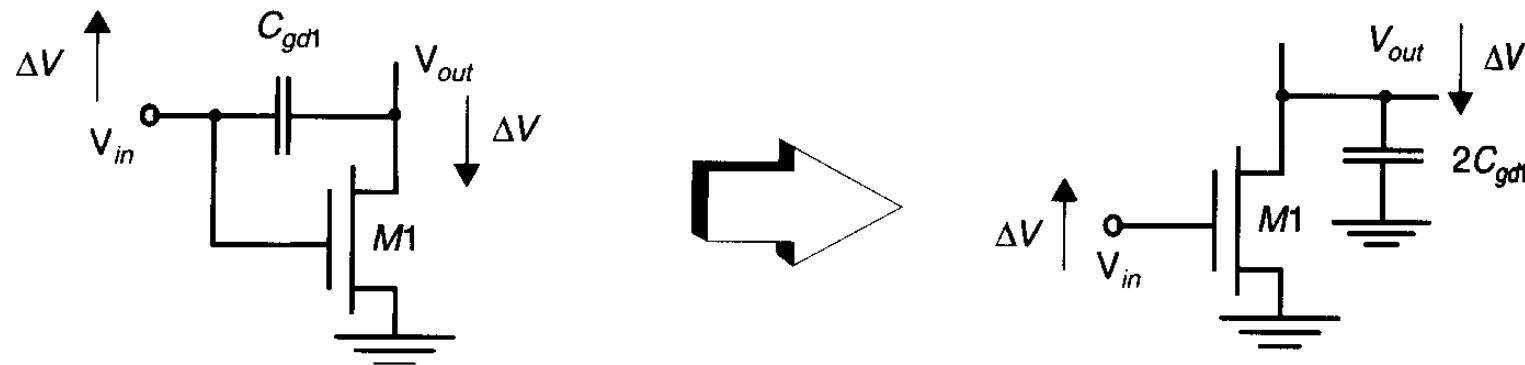

- Effective voltage change over the gate-drain capacitor is actually twice the output voltage swing
- Contribution of gate-drain capacitor should be counted twice

# Junction Capacitance


- Non-linear capacitor modeled by linear capacitor with the same change in charge for the voltage range of interest

$$C_{eq} = K_{eq} C_{j0}$$


$$K_{eq} = \frac{-\phi_0^m}{(V_{high} - V_{low})(1-m)} \left[ (\phi_0 - V_{high})^{1-m} - (\phi_0 - V_{low})^{1-m} \right]$$

- Linearize over the interval {5V, 2.5V} for the high-to-low transition and {0, 2.5V} for the low-to-high transition
- Correspond to { $V_{high}=-5V$ ,  $V_{low}=-2.5V$ } and { $V_{high}=0$ ,  $V_{low}=-2.5V$ } for NMOS

## Delay in function of $V_{DD}$

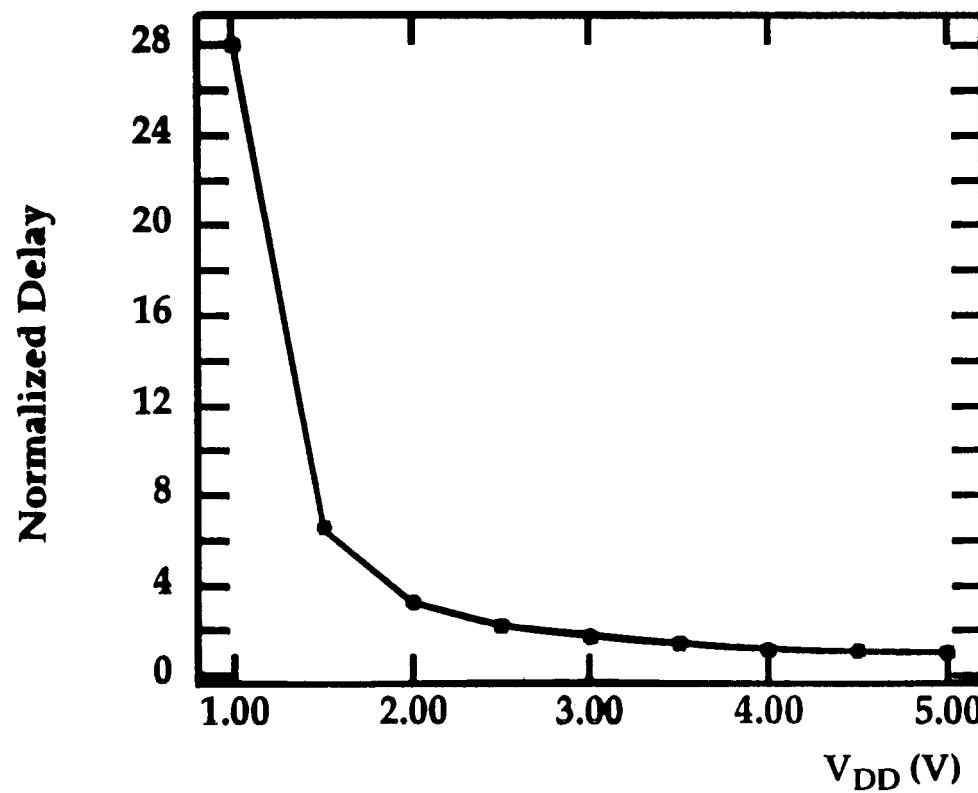
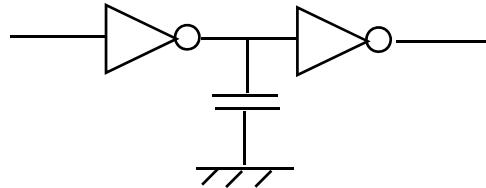
# Sizing of Inverter Loaded by an Identical Gate



Load cap. of first gate:

$$C_L = (C_{dp1} + C_{dn1}) + (C_{gp2} + C_{gn2}) + C_w$$

where

$C_{dp1}, C_{dn1}$  → diffusion capacitance of first gate

$C_{gp2}, C_{gn2}$  → gate capacitance of second gate

$C_w$  → wiring capacitance

If PMOS devices are  $\alpha$  times larger than the NMOS ones,

$$\alpha = \frac{(W/L)_p}{(W/L)_n}$$

all transistor capacitances will scale in approximately the same way

# Sizing of Inverter

$$C_{dp1} \approx \alpha C_{dn1}$$

$$C_{gp2} \approx \alpha C_{gn2}$$

$$\therefore C_L = (1 + \alpha)(C_{dn1} + C_{gn2}) + C_w$$

$$\begin{aligned} t_p &= \frac{t_r + t_f}{2} = \frac{C_L}{2V_{DD}} \left( \frac{A_n}{\beta_n} + \frac{A_p}{\beta_p} \right) \\ &= \frac{C_L}{2V_{DD} \cdot \beta_n} \left( A_n + \frac{A_p \beta_n}{\beta_p} \right) \\ &= \frac{C_L}{2V_{DD} \cdot \beta_n} \left( A_n + \frac{A_p \mu_n}{\mu_p} \cdot \frac{(W/L)_n}{(W/L)_p} \right) \\ &= \frac{C_L}{2V_{DD} \cdot \beta_n} \left( A_n + \frac{A_p \mu_n}{\mu_p \alpha} \right) \end{aligned}$$

# Sizing of Inverter

$$\begin{aligned} t_p &= \frac{C_L}{2V_{DD} \cdot \beta_n} \left( A_n + \frac{A_p \mu_n}{\mu_p \alpha} \right) \\ &= \frac{(1+\alpha)(C_{dn1} + C_{gn2}) + C_w}{2V_{DD} \cdot \beta_n} \left( A_n + \frac{A_p \mu_n}{\mu_p \cdot \alpha} \right) \end{aligned}$$

Let  $\frac{\partial t_p}{\partial \alpha} = 0$  to get optimal  $\alpha$


$$\alpha_{opt} = \sqrt{\frac{\mu_n}{\mu_p} \frac{A_p}{A_n} \left( 1 + \frac{C_w}{C_{dn1} + C_{gn2}} \right)}$$

If  $C_w \ll C_{dn1} + C_{gn2}$ ,  $A_p = A_n$

$$\alpha_{opt} \approx \sqrt{\frac{\mu_n}{\mu_p}} \approx 1.73 \rightarrow \text{Contrast to 3 which is normally used in the non-cascaded case}$$
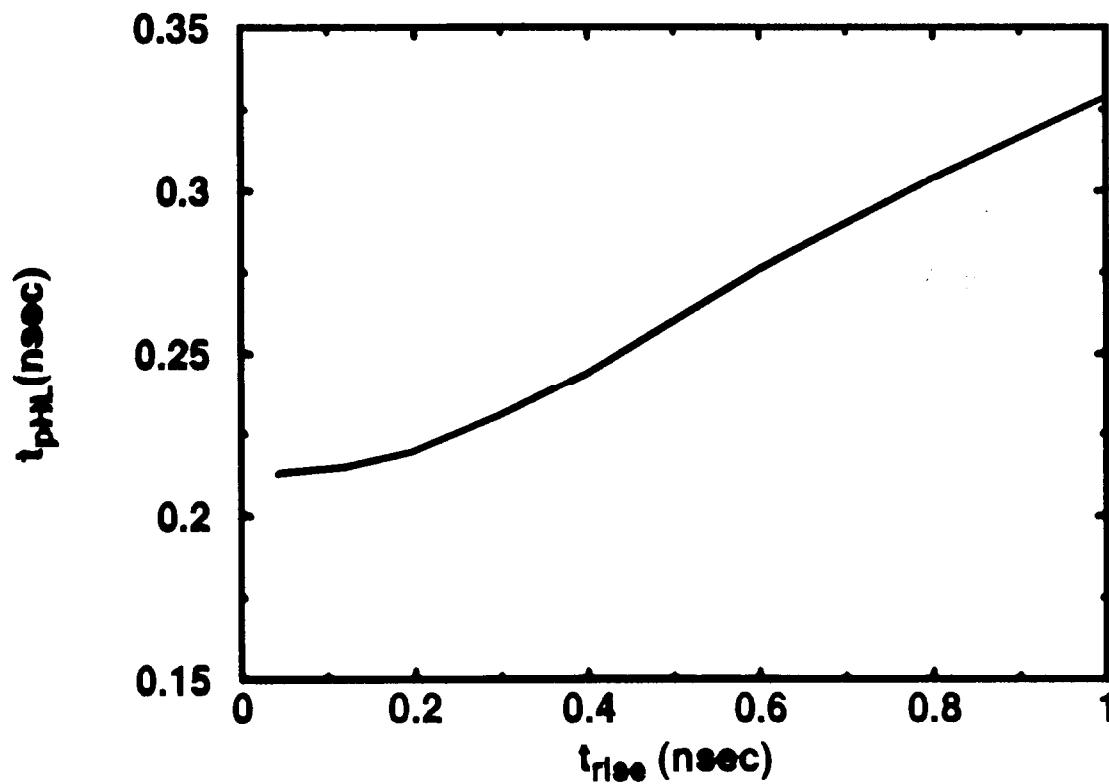
# Impact of Rise Time on Delay

$$t_{PHL}(\text{actual}) = \sqrt{t_{pHL}^2(\text{step}) + (t_r / 2)^2}$$




Minimum-size inverter with fanout of a single gate

# Velocity Saturation

- Under long channel model, saturation current  $\propto V_{DD}^2$
- In small-geometry devices, this no longer holds:  $I_{av} \propto V_{DD}$
- Therefore, for  $V_{DD} \gg V_T$  we have,

$$t_p \approx \frac{C_L}{2} \left( \frac{1}{k_p} + \frac{1}{k_n} \right) \quad k_{n,p} = \kappa v_{SAT} C_{ox} W_{n,p}$$

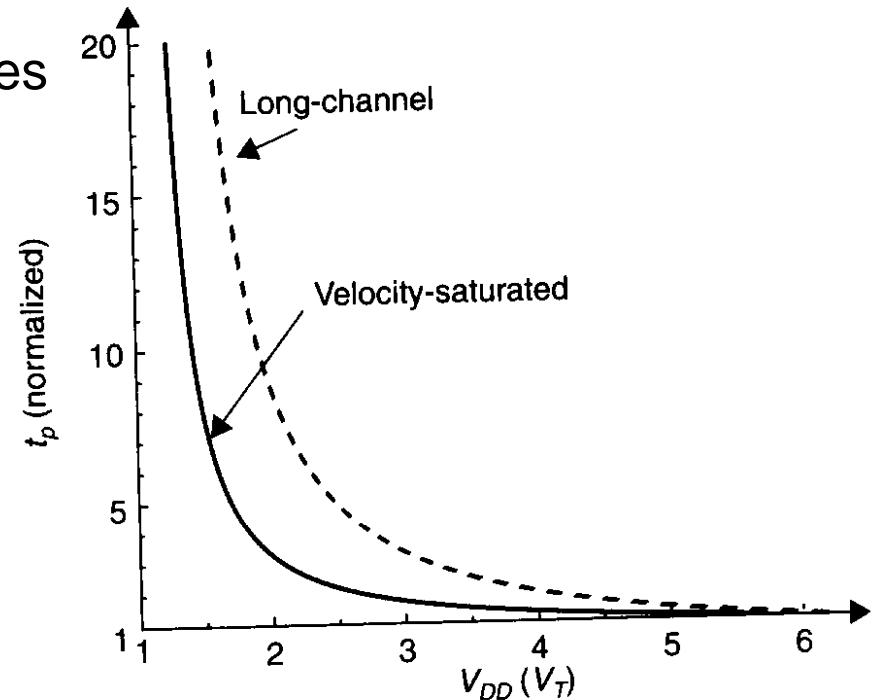- Running velocity saturated devices at high  $V_{DD}$  is not beneficial
- Lowering  $V_{DD}$  below  $2V_T$  sharply increases delay




## Source/Drain Resistance

- In small-geometry devices, source and drain resistance affects switching currents
  - Source of the transistor is no longer grounded, body effect increases threshold voltage
  - $V_{gs}$  is also reduced
  - Current is reduced

# Power Consumption

- Static Power
  - Leakage current
  - Sub-threshold conductance
- Dynamic Power
  - Capacitive Power due to charging/discharging of capacitive load
  - Short-circuit power due to direct path currents when there is a temporary connection between power and ground

# Static Power Consumption

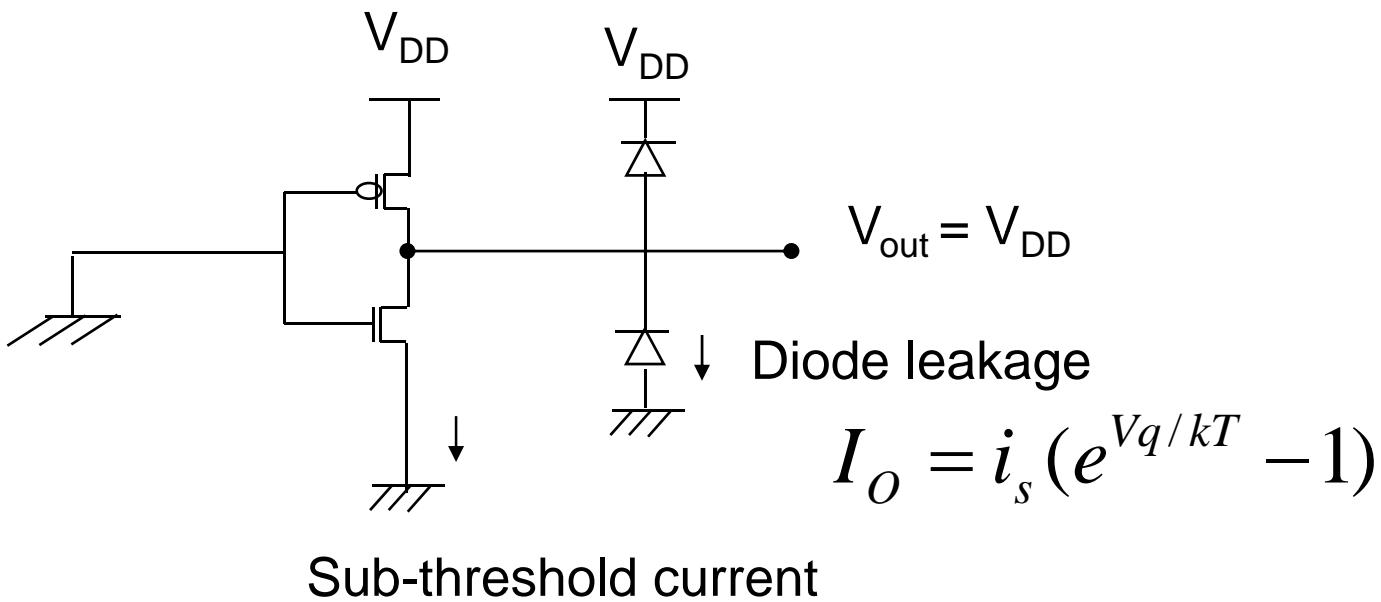


$$P_{\text{static}} = I_{\text{leakage}} \cdot V_{DD}$$

## Static Consumption



- Leakage current through the reverse biased diode junctions
- For typical devices it is between  $0.1\text{nA} - 0.5\text{nA}$  at room temperature
- For a die with 1 million devices operated at 5 V, this results in  $0.5\text{mW}$  power consumption → not much
- Junction leakage current is caused by thermally generated carriers -> therefore is a strong function of temperature
- More important is sub-threshold leakage when threshold voltage is close to 0

# Dynamic Consumption due to $C_L$

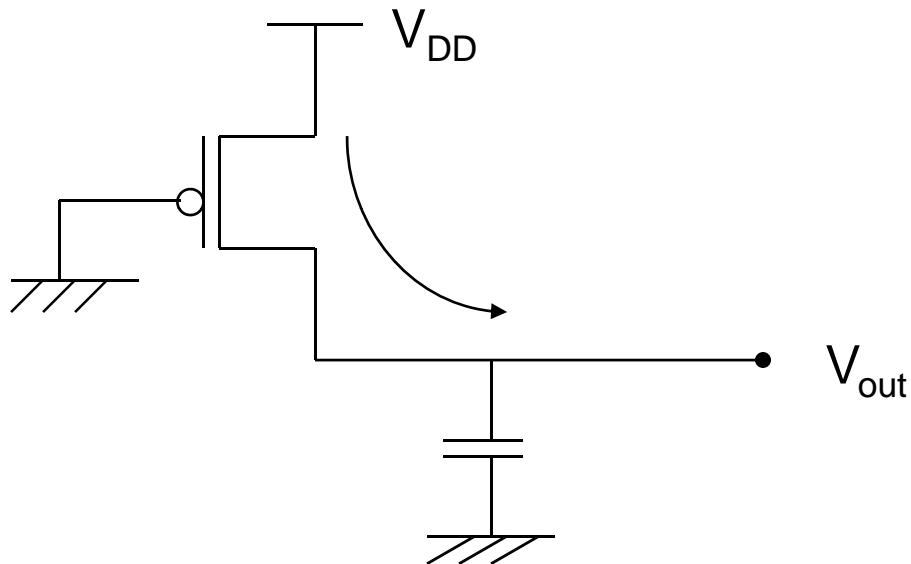

- low-to-high transition
- Assume 0 rise and fall times

# Dynamic Power due to $C_L$

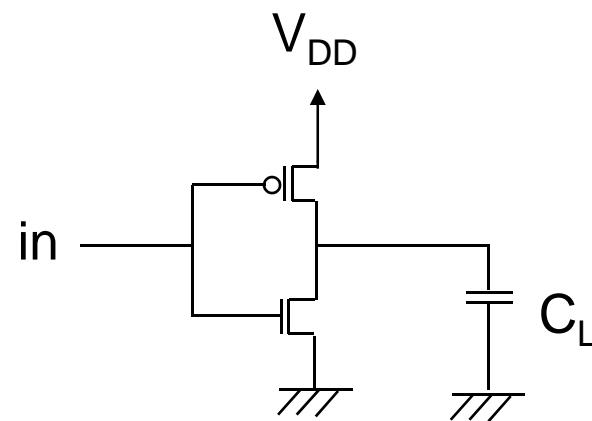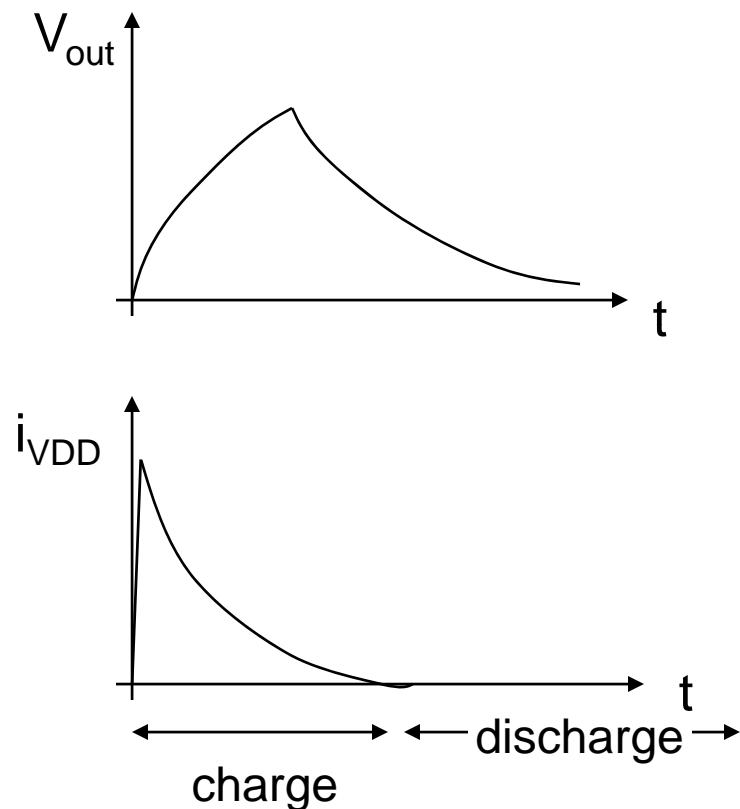

Define:

$E_{VDD}$  : energy taken from supply during a transition

$E_C$ : energy stored on capacitor at the end of transition

# Energy Consumed and Stored

$$\begin{aligned} E_{V_{DD}} &= \int_0^\infty i_{VDD}(t)V_{DD}dt = V_{DD} \int_0^\infty C_L \frac{dV_{out}}{dt} dt \\ &= C_L V_{DD} \int_0^{V_{DD}} dV_{out} \\ &= C_L V_{DD}^2 (= QV_{DD}) \end{aligned}$$

$$\begin{aligned} E_C &= \int_0^\infty i_{VDD}(t)V_{out}dt = \int_0^\infty C_L \frac{dV_{out}}{dt} V_{out} dt \\ &= C_L V_{DD} \int_0^{V_{DD}} V_{out} dV_{out} \\ &= \frac{C_L \cdot V_{DD}^2}{2} \end{aligned}$$

Half the energy is stored in Capacitor ! Other half is dissipated in the PMOS transistor !!

For each switching cycle ( L → H & H → L), amount of energy dissipated in  $C_L \cdot V_{DD}^2$


$$P_{\text{dynamic}} = C_L \cdot V_{DD}^2 \cdot f$$

- Example
  - 1.2 $\mu$  CMOS chip
  - 100 MHz clock rate
  - Average load capacitance of 30 fF/gate
  - 5V power supply
- Power consumption/gate = 75  $\mu$ W
- Design with 200,000 gates: 15W !
- Pessimistic evaluation: not all gates switch at the full rate
- Have to consider the activity factor  $\alpha$ : Effective switching capacitance =  $\alpha C_L$
- Reducing  $V_{DD}$  has a quadratic effect on  $P_{\text{dynamic}}$

# Direct Path Current

- inputs have finite rise and fall times
- Direct current path from  $V_{DD}$  to GND while PMOS and NMOS are ON simultaneously for a short period

$$P_{SC} = I_{mean} \cdot V_{DD}$$

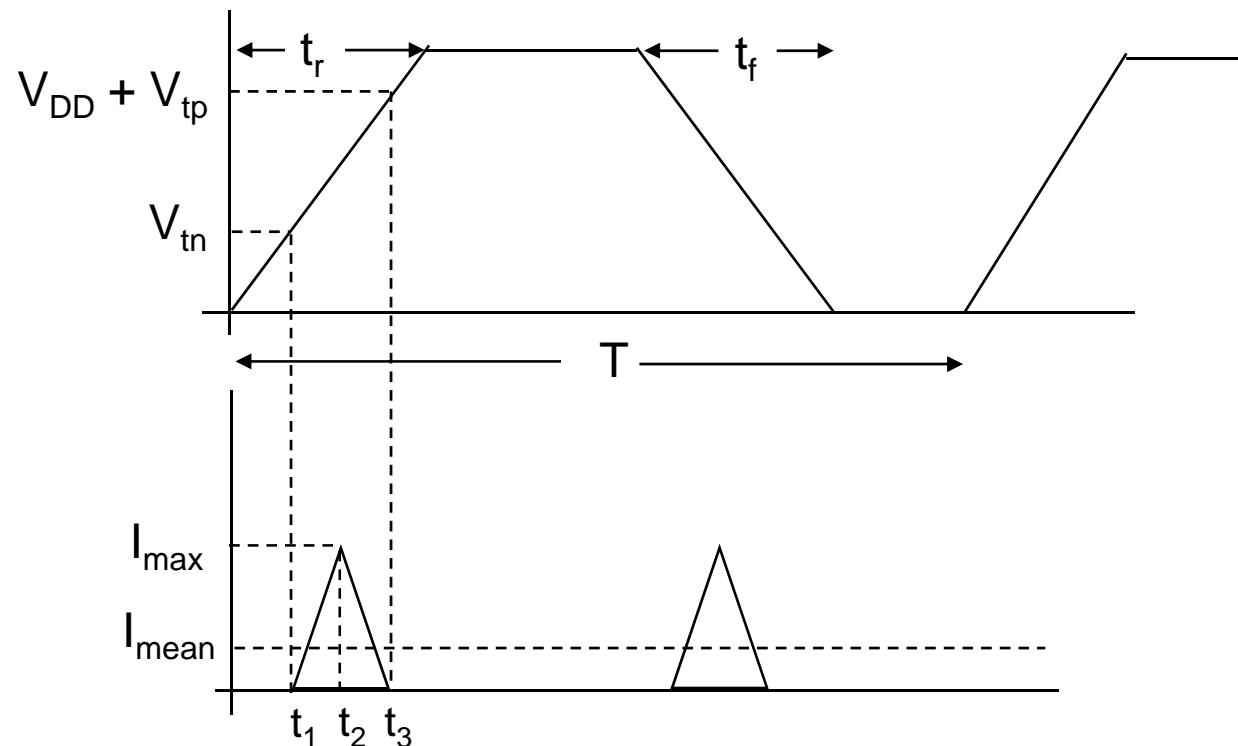

# Symmetrical Inverter Without Load

$$I_{mean} = 2 \left[ \frac{1}{T} \int_{t_1}^{t_2} I(t) dt + \frac{1}{T} \int_{t_2}^{t_3} I(t) dt \right]$$

If  $V_{tn} = -V_{tp} = V_T$  and  $\beta_n = \beta_p = \beta$   
and that the behavior around  $t_2$  is symmetrical

$$I_{mean} = 2 \times \frac{2}{T} \int_{t_1}^{t_2} \frac{\beta}{2} (V_{in}(t) - V_t)^2 dt$$

with  $V_{in}(t) = \frac{V_{DD}}{t_r} t$

$$t_1 = \frac{V_t}{V_{DD}} \cdot t_r$$

$$t_2 = \frac{t_r}{2}$$


$$t_r = t_f = t_{rf}$$

# Symmetrical Inverter Without Load


$$\begin{aligned} I_{mean} &= \frac{2\beta}{T} \int_{t_{rf}V_T/V_{DD}}^{t_{rf}/2} \left( \frac{V_{DD}}{t_{rf}} \cdot t - V_t \right)^2 dt \\ &= \frac{2\beta}{T} \left[ \frac{t_{rf}}{3V_{DD}} \left( \frac{V_{DD}}{t_{rf}} \cdot t - V_t \right)^3 \right]_{t_{rf}V_T/V_{DD}}^{t_{rf}/2} \\ &= \frac{2t_{rf}}{3T} \cdot \frac{\beta}{V_{DD}} \left( \frac{V_{DD}}{2} - V_t \right)^3 \\ &= \frac{t_{rf}}{12T} \cdot \frac{\beta}{V_{DD}} (V_{DD} - 2V_t)^3 \end{aligned}$$

$$P_{sc} = \frac{\beta}{12} (V_{DD} - 2V_t)^3 \frac{t_{rf}}{T}$$


# Short Circuit Current with Loads

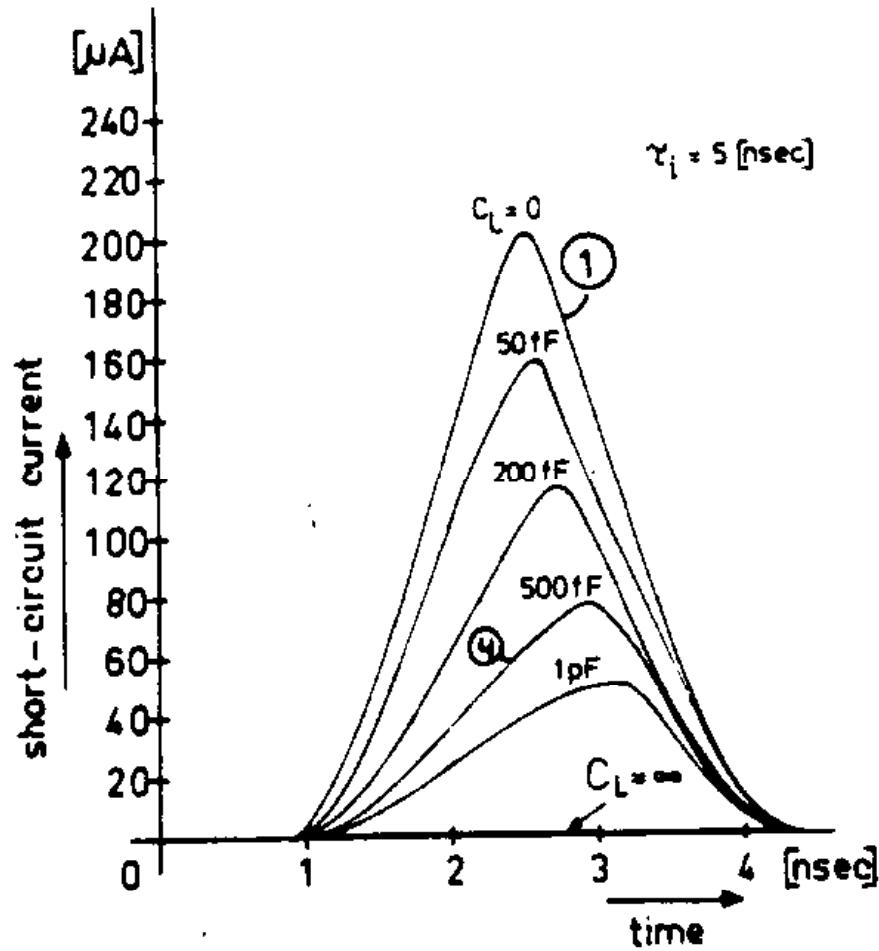

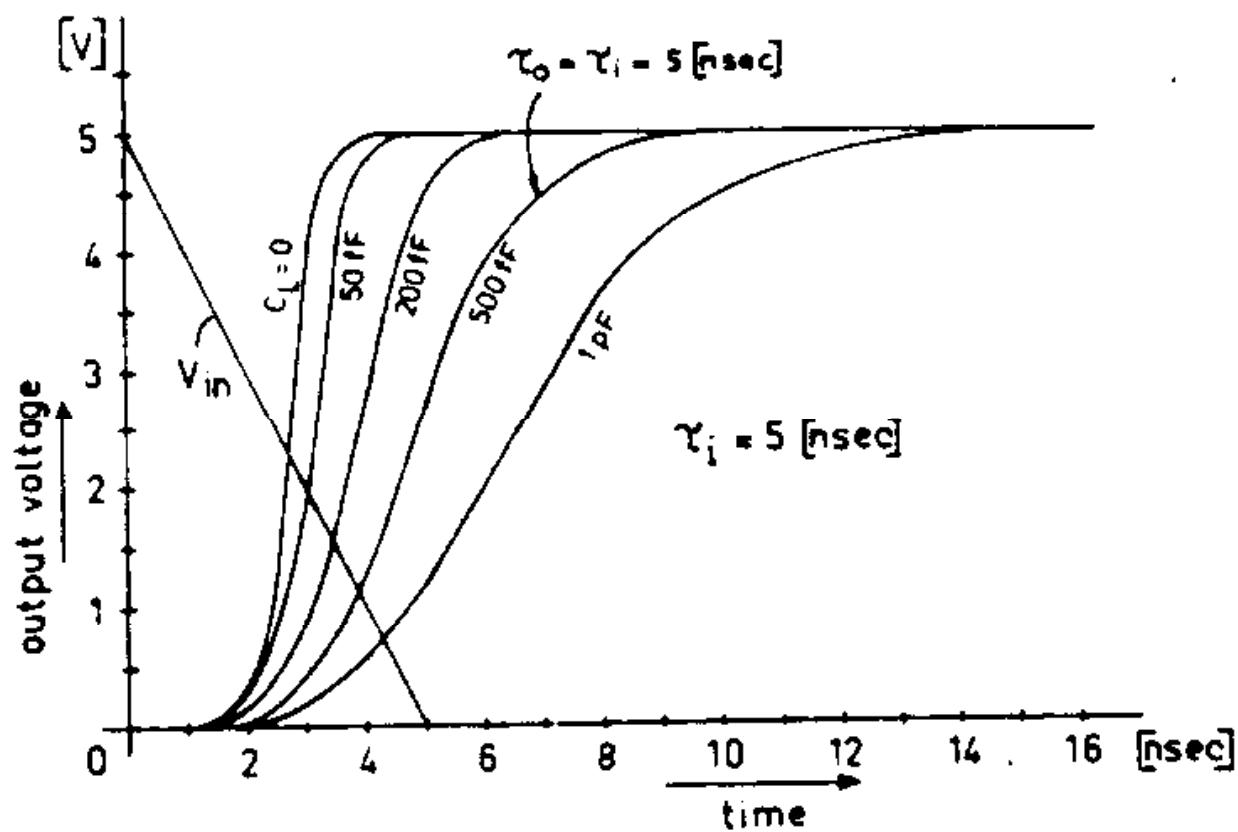
# Output Transitions under Different Loads


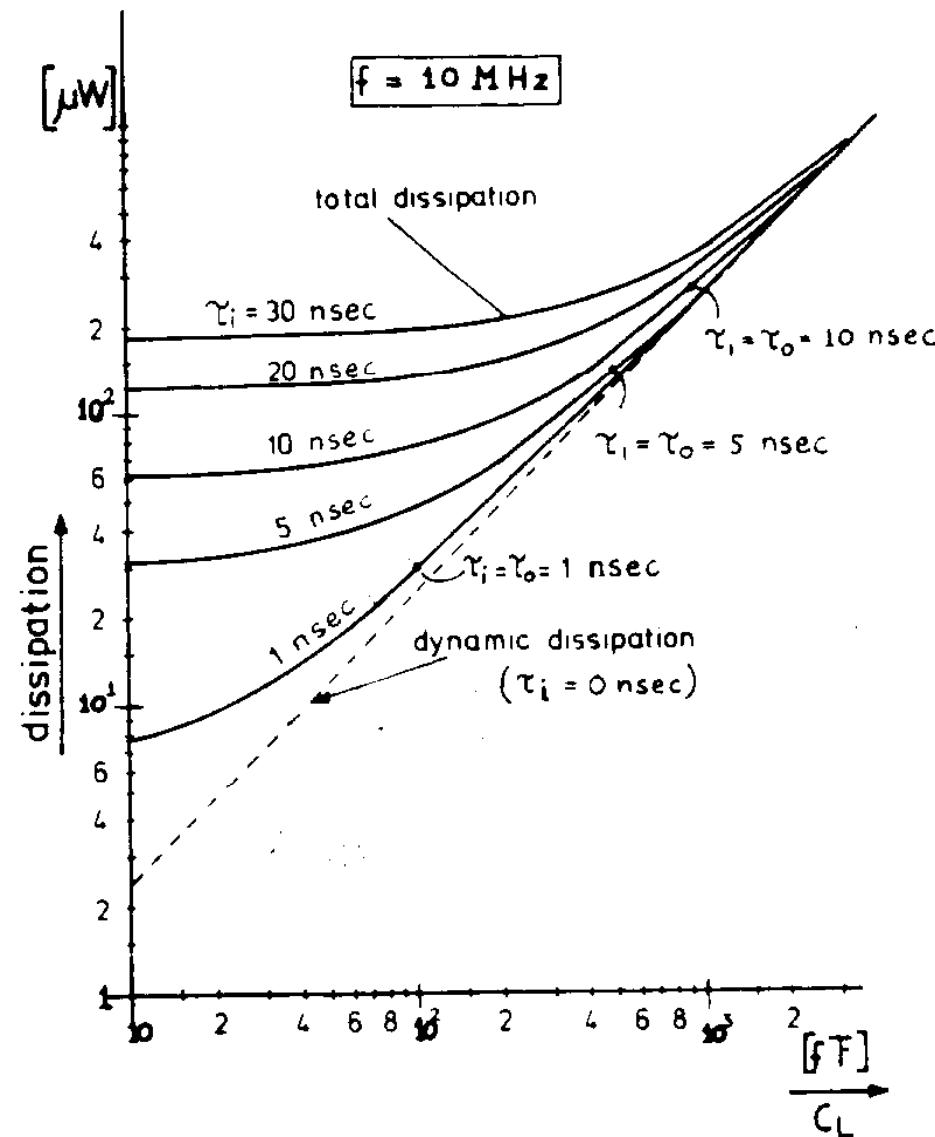
# $C_L$ Power vs. SC Power under Different Loads


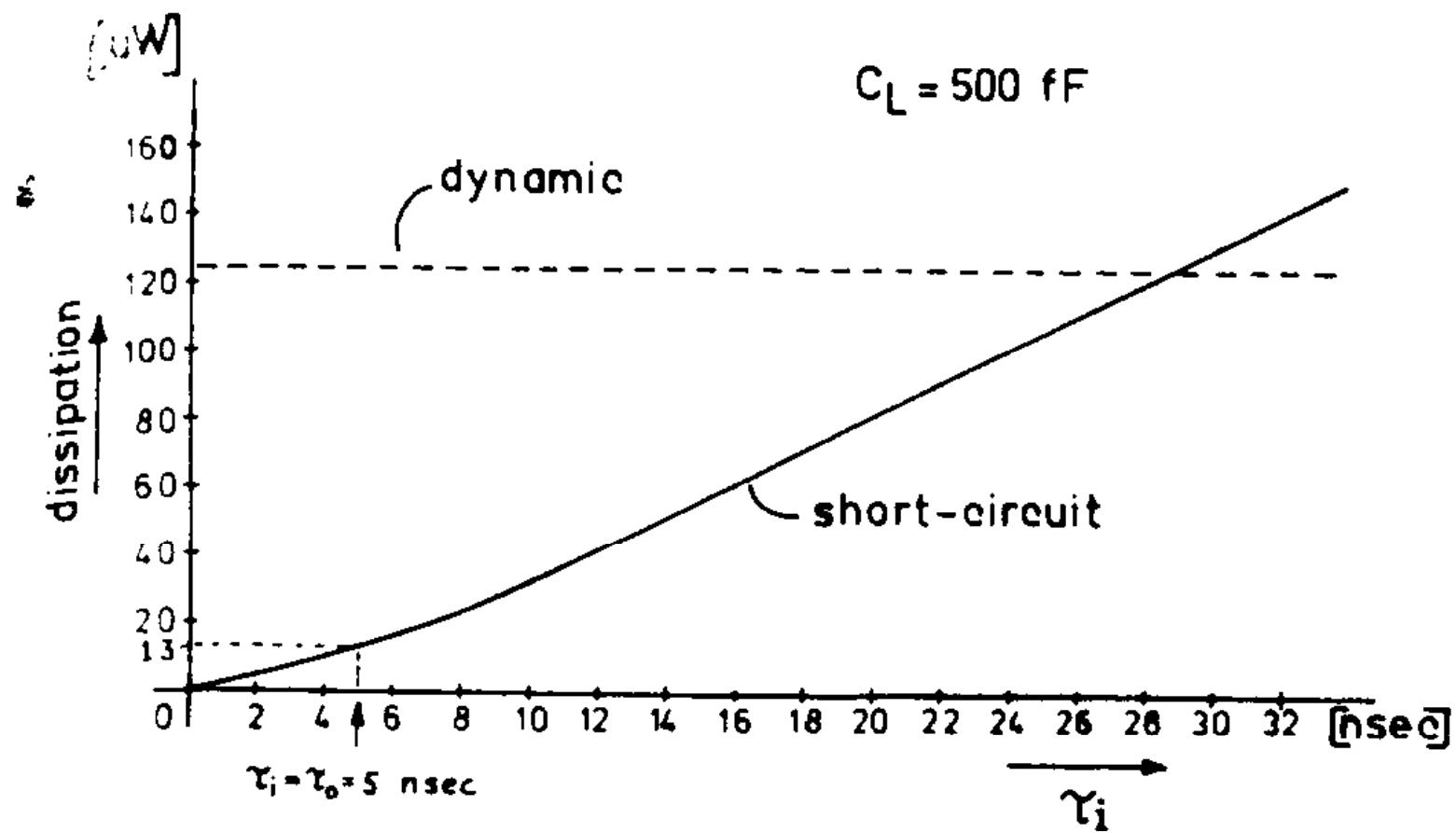
## $C_L$ Power vs. SC Power under Different Inputs




# Impact of Load Capacitance on SC Current

- Large capacitance
  - Fast input transition, slow output transition
  - Input moves through the transient region before output begins to change
  - Short-circuit current close to zero
- Small capacitance
  - Relatively slower input transition, fast output transition
  - Both devices in saturation during most of the transition
  - Maximum short-circuit current
- [Veendrick84]: rise/fall times of all signals should be kept constant within a range to keep SC power minimal, 10%~20% of total dynamic power

# Technology Evolution


<b>Year of Introduction</b>	<b>1994</b>	<b>1997</b>	<b>2000</b>	<b>2003</b>	<b>2006</b>	<b>2009</b>
Channel length ( $\mu\text{m}$ )	0.4	0.3	0.25	0.18	0.13	0.1
Gate oxide (nm)	12	7	6	4.5	4	4
$V_{DD}$ (V)	3.3	2.2	2.2	1.5	1.5	1.5
$V_T$ (V)	0.7	0.7	0.7	0.6	0.6	0.6
NMOS $I_{Dsat}$ (mA/ $\mu\text{m}$ ) (@ $V_{GS} = V_{DD}$ )	0.35	0.27	0.31	0.21	0.29	0.33
PMOS $I_{Dsat}$ (mA/ $\mu\text{m}$ ) (@ $V_{GS} = V_{DD}$ )	0.16	0.11	0.14	0.09	0.13	0.16

# Technology Scaling (1)

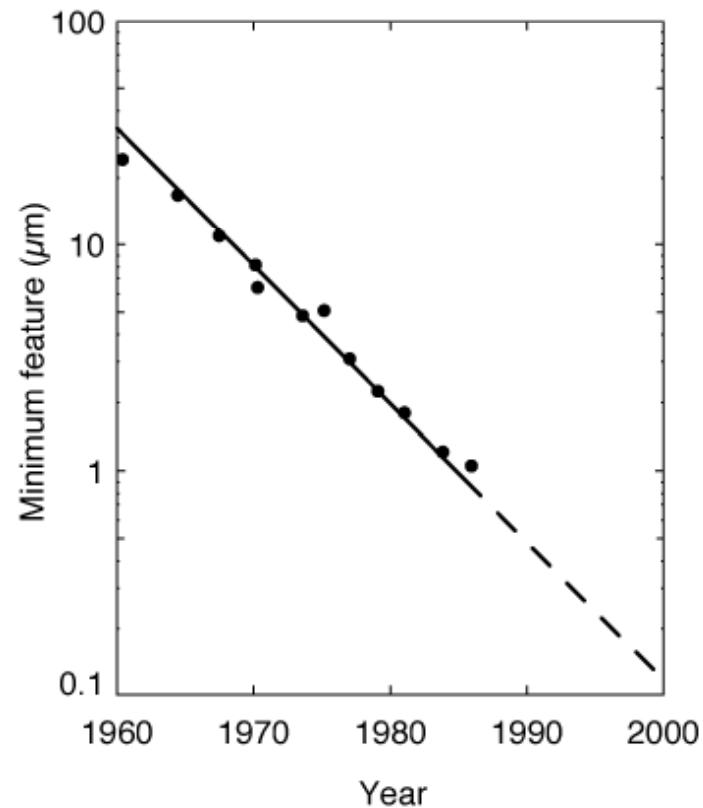


Minimum Feature Size

# Technology Scaling

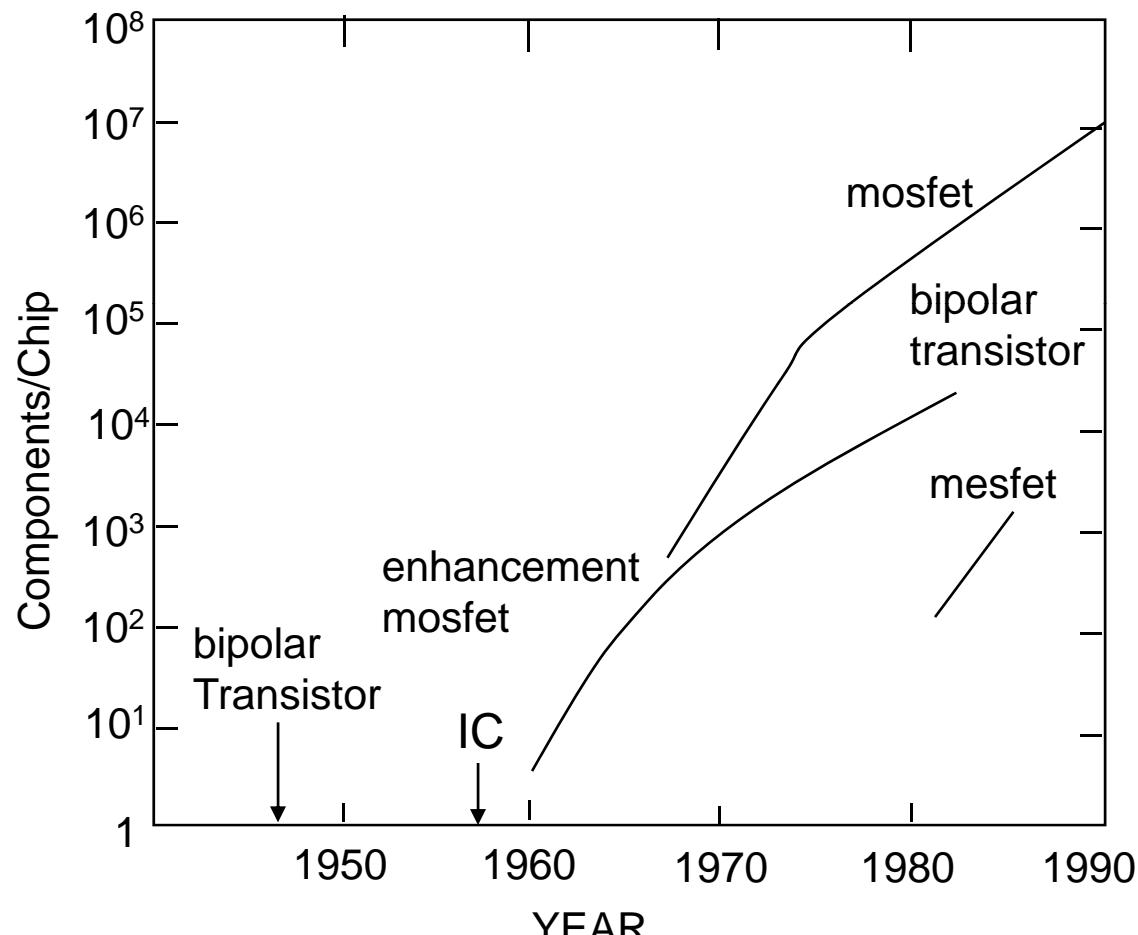

Number of components per chip

# Propagation Delay Scaling

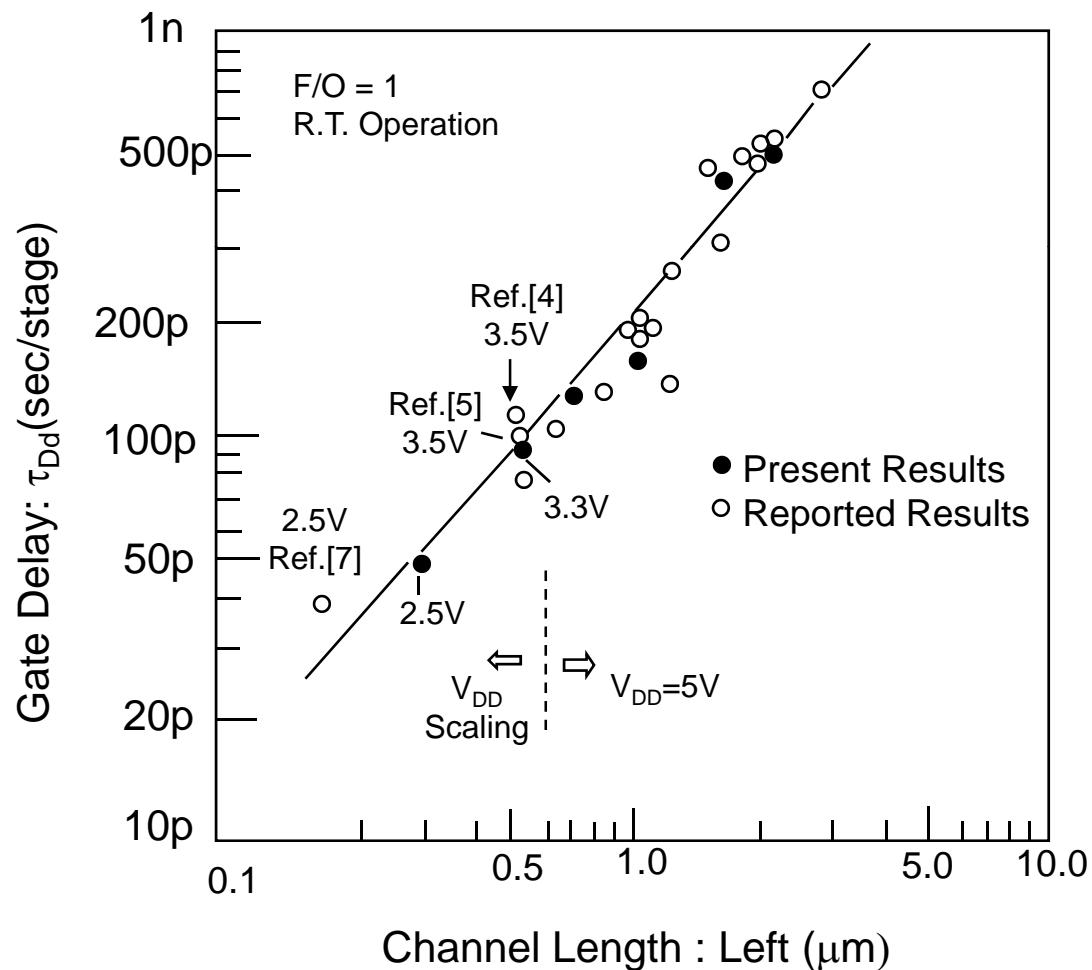

# Technology Scaling Models

- **Full Scaling (Constant Electrical Field)**

ideal model — dimensions and voltage scale together by the same factor  $S$

- **Fixed Voltage Scaling**

most common model until recently — only dimensions scale, voltages remain constant

- **General Scaling**

most realistic for todays situation — voltages and dimensions scale with different factors

# Scaling Relationships for Long channel Devices

Parameter	Relation	Full Scaling	General Scaling	Fixed Voltage Scaling
$W, L, t_{ox}$		$1/S$	$1/S$	$1/S$
$V_{DD}, V_T$		$1/S$	$1/U$	$1$
$N_{SUB}$	$V/W_{depl}^2$	$S$	$S^2/U$	$S^2$
Area/Device	$WL$	$1/S^2$	$1/S^2$	$1/S^2$
$C_{ox}$	$1/t_{ox}$	$S$	$S$	$S$
$C_L$	$C_{ox}WL$	$1/S$	$1/S$	$1/S$
$k_n, k_p$	$C_{ox}W/L$	$S$	$S$	$S$
$I_{av}$	$k_{n,p} V^2$	$1/S$	$S/U^2$	$S$
$t_p$ (intrinsic)	$C_L V / I_{av}$	$1/S$	$U/S^2$	$1/S^2$
$P_{av}$	$C_L V^2 / t_p$	$1/S^2$	$S/U^3$	$S$
PDP	$C_L V^2$	$1/S^3$	$1/SU^2$	$1/S$

# Scaling of Short Channel Devices

Parameter	Relation	Full Scaling	General Scaling	Fixed Voltage Scaling
$I_{av}$	$C_{ox}WV$	$1/S$	$1/U$	1
$J_{av}$	$I_{av}/\text{Area}$	$S$	$S^2/U$	$S^2$
$t_p$ (intrinsic)	$C_L V / I_{av}$	$1/S$	$1/S$	$1/S$
$P_{av}$	$C_L V^2 / t_p$	$1/S^2$	$1/U^2$	1

## Homework Problem (due next Thursday)

- Design a static CMOS inverter with 0.4pF load capacitance. Make sure that you have equal rise and fall times. Layout the inverter using the Mentor tools, extract parasitics, and simulate the extracted circuit on HSPICE to make sure that your design conforms to the specification.
- Do the same analysis for a three input NAND gate.