

# Combinational Logic Gates in CMOS

## References:

Adapted from: *Digital Integrated Circuits: A Design Perspective*, J. Rabaey, Prentice Hall © UCB

*Principles of CMOS VLSI Design: A Systems Perspective*,  
N. H. E. Weste, K. Eshraghian, Addison Wesley


Adapted from: EE216A Lecture Notes by Prof. K. Bult ©  
UCLA

# Design Techniques for Large Fan-In


- Transistor Sizing
- Progressive Transistor Sizing
- Transistor Ordering
- Logic Design to reduce the gate fan-in
 
# Progressive Sizing


- When parasitic capacitance is significant (e.g., when fan-in is large), needs to consider distributed RC effect
- Increasing the size of M1 has the largest impact in terms of delay reduction
- $M_1 > M_2 > M_3 > \dots > M_N$


 
# Delay Optimization by Transistor Ordering




Critical signal next to supply

 


Critical signal next to output

# Improved Logic Design

 


Reduce the fan-in to each gate

Example:  $F = ((A + B + C).D)$

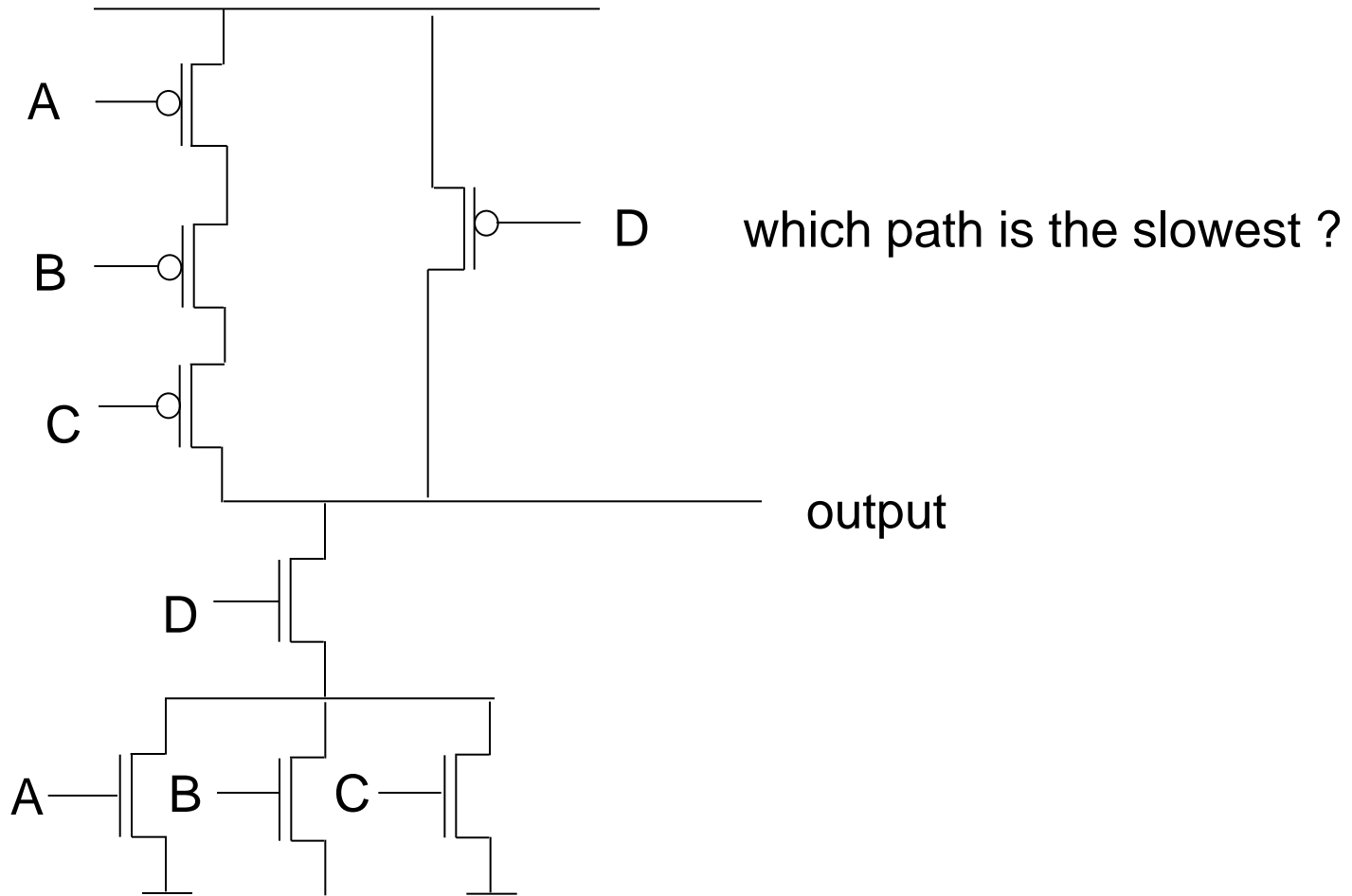


Example:  $F = \overline{((A+B +C).D)}$

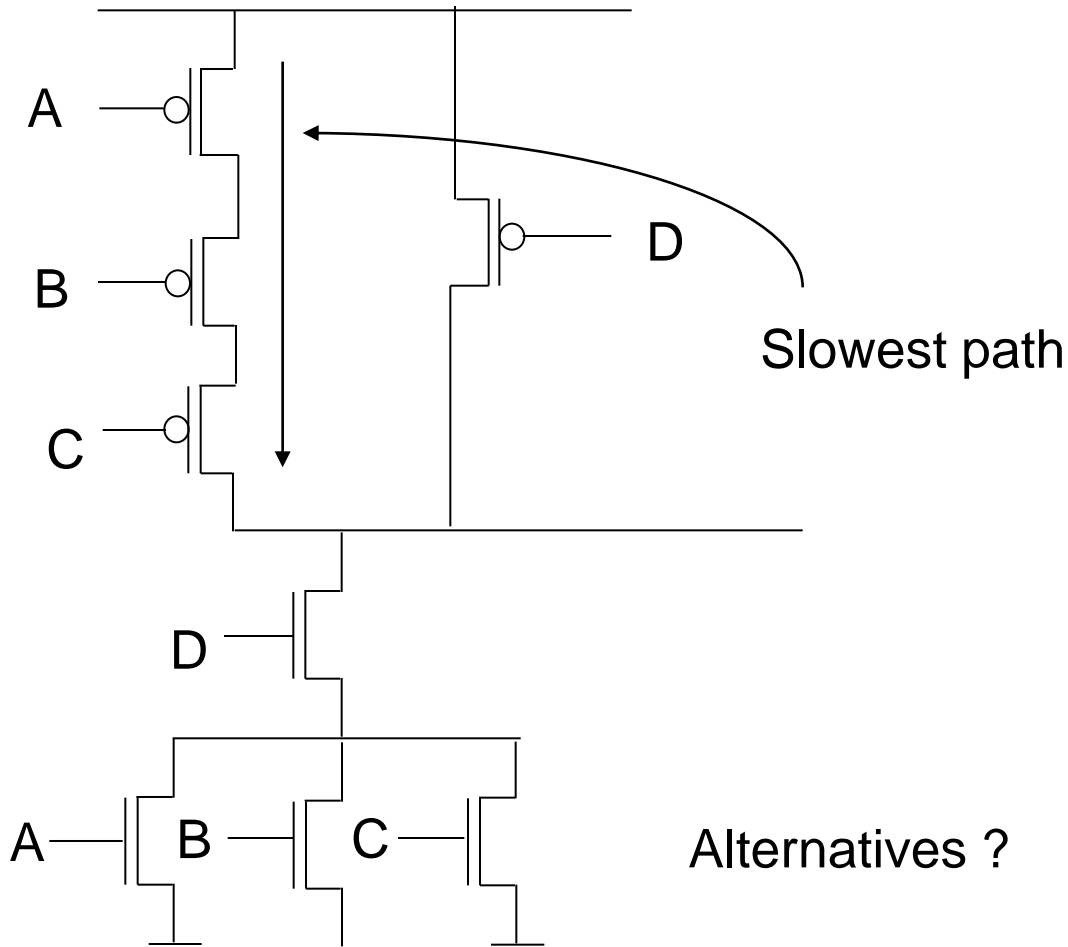

If minimum-size:  $t_{dr} \approx 6 \times t_{df,inv}$

$t_{df,inv}$  = delay of a minimum inverter

Example:  $F = \overline{((A+B+C).D)}$

 


If minimum-size:  $t_{dr} \approx 7 \times t_{df.inv}$

→ this approach is advantageous if driving larger load




# Design of an 8-Input AND


Approach 1

 


Approach 2

 

Approach 3

 
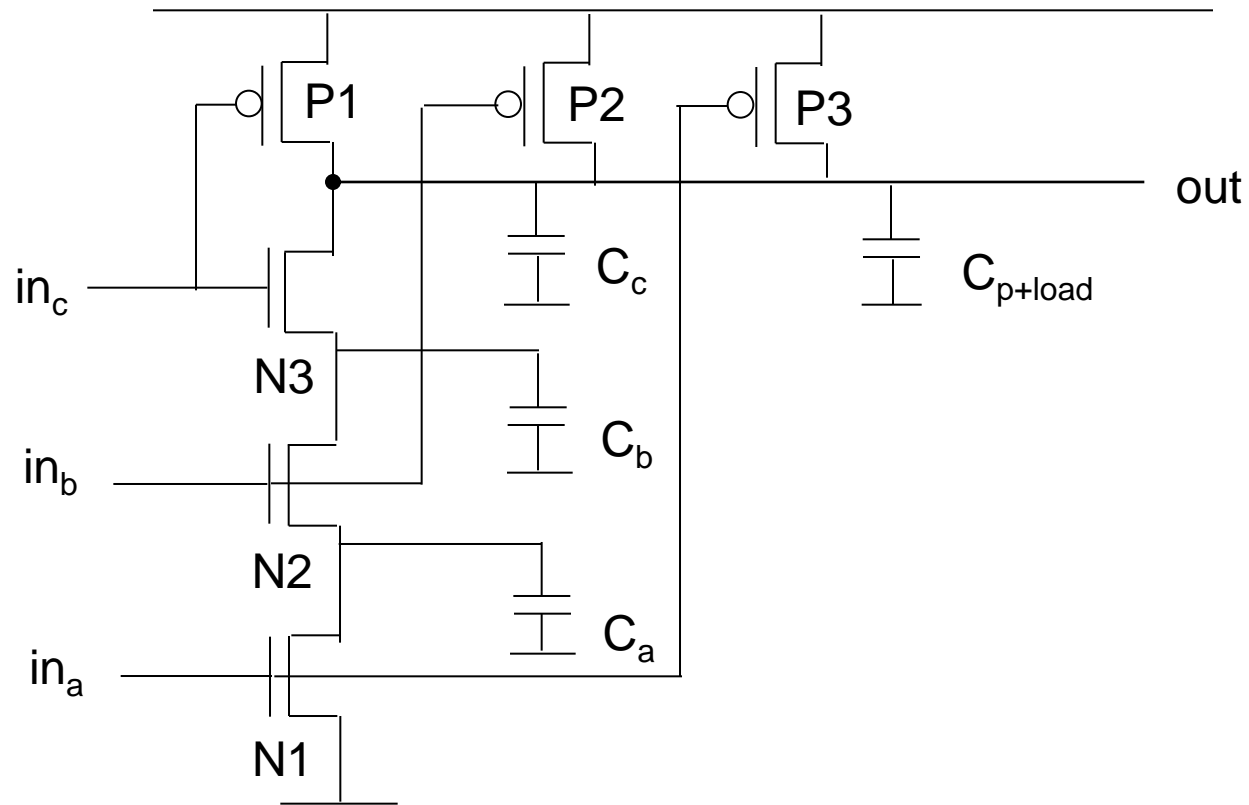
# 3-input NAND Gate with Parasitic Capacitors



# Macro Modeling for Worst Case Analysis

$$t_{df} = \frac{[R_{N1} C_a] + [(R_{N1} + R_{N2}) C_b] + [(R_{N1} + R_{N2} + R_{N3}) C_c]}{[(R_{N1} + R_{N2} + R_{N3}) C_p] + [(R_{N1} + R_{N2} + R_{N3}) C_{load}]}$$

Internal delay

External load

$$t_d = T_{d, internal} + \lambda \times C_{load}$$

# Macro Modeling

$$t_{df} = \frac{m^2 + m}{2} R_N C_j + \frac{mR_N}{n} (mpC_j + C_L)$$

m: fan-in

n: sizing factor of NMOS transistors

p: sizing factor of PMOS transistors

$C_{inv,min}$  = total gate capacitance of minimum size inverter

k = “fan-out” corresponding to  $C_L$

$$C_j = r C_{inv,min}$$

$$t_{df} = R_N \left( \frac{(m^2 + m)C_j}{2} + \frac{m^2 p C_j}{n} + \frac{mk C_{inv,min}}{n} \right)$$

Keep  $m^2$  and  $m^2p/n$  and  $mk/n$  reasonable

# Macro Modeling for NOR Gate

$$t_{dr, NOR} = R_P \left( \frac{(m^2 + m)C_j}{2} + \frac{m^2 n C_j}{p} + \frac{mkC_{inv, min}}{p} \right)$$

Keep  $m^2$  and  $m^2 n/p$  and  $mk/p$  reasonable

$$t_{df, NOR} = R_N \left( mC_j + \frac{mpC_j}{n} + \frac{kC_{inv, min}}{n} \right)$$

Keep  $n$  as small as possible to minimize the impact on rise-delay

# Design Strategy

- Use minimum sized transistors
- Analyze critical path (slowest, maybe more than 1)
- Look at alternative implementations (substitute NOR's ?)
- Compare and choose best
- Analyze critical path(s) and optimize transistor sizing


# Complementary Logic

- $2n$  transistors
- Complicated wiring
- No functional sizing required


# Ratioed Logic




# Ratioed Logic

 

(a) Resistive load

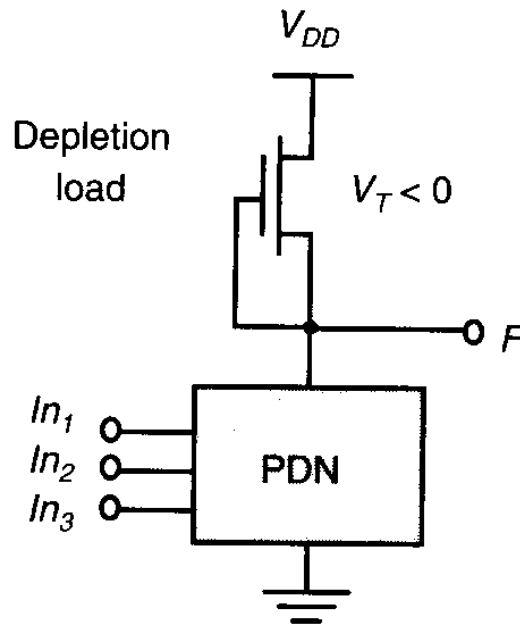

(b) Depletion load NMOS

 


(c) Pseudo-NMOS

Reduce the number of devices over complementary logic

# Ratioed Logic

- Use PDN to implement the function (which is the negation of the network)
- Total number of devices:  $n$  for the input, 1 for the static load
- Minimum load is 1 unit-gate load
- Functional sizing is required to optimize noise margin


# Functional Sizing in Ratioed Logic

 

(a) Resistive load

- $N$  transistors
- $V_{OH} = V_{DD}$
- $$V_{OL} = \frac{R_{PDN}}{R_{PDN} + R_L} V_{DD}$$
- Asymmetrical response
- Static power consumption
- $t_{pLH} = 0.69 R_L C_L$
- $t_{pHL} = 0.69 (R_L \parallel R_{PDN}) C_L$

# Current Source as the Static Load

 


$$t_{pLH} = \frac{C_L V_{swing} / 2}{I_{ave}}$$

- If current source equals  $V_{DD}/R_L$   
= initial charging current from  
the resistive load

$$t_{pLH} = \frac{C_L R_L}{2}$$

- More than 25% reduction  
compared to resistive load

# Load Lines of Ratioed Gates

 


# NMOS Depletion Load

Use depletion mode NMOS transistor as pull-up

$V_{tdep}$  of depletion transistor is  $< 0$  V

The depletion mode transistor is always ON:  
gate and source connected  $\Rightarrow V_{gs} = 0$

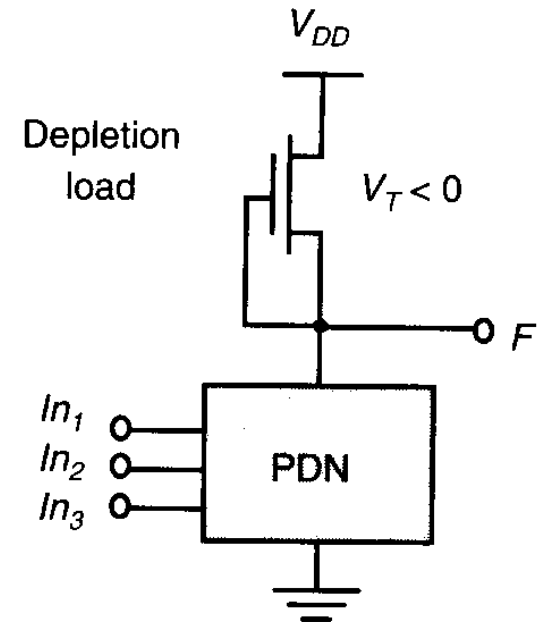$V_{in} = 0 \Rightarrow$  transistor pull down is off  $\Rightarrow V_{out}$  is high



(b) Depletion load NMOS

# Voltage Output Low

Driver is in linear region with input high

Load is in saturation region

$$\beta_{driver} \left( (V_{DD} - V_{tn})V_{OL} - \frac{V_{OL}^2}{2} \right) = \frac{\beta_{load}}{2} (-V_{tdep})^2$$

Assume:  $V_{DD} = 5.0V$   
 $V_{tn} = 1.0V = -V_{tdep}$

Proper design:  $V_{ol} < V_{tn}$

Let:  $V_{ol} = 0.5V$

$$\frac{\beta_{driver}}{\beta_{load}} = 0.267$$

# Gate Threshold Voltage

Gate threshold voltage =  $V_{inv}$   
= Input voltage at which  $V_{in} = V_{out}$

Assume that both driver and load are in saturation with input  $V_{inv}$


$$I_{DS (sat)} = \frac{\beta_{driver}}{2} (V_{gs} - V_t)^2$$
$$\therefore \frac{\beta_{driver}}{2} (V_{inv} - V_t)^2 = \frac{\beta_{load}}{2} (-V_{dep})^2$$

Hence, 
$$V_{inv} = V_t - V_{dep} \sqrt{\frac{\beta_{load}}{\beta_{driver}}}$$

If  $\beta_{driver}$  is increased relative to  $\beta_{load}$  then,  $V_{inv}$  decreases



# PMOST Load with Constant $V_{GS}$

 

(c) Pseudo-NMOS

$$V_{oh} = 5.0V$$

$$V_{ol} = ???$$

$$I = 0.5\beta_p \cdot (V_{dd} - V_{tp})^2$$

$$I = \beta_n \cdot ((V_{dd} - V_{tn})V_{ol} - 0.5V_{ol}^2)$$

$$\frac{\beta_n}{\beta_p} = \frac{0.5(V_{dd} - V_{tp})^2}{((V_{dd} - V_{tn})V_{ol} - 0.5V_{ol}^2)}$$

## Sizing for $V_{OL}$

$$\frac{\beta_n}{\beta_p} = \frac{0.5(V_{dd} - V_{tp})^2}{((V_{dd} - V_{tn})V_{ol} - 0.5V_{ol}^2)}$$

Assume:  $V_{dd} = 5.0V$   
 $V_{tn} = V_{tp} = 1.0V$

Proper design:  $V_{ol} < V_{th}$

Let:  $V_{ol} = 0.5V$

$$\frac{\beta_n}{\beta_p} = 4.26$$

# Sizing for Gate Threshold Voltage

N-device: saturated ( $V_{out} > V_{in} - V_{tn}$ )

$$I_{dsn} = \frac{\beta_n}{2} (V_{in} - V_{tn})^2$$

P-device: non-saturated

$$V_{gsp} = -V_{DD}$$

$$I_{dsp} = \beta_p [(-V_{DD} - V_{tp})(V_{out} - V_{DD}) - \frac{(V_{out} - V_{DD})^2}{2}]$$

Equating the two currents we obtain,

$$\frac{\beta_n}{2} (V_{in} - V_{tn})^2 = -\beta_p [(-V_{DD} - V_{tp})(V_{out} - V_{DD}) - \frac{(V_{out} - V_{DD})^2}{2}]$$

# Sizing for Gate Threshold Voltage

Solving for  $V_{out}$

$$V_{out} = -V_{tp} + \sqrt{(V_{DD} + V_{tp})^2 - C}$$

Where  $C = k (V_{in} - V_{tn})^2$


$$k = \frac{\beta_n}{\beta_p}$$

Also, 
$$\frac{\beta_n}{\beta_p} = \frac{(V_{DD} + V_{tp})^2 - (V_{out} + V_{tp})^2}{(V_{in} - V_{tn})^2}$$

To make gate threshold voltage =  $0.5V_{DD}$

$$\frac{\beta_n}{\beta_p} = 6.11$$

# Forcing the Voltage Output Low

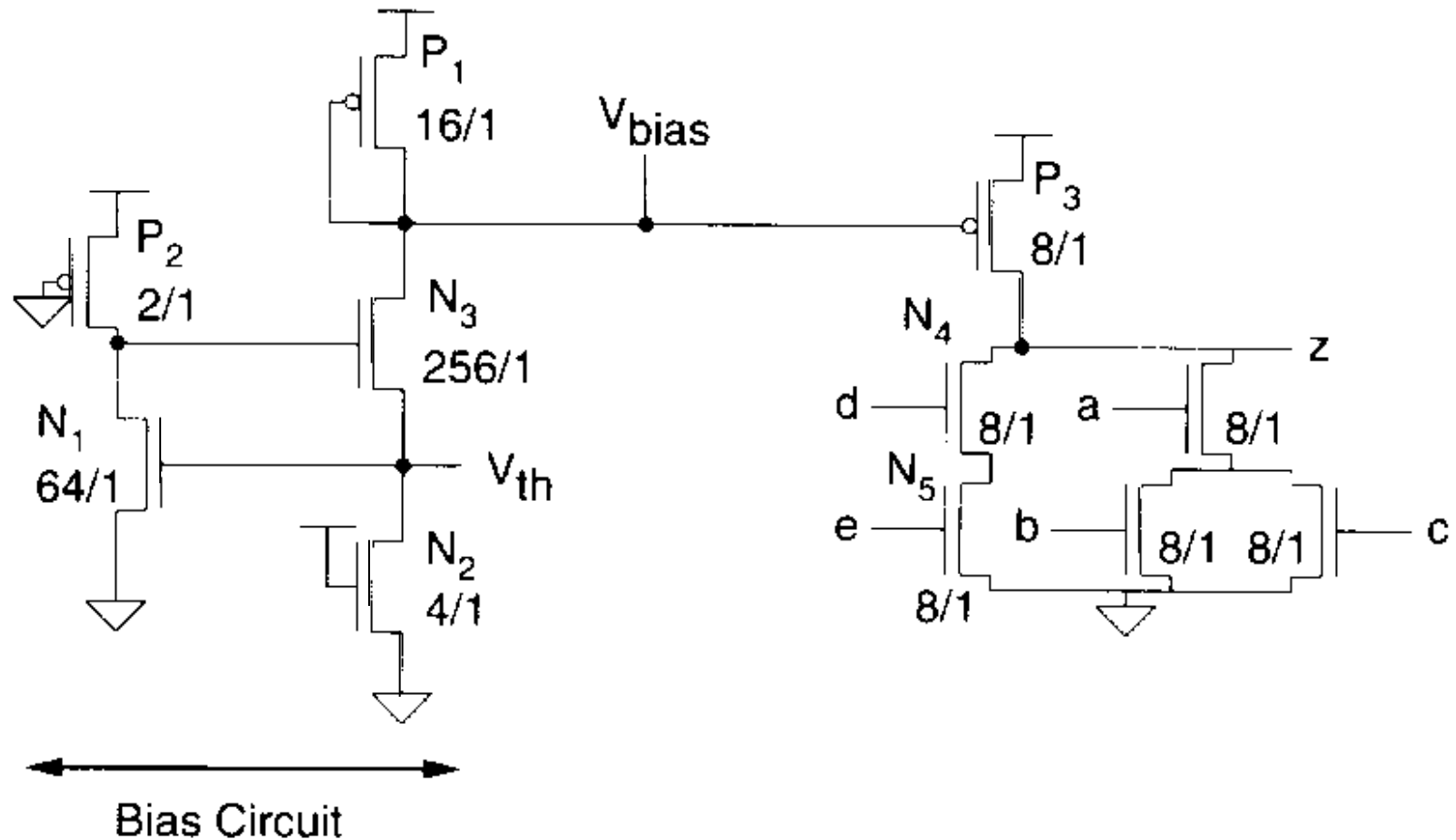

# Propagation Delay of Pseudo-NMOS Inverter

- Use average current

$$I_{av}(L \rightarrow H) = \frac{1}{2} \left[ \frac{\beta_P}{2} (-V_{DD} - V_{tp})^2 + \beta_P (-V_{DD} - V_{tp}) \left( \frac{-V_{DD}}{2} \right) - \left( \frac{V_{DD}^2}{8} \right) \right]$$

$$I_{av}(H \rightarrow L) = \frac{1}{2} \left[ \frac{\beta_N}{2} (V_{DD} - V_{tn})^2 + \beta_N (V_{DD} - V_{tn}) - \beta_P (V_{DD} + V_{tn}) \frac{-V_{DD}}{2} + (\beta_N - \beta_P) \frac{V_{DD}^2}{8} \right]$$

- Propagation delay

$$t_p = \frac{C_L (V_{DD} / 2)}{I_{av}}$$

# Power Consumption

- Consume power when the output is low

$$I_{av,low} = \frac{\beta_P}{2} (-V_{DD} - V_{tp})^2$$


$$P_{av,low} = V_{DD} I_{av,low} = \frac{\beta_P}{2} V_{DD} (V_{DD} + V_{tp})^2$$

## Trade-offs to be Considered

- To reduce static power,  $I_{\text{Load}}$  should be low
- To obtain a reasonable  $NM_L$ ,  $V_{\text{OL}} = I_{\text{Load}} R_{\text{PDN}}$  should be low
- To reduce  $t_{\text{pLH}} \approx C_L V_{\text{DD}} / (2I_{\text{Load}})$ ,  $I_{\text{Load}}$  should be high
- To reduce  $t_{\text{pHL}} \approx 0.69 R_{\text{PDN}} C_L$ ,  $R_{\text{PDN}}$  should be kept small




# Pseudo-NMOS NOR Gate

 


- Fan-in of  $N$  inputs requires only  $N+1$  transistors, smaller parasitic capacitance and area
- Smaller load to preceding gate
- Static power consumption at output low
- Pseudo-NMOS gates can be used effectively when speed is importance and majority of the output is high

# Pseudo-NMOS NAND Gate

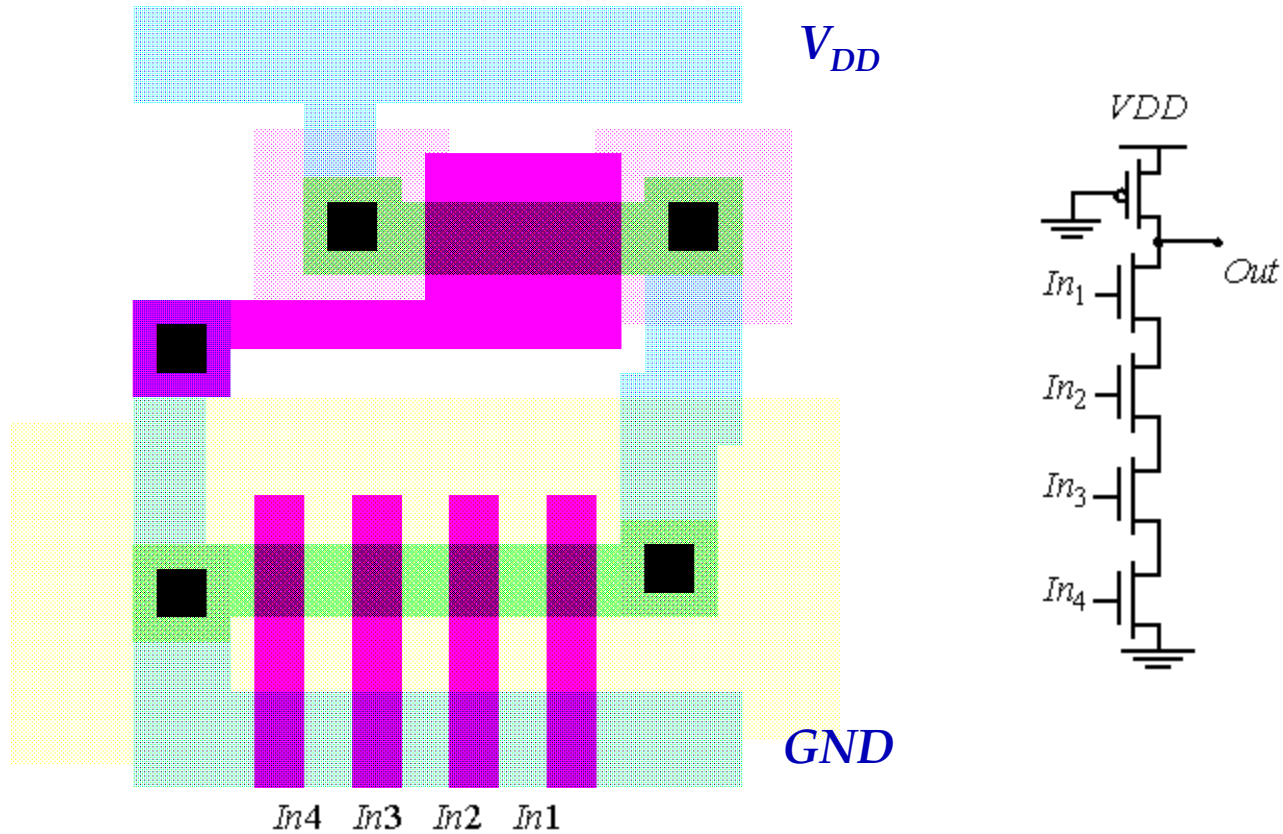


$$C_{L,pseudo} = 0.5 C_{L,CMOS} \text{ (Fan-out of 1)}$$

# Improved Loads (2)

 

**Dual Cascode Voltage Switch Logic (DCVSL)**

# Example

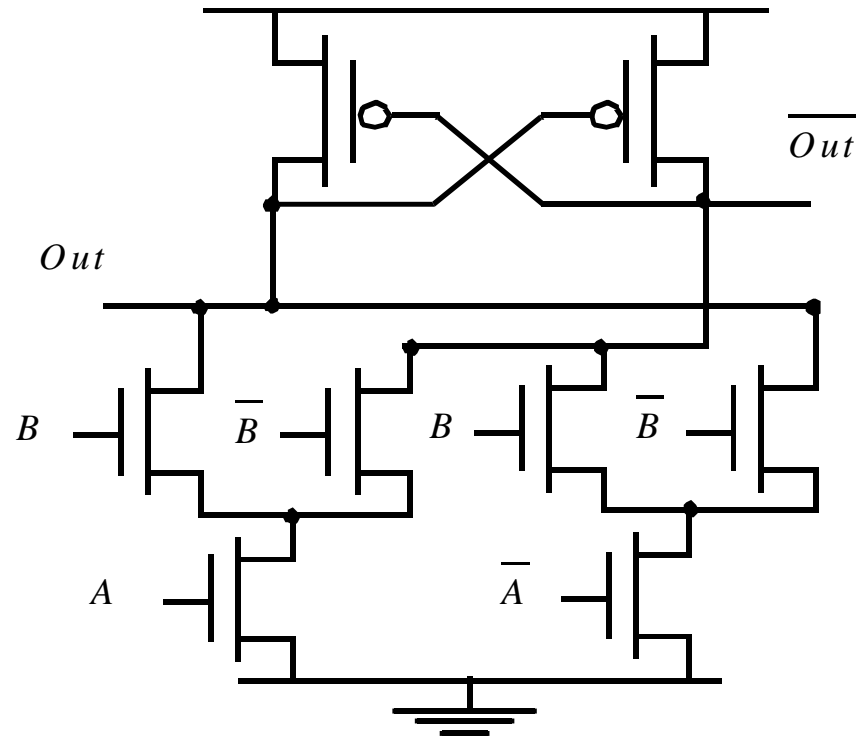

XOR-NXOR gate