



Design of Scaled CMOS Circuits in the Nano-meter Regime: Dynamic Energy Dissipation

Kaushik Roy

Professor of Electrical & Computer Engineering
Purdue University

Switching/Dynamic Power

Switching Power


- Signal properties

- Signal probability, P_1 , - probability of a signal being logic ONE
- Signal activity, a_1 , - probability of signal switching(0->1, or 1->0)

- Energy dissipated per transition

$$E_{V_{DD}} = \int_0^{\infty} i_{V_{DD}}(t) V_{DD} dt = V_{DD} \int_0^{\infty} C_L \frac{dv_{out}}{dt} dt$$
 
$$= C_L V_{DD} \int_0^{V_{DD}} dv_{out} = C_L V_{DD}^2$$



$$E_C = \int_0^{\infty} i_{V_{DD}}(t) v_{out} dt = \int_0^{\infty} C_L \frac{dv_{out}}{dt} v_{out} dt = C_L \int_0^{V_{DD}} v_{out} dv_{out} = C_L V_{DD}^2 / 2$$

Energy dissipated for 1->0 or 0->1 transition: $C_L V_{DD}^2 / 2$


$$P_{dynamic} = C_L \cdot V_{DD}^2 \cdot f$$

- Example

- 1.2 μ CMOS chip
- 100 MHz clock rate
- Average load capacitance of 30 fF/gate
- 5V power supply

- Power consumption/gate = 75 μ W
- Design with 200,000 gates: 15W !
- Pessimistic evaluation: not all gates switch at the full rate
- Have to consider the activity factor α : Effective switching capacitance = αC_L
- Reducing V_{DD} has a quadratic effect on $P_{dynamic}$

Average Number of Transitions

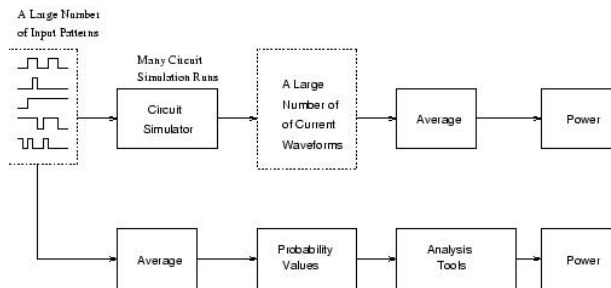


Switching at internal nodes depends on input signals.

Model input signals as stochastic process. Each signal having some properties:


- Signal probability
- Signal activity

Direct Path Current

 
- inputs have finite rise and fall times
- Direct current path from V_{DD} to GND while PMOS and NMOS are ON simultaneously for a short period



Short Circuit Current with Loads

 

Spurious Transition at a Node

 


Hazardous transition occurs at the output of AND gate due to different delays through two different paths converging at the inputs to the AND gate.

- Assume each gate has unit delay
- Width of the glitch depends on the delays through the logic gates and interconnects.

Energy Dissipation in RC Circuits & Brief Intro to Energy Recovery

Revisit Dynamic Energy Consumption: Simple R-C model of Pass pMOS transistor

 Consider a pMOS pass transistor with a capacitive load C at the output. The voltage at the power terminal swings from 0 to V_{dd} to charge the node capacitance through the transistor channel. The channel is modeled by a normal resistance R in fig (a).



Let us compute energy dissipated while charging capacitance C from 0 to V_{dd} in time T with a linear supply voltage as shown in fig (b).

RC Circuit: Energy Dissipation

The voltage relations are shown here.

$$RC\left(\frac{dV_C}{dt}\right) + V_C = \Phi$$

The supply voltage can be expressed as

$$V_C = \begin{cases} 0, & t < 0 \\ \left(\frac{V_{dd}}{T}\right)t, & 0 \leq t < T \\ V_{dd}, & t > T \end{cases}$$

RC Circuits (contd.)

Solving the voltage equation, we've

$$V_C = \begin{cases} 0, & t < 0 \\ \Phi - \left(\frac{RC}{T}\right)V_{dd}\left(1 - e^{-\frac{t}{RC}}\right), & 0 \leq t < T \\ \Phi - \left(\frac{RC}{T}\right)V_{dd}\left(1 - e^{-\frac{t}{RC}}\right)e^{-\frac{(t-T)}{RC}}, & t > T \end{cases}$$

The energy dissipation in the charging process can be calculated as

$$E_{linear} = \int_0^T iV_R dt + \int_T^{\infty} iV_R dt$$

RC Circuits (contd.)

Term wise expanding, the first term can be expressed as

$$\begin{aligned}
 \int_0^T iV_R dt &= \int_0^T \frac{(\Phi - V_C)^2}{R} dt \\
 &= \int_0^T \left[\frac{V_{dd}}{T} RC \left(1 - e^{-\frac{t}{RC}}\right) \right] / R dt \\
 &= \left(\frac{RC}{T}\right)^2 CV_{dd}^2 \int_0^{\frac{T}{RC}} \left(1 - e^{-\frac{t}{RC}}\right)^2 d\left(\frac{t}{RC}\right) \\
 &= \left(\frac{RC}{T}\right) CV_{dd}^2 \left[1 - \frac{3}{2} \left(\frac{RC}{T}\right) + 2 \left(\frac{RC}{T}\right) e^{-\frac{T}{RC}} - \frac{1}{2} \left(\frac{RC}{T}\right) e^{-\frac{2T}{RC}} \right]
 \end{aligned}$$

The second term of the energy dissipation

$$\begin{aligned}
 \int_T^\infty iV_R dt &= \int_T^\infty \frac{(\Phi - V_C)^2}{R} dt \\
 &= \frac{RC}{T} CV_{dd}^2 \left(1 - e^{-\frac{T}{RC}}\right)^2 \int_T^\infty e^{-\frac{(t-T)}{RC}} dt \\
 &= \left(\frac{RC}{T}\right)^2 CV_{dd}^2 \left[\frac{1}{2} \left(1 - e^{-\frac{T}{RC}}\right)^2 \right]
 \end{aligned}$$

Final energy expression

$$E_{linear} = \left(\frac{RC}{T}\right) CV_{dd}^2 \left[1 - \frac{RC}{T} + \frac{RC}{T} e^{-\frac{T}{RC}} \right]$$

Energy Dissipation: 2 Cases

Let us consider the two extreme cases, when $T \gg RC$


$$E_{linear} = \left(\frac{RC}{T}\right)CV_{dd}^2$$

And when $T \ll RC$, as in normal CMOS

$$E_{linear} = \left(\frac{RC}{T}\right)CV_{dd}^2 \left[1 - \frac{RC}{T} + \frac{RC}{T} \left(1 - \frac{T}{RC} + \frac{1}{2} \left(\frac{T}{RC}\right)^2\right)\right]$$


$$= \frac{1}{2} CV_{dd}^2$$

Adiabatic Switching Concept (continued)

 


Charging and discharging in CMOS

(a)

 

Charging and Discharging in Adiabatic fashion


(b)

 

$$\text{Energy dissipation} = CV^2$$

$RC \sim 0.1 \text{ ns}$ for current technology.

(c)

 


$$\text{Energy dissipation} = 2(RC/T)CV^2$$


If $T = 2 \text{ ns}$, 90% of power saved by Adiabatic Switching

(d)


Basic recovery process

 

(c)

 


(d)

 


(e)

Adiabatic Digital System

 

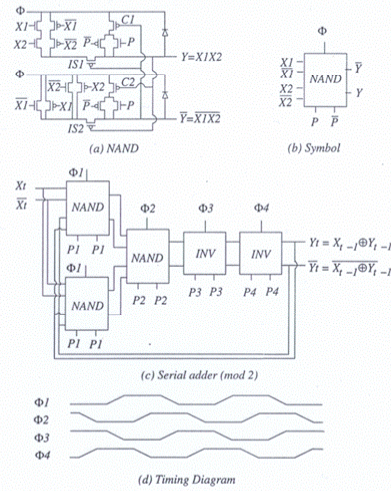A Bit-Serial Adder using Partially Reversible Logic




- 4 phases of clock required
- Using local signal to control the recovery path. Hence, inverse function is not required
- Differential signaling is used

A Buffer (Inverter) Chain using Reversible Logic



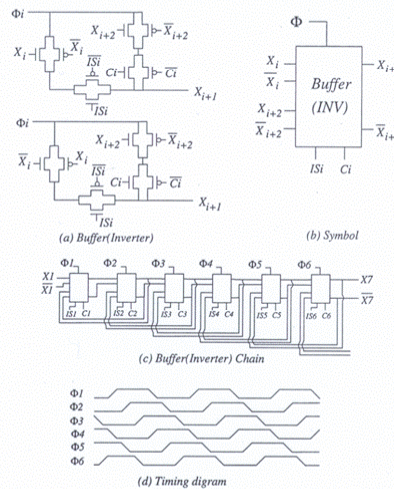
- 6 phases of clock required
- Inverse logic naturally available
- Charge recovery path can be controlled by inverse function (next stage gate in buffer chain)
- In general, reversibility is not available



Quasi-Static Energy Recovery Logic (QSERL)



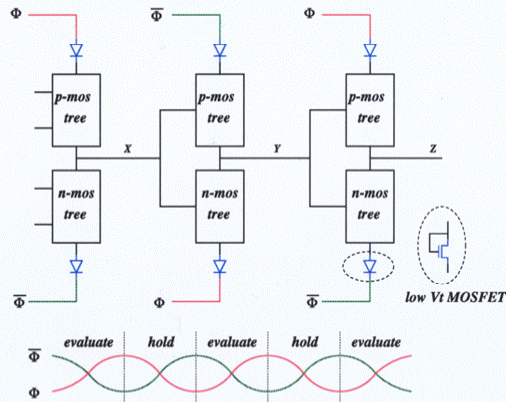
- Two phase clocks
- Comparable complexity with static CMOS
- Low threshold voltage MOSFET as the diode
- Lower switching activity than dynamic adiabatic logic



A Full Adder Using QSERL



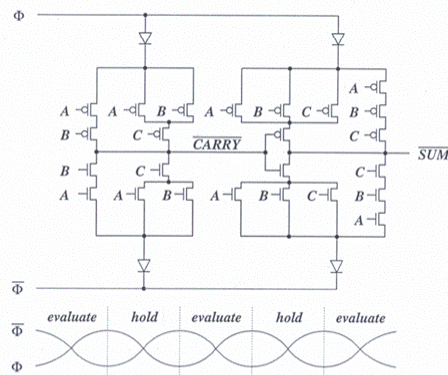- A quasi-CMOS adiabatic adder
- Works in both static CMOS and adiabatic mode
- A 2x2 adiabatic multiplier using this adder implemented



Summary of Simulation Results of Adiabatic Logic Blocks




- A buffer chain using reversible logic
 - At 1 MHz, 94% of energy recovered
 - At 111 MHz, 68% of energy recovered
- A bit-serial adder using partially reversible logic
 - At 1 MHz, 90% of energy recovered
 - At 111 MHz, 61% of energy recovered
- A 2x2 multiplier using QSERL logic
 - At 20 MHz, 60% of energy saved
 - At 100 MHz, 35% of energy saved

A Generic Resonant Scheme for Energy Recovery



 
- Ideally, the circuit oscillates between 0 and $2V_{ref}$
- Pull-up and pull-down paths to replenish the energy to keep oscillation going
- Extra circuits to generate control signal Sp and Sn
- External control signals Sp and Sn are 180 degree out of phase



A Generic Resonant Scheme (continued)



 - Serial connected control transistor **SO** limits the energy recovery efficiency
- Extra circuitry to generate **Sp** and **Sn**
- Energy in charging the gate capacitances of **Sp** and **Sn** are dissipated
- It requires an additional reference voltage source
- Single phase clock is generated. More than one resonant circuit is required




Motivation For Reducing Clock Power




- **Power Consequences:**
 - Increased cooling cost
 - Shortens battery lifetime in portable applications
- **Clock power is significant**
 - For microprocessors clock distribution power can range from 30% to 50%
- **Clock power reduction is a promising approach to low power**
 - Energy Recovery from the clock network

Power Distribution of Pentium II

 

Ref: ISCAS01, Q.K. Zhu

 
Power Distribution of McKinley (Itanium) Processor




Ref: ISSCC01, McKinley

- Resonant clock generator
- Sinusoidal clock
- Clock network: distributed RC load
- To adjust frequency, L is changed according to:


$$f = \frac{1}{2\pi\sqrt{LC}}$$

 


 
- Integrated 1024 flip-flops across an area of 4mmX4mm
- Compared proposed flip-flops to 3 square wave flip-flops
 - Hybrid-latch Flip-Flop
 - Conditional Capture Flip-Flop
 - Transmission Gate Flip-Flop
- Distributed RC model was extracted from layout
- In square wave case, clock tree was driven by a single buffer



Approximate Sinusoidal Generated

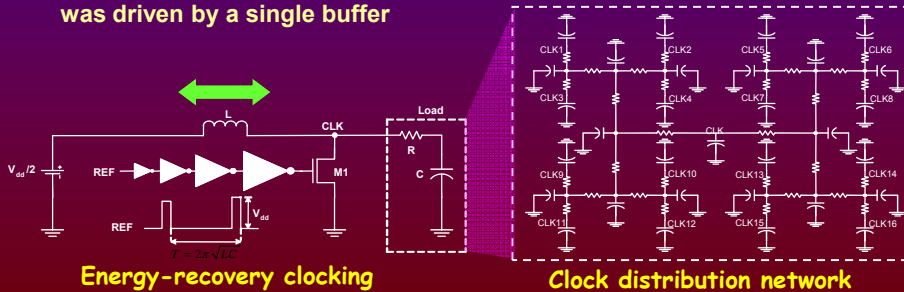

  Results include clock network and flip-flops




HLFF: Hybrid Latch Flip-Flop CCF: Conditional Capture Flip-Flop TGFF: Transmission Gate Flip-Flop

- Negligible power overhead for clock generation
- Over 90% power savings over the clock tree!
- Total power savings including flip-flops over square-wave clocking:
 - Up to 83% for 0% data switching activity
 - Up to 65% for 25% data switching activity
 - Up to 49% for 50% data switching activity

65% power reduction at typical data switching rate


Dynamic Energy Minimization

Architecture-Driven Voltage Scaling

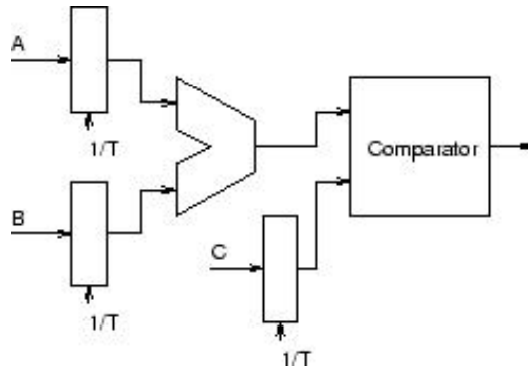

Data Path Operator


Architecture-Driven Voltage Scaling

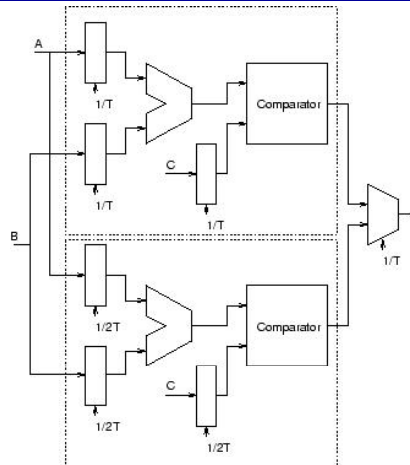

$$P_{par} = (2.15C)(0.58V)^2(0.5f) \approx 0.36P$$

Parallel implementation


Architecture-Driven Voltage Scaling

 

Pipelined implementation


$$P_{pipe} = (1.15C)(0.58V)^2(f) \approx 0.39P$$

 Power Optimization Using Operation Reduction




Reducing operations maintaining throughput

 Power Optimization Using Operation Reduction




Reducing operations with less throughput

 Power Optimization Using Operation Substitution



Substituting addition for multiplication

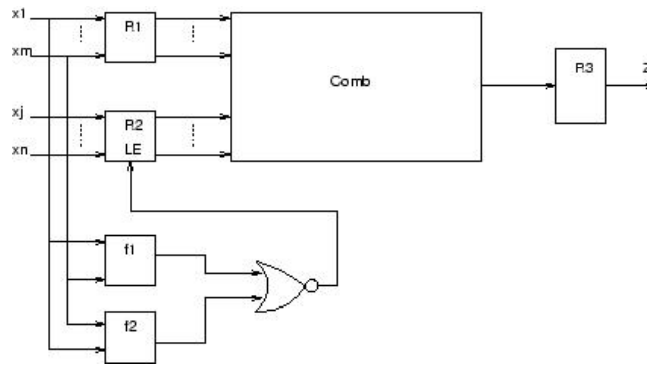
Precomputation-Based Optimization for Low Power



Precomputation architecture

$$f_1 = 1 \Rightarrow Z = 1 \quad f_2 = 1 \Rightarrow Z = 0$$

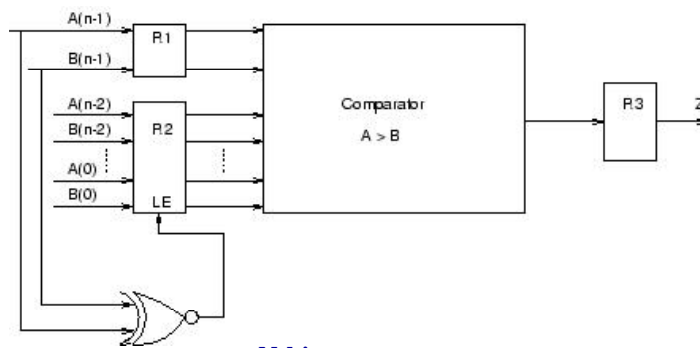
Precomputation-Based Optimization for Low Power



N-bit comparator

$$f_1 = A(n-1) \cdot \overline{B(n-1)} \quad f_2 = \overline{A(n-1)} \cdot B(n-1)$$

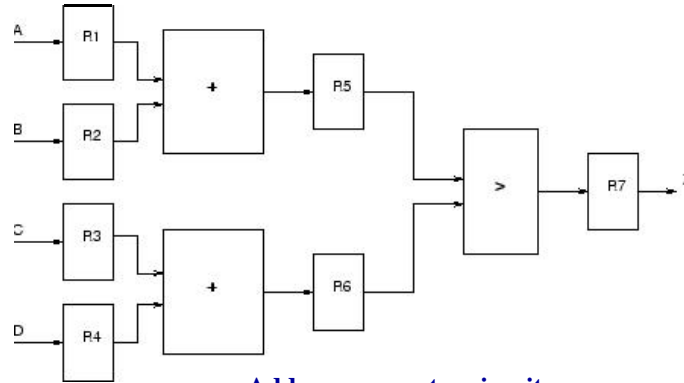Precomputation-Based Optimization for Low Power




Adder-comparator circuit

$$f_1 = A(n-1) \cdot B(n-1) \cdot \overline{C(n-1)} \cdot \overline{D(n-1)}$$

$$f_2 = \overline{A(n-1)} \cdot \overline{B(n-1)} \cdot C(n-1) \cdot D(n-1)$$

 Precomputation-Based Optimization for Low Power




Precomputation using Shannon's expansion


$$Z = x_j Z_{x_j} + \overline{x_j} Z_{\overline{x_j}}$$

Multi-Voltage Scheduling

 Bottlenecks for single V_{dd} , V_T , Clock




Schedule to exploit slack

 

Multi-Voltage IC Design Issues

Level Conversions

 

DC-DC Efficiency

- need efficiency of at least $\frac{V_{HI}^2}{V_{LO}^2}$ to break even

$$\frac{V_{HI}^2}{V_{LO}^2}$$

Layout:

- separate power and ground routing
- substrate contacts between voltage regions

Multi-Voltage Results

- Summary of results:
 - up to 50% energy savings 1 vs. 2 voltages
 - less than 15% additional savings 2 vs. 3
 - area penalties vary from 0 up to 170%

Clock Gating

Why Clock Gating?

- Power breakdowns for processors

Pentium Pro


Instruction Fetch	22.2%
Register Alias Table	6.3%
Reservation Stations	7.9%
Reorder Buffer	11.1%
Integer Exec. Unit	14.3%
Data Cache Unit	11.1%
Memory Order Buffer	6.3%
FP Exec. Unit	7.9%
Global Clock	7.9%
Branch Target Buffer	4.7%

Alpha 21264

Caches	16.1%
Out-of-Order Issue Logic	19.3%
Memory Management Unit	8.6%
FP Exec. Unit	10.8%
Integer Exec. Unit	10.8%
Total Clock Power	34.4%


Principle of Clock Gating

- Clock gating a dynamic logic gate

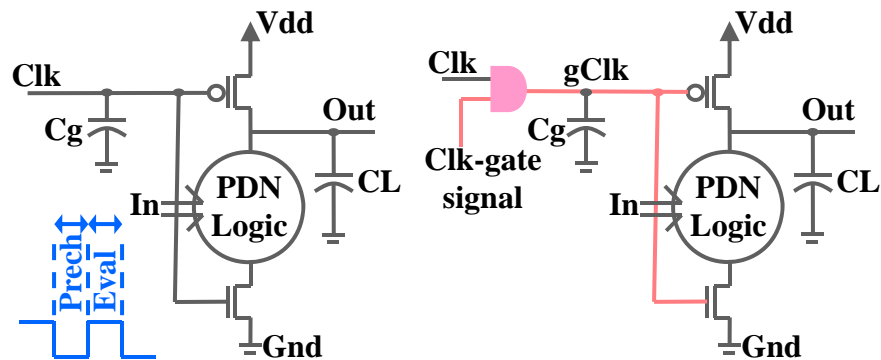


Gated-Clock FSM

 If the FSM enters a state with a self-loop, the signal F_a is asserted and the clock is turned off.




 Limitation:
Only applicable to FSMs where the outputs do not depend directly on the primary inputs (*i.e.*, Moore FSMs).



FSM Transformation

 - Locally transform a Mealy FSM into a Moore FSM




S0: Same output for all of self-loops.

S1: The output depends on the inputs for the diff. self-loops.


Deterministic Clock Gating (DCG) for High Performance Processors

- Target high-performance processors
- Resource use known in advance deterministically
- No prediction overhead
- More power savings
- Virtually no performance loss

DCG Applied to Back-end Stages, Latches

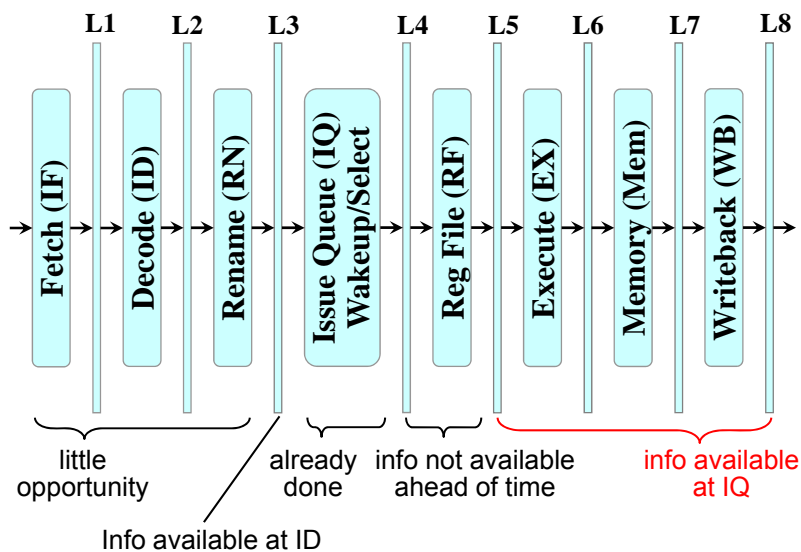

Effectiveness of DCG

 


Average power savings: DCG 20%; PLB-orig 5.6%; PLB-ext 10%
 Performance loss: DCG ~0%; PLB-orig & PLB-ext 2.8%

VSV: Variable Supply-Voltage Scaling

VSV: L2-Miss-Driven Variable Supply-Voltage

 
- CPU usually end up stalling on L2 misses
- **L2 miss** as trigger to transit from high to low V_{DD}



Implementation of VSV


Alpha 21264 floorplan

 Fixed V_{DD}^H transition energy overhead




Two steady operation modes: *high-performance* & *low-power*

High- to Low-Power Mode Transition

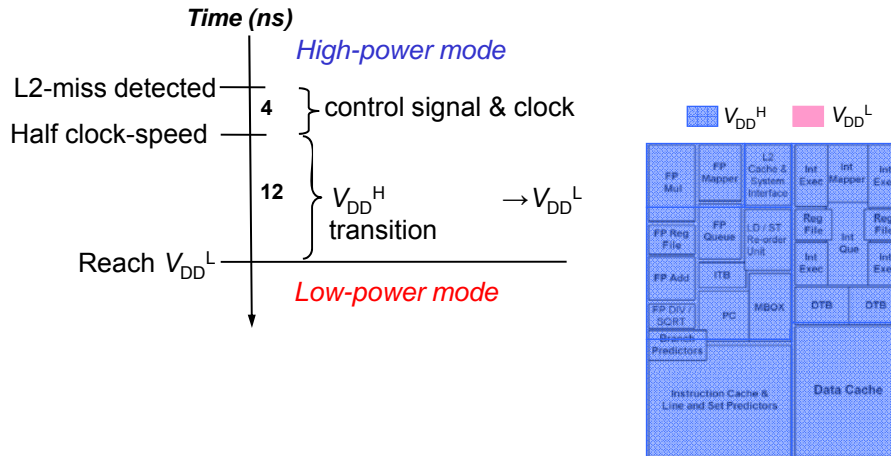


- Not so simple: What if high ILP overlaps misses?

High- to Low-Power Mode Transition

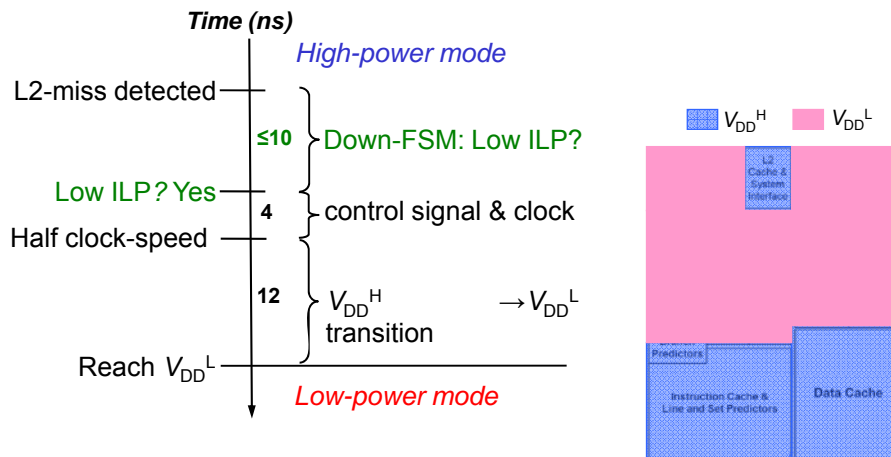


- Go to low-power mode **only if** low ILP
- **Down-FSM** avoids unnecessary performance loss

Low- to High-Power Mode Transition

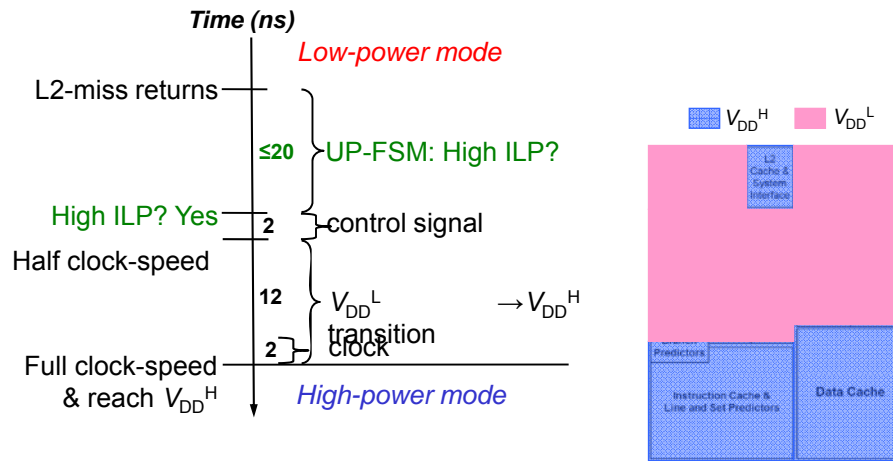


- Back to high-power mode when **LAST** L2 miss returns
- **Up-FSM** increase power savings

Effectiveness

 

- FSMs effectively avoid performance degradation
- Average CPU power savings : performance loss
 - 7% : 1% for all SPEC2K programs
 - 21% : 2% for programs with MR > 4.0

Impact of Time-Keeping Prefetching

 


- Average CPU power savings : performance loss
 4% : 1% for all SPEC2K programs
 12% : 2% for programs with MR > 4.0

Low-Power VLSI Signal Processing (Low-complexity DSP)

Shared Multiplier

- Reduction of redundant computation by increasing computation re-use
- Complexity reduction in FIR implementation
- High performance
- Low power
- Works efficiently if embedded in large DSP systems

Vector scaling operation

 

< Transposed direct form FIR filter >

$$[c_0, c_1, c_2, \dots, c_{M-2}, c_{M-1}] \times X(n)$$

- FIR filtering operation can be expressed as a product of coefficient vector C and scalar $X(n)$

- Vector Scaling Operation , $Y = C \cdot x$

Shared Multiplier Algorithm

- Specifically targets the reduction of *redundant* computation in the vector scaling operation.

< Coefficient Decomposition >

$$c = 111010001100 \qquad c = 2^9(111) + 2^7(1) + 2^2(11)$$

alphabet set = {1, 11, 111}

Alphabets - chosen basic bit sequences


Alphabet set - a set of alphabets that covers all the coefficients in vector C

$$c \cdot x = 111010001100 \cdot x$$


$$c \cdot x = 2^9(0111 \cdot x) + 2^7(0001 \cdot x) + 2^2(0011 \cdot x)$$

if $0111 \cdot x$, $0001 \cdot x$ and $0011 \cdot x$ are available, $c \cdot x$ can be significantly simplified as add and shift operation

Shared Multiplier Architecture

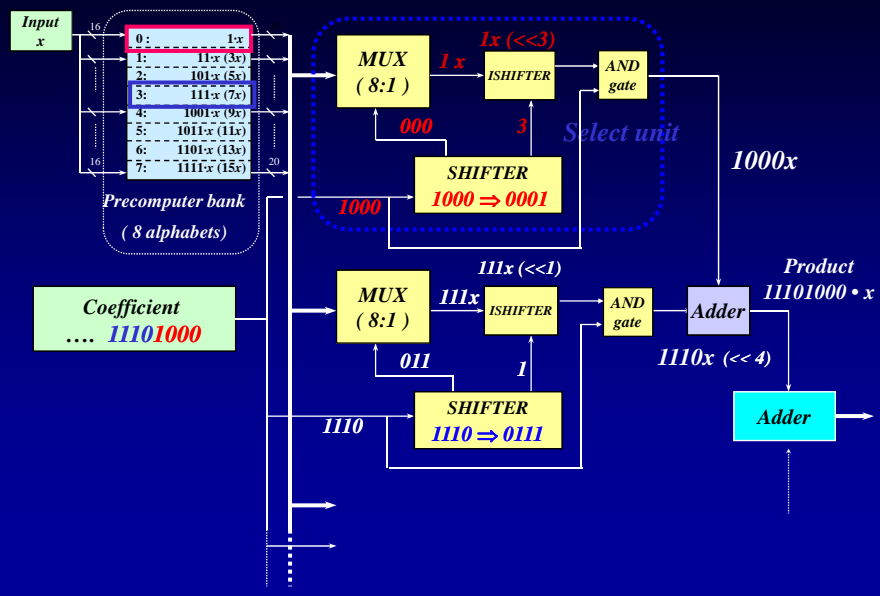

16x16 Shared Multiplier Implementation

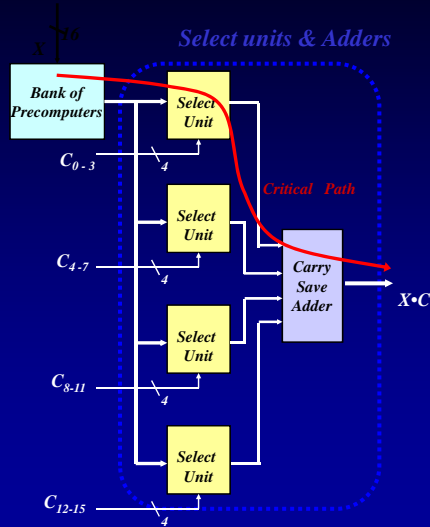


- 16 × 16 Wallace tree multiplier (WTM) and carry save array multiplier (CSAM) are also implemented for comparison.

	Precomputer	Select units & Adders	WTM	CSAM
Delay	6.923 ns	11.231 ns	16.638 ns	23.398 ns
Power	18.06 mW	18.91 mW	22.80 mW	21.78 mW
Area	162340 μm^2	252120 μm^2	241000 μm^2	175640 μm^2


• CMU library (0.35 μm technology)

FIR filter using Shared Multiplier

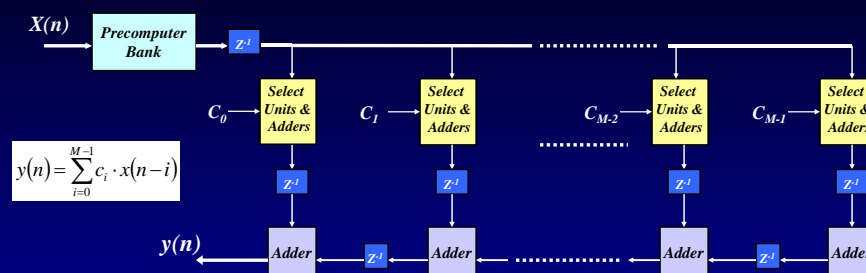

- Computations $a_k \cdot x$ are performed just once for all alphabets and these values are shared by all the select units
- Only select unit and adders lie on the critical path

FIR filter using WT & CSAM

 


Filter	FIR filter using Shared Multiplier	FIR filter using Wallace Tree	FIR filter using Carry Save Array
Clock Cycle	13 ns	18 ns	25 ns
Power	398.4 mW	412.2 mW	401.1 mW
Area	$4.41 \times 10^6 \mu\text{m}^2$	$3.87 \times 10^6 \mu\text{m}^2$	$3.15 \times 10^6 \mu\text{m}^2$

• CMU library (0.35 μm technology) • Power measured with clock frequency : 25ns

Numerical Results

	Radix-16 CSHM (Synth.)	CSHM (Custom)	WTM (Synth.)	CSM (Synth.)
Power Consumption at 10 ns CLK (mW)	226.1	286.6	344.3	357.1
Min. CLK Cycle (ns)	5	7	8.5	10
Area ($\times \text{mm}^2$)	4.1	5.0	4.4	4.1

 
← 16%
← 19%
← 34%
← 37%
← 18%
← 30%
← 41%
← 50%



DFE using Shared Multiplier

- *Coefficient Update*
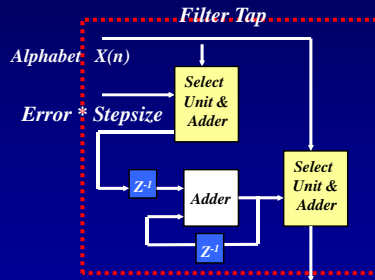
$$C_{k+1} = C_k + StepSize \times Error \times V_k$$



Filter	Clock Cycle	Area
DFE using CSHM	96.67 ns	4.06*10 ⁷ μm ²
DFE using WTM	112.73 ns	2.51*10 ⁷ μm ²
DFE using CSAM	117.23 ns	2.51*10 ⁷ μm ²

- CMU library (0.35 μm technology)

DCT: Shared Multiplier Application

DCT (Discrete Cosine Transform)

- The number of *alphabets* can be reduced by modifying the coefficients in DCT matrix
- Only $1x$ & $3x$ are required for the Precomputer bank
- Performance and Power improvement in *Precomputer bank* and *Select unit*.
- DCT with the modified coefficients generates acceptable quality of image

Shared Multiplier Application


DCT (Discrete Cosine Transform)

$$X_{kl} = \frac{c(k)c(l)}{4} \sum_{i=0}^7 \sum_{j=0}^7 x_{ij} \cos\left(\frac{(2i+1)k\pi}{16}\right) \cos\left(\frac{(2j+1)l\pi}{16}\right)$$

$$k, l = 0, 1, \dots, 7 \text{ and } c(k) = \begin{cases} \frac{1}{\sqrt{2}}, & k=0 \\ 1, & \text{otherwise} \end{cases}$$

$$T = \begin{bmatrix} d & d & d & d & d & d & d & d \\ a & c & e & g & -g & -e & -c & -a \\ b & f & -f & -b & -b & -f & f & b \\ c & -g & -a & -e & e & a & g & -c \\ d & -d & -d & d & d & -d & -d & d \\ e & -a & g & c & -c & -g & a & -e \\ f & -b & b & -f & -f & b & -b & f \\ g & -e & c & -a & a & -c & e & -g \end{bmatrix}$$

• $Z = TX^t, Z = TX^t$

 

Note the **symmetry** of the DCT coef. matrix

DCT (Background)

- Using the Symmetry of the DCT coefficient matrix, the matrix multiplication is simplified.


• $Z = TX^t, X = TZ^t$

Even DCT

$$\begin{bmatrix} z_0 \\ z_2 \\ z_4 \\ z_6 \end{bmatrix} = \begin{bmatrix} d & d & d & d \\ b & f & -f & -b \\ d & -d & -d & d \\ f & -b & b & f \end{bmatrix} \begin{bmatrix} x_0 + x_7 \\ x_1 + x_6 \\ x_2 + x_5 \\ x_3 + x_4 \end{bmatrix}$$

Odd DCT
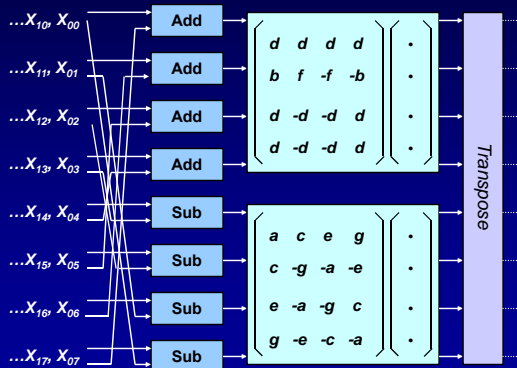
$$\begin{bmatrix} z_1 \\ z_3 \\ z_5 \\ z_7 \end{bmatrix} = \begin{bmatrix} a & c & e & g \\ c & -g & -a & -e \\ e & -a & g & c \\ g & -e & c & -a \end{bmatrix} \begin{bmatrix} x_0 - x_7 \\ x_1 - x_6 \\ x_2 - x_5 \\ x_3 - x_4 \end{bmatrix}$$



DCT using Shared Multiplier

$$X_{kl} = \frac{c(k)c(l)}{4} \sum_{i=0}^7 \sum_{j=0}^7 x_{ij} \cos\left(\frac{(2i+1)k\pi}{16}\right) \cos\left(\frac{(2j+1)l\pi}{16}\right)$$

• $Z = TX^t$, $X = TZ^t$

Even DCT

$$\begin{bmatrix} z_0 \\ z_2 \\ z_4 \\ z_6 \end{bmatrix} = \begin{bmatrix} d & d & d & d \\ b & f & -f & -b \\ d & -d & -d & d \\ f & -b & b & f \end{bmatrix} \begin{bmatrix} x_0 + x_7 \\ x_1 + x_6 \\ x_2 + x_5 \\ x_3 + x_4 \end{bmatrix}$$

Odd DCT

$$\begin{bmatrix} z_1 \\ z_3 \\ z_5 \\ z_7 \end{bmatrix} = \begin{bmatrix} a & c & e & g \\ c & -g & -a & -e \\ e & -a & g & c \\ g & -e & c & -a \end{bmatrix} \begin{bmatrix} x_0 - x_7 \\ x_1 - x_6 \\ x_2 - x_5 \\ x_3 - x_4 \end{bmatrix}$$

8bit DCT Coefficients

Original 8-bit DCT coefficient			
Coefficient	Value	Binary code	Pre-computer bank Needed
a	0.49	0011 1111	3x, 15x
b	0.46	0011 1011	3x, 11x
c	0.42	0011 0101	3x, 5x
d	0.35	0010 1101	1x, 13x
e	0.28	0010 0100	1x
f	0.19	0001 1000	1x
g	0.10	0000 1100	3x

Modified 8-bit DCT coefficient			
Coefficient	Value	Binary code	Pre-computer bank Needed
a'	0.50	0100 0000	1x
b'	0.47	0011 1100	3x
c'	0.41	0011 0100	1x, 3x
d'	0.34	0010 1100	1x, 3x
e'	0.28	0010 0100	1x
f'	0.19	0001 1000	1x
g'	0.12	0000 1100	3x

- Only 1x & 3x are required in the Modified 8-bit DCT Coefficient

DCT using Shared Multiplier



< DCT with original 8 bit coefficient >



< DCT with modified 8 bit coefficient >

- DCT with the modified coefficients generates acceptable quality of image

Shared Multiplier: Summary

- Reduces computational complexity
- Possible to trade-off power/performance by judiciously selecting coefficients and alphabets

Differential Coefficients Method (DCM)

< FIR Filtering operation >

- An “ n ” tap FIR Filter performs the following computation :

$$Y_j = \sum_{k=0}^{n-1} C_k X_{j-k}$$

- C 's are the filter coefficients
- X and Y are the input and output sequences.
- The filter output Y typically obtained by :
 - Computing each product term by multiplication
 - Summing up the product terms
- Called *Direct Form (DF)* computation of the FIR output

FIR Filters using Differential Coefficients

- Excepting the first coefficient the C's can be expressed as :

$$C_k = C_{k-1} + \delta_{k-1/k}^1$$

- The delta's are called the "**First Order Differences**"
- By expanding the expression for consecutive Y's and subtracting we get :

$$Y_{j+1} = Y_j + C_0 X_{j+1} + \sum_{k=1}^{N-1} \delta_{k-1/k}^1 X_{j-k+1} - C_{N-1} X_{j-N+1}$$

- The "**First Order Partial Sum**" is defined as :

$$\sum_{k=1}^{N-1} \delta_{k-1/k}^1 X_{j-k+1} = \{S_P^1\}_{t=j+1}$$

Advantages of the FD algorithm

- To obtain Y we now do the following :
 - Retrieve the previously computed Y
 - Compute the "partial sum" and the two other product terms by multiplication
 - Add these to obtain the current Y
 - Store the current Y
- Called the "**First Order Differences Algorithm**" (**FD**) for computing the FIR Filter output
- Computational savings of FD algorithm:
 - only if differences (delta's) are smaller than C's
 - product term computation simplified as the differences have reduced word-width

Algorithm using generalized differences

- Generalized m -th order differences defined as :

$$\delta_{k-m/k}^m = \delta_{k-m+1/k}^{m-1} - \delta_{k-m/k-1}^{m-1}$$

- We can thus generalize the recurrence for Y as :


$$Y_{j+1} = Y_j + C_0 X_{j+1} + \sum_{k=1}^{m-1} \left[\left\{ S_p^k \right\}_{t=j} + \delta_{0/k}^k X_{j-k+1} \right.$$

$$\left. - \delta_{N-k-1/N-1}^k X_{j-N+1} \right] - C_{N-1} X_{j-N+1} + \sum_{k=m}^{N-1} \delta_{k-m/k}^m X_{j-k+1}$$

- Multiplications involve only m -th order differences
- Greater computational savings possible if the m -th order differences are even smaller than the coefficients

Example: Low Pass Filter

 
- Example : FIR Filter with 100 taps
- Shift and Add model for multiplication
- Energy dissipated data from a low-power library



Canonical Signed Digits (CSD)

- Canonical Signed Digits (**CSD**) is another commonly used technique for simplifying multiplications in FIR filters
- Reduces switching-power by reducing number of ones in multiplier
- Typically a 33% reduction in the number of ones (and hence additions) is obtained using CSD
- **Compared to CSD, DCM has 40% better power dissipation**
- **Modifications to DCM is possible for near multiplier-less filters**

Coefficient Reordering

 

- We represent this problem using a graph in which vertices represent the coefficients and edges represent the resources required when the differential coefficient corresponding to the edge is used in the computation
- The optimal solution is the well-known problem of finding the *Hamiltonian cycle* of smallest weight of this graph (*minimum spanning tree*), thus achieving even lower complexity


Implementation of DCM1

Compute the Hamiltonian cycle in G

$K = \{k_0, \dots, k_{M-1}\}$ = set of ordering of indices of the coefficients


(e.g. In DCM $K = \{0, 1, 2, 3, \dots, M-1\}$, $\Delta c_j = c_{1+j} - c_j$)

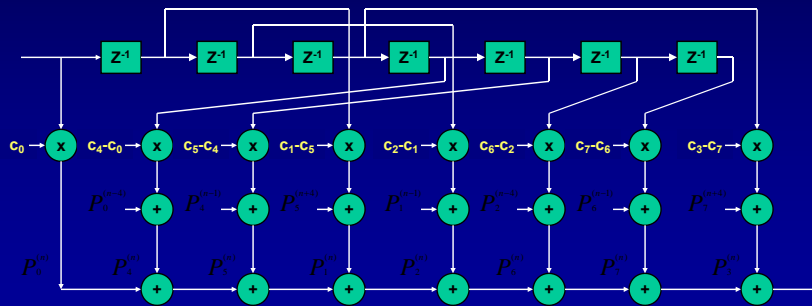Then $\Delta c_i = c_{k_{i+1}} - c_{k_i}$ and $P_{k_i}^{(n)} = (c_{k_i} - c_{k_{i+1}})x^{(n-k)} + P_{k_{i+1}}^{(n-k, k_{i+1})}$



Obtaining the Reduced Form

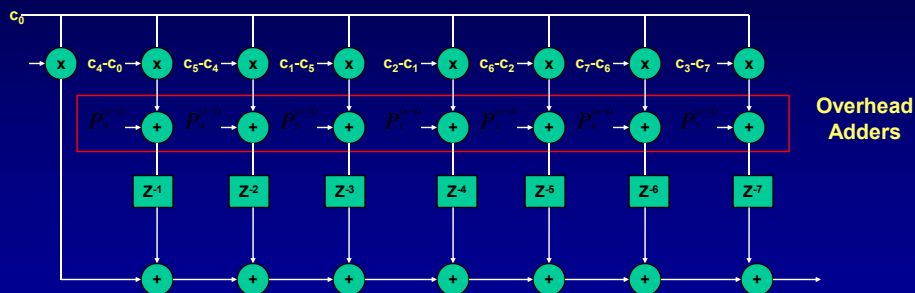
Step 1 : Move the delay elements into branches



Obtaining the Reduced Form

Step 2 : Move the delay elements out of the branches and connect the appropriate partial product.

- Overhead = M-1 Add operations.

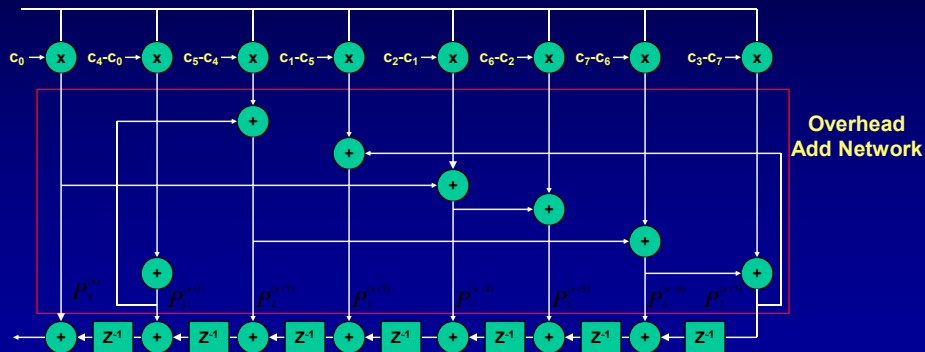

Low Complexity FIR Filters with FPC

- Factorization of Perturbed Coefficients (FPC) is a method to design digital filters which require less computation.
- **Factorization** allows common factors between coefficients in the filter to be used to share computation.
- **Perturbation** maximizes the benefits of factorization by guaranteeing “good” common factors.
- FPC **constrains** the frequency response within acceptable limits.

Factorization

- The output of an FIR filter is:

$$y(n) = \sum_{i=0}^{M-1} C_i x(n-i)$$

- If two coefficients have a common factor there is a calculation that can be shared.

(i.e., If $C_1 = F_1 * F_2$ & $C_2 = F_1 * F_3$, the value of $F_1 * x(n)$ can be reused.)

- The problem is the lack of common factors across multiple coefficients.

Perturbation

- Every whole number is unique product of prime factors. Thus the coefficients can be expressed as:


$$C_i = \prod_{k=1}^{Q(n)} \{ f_n(k) \}^{Pn(k)}$$

- To maximize the number of common factors, generate the coefficients from a small set of prime factors.
- To minimize the impact on the filter output, these should be the first several prime factors: $f = \{2,3,5,7,11...\}$

FPC Algorithm

- Start with Parks-McClellan and Least Squares filters. These provide our bounds.
- Use these filter coefficients to find an intermediate filter.
- Perturb the coefficients of this new filter until they are products of only the first few prime numbers (2,3,5,7,11...) AND still within bounds.
- Build factorization tree that give all of the coefficients.

Sample Filter Response

 

FPC Results


- FPC can be applied to filters of various types and sizes to give a 24-43% savings in the amount of computation.

Filter	Type	Pass-band	Stop-band	PM taps	LS taps	Savings
EX	LPF	0.0-0.25	0.55-1.0	8	10	24%
A	HPF	0.7-1.0	0.0-0.6	57	75	43%
B	LPF	0.0-0.4	0.5-1.0	54	78	28%
C	BPF	0.5-0.6	0-0.35, 0.75-1	54	76	24%
D	HPF	0.475-1.0	0.0-0.4	91	115	36%
E	LPF	0.0-0.2	0.25-1.0	71	121	39%
F	BPF	0.4-0.5	0-0.3, 0.6-1	85	111	30%
G	HPF	0.75-1.0	0.0-0.7	123	161	39%
H	LPF	0.0-0.575	0.625-1.0	131	167	25%

LPF: Low-Pass Filter
 BPF: Band-Pass Filter
 HPF: High-Pass Filter
 TAPS: Size of filter
 (# of coefficients)


Other Silicon Solutions

 - FINFET's and Double Gate MOSFET's
- Better short channel effect
- Intrinsic channel
- Better scalability




Advantages of Double Gate Devices

 - Short channel effect control
 - Better scalability
 - Lower subthreshold current
- Higher On Current
- Near-Ideal Subthreshold slope
- Elimination of V_t variation due to Random dopant fluctuation



DG devices are very promising for circuit design in sub-50nm technology

 How do we design circuits in Double Gate technologies ?




Use the “good” DG devices in place of single gate bulk-CMOS/PD-SOI devices

Are there any new challenges?


How can we take advantages of DG technologies?

Nano-Scaled Double Gate Devices

 



DGMOS

Planar double-gate structure

 


FinFET or Tri-Gate

Quasi-planar DG structure

  


Ground Plane SOI MOS

Shared back gate DG devices

 

Independent gate FinFET



Asymmetric DG Devices

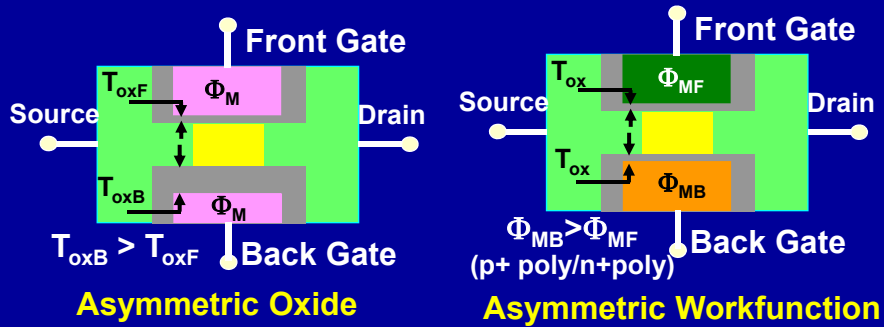

- **Asymmetric DG devices has different front and back gate properties**
 - Front gate is stronger and has more control over the channel than the back gate


What opportunities do we have for circuit design in DG technologies?

3-Terminal DG Devices

 
 


3-Terminal DG devices are essentially "better" single gate devices

3-Terminal DG Devices

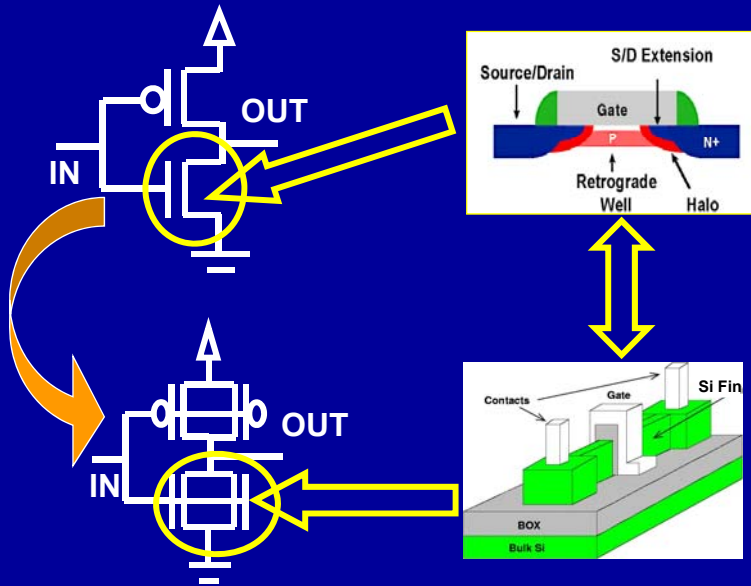


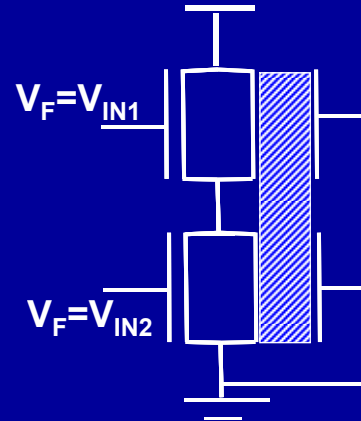 DG Devices with Shared Back Gate (GP-SOI)





GP-SOI devices are similar to bulk-CMOS devices with substrate biasing option

Back-Biased Circuits in GP-SOI

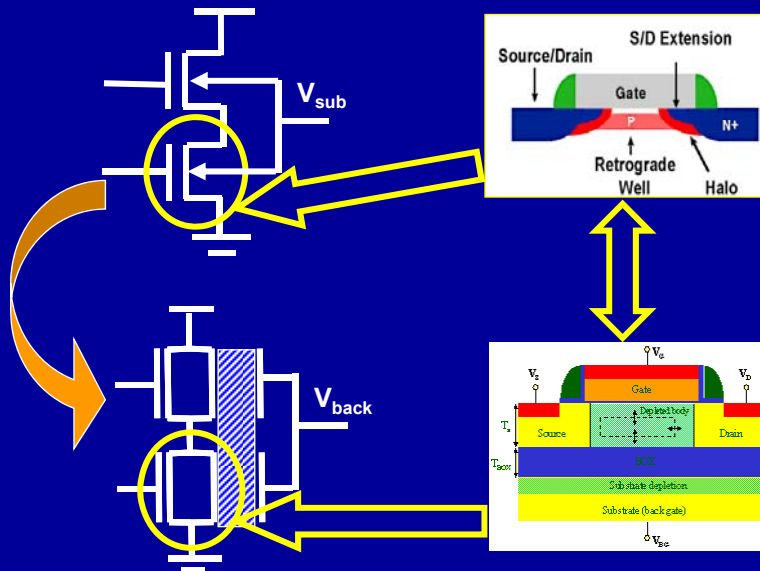

  
DG Devices with Independent Front and Back Gates




Independent gate devices can have separate input at front and back gates

Unique in DG technologies → Design of new circuit styles


4-Terminal DG Devices

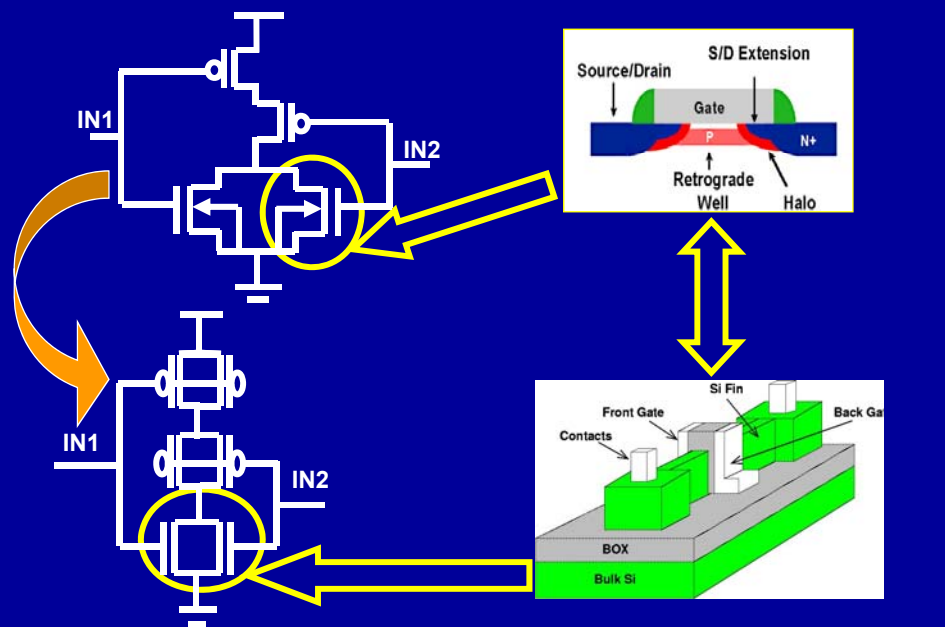

 
Circuits Design in Double Gate Technologies



 3-T DG devices
 Directly Translate
 single gate designs
 Width quantization,
 T_{si} variations,




 
**DG devices with
 shared back gate
 GP-SOI**
 Back biased circuits
 Dynamic V_t circuits



4-T DG Devices
 Unique for DG
 Isolated front and
 back gate can have
 diff. inputs
 New circuit styles




Dynamic V_t Circuits in GP-SOI Technology

Back Biasing for Dynamic- V_t

  


Applying bias to the back gate can modify “on” and “off” currents of the device

Back Biasing for Dynamic- V_t

   


Back-biasing in GP-SOI is more effective than body-biasing in bulk

Digital Back Bias (DBB) in GP-SOI

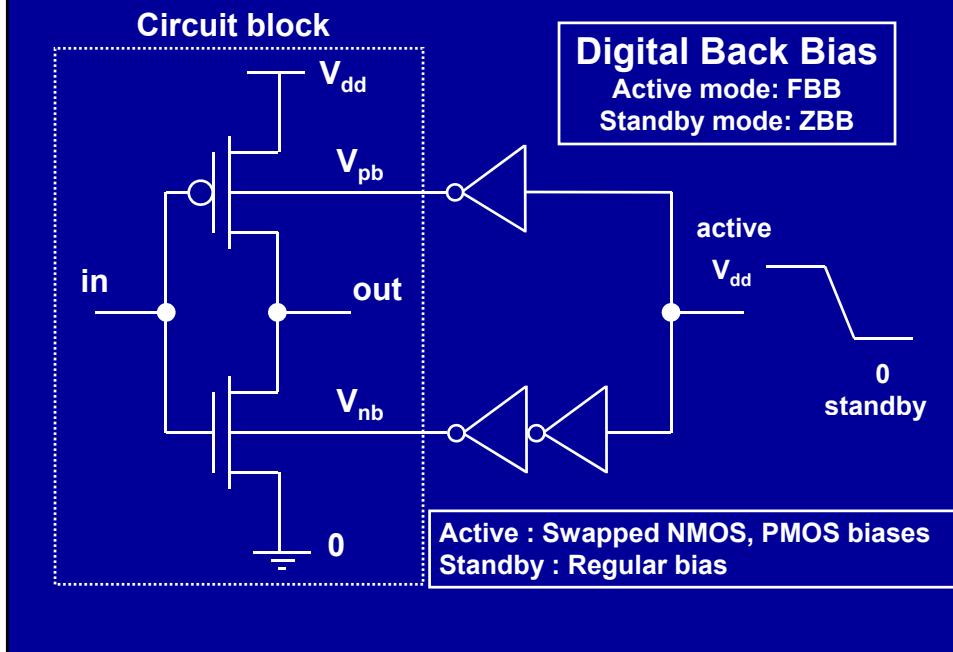





Dynamic Digital Back Biasing with GP-SOI

 



Dynamic DBB improves performance and leakage

Digital Circuit Design using Independent Gate Operation in Double-Gate Devices


4-Terminal Operation of DG (Symmetric)

    

4-Terminal Operation of DG (Asymmetric)

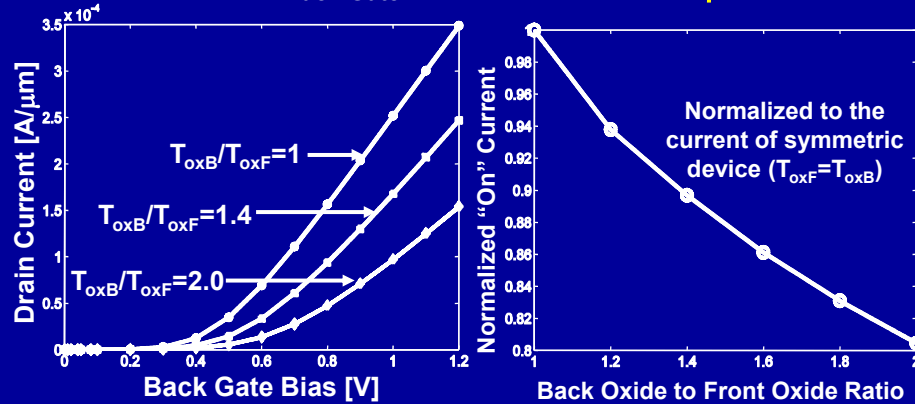 

 Digital Circuits using Independent Gate Devices




Schmitt Trigger
New circuit style
Lower power and smaller area


Pre-Charge Evaluate Logic
Domino & Skewed CMOS
Better power-delay

Sense-Amplifier
Higher performance
Better robustness
Smaller area

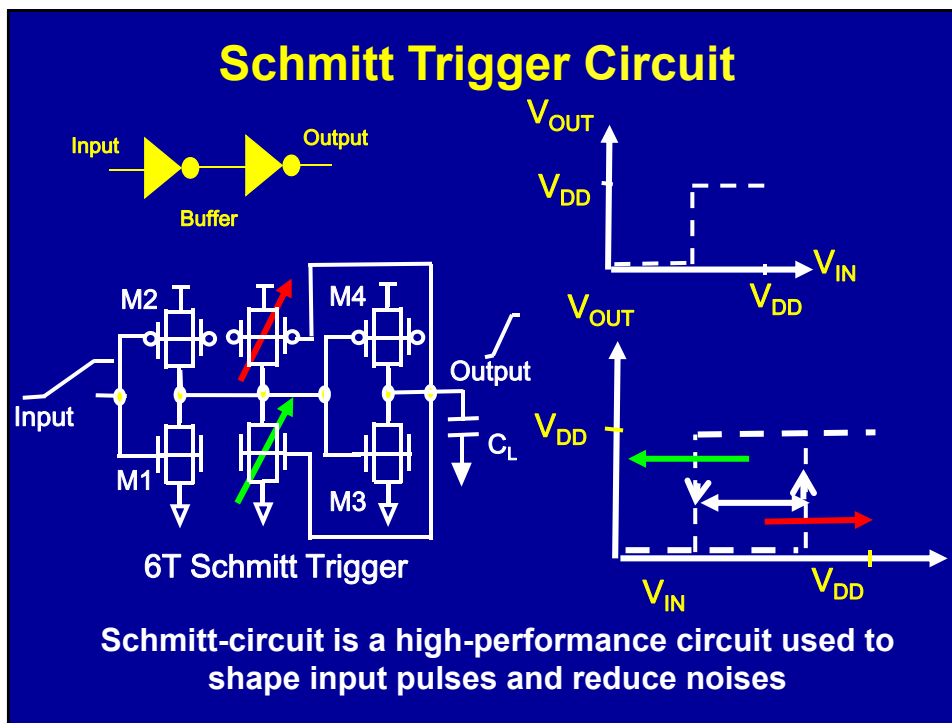4-Transistor Schmitt Trigger Circuit using Independent Gate Devices




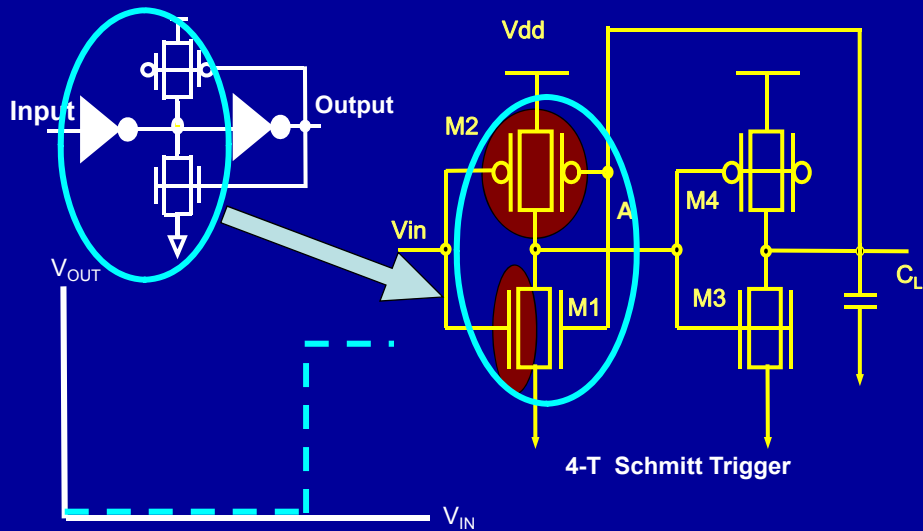4-T Schmitt Trigger using Independent Gate




Independent control of the back gate reduces the number of transistors in the Schmitt Trigger circuit

 4-T Schmitt Trigger using Independent Gate




Independent control of the back gate reduces the number of transistors in the Schmitt Trigger circuit

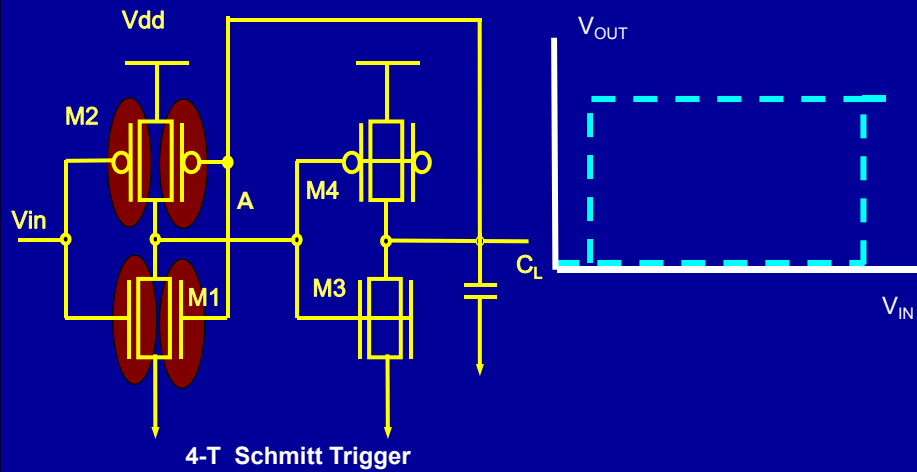4-T Schmitt Trigger using Independent Gate





4-T Schmitt Trigger with symmetric devices can have large hysteresis window

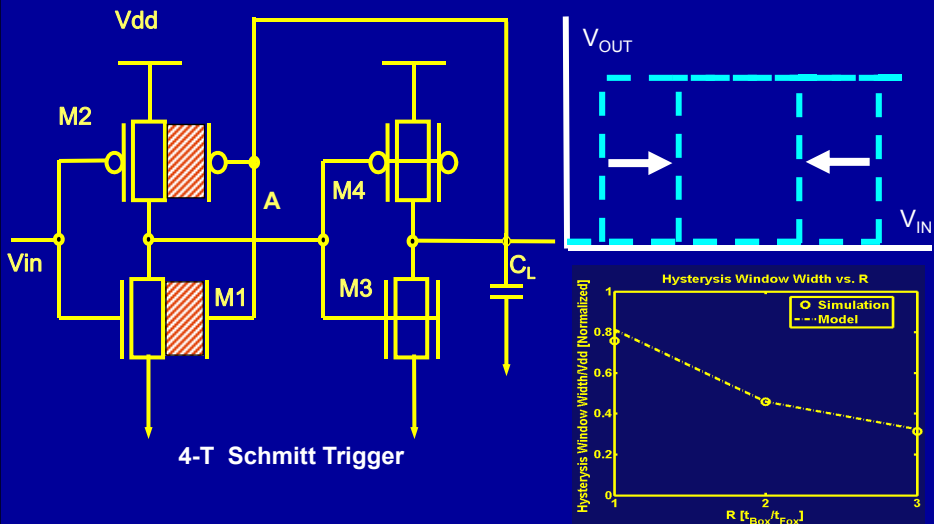4-T Schmitt Trigger using Independent Gate



Hysteresis window in 4-T Schmitt-Trigger can be designed using Asymmetric DG devices

  
4-T Schmitt Trigger using Independent Gate



4-T Schmitt-Trigger designed using Asymmetric devices can achieve lower power at high noise immunity corner



Pre-Charge Evaluate Logic Circuits using Independent Gate Devices

Independent Gate Dynamic Logic



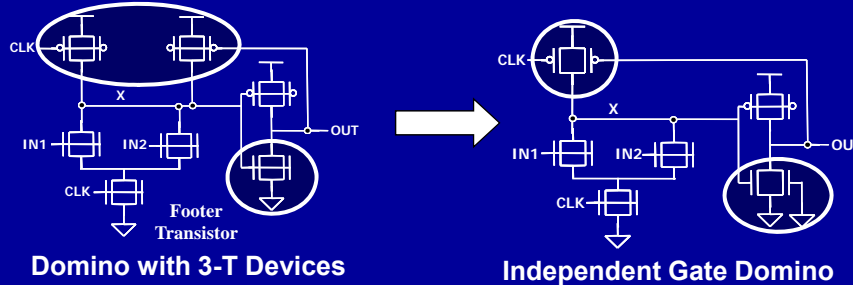


Domino with 3-T Devices


Independent Gate Domino

  

Skewed Logic

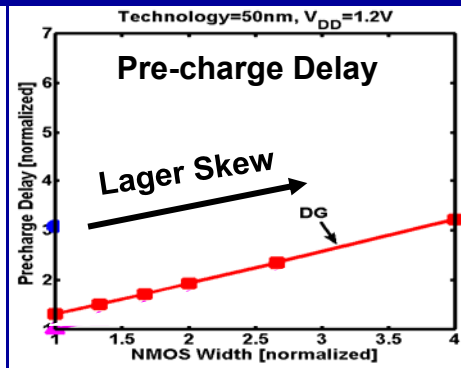  


Independent Gate Skewed Logic

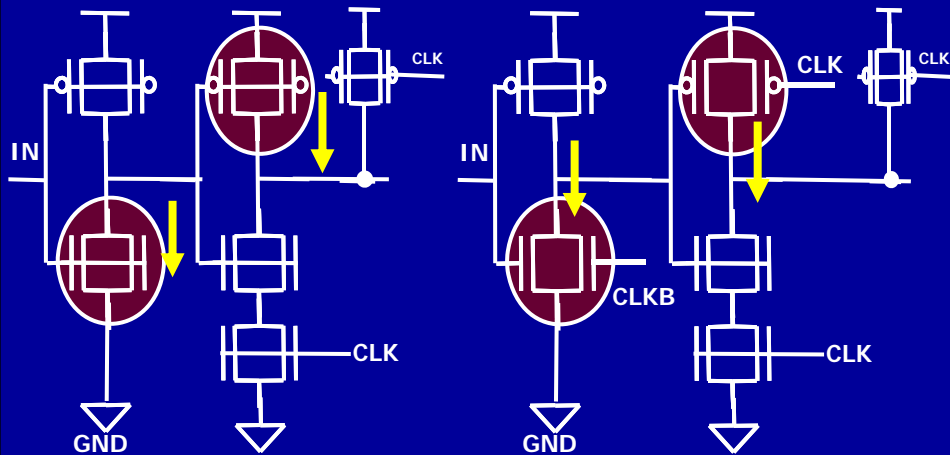

DG Skewed Logic


IG Skewed Logic

Independent Gate Skewed Logic

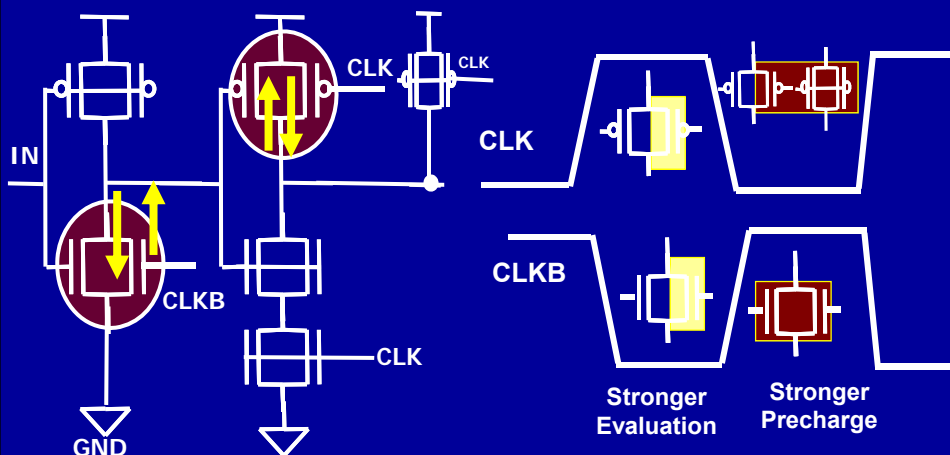


IG Skewing reduces evaluation and precharge delay

Independent Gate Skewed Logic

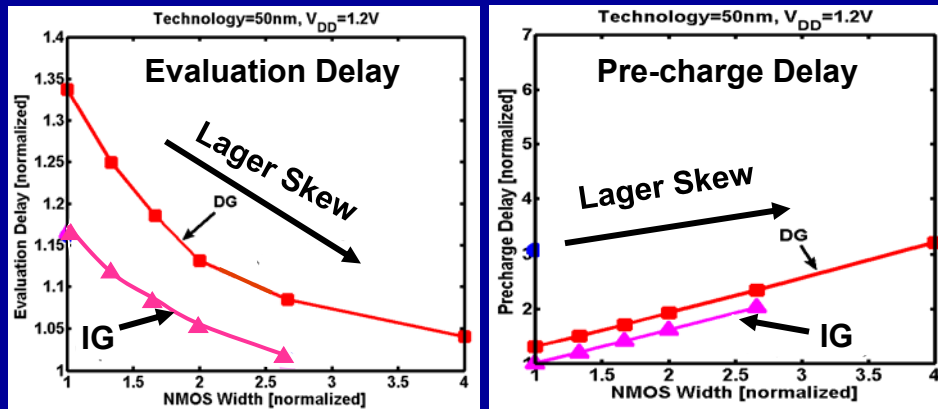

IG Skewing reduces evaluation and precharge delay


Independent Gate Skewed Logic

 


Independent gate operation results in higher performance and lower power in skewed logic

High-Performance Sense-Amplifier using Independent Gate Devices

Sense Amplifier using 3-T Devices

 


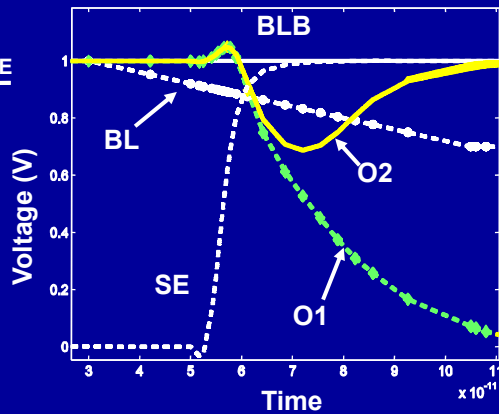Sense Amplifier Circuit designed using 3-T devices




Voltage difference between BL and BLB produces current difference between ND1 and ND2

Independent Gate Sense Amplifier

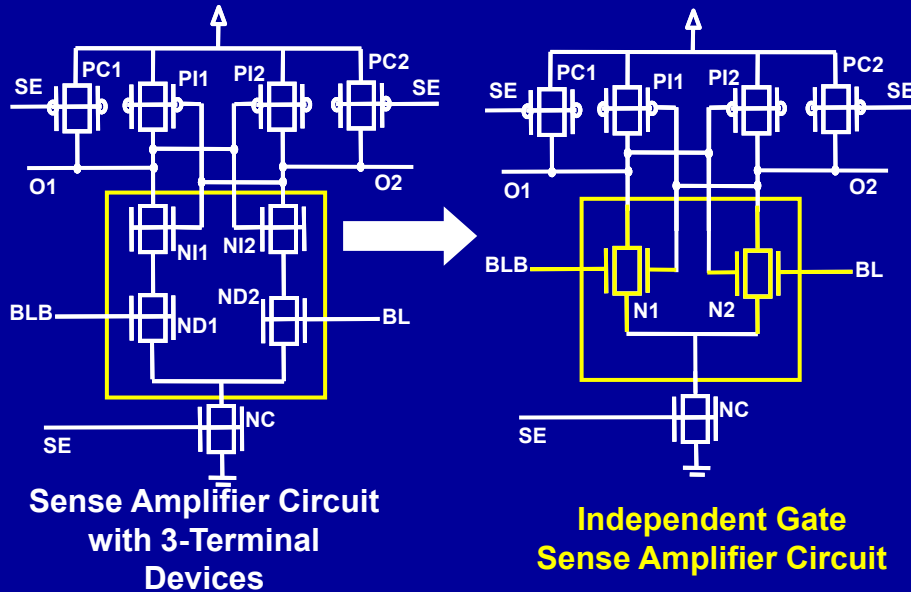

Process Variation Tolerance of IGSA

 

- **IGSA shows better performance and robustness**
 - Lower sensing delay
 - Better tolerance to Tsi mismatch

Conclusions

- Power considerations (both dynamic and leakage) are very important for scaled technologies
- Process parameter variation is also expected to be a major concern. There is a need for leakage statistical design techniques to improve power dissipation and yield
- An integrated approach to design – device/circuit/arch. – is essential for an optimized design
- New failure modes have to be considered for nano-scale designs
 - Process parameter variations
 - High Leakage
 - Soft failures
- New technologies may come to the rescue!
 - DG-MOSFET, FINFET's, CNFET's, Molecular RTD's,