


SRAM - Basics

Jaydeep P. Kulkarni

`jaydeep@ecn.purdue.edu`


Slides are adopted from Prof. Kaushik Roy, Prof. Chris Kim , Prof. Saibal Mukhopadhyay, and Prof. Jan Rabaey's slides

Semiconductor Memory Trends

 


From [Itoh01]

Why SRAMs are Important


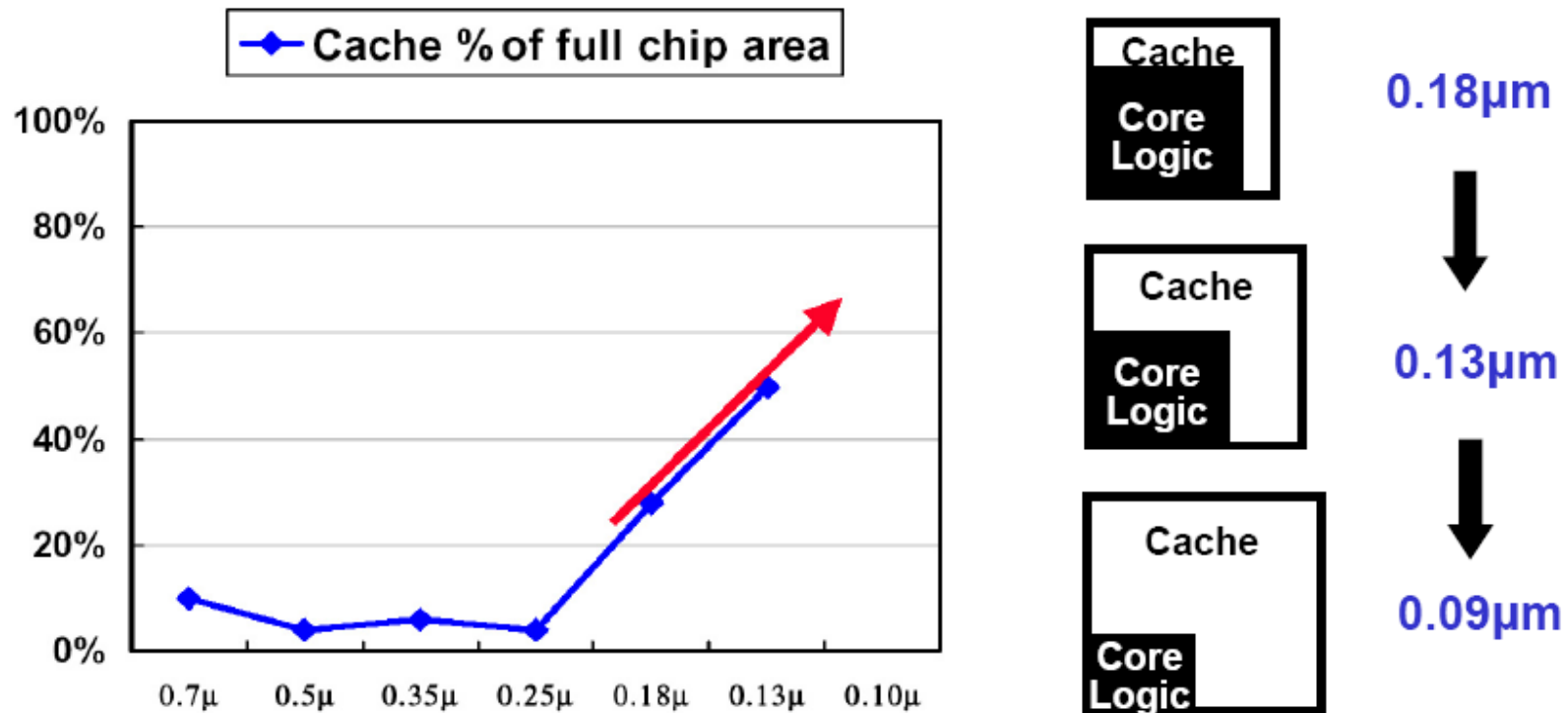


- Memories have better power efficiency compared to logic
- ~9.9B out of 10B transistors will be used for SRAMs
- Company with better SRAM design will dominate

Positive Feedback: Bi-Stability

 


Meta-Stability

  


Gain should be larger than 1 in the transition region

SRAM Memory Cell

 

- **NMOS access transistors**
- **Read and write uses the same port: need sufficient margins**
- **One wordline to access cell**
- **Two bit lines (BL, BLB) to carry the data**
- **Almost minimum size transistors for small cell area**


SRAM Read Operation

 

- Both bit lines are precharged to Vdd
- Wordline is fired for one of the cells on bit line
- Cell pulls down either BL or BLB
- Sense amp regenerates the differential signal
- Data should not flip after read access
- Driver TR must be stronger than access TR


SRAM Read Operation
 
$$\textit{bitline delay} = \frac{C_{\textit{bitline}} \Delta V_{\textit{bitline}}}{I_{\textit{cell}}}$$




- $C_{\textit{bitline}}$ is large due to large number of cells attached
- $I_{\textit{cell}}$ is small due to high density cells
- $\Delta V_{\textit{bitline}}$ has to be minimized for high speed
 - < 100mV bitline voltage difference generated by SRAM cell
 - Let the sense amplifier finish the job
 - Increased noise sensitivity, circuit complexity


Variation in Process Parameters

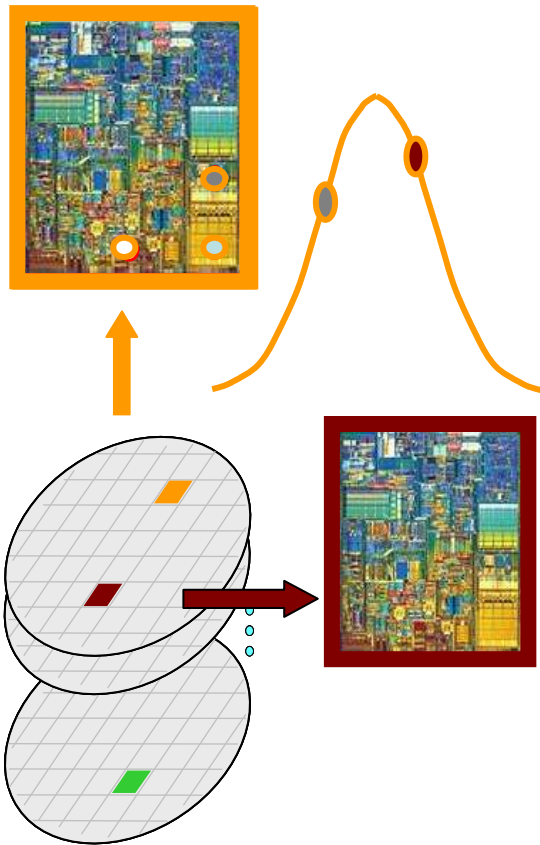

Inter and Intra-die Variations

 




Line Edge Roughness (LER)

 

Random Dopant Fluctuation (RDF)

- SRAM Transistors – Minimum geometry
- Inter-die and Intra-die variations
- LER, RDF induced device mismatch

Parametric Failures: Read Failure


 
 
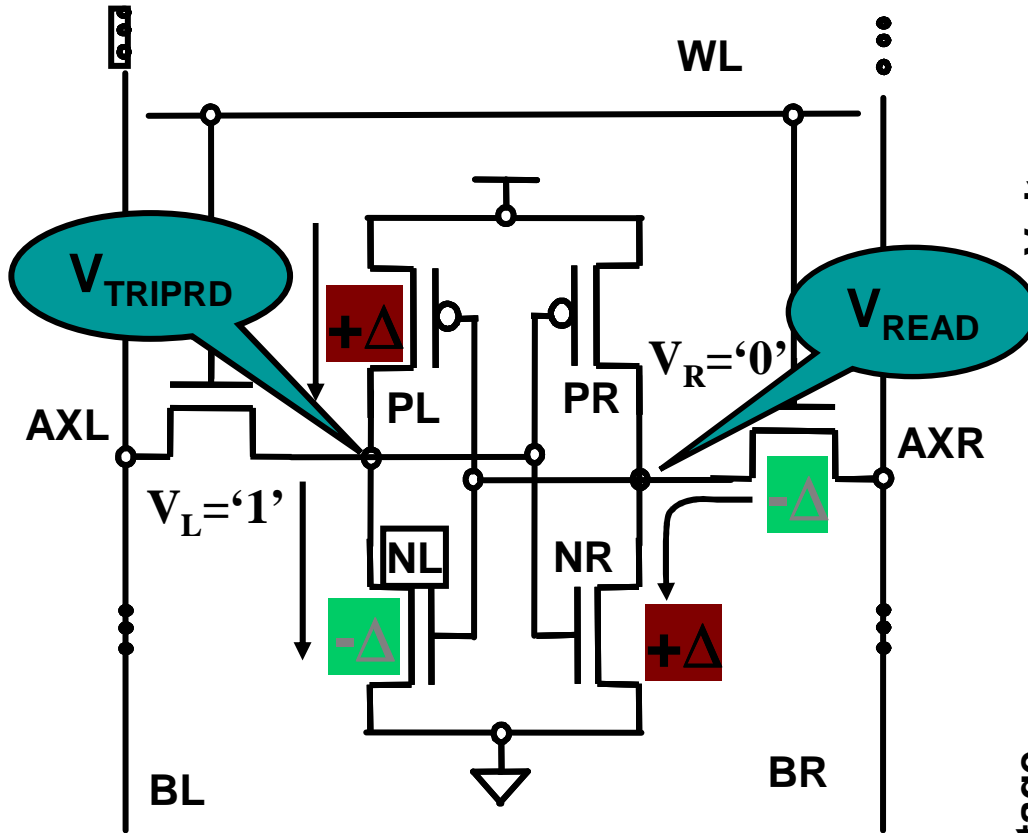


$$P_{RF} = P(V_{READ} > V_{TRIPRD})$$


Read failure => Flipping of Cell Data while Reading

Mechanisms of Parametric Failures


11

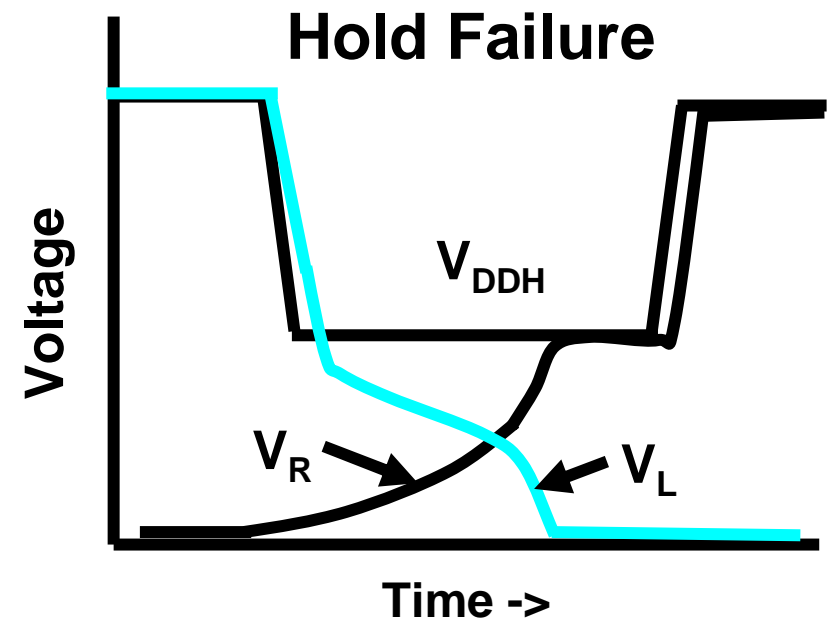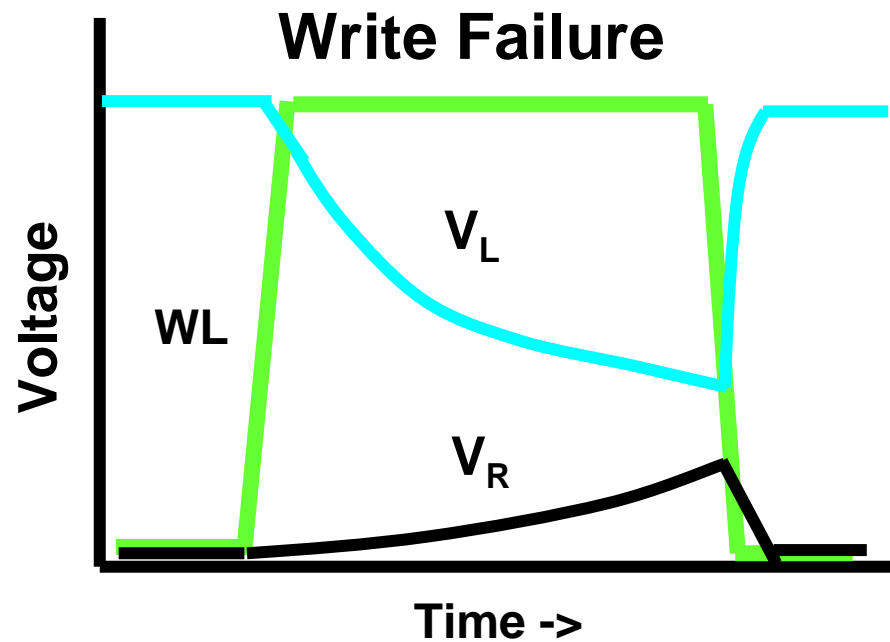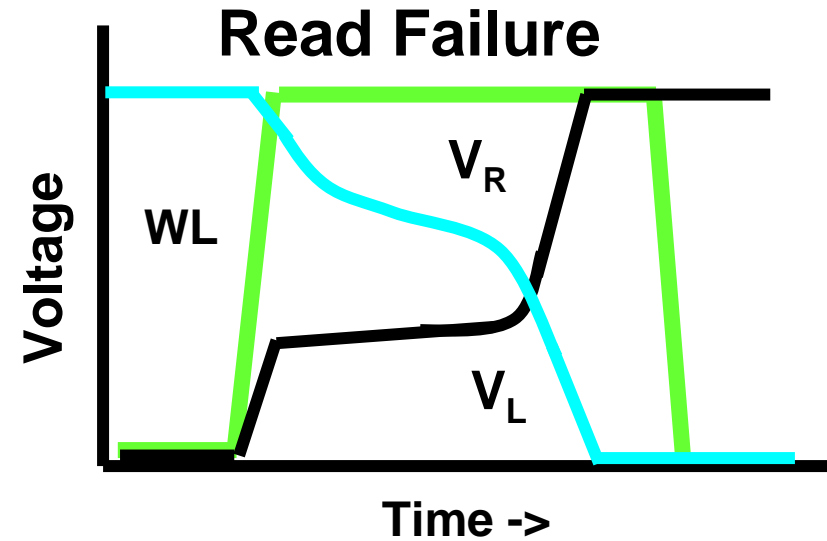 

SRAM Read Operation: Precharge

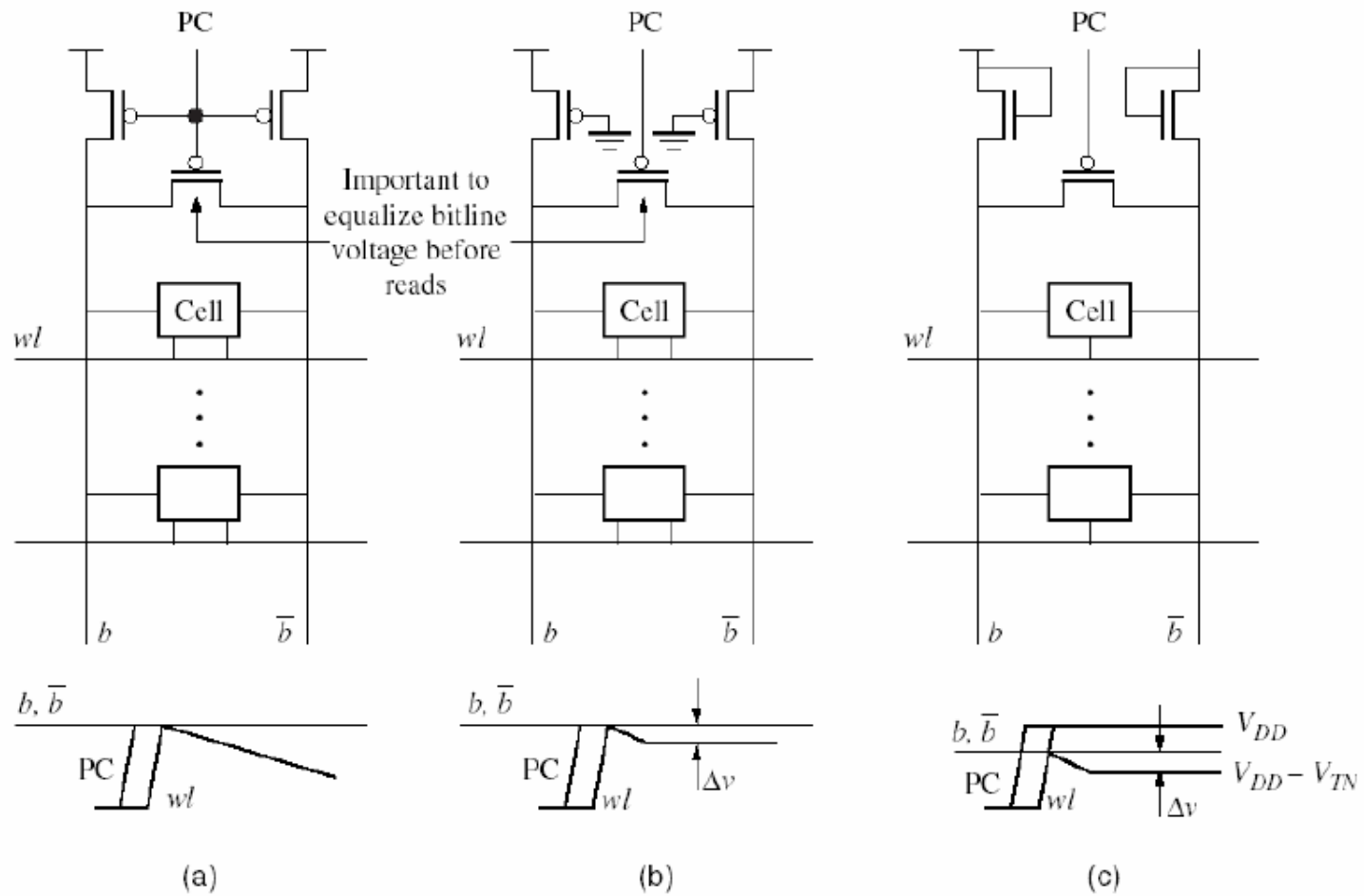


SRAM Cell Read Margin


 


- **When cell is not accessed ($WL=0$)**
 - Data is safely kept inside the cell
 - High noise margin
- **When cell is accessed ($WL=V_{dd}$)**
 - Access transistor acts as a noise source
 - Data '0' is pulled up to V_x
 - Cell data can flip if V_x rises above V_{tn}


Static Noise Margin

 

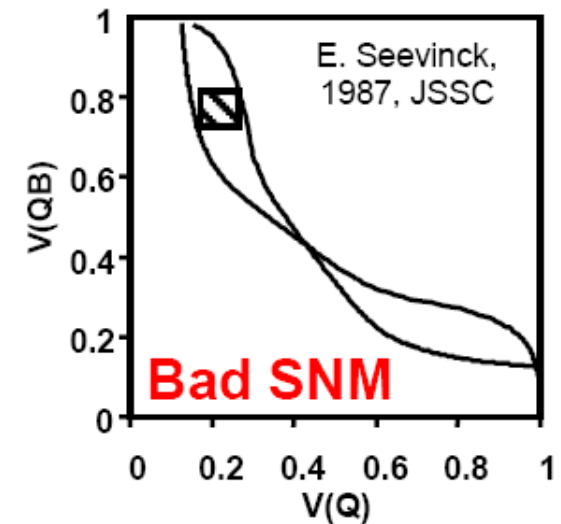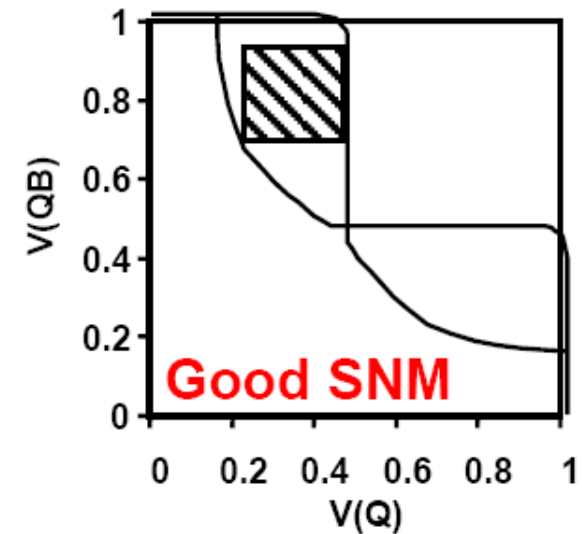- Destructive read problem
- The size of the largest square enclosed in the butterfly curves = read static noise margin



Techniques to Improve Read Margin

 


Cell beta ratio =
 $(W/L)_{\text{drv}} / (W/L)_{\text{access}}$

J. Rabaey

- Increasing the size of the driver NMOS improves read margin
- But remember, area is the number one constraint in memory design
- Increasing cell size a not a good trade off


Techniques to Improve Read Margin

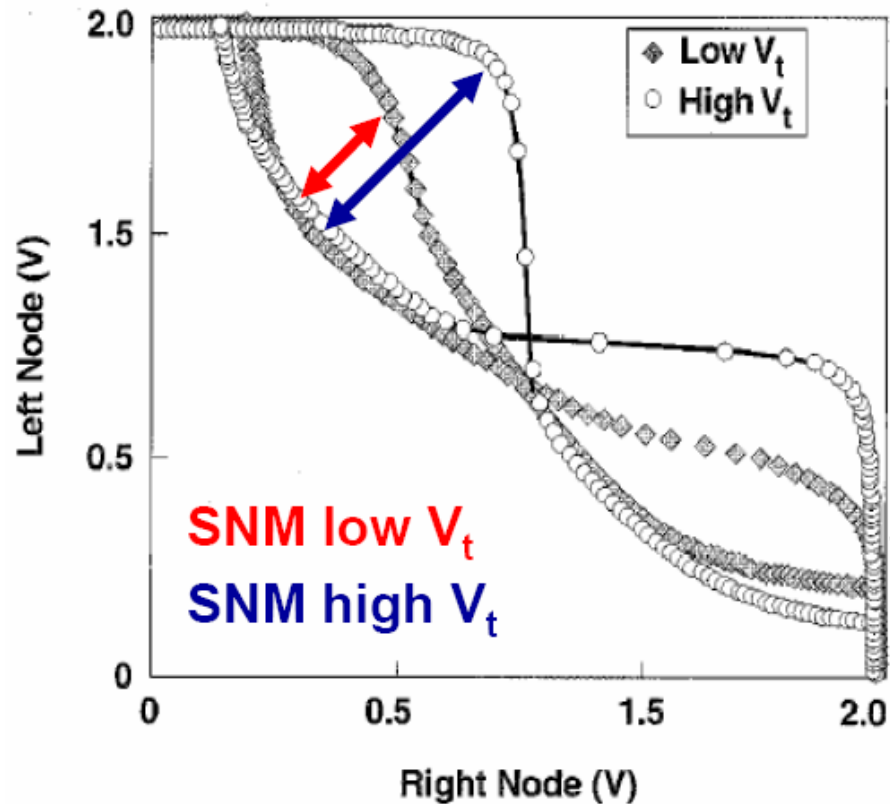- High V_t transistors
 - Internal node on low side needs to rise to V_t or more
 - Virtually never happens when V_t is larger than half V_{dd}
 - Cell is extremely stable at ultra-low power design point
 - Beta ratio constraint is relaxed \rightarrow smaller driver and larger access TR can be used for faster read and write





Techniques to Improve Read Margin

 - **Boosted cell supply**
 - Supply voltage of SRAM cell is higher than outside
 - Makes driver stronger than access, suppressing the rise in the low side
 - Effectively improves the beta ratio
 - Driver NMOS can be downsized, decreasing cell size




SRAM Write Operation

  

- Launch the write data on BL and BLB
- Word line signal is fired
- Low bit line value flips cell data
- Access TR must be stronger than PMOS load


SRAM Cell Write Margin

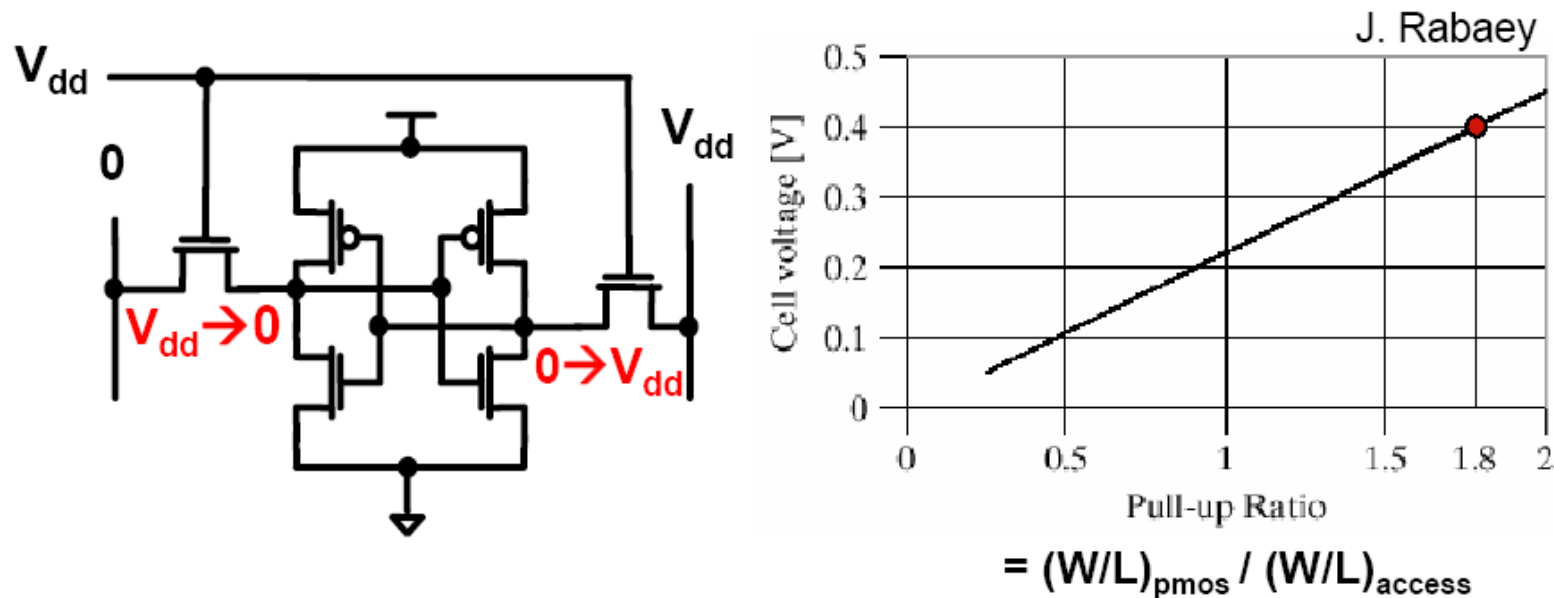


- Access transistor must be stronger than PMOS to pull the node below the trip point (typical pull-up ratio ~ 1.5)
- To avoid cell size increase, correct pull-up ratio achieved by controlling V_{tn} and V_{tp}

Techniques to Improve Write Margin

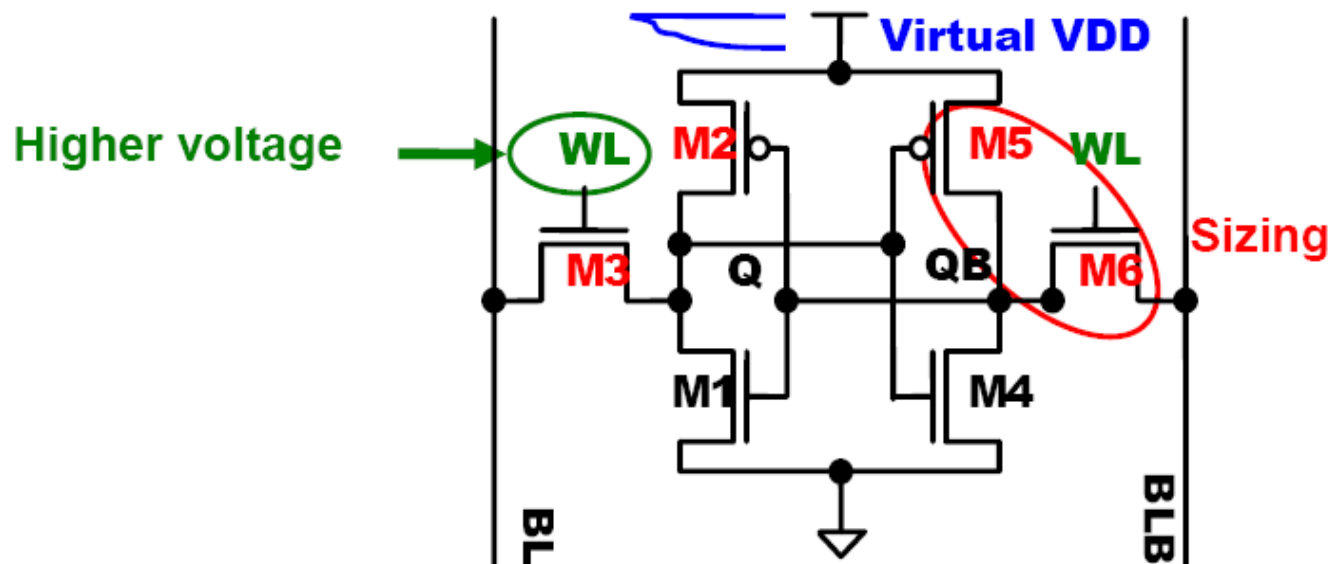
- Sizing: access TR vs. PMOS in latch
- Higher WL voltage for access TR
- Virtual VDD



SRAM Bitcell Layouts

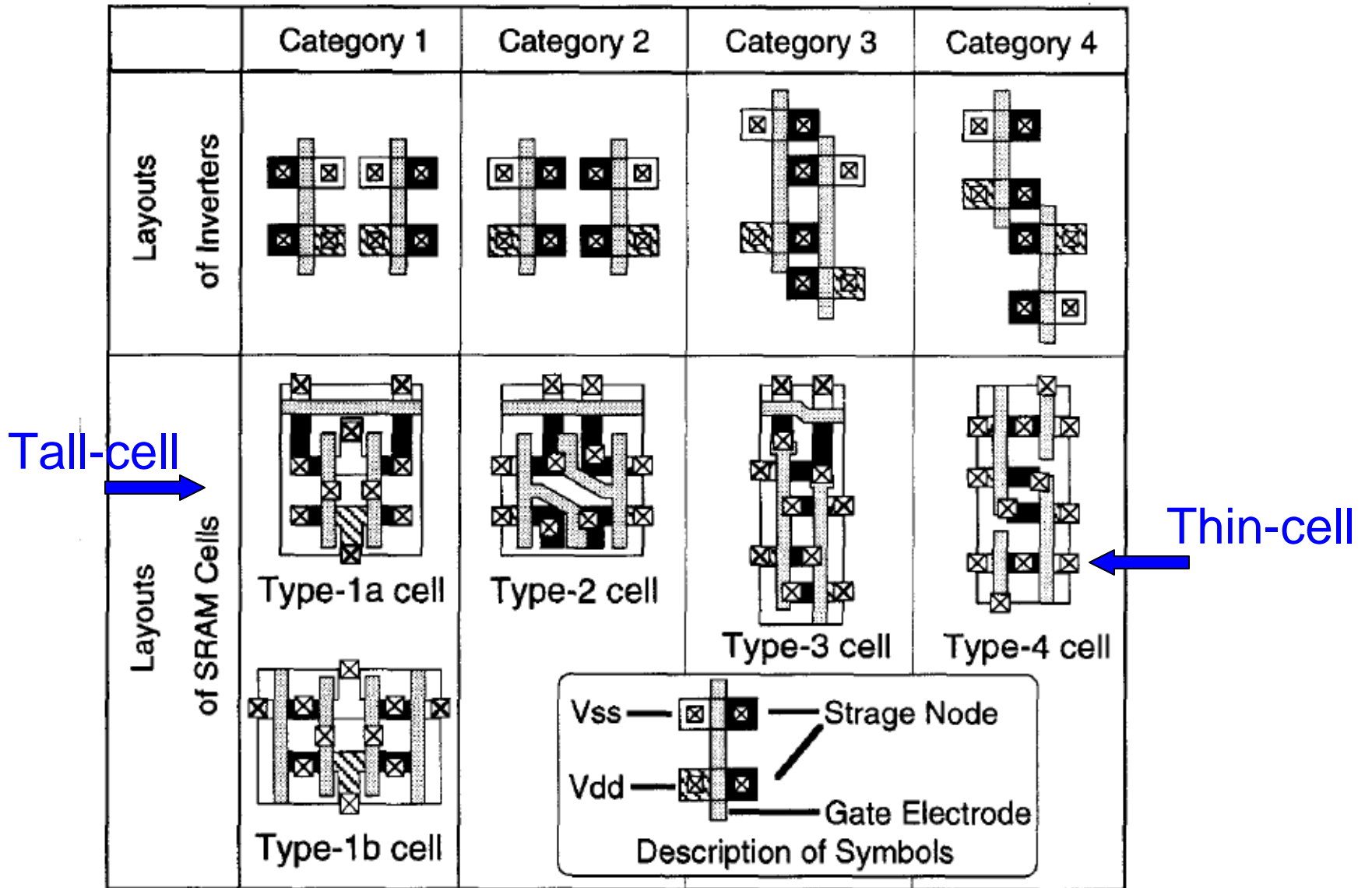

Tall Cell Layout

 


Compact cell

Bitlines: M2



Wordline: strapped in M3

Thin Cell Layout

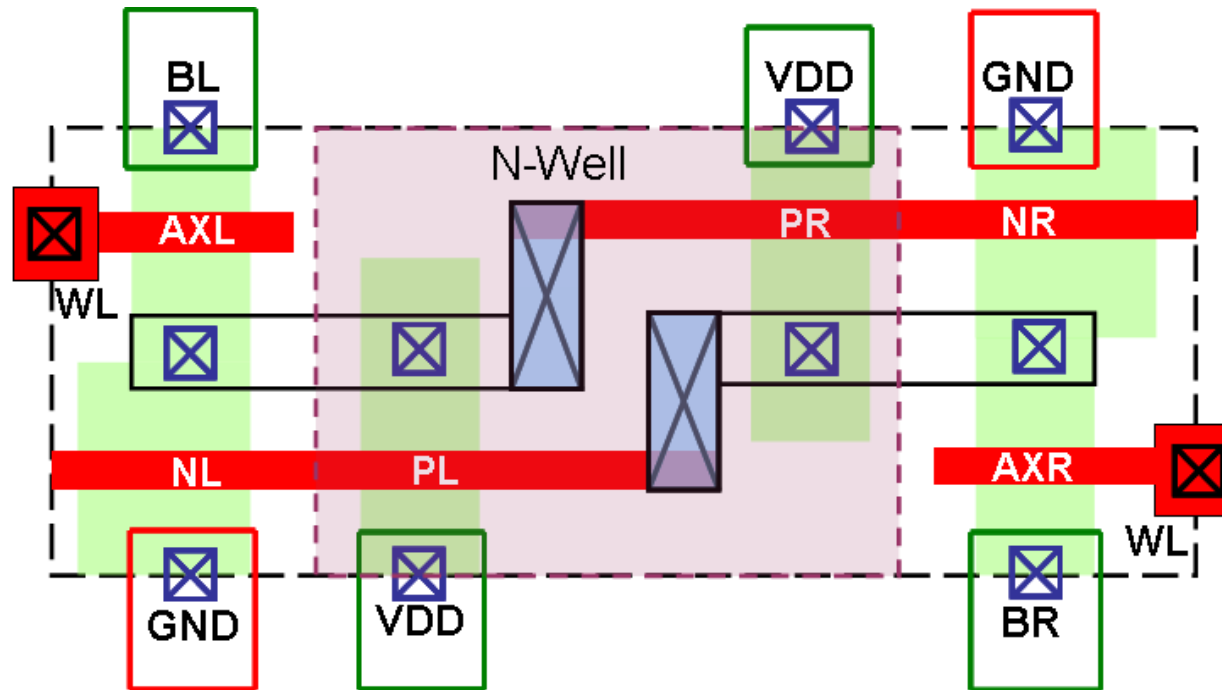


- 2 Poly-pitch, N-well continuous, Shared Contacts
- WL (Horizontal), BL(Vertical), Lower bitline capacitance

Upsizing Thin-cell size

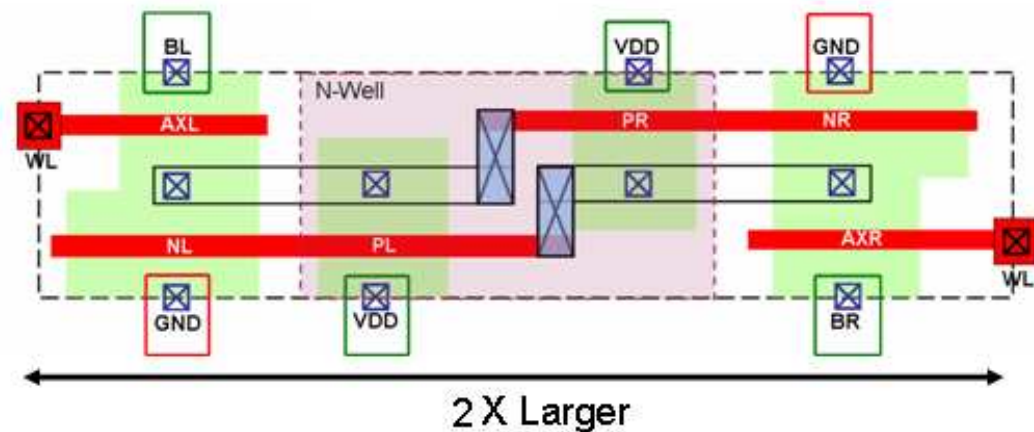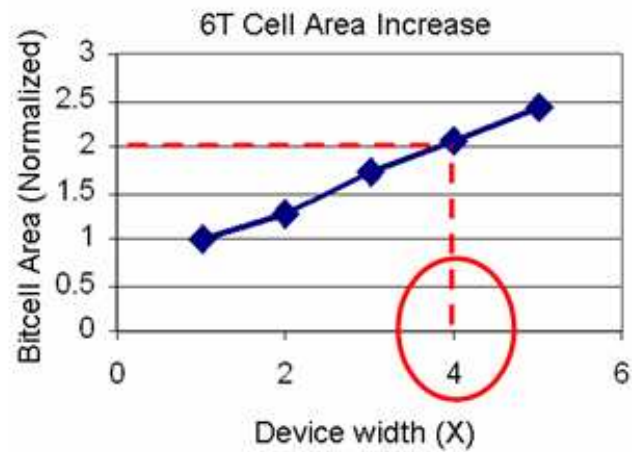

Increasing cell area by 2X increase device widths by 4X !


Trends in Memory Cell Area

 


From [Itoh01]

Array-Structured Memory Architecture

 Problem: ASPECT RATIO or HEIGHT \gg WIDTH




Hierarchical Memory Architecture

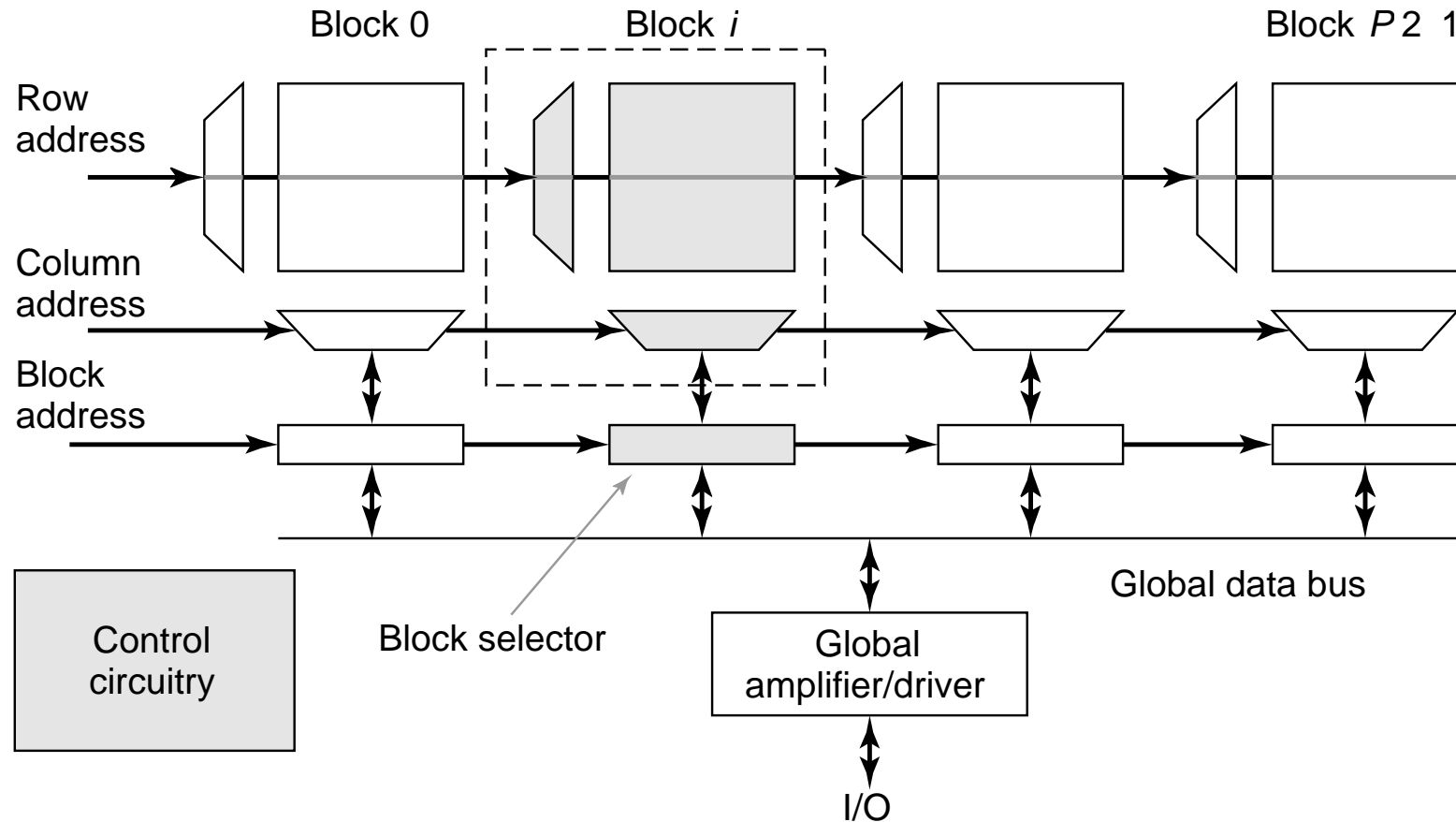

Advantages:

1. Shorter wires within blocks
2. Block address activates only 1 block => power savings

Memory Architecture: Decoders

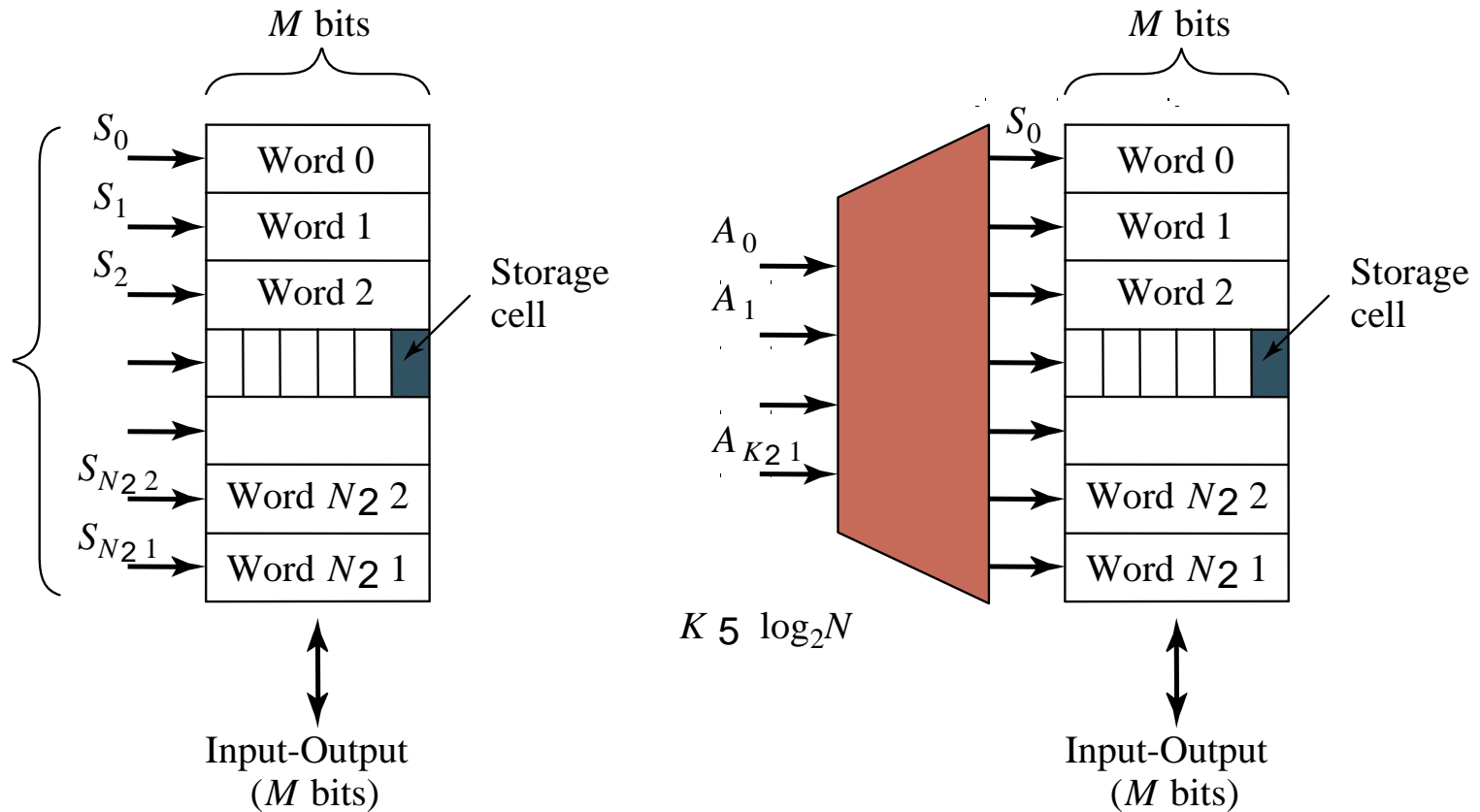


Intuitive architecture for $N \times M$ memory
 Too many select signals:
 N words == N select signals


Decoder reduces the number of select signals
 $K = \log_2 N$

Hierarchical Decoders

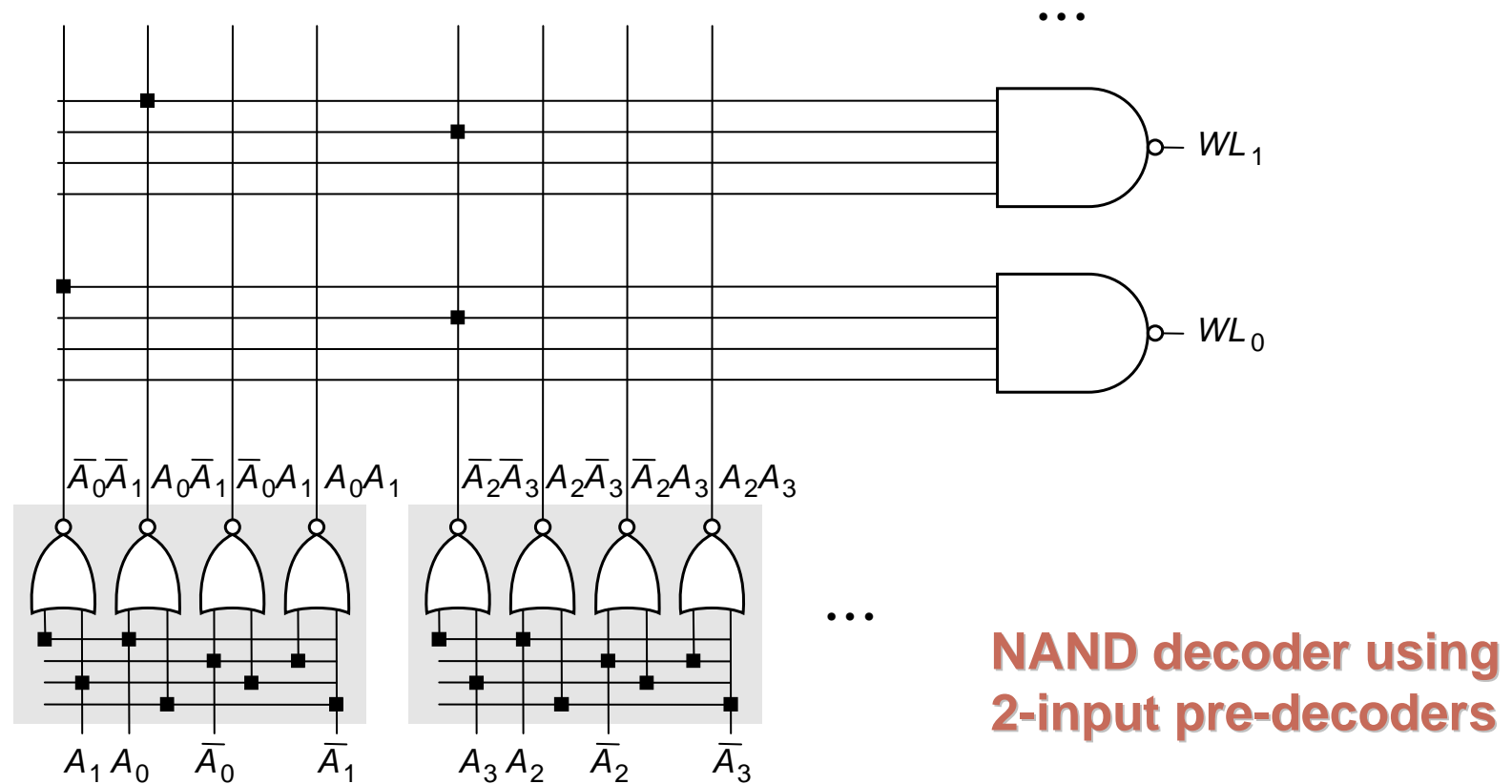
Multi-stage implementation improves performance



Dynamic Decoders

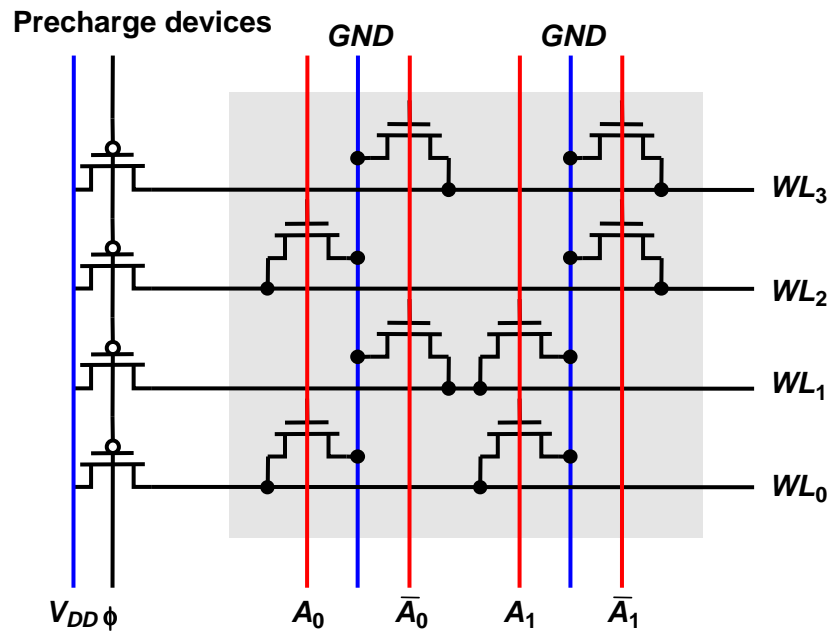


2-input NOR decoder

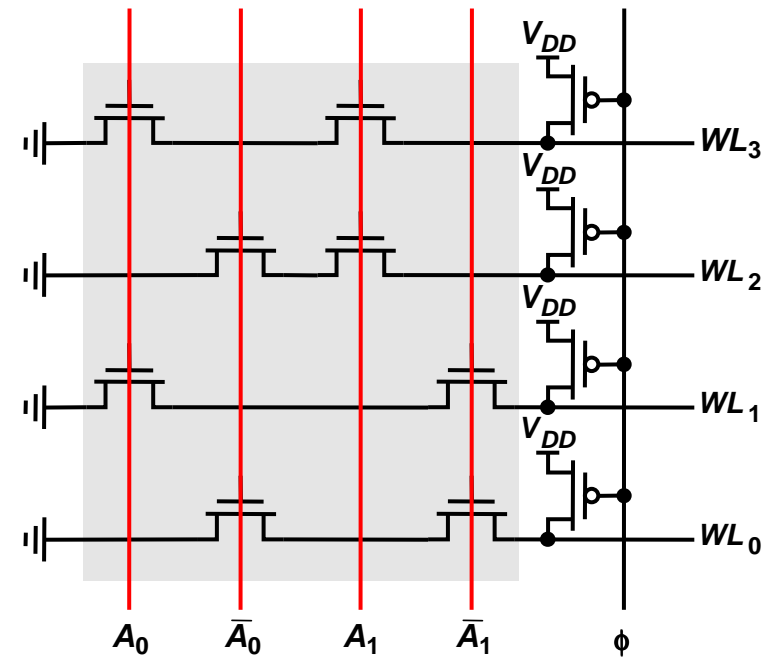

2-input NAND decoder

Column Decoder

 


Advantages: speed (t_{pd} does not add to overall memory access time)

Only one extra transistor in signal path

Disadvantage: Large transistor count

Tree based column decoder

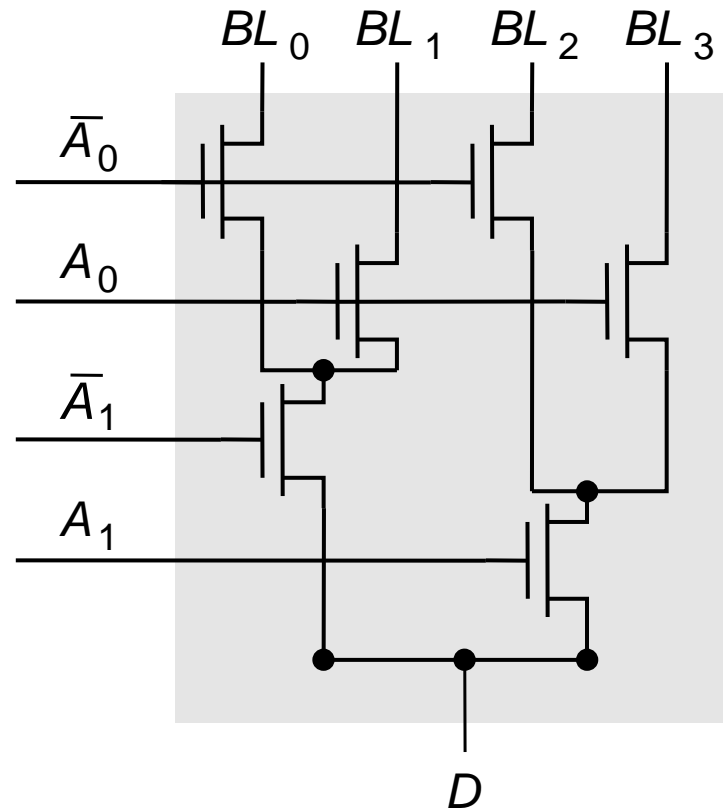

Number of devices drastically reduced

Delay increases quadratically with # of sections; prohibitive for large decoders

Solutions: buffers

progressive sizing

combination of tree and pass transistor approaches

Sense Amplifiers


$$t_p = \frac{C \times \Delta V}{I_{av}}$$

make ΔV as small as possible


large

small


Idea: Use Sense Amplifier

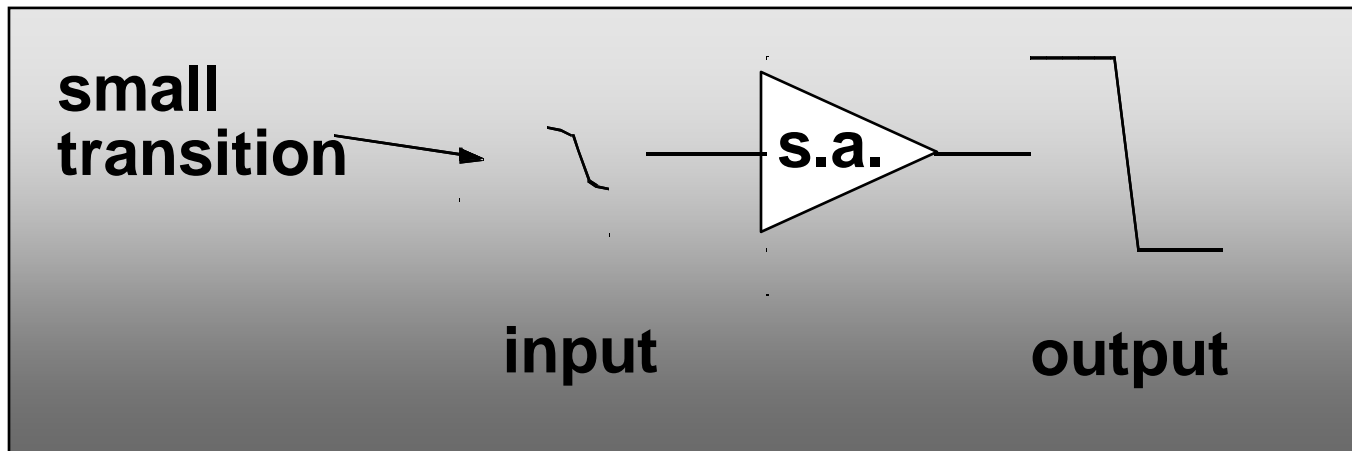


Differential Sense Amplifier

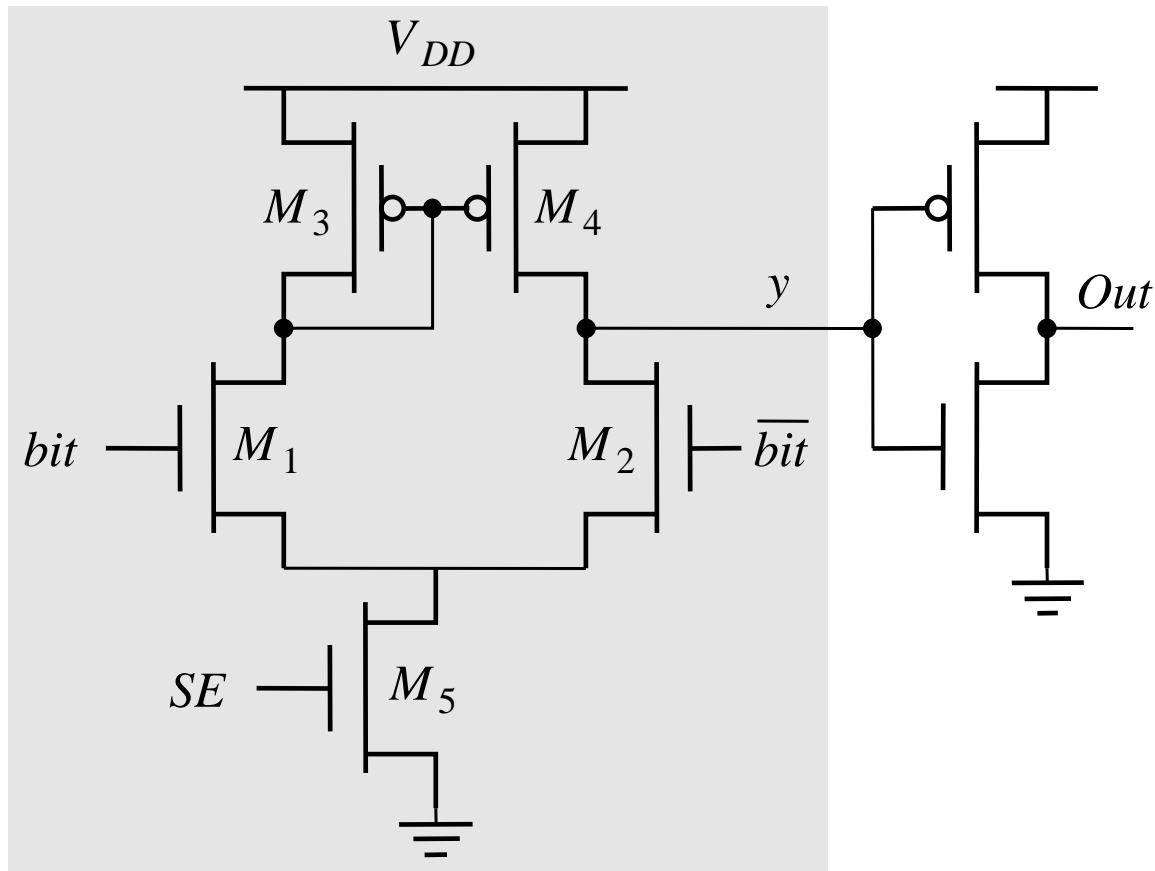

Differential Sensing — SRAM

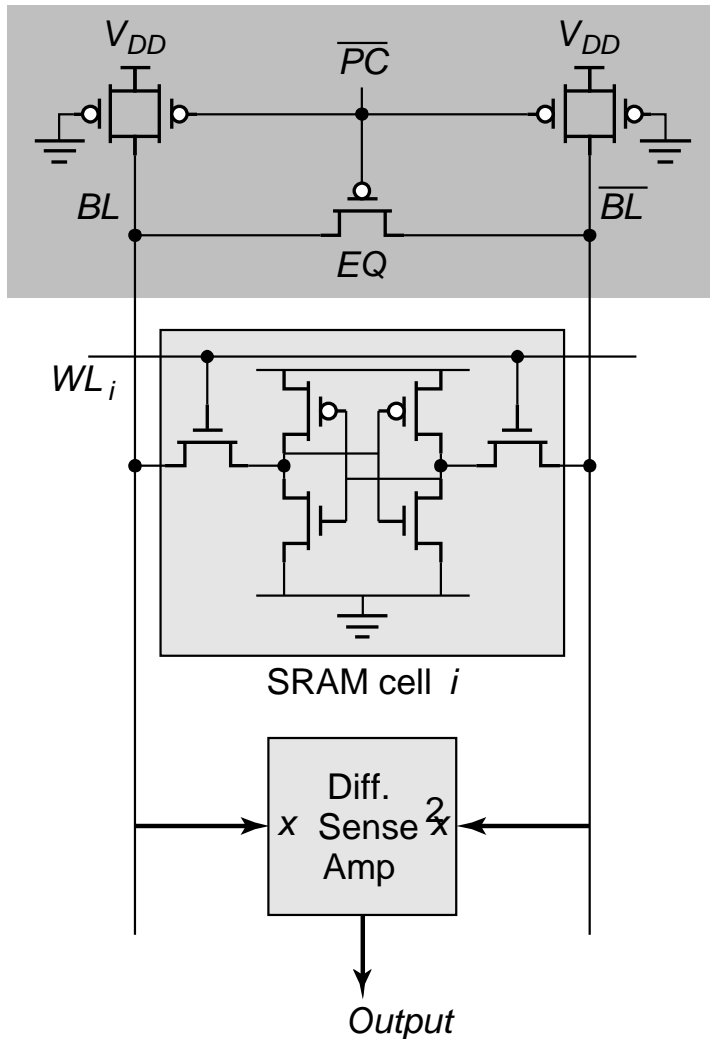


(a) SRAM sensing scheme


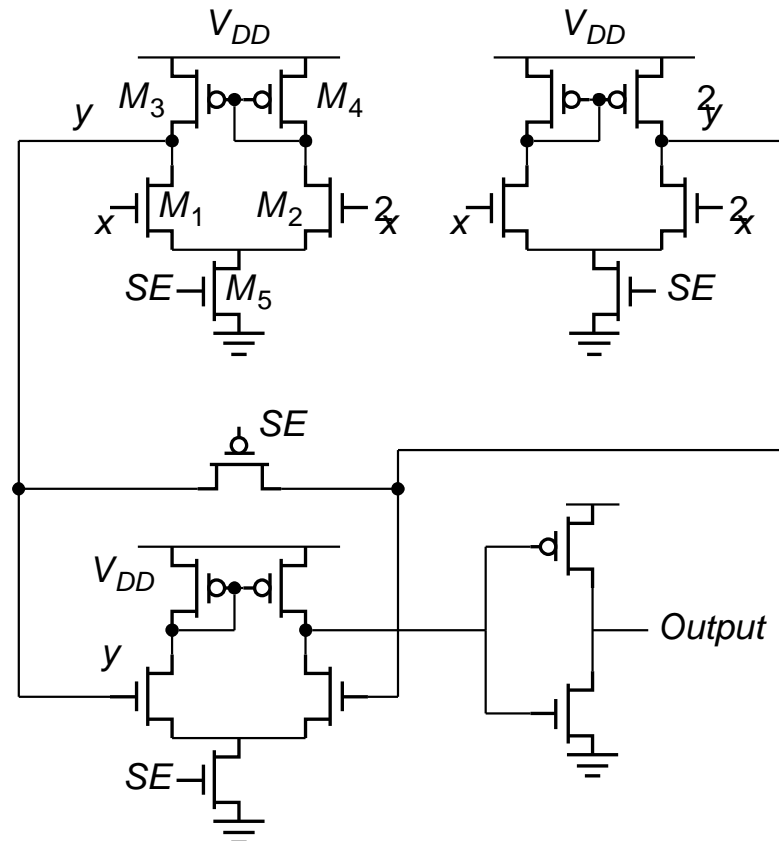


(b) two stage differential amplifier

Decoupled Sense Amplifier

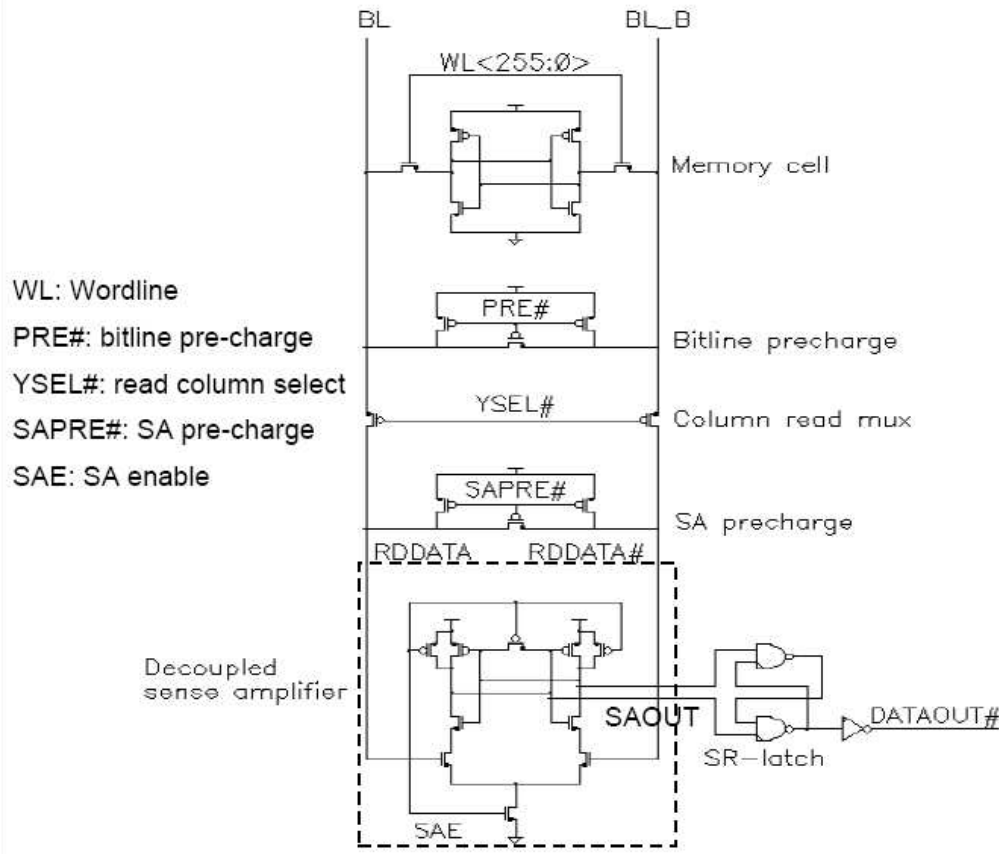


  WL: Wordline
 PRE#: bitline pre-charge
 YSEL#: read column select
 SAPRE#: SA pre-charge
 SAE: SA enable



Simulation timing diagram

SRAM Cell Leakage

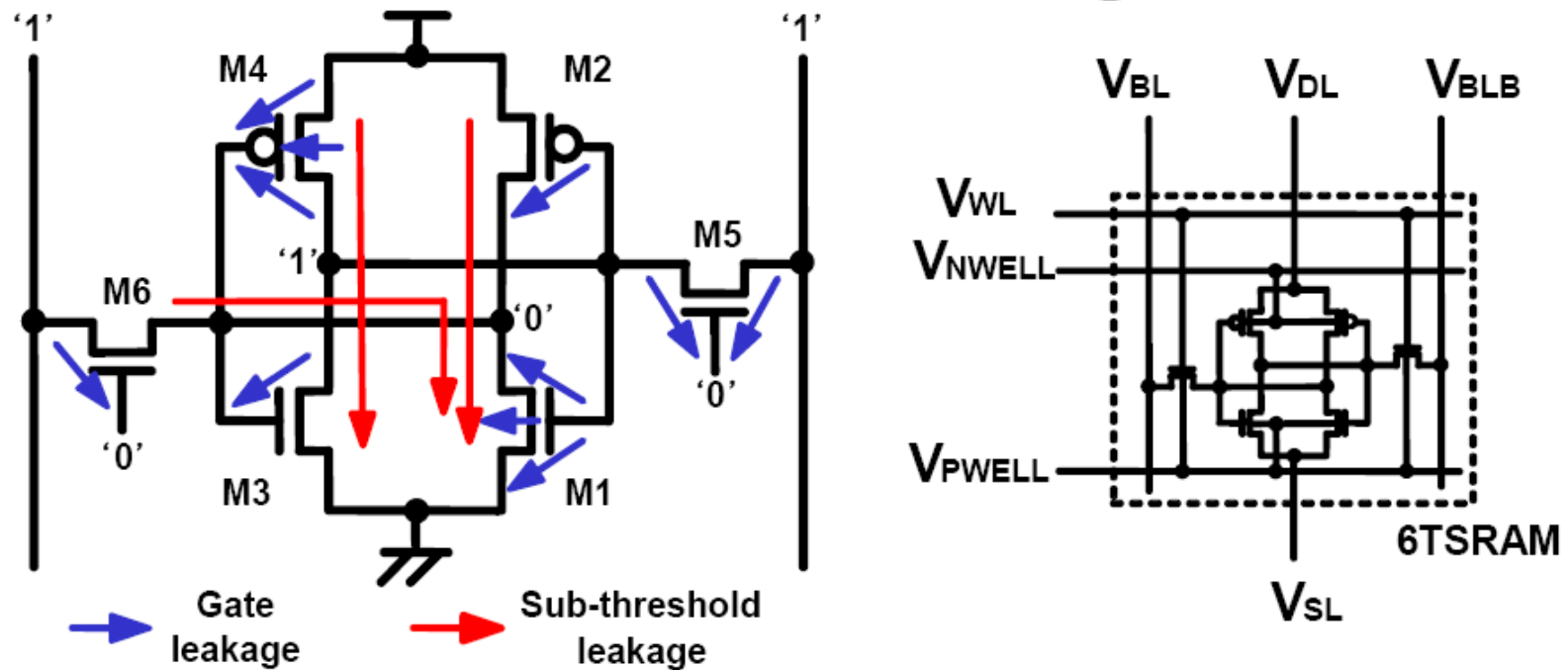


- Switch off cells into a low leakage state when they are not used
- 7 degrees of freedom to reduce 6T SRAM leakage

Leakage Reduction Schemes


Schemes	Source Biasing (V_{SL})	Reverse Body-Biasing (V_{PWELL} , V_{NWELL})	Dynamic V_{DD} (V_{DL})	Floating Bitlines (V_{BL} , V_{BLB})	Negative Word Line (V_{WL})
Leakage reduction	Sub: ↓↓ Gate: ↓↓	Sub: ↓↓ *BTBT: ↑	Sub, gate: ↓ *Bitline leak: -	Sub: ↓ Gate: ↓	Sub: ↓ *Gate: ↑
Delay	*Delay increase	No delay increase	No delay increase	No delay increase	No delay increase
Overhead	Low transition overhead	Large transition overhead	Large transition overhead	*Precharge latency overhead	*Low charge pump efficiency
Stability	Impact on SER	No impact on SER	*Worst SER	No impact on SER	No impact on SER, voltage stress

Source Biasing SRAM Scheme

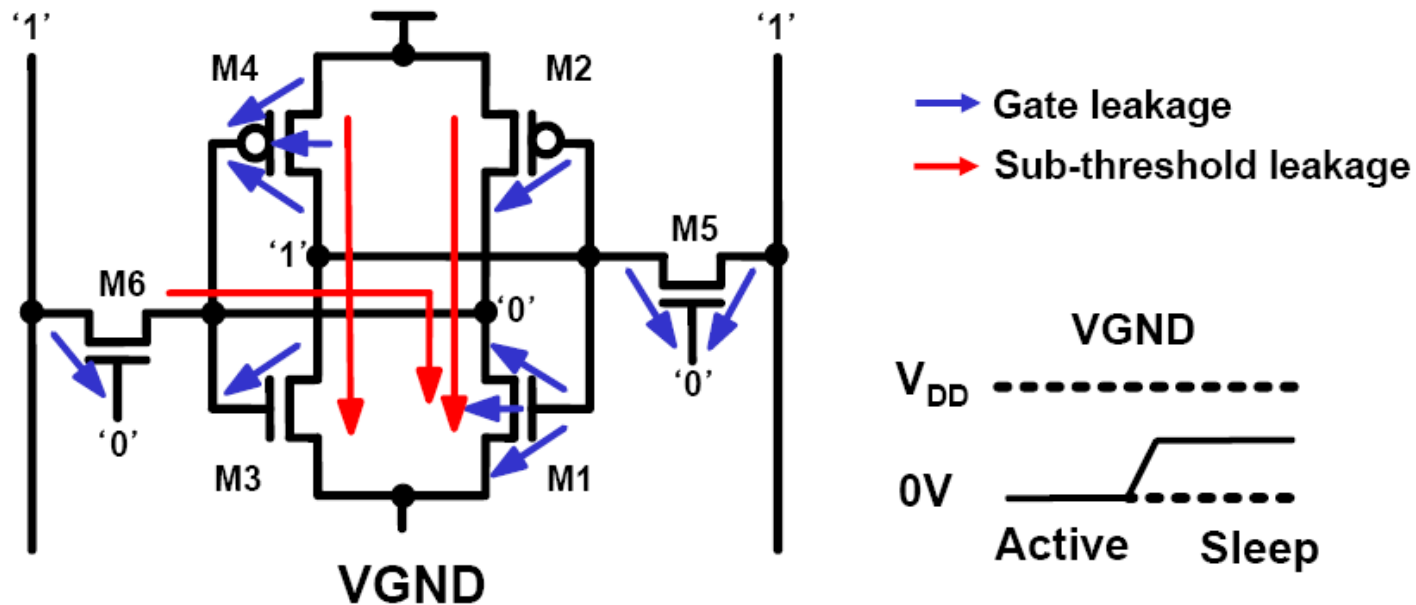


- Negative V_{GS} in access transistors
- Lower DIBL, body effect, less voltage stress
- Reduces both sub-threshold and gate leakage

Comparison with Dynamic V_{dd}

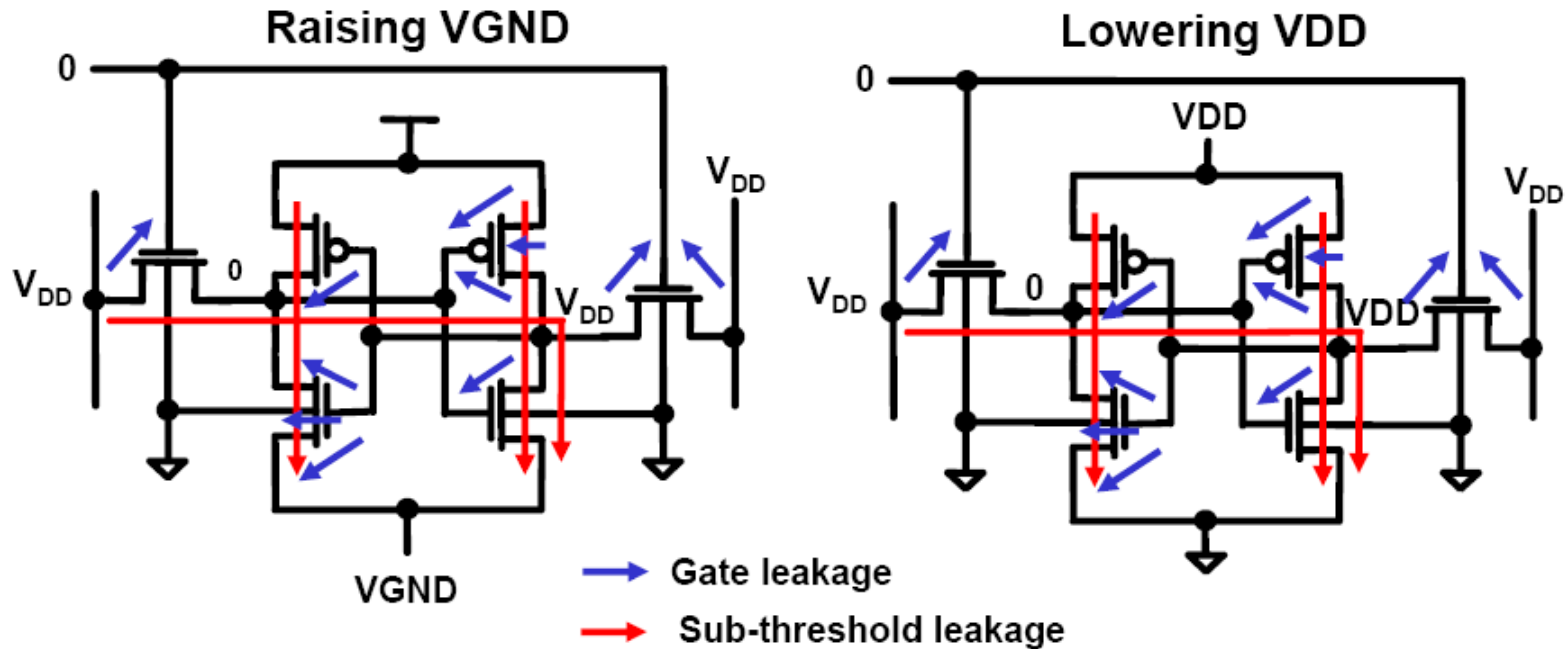

- Negative V_{GS} in access transistors
- Lower DIBL, body effect, less voltage stress
- Reduces both sub-threshold and gate leakage


Data Retention During Sleep Mode

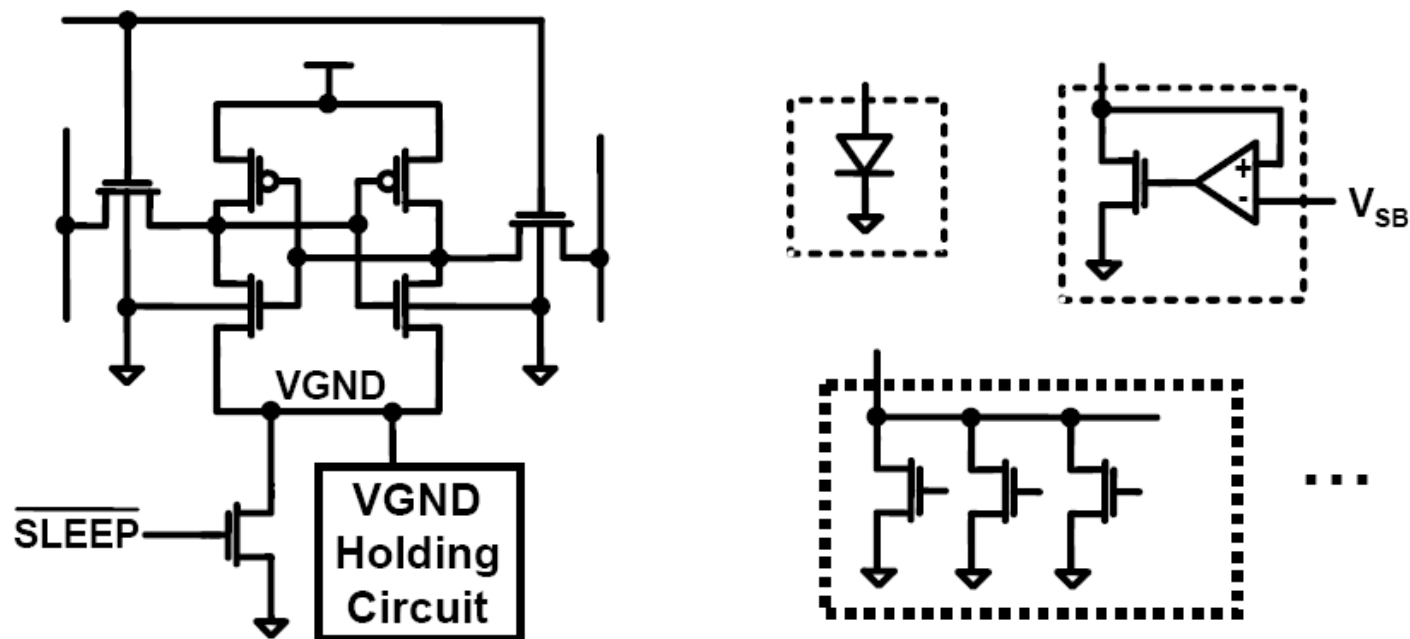

- Sleep transistor cuts off VGND from ground during sleep mode
- VGND is strapped using different circuit schemes


Bitline Leakage Problem

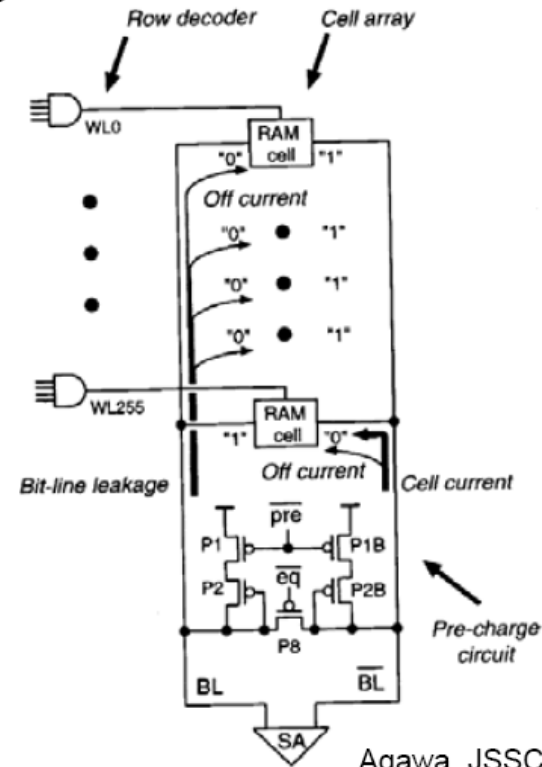- Access TR leakage acts as noise current for sense amp
- Slow or incorrect read/write operation
- This is a functionality issue caused by increasing leakage
- Must consider worst case process and data condition
- Prohibits the use of long bitlines \rightarrow impacts SRAM density




Agawa, JSSC 2001

Bitline Leakage Problem

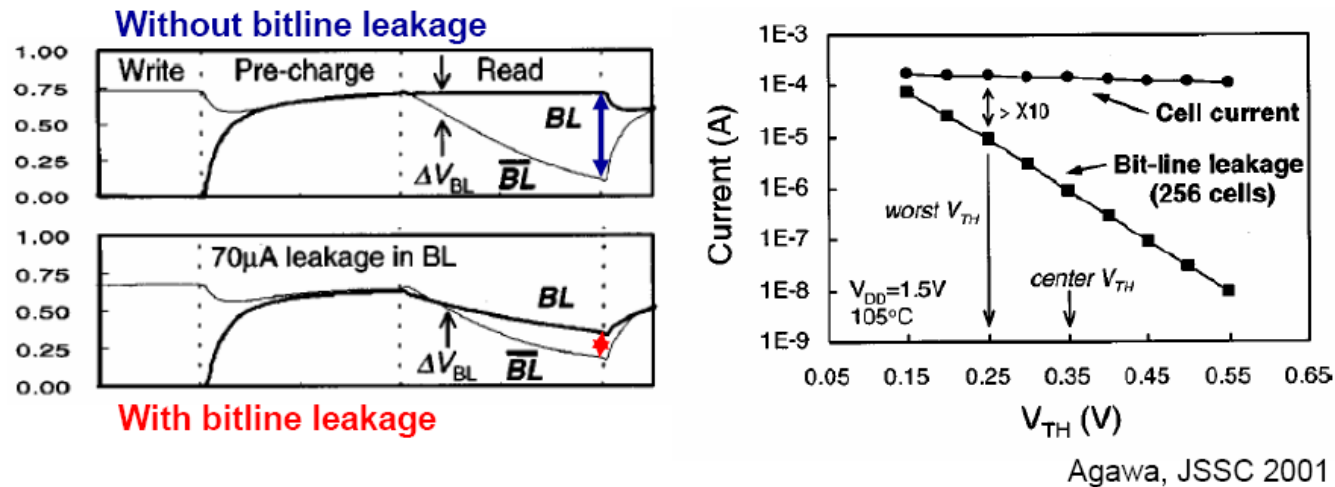


- Worst case bitline difference voltage is reduced
- This would mean that unlike in random logics, lower V_t can slow down performance in SRAMs
- Circuit solutions
 - Compensate leakage, reduce leakage, or equalize leakage

Bitline Leakage Compensation

 


Concept

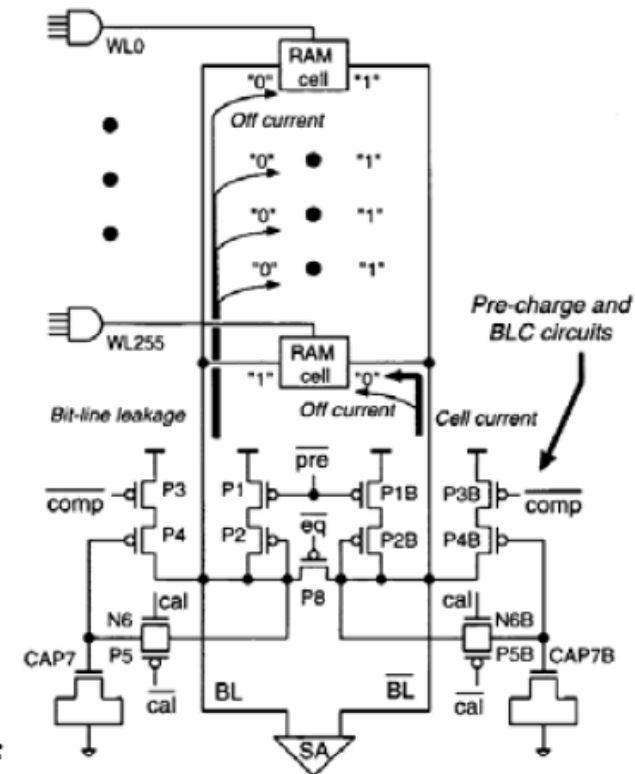- Precharge phase: Measure the amount of bitline leakage during
- Evaluation phase: Duplicate and inject the same amount of current into the bitline




Agawa, JSSC 2001


Bitline Leakage Compensation (cont'd)

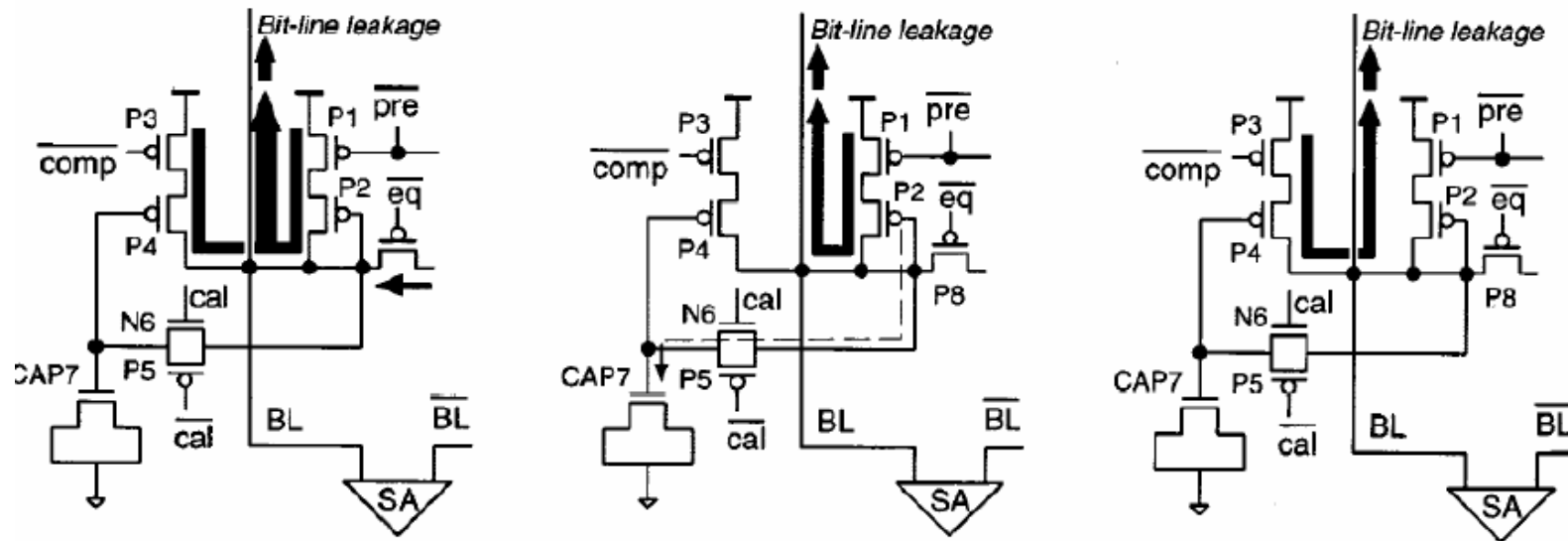

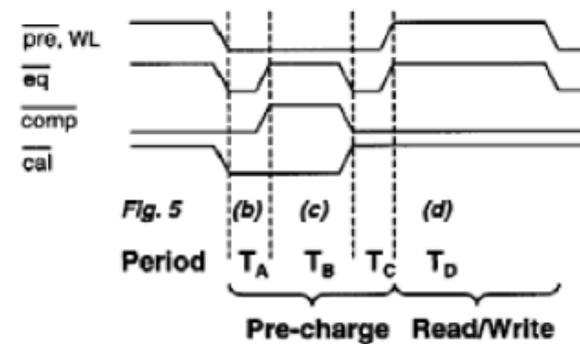- Precharge using P2, P4
- Measure leakage using P2
- Compensate during read/write cycle using P4




Bitline Leakage Compensation - II

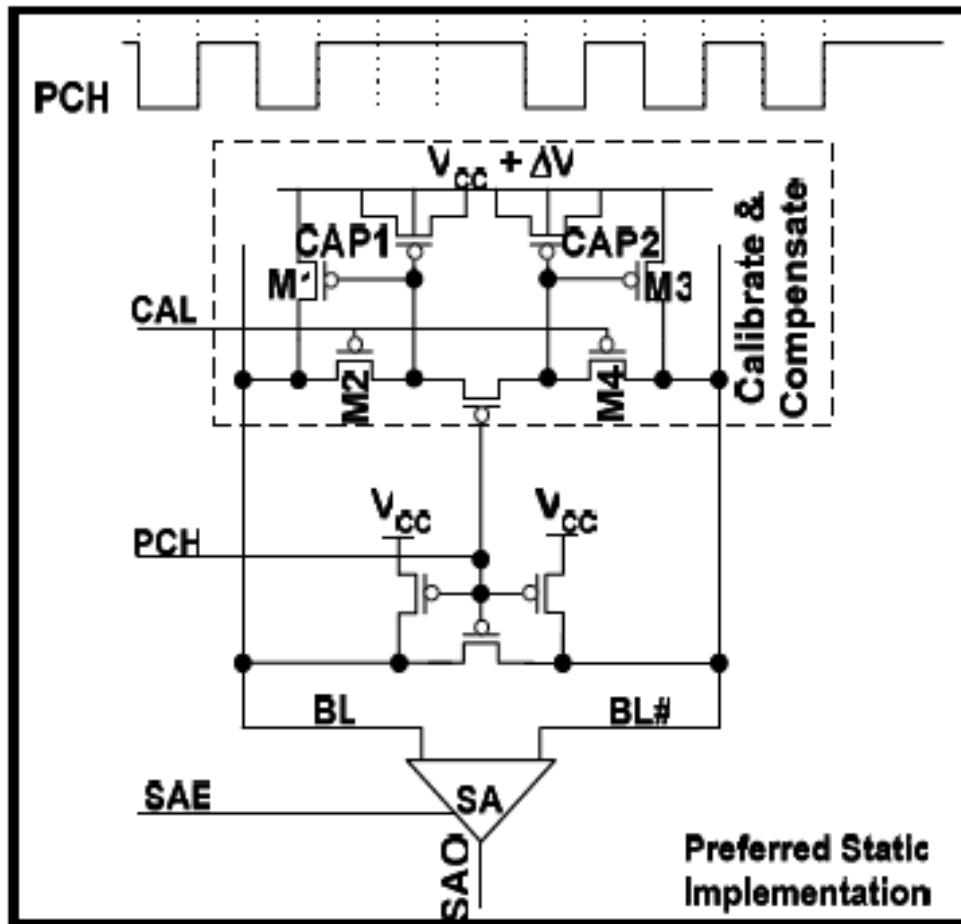

- Less transistor count
- Easy to implement in within column pitch
- No complicated timing
- Calibration after every write

Bitline Leakage Reduction


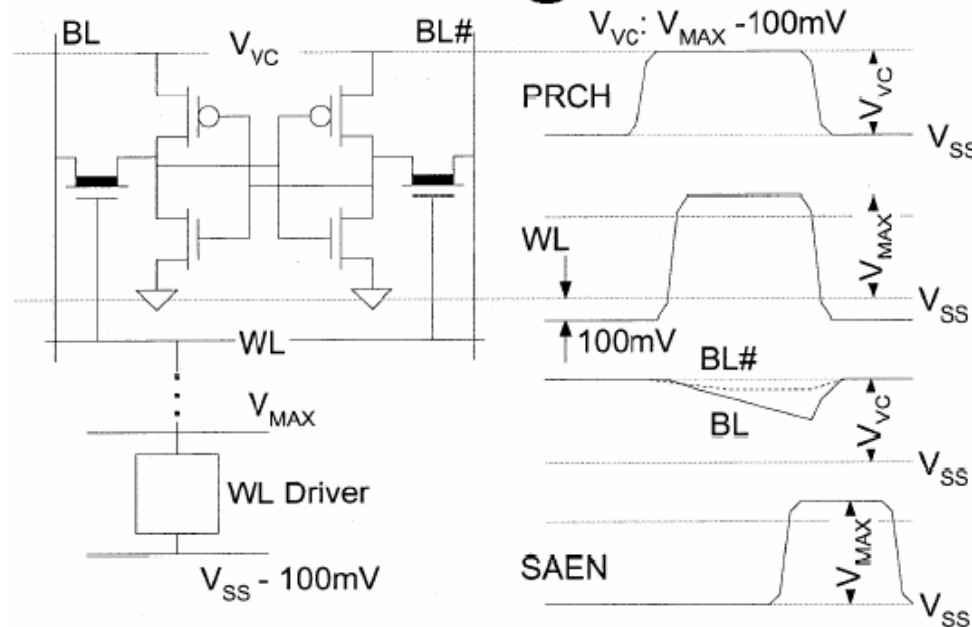


Ye, VLSI 2003

- Wordline underdrive during idle mode to reduce leakage through access TR
- Low V_t access transistor for fast read
- Cell and precharge voltage lower than global $V_{CC} (=V_{max})$
 - This ensures that V_{gs} and V_{ds} doesn't exceed V_{max}

Bitline Leakage Equalization

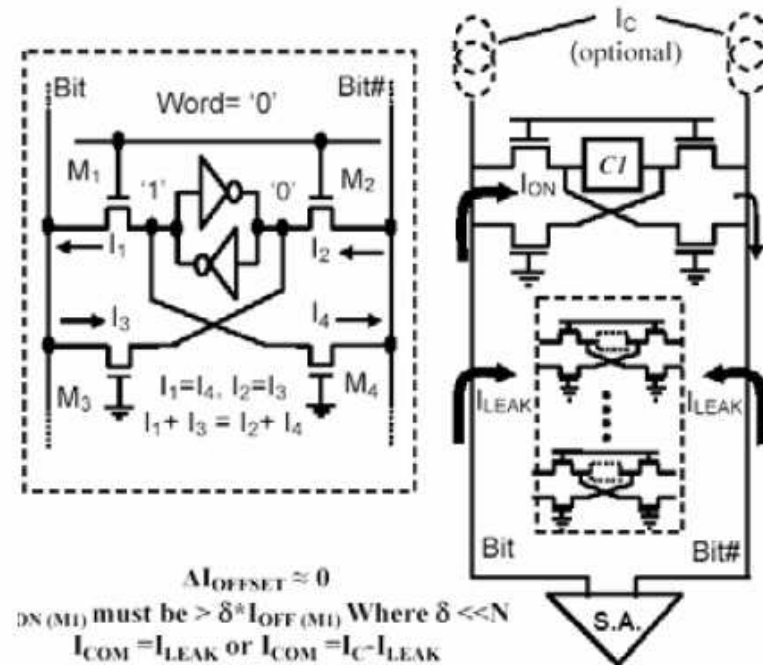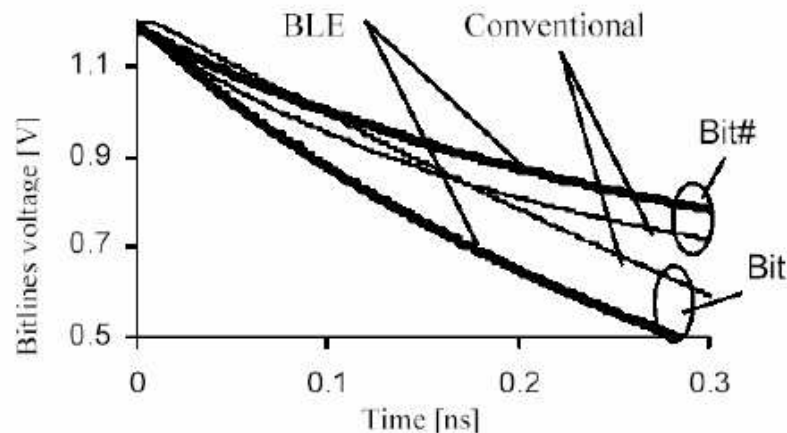- 8T SRAM cell with 40% area hit
- Dummy transistors M3 and M4 inject same amount of leakage to each bitlines
- Both bitlines discharge together due to equalized bitline leakage
- Less practical due to area impact



Alvandpour, ESSCIRC 2003

